

P 3.3-4

$$V_1 = \frac{16}{16+8} \times 12 = 8V$$

$$V_2 = \frac{4}{4+8} \times 12 = 4V$$

$$V_3 - V - V_1 = 0 \rightarrow V = -4V$$

