

Course on Linear Circuits

Jennifer Hasler

Course Website:

- <http://hasler.ece.gatech.edu/Courses/ECE2040/index.html>
- Priority for open materials
- Short Lecture (YouTube) Nuggets

Mixture of objective & subjective


- Objective → Exams
- Subjective → Labs (often groups of 2)

Other rules

- No recording / pictures allowed in class
- Groups start in a self-organized manner
- Read the Syllabus

My Research Interests:

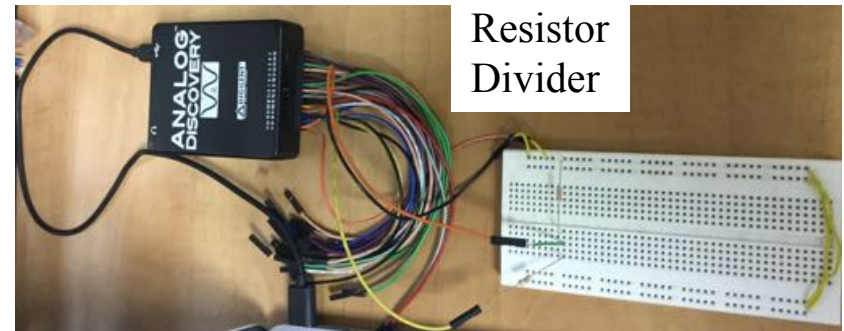
- Floating-Gate Devices & Circuits, Nonvolatile
- Wearable computing, always-on computing, etc.
- Circuits for Machine Learning, AI, Neuroscience
- Configurable, CAD tools
- Sensory interfaces




A few points of my history:

- Began as faculty at GT in 1997
- Ph.D. in Computation and Neural Systems (Caltech, 1997)
- Grew up in FL and AZ, B.S.E. & M.S. ASU (1991)
- First startup, GTronix (2002-2010), acquired by TI
- MDiv, Emory University 2020

Circuit Measurement Anywhere

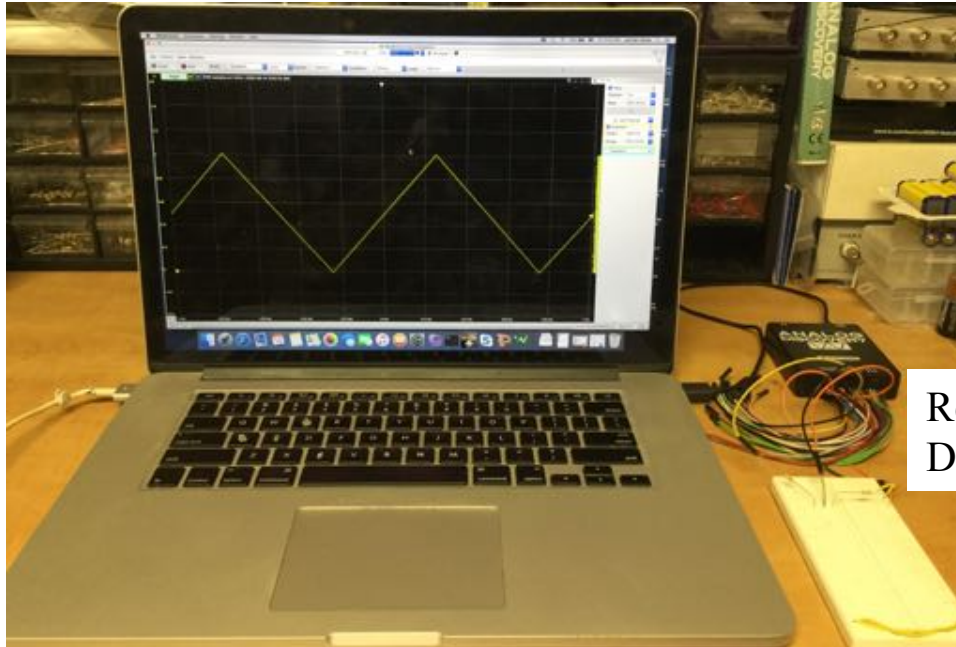

Resistor
Divider

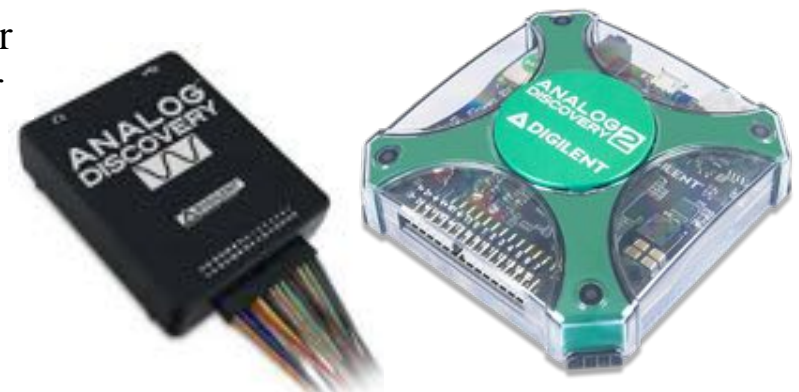

Laboratory measurements anywhere:

- Laboratory experiments can be done anywhere
- Electronics everywhere, so relatively inexpensive labs
- Utilize an acquisition system
(e.g. scope/function generator)

Class laboratory concepts:

- Need a data acquisition system
- Work on experiments before a class session
- Focus on understanding material deeply

Circuit Graph Concepts


Wire

(only connection,
no R, L, C)


Flattened 2-Dim graph

Often: DC path to GND
(→ no charge storage)

Kirchoff's Current Law (KCL)

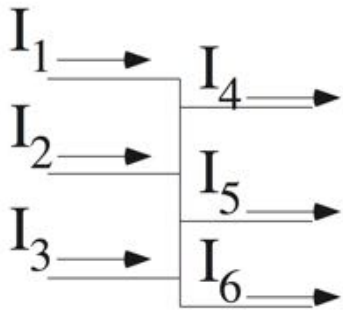


Kirchoff's Voltage Law (KVL)

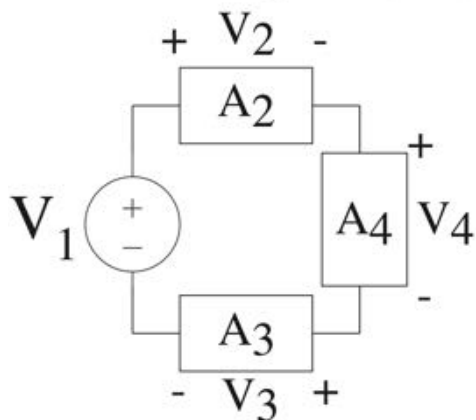


Independent Sources

Voltage Source

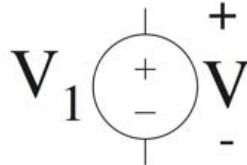


Current Source

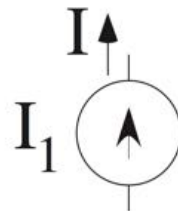


Dependent Sources




Voltage Source

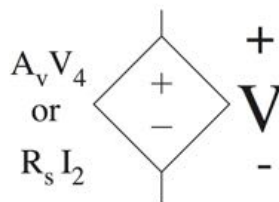


Current Source

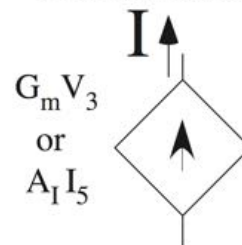

Circuit Graph Concepts

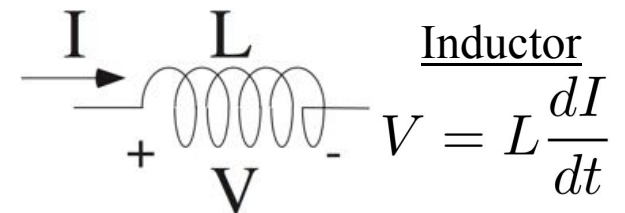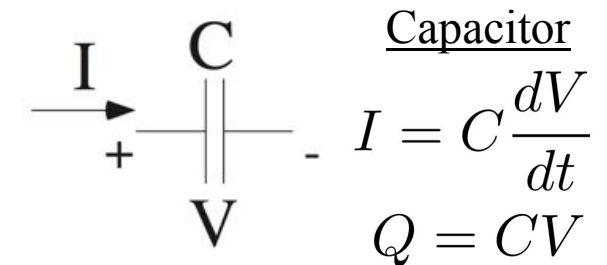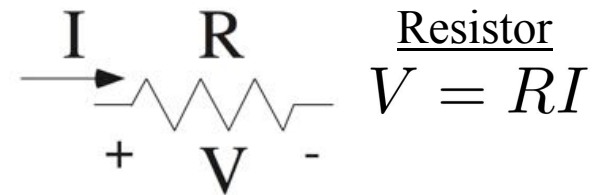

Example: Resistive Voltage Divider

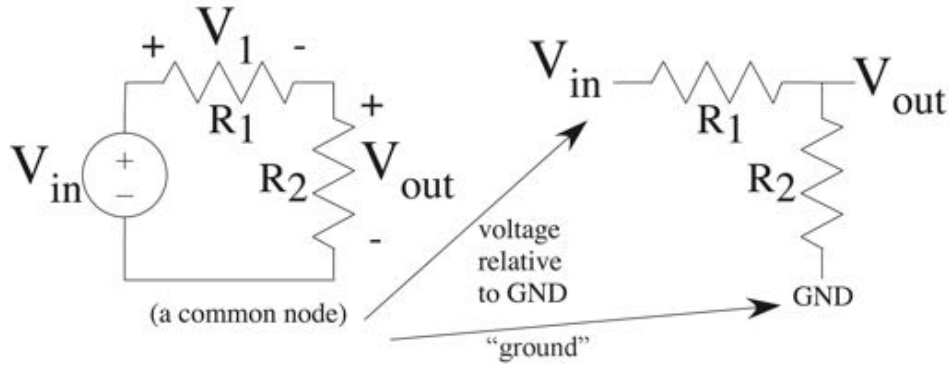

$$V_{in} = V_1 + V_{out} \quad V_{in} = \frac{R_1}{R_2} V_{out} + V_{out}$$

$$I = \frac{V_1}{R_1} = \frac{V_{out}}{R_2} \quad V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$


Capacitive Divider?

$$V_{in} = V_1 + V_{out}$$


$$Q_1 = C_1 V_1$$

$$Q_2 = C_2 V_{out}$$

... ?

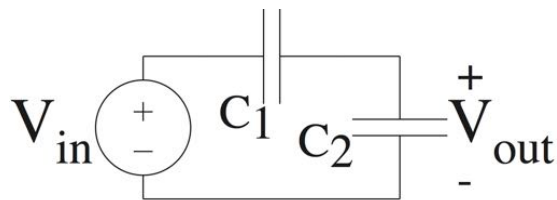

Example: RC First-Order Low-Pass Filter


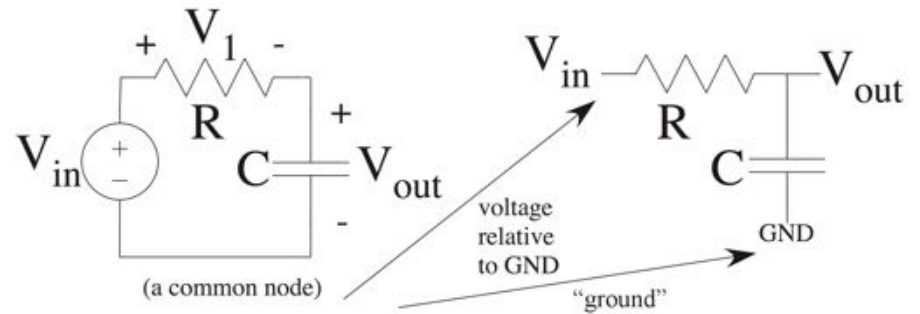


$$V_{in} = V_1 + V_{out} \quad \tau = RC \rightarrow V_1 = \tau \frac{dV_{out}}{dt}$$

$$\frac{V_1}{R} = C \frac{dV_{out}}{dt}$$



$$\tau \frac{dV_{out}}{dt} + V_{out} = V_{in}$$

Resistors: Serial & Parallel

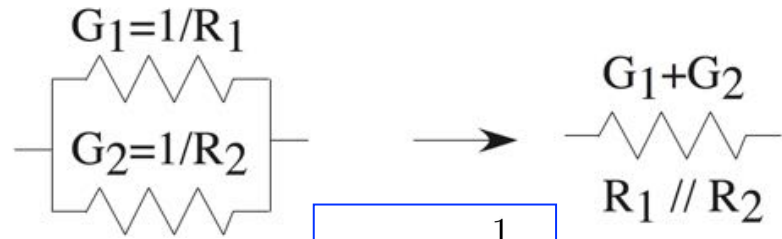
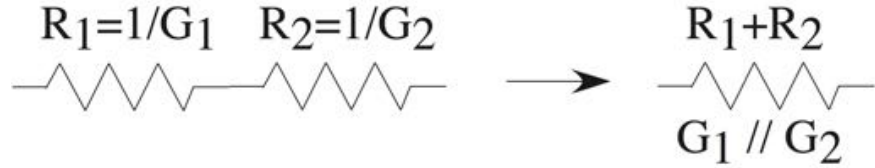


$$a//b = \frac{1}{\frac{1}{a} + \frac{1}{b}}$$




Inductors: Serial & Parallel

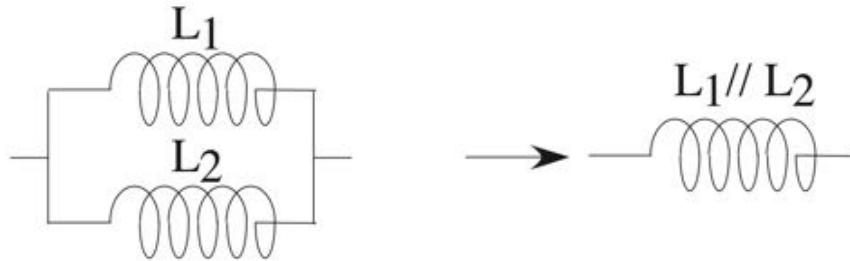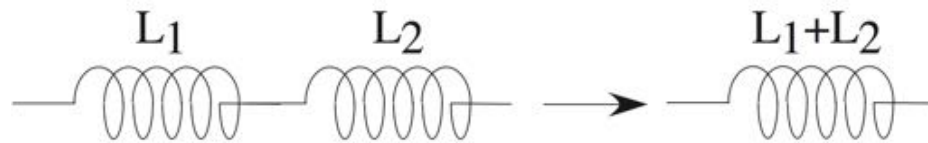


Capacitors: Serial & Parallel

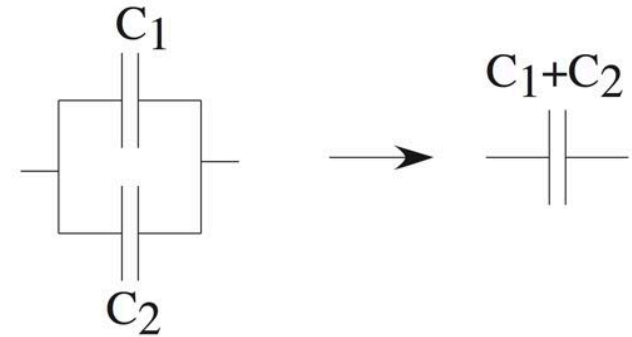
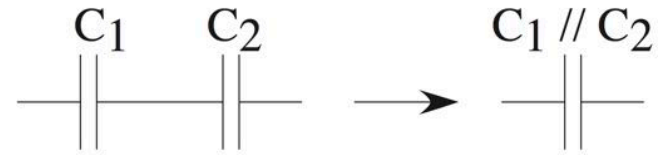


Parallel-Series Simplification

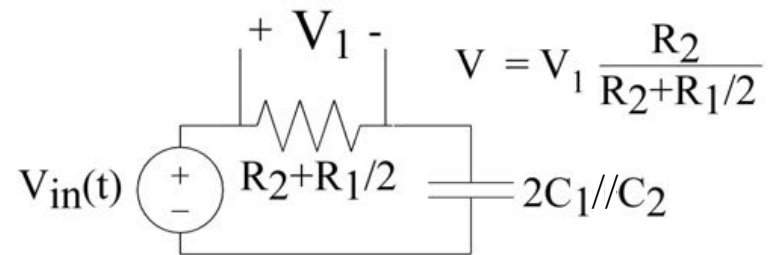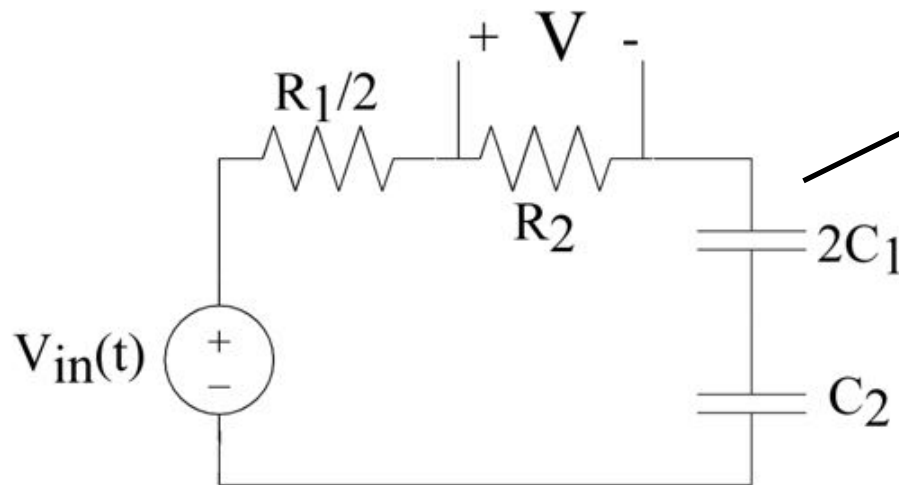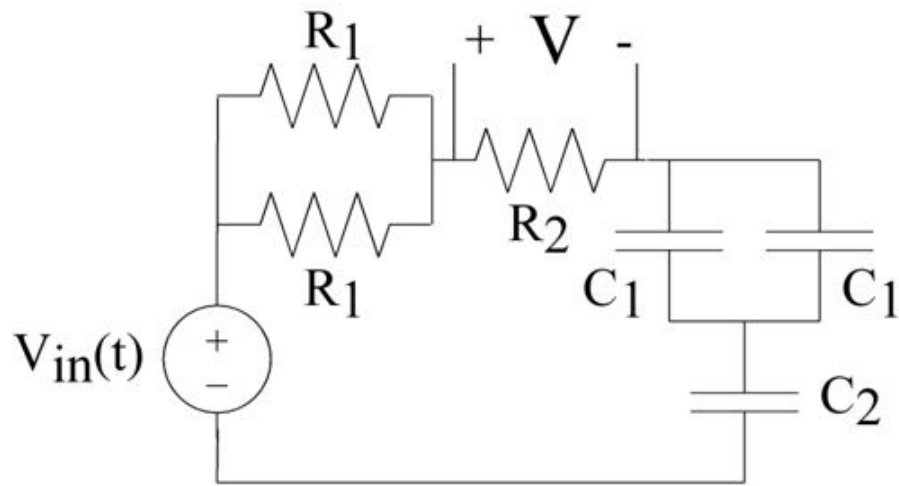

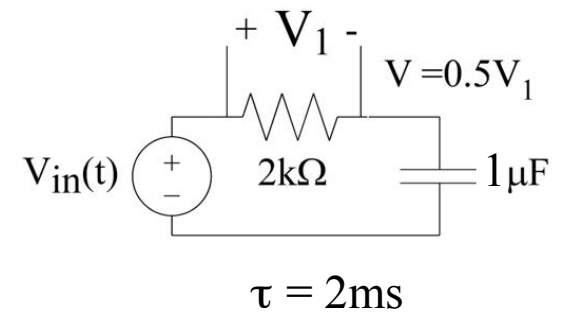$R_1 = 2\text{k}\Omega$
 $R_2 = 1\text{k}\Omega$
 $C_1 = 1\mu\text{F}$
 $C_2 = 2\mu\text{F}$



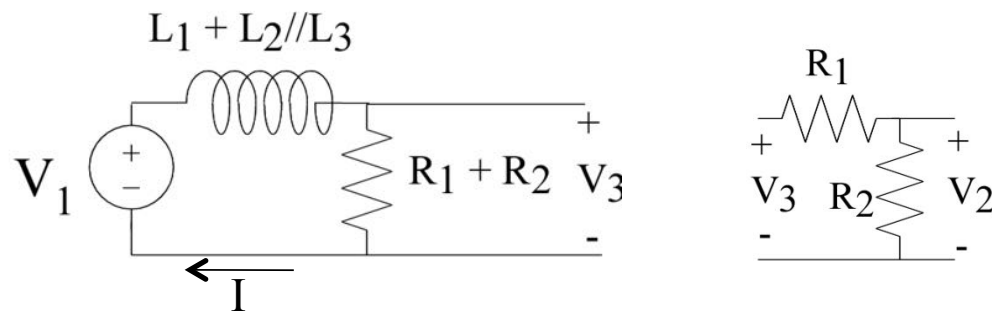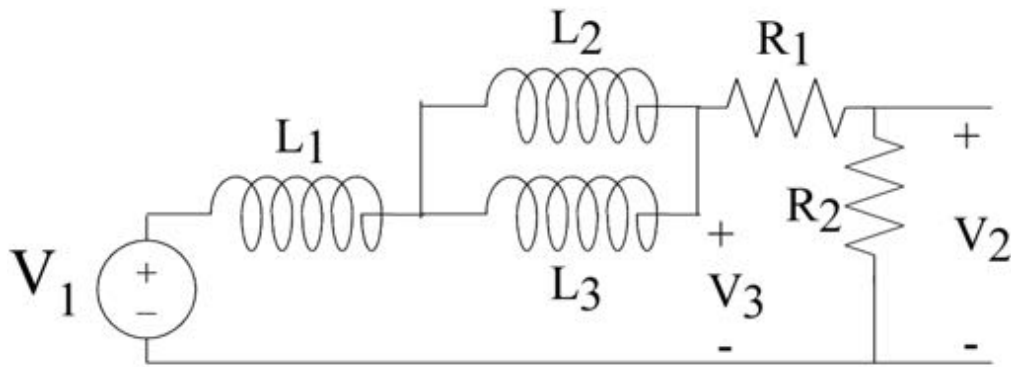

$$L_1 = 5\text{mH} \quad L_3 = 10\text{mH}$$

$$L_2 = 10\text{mH} \quad R_1 = 15\text{k}\Omega$$

$$R_2 = 5\text{k}\Omega$$

$$L_1 + (L_2 // L_3) = 10\text{mH}$$

$$R_1 + R_2 = 20\text{k}\Omega$$

$$\tau = 0.5\mu\text{s} \quad \tau \frac{dV_2}{dt} + V_2 = \frac{1}{4} V_1$$

$$V_1 = (L_1 + (L_2 // L_3)) \frac{dI}{dt} + V_3$$

$$V_3 = I (R_1 + R_2)$$

$$V_1 = \frac{L_1 + (L_2 // L_3)}{R_1 + R_2} \frac{dV_3}{dt} + V_3$$


$$\tau = \frac{L_1 + (L_2 // L_3)}{R_1 + R_2}$$

$$\tau \frac{dV_3}{dt} + V_3 = V_1$$

$$V_2 = V_3 \frac{R_2}{R_1 + R_2}$$

$$\tau \frac{dV_2}{dt} + V_2 = \frac{R_2}{R_1 + R_2} V_1$$

An Example Circuit Solution

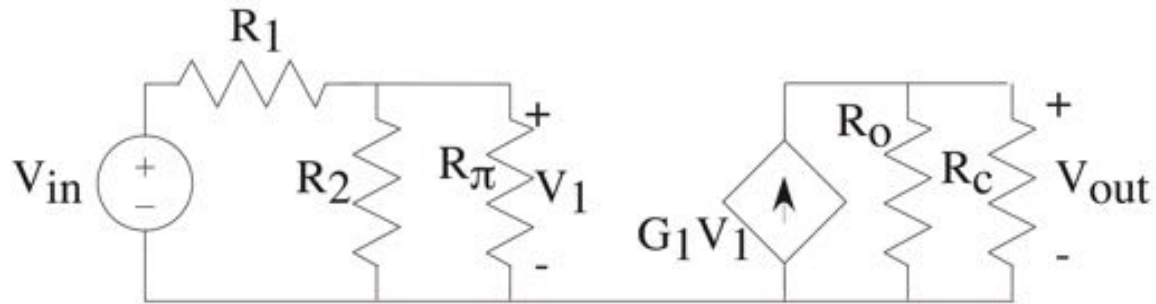


How to think through such a circuit?

- Parallel Combination of Resistors for V_1
- Resistive voltage divider for V_1
- Current divider from the voltage-controlled I source

$$V_1 = V_{in} \frac{R_2 // R_\pi}{R_1 + R_2 // R_\pi}$$

$$V_{out} = G_1 V_1 (R_o // R_c)$$
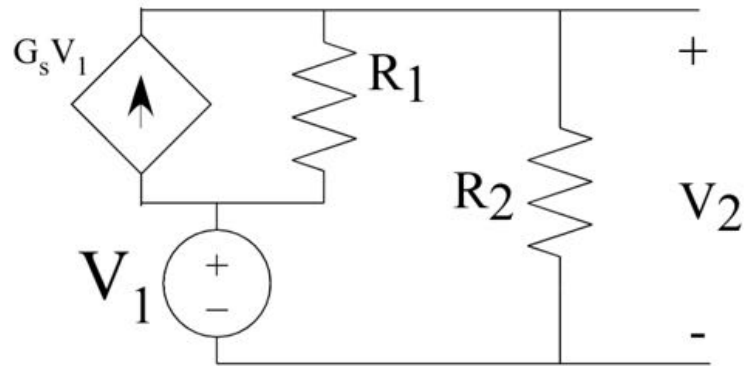
$$V_{out} = V_{in} \frac{G_1 (R_o // R_c) (R_2 // R_\pi)}{R_1 + R_2 // R_\pi}$$



KCL @ V_2 :

$$G_s V_1 + \frac{V_1 - V_2}{R_1} = \frac{V_2}{R_2}$$

$$\left(G_s + \frac{1}{R_1}\right) V_1 = \frac{V_2}{R_1} + \frac{V_2}{R_2}$$

$$\left(G_s + \frac{1}{R_1}\right) V_1 = \frac{V_2}{R_1 // R_2}$$

$$V_2 = (R_1 // R_2) \left(G_s + \frac{1}{R_1}\right) V_1$$

$$R_1 = 200\text{k}\Omega$$


$$R_2 = 20\text{k}\Omega$$

$$G_s = 1 / 100\Omega$$

$$G_s \gg \frac{1}{R_1} \quad R_1 // R_2 \rightarrow R_2$$

$$V_2 = G_s R_2 V_1 \quad \boxed{V_2 = 200 V_1}$$

Node Voltage Solutions: KCL at nodes

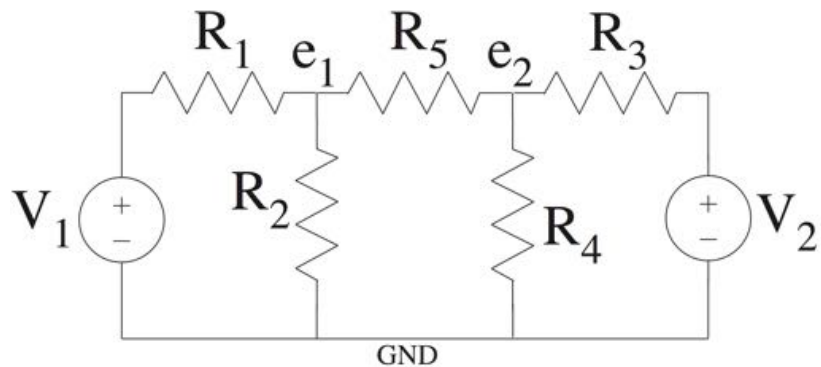

Node 1:

$$(V_1 - e_1)G_1 + (e_2 - e_1)G_5 + (0 - e_1)G_2 = 0$$

$$V_1G_1 + e_2G_5 - e_1(G_1 + G_2 + G_5) = 0$$

Node 2:

$$(V_2 - e_2)G_3 + (e_1 - e_2)G_5 + (0 - e_2)G_4 = 0$$

$$V_2G_3 + e_1G_5 - e_2(G_3 + G_4 + G_5) = 0$$

G Matrix is symmetric, positive definite

Diagonal terms = sum of conductances on the node


Off Diagonal terms = - sum of resistances between nodes

$$\mathbf{G} = \begin{bmatrix} G_1 + G_2 + G_5 & -G_5 \\ -G_5 & G_3 + G_4 + G_5 \end{bmatrix}$$

$$\mathbf{i} = \begin{bmatrix} G_1 V_1 \\ G_3 V_2 \end{bmatrix} \quad \mathbf{v} = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

Solve: $\mathbf{G} \mathbf{v} = \mathbf{i}$

KVL Equations: Solving for I

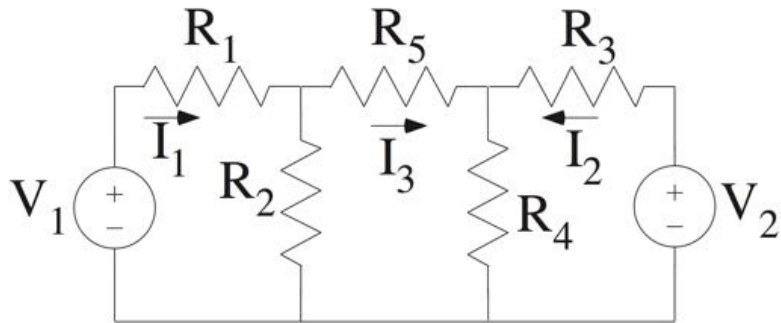

Mesh 1:

$$-V_1 + I_1 R_1 + (I_1 - I_3) R_2 = 0$$

$$-V_1 + (R_1 + R_2) I_1 - R_2 I_3 = 0$$

Mesh 2:

$$-V_2 + R_3 I_2 + R_4 (I_3 + I_2) = 0$$

$$-V_2 + R_4 I_3 + (R_3 + R_4) I_2 = 0$$

Mesh 3:

$$R_2 (I_3 - I_1) + R_5 I_3 + R_4 (I_3 + I_2) = 0$$

$$-R_2 I_1 + (R_2 + R_4 + R_5) I_3 + R_4 I_2 = 0$$

$$\mathbf{R} = \begin{bmatrix} R_1 + R_2 & 0 & -R_2 \\ 0 & R_3 + R_4 & -R_4 \\ -R_2 & -R_4 & R_2 + R_4 + R_5 \end{bmatrix}$$



$$\mathbf{i} = \begin{bmatrix} I_1 \\ -I_2 \\ I_3 \end{bmatrix} \quad \text{(mesh currents in same direction)} \quad \mathbf{v} = \begin{bmatrix} V_1 \\ -V_2 \\ 0 \end{bmatrix}$$

Solve: $\mathbf{R} \mathbf{i} = \mathbf{v}$

\mathbf{R} Matrix is symmetric, positive definite

Diagonal terms = sum of mesh Resistances

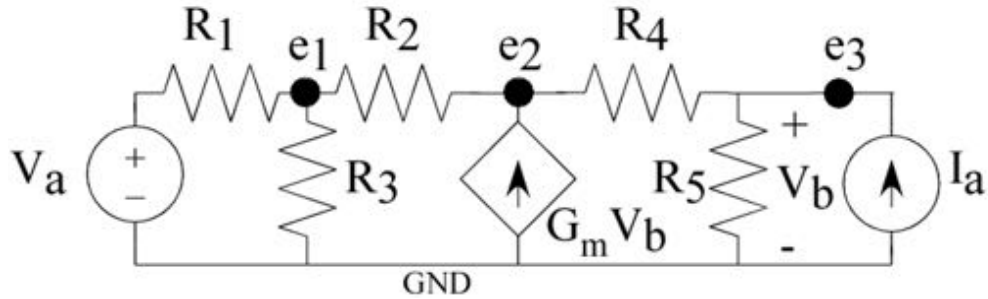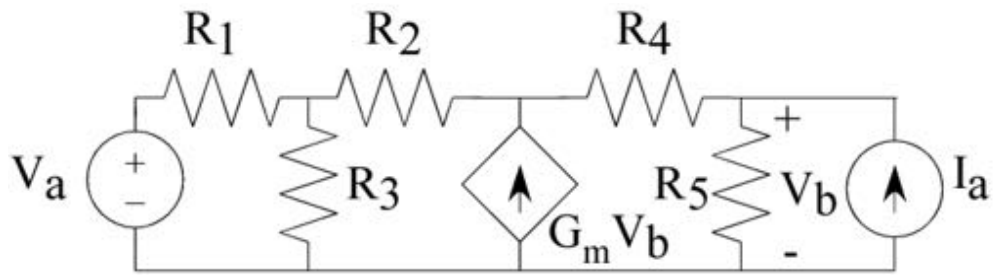Off Diagonal terms = - sum of resistances between meshes



$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_2} & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_4} - G_m \\ 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} \frac{V_a}{R_1} \\ 0 \\ I_a \end{bmatrix}$$

$$R_1 = 1\text{M}\Omega$$

$$R_4 = 1\text{M}\Omega$$

$$R_2 = 1\text{M}\Omega$$

$$R_5 = 2\text{M}\Omega$$

$$R_3 = 2\text{M}\Omega$$



$$G_m = 1/10\text{k}\Omega$$

$$V_a = 1\text{V}$$

$$I_a = 1\mu\text{A}$$

$$\begin{bmatrix} 2.5 & -1 & 0 \\ -1 & 2 & -101 \\ 0 & -1 & 1.5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 1 \end{bmatrix}$$
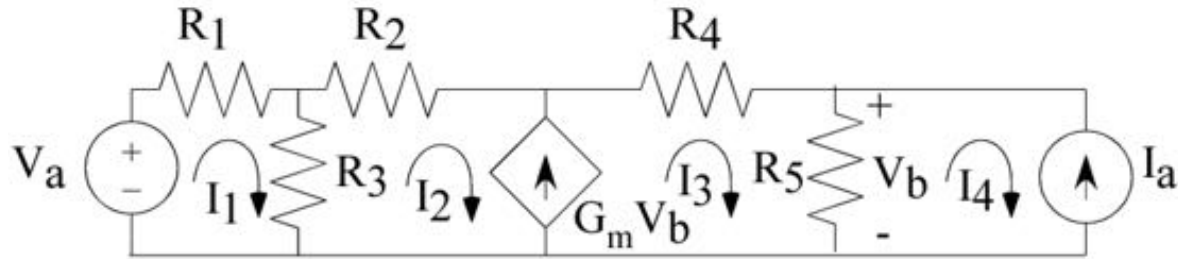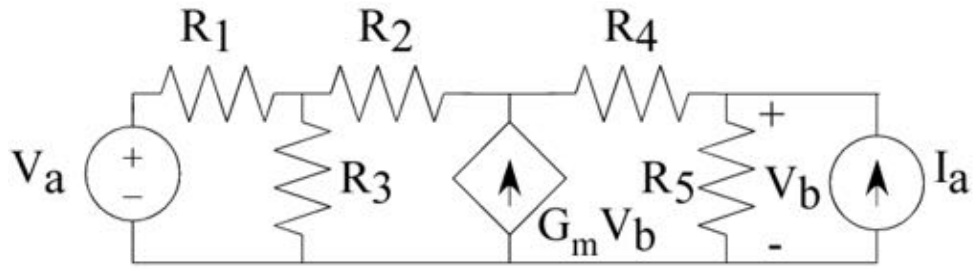
$$\begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} -12.2\text{mV} \\ -1.03\text{V} \\ -20.3\text{mV} \end{bmatrix}$$



$$V_b = R_5(I_3 - I_4)$$

$$I_4 = -I_a \quad I_3 - I_2 = G_m R_5(I_3 - I_4)$$

$$I_2 + (G_m R_5 - 1)I_3 - (G_m R_5)I_4 = 0$$

$$\begin{bmatrix} R_1 + R_3 & -R_3 & 0 & 0 \\ -R_3 & R_2 + R_3 & R_4 + R_5 & -R_5 \\ 0 & 1 & G_m R_5 - 1 & -G_m R_5 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} V_a \\ 0 \\ 0 \\ -I_a \end{bmatrix}$$

Dependent Source Constraint


Supermesh

$$\begin{matrix} R_1 = 1\text{M}\Omega & R_4 = 1\text{M}\Omega \\ R_2 = 1\text{M}\Omega & R_5 = 2\text{M}\Omega \\ R_3 = 2\text{M}\Omega & G_m = 1/10\text{k}\Omega \end{matrix} \begin{bmatrix} 3 & -2 & 0 & 0 \\ -2 & 3 & 3 & -2 \\ 0 & 1 & 199 & -200 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} V_a \\ 0 \\ 0 \\ -I_a \end{bmatrix}$$

I_1 through I_4 : μA units

$$V_a = 1\text{V}, I_a = 1\mu\text{A}$$
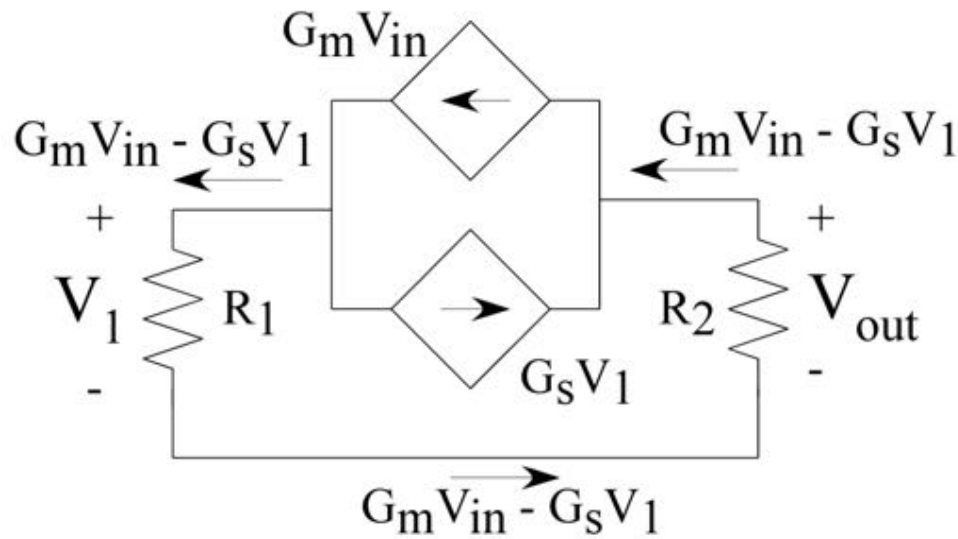
$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} 73.7\text{nA} \\ 389\text{nA} \\ 1.007\mu\text{A} \\ 1\mu\text{A} \end{bmatrix}$$



$$V_1 = R_1(G_m V_{in} - G_s V_1)$$

$$V_1 = V_{in} \frac{G_m R_1}{1 + G_s R_1}$$

$$V_{out} = -R_2(G_s V_1 - G_m V_{in})$$

$$V_{out} = -G_m R_2 \left(\frac{G_s R_1}{1 + G_s R_1} - 1 \right) V_{in}$$

$$V_{out} = -V_{in} \frac{G_m R_2}{1 + G_s R_1}$$

$$R_1 = 10\text{k}\Omega$$


$$R_2 = 100\text{k}\Omega$$


$$G_m = 1/200\Omega$$

$$G_s = 1/100\Omega$$

$$V_1 = (50/101) V_{in} \sim 0.5 V_{in}$$
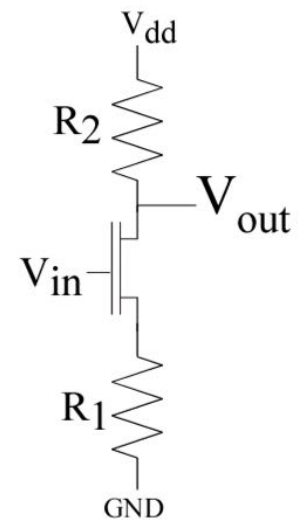
$$V_{out} = -(500/101) V_{in} \sim -5 V_{in}$$



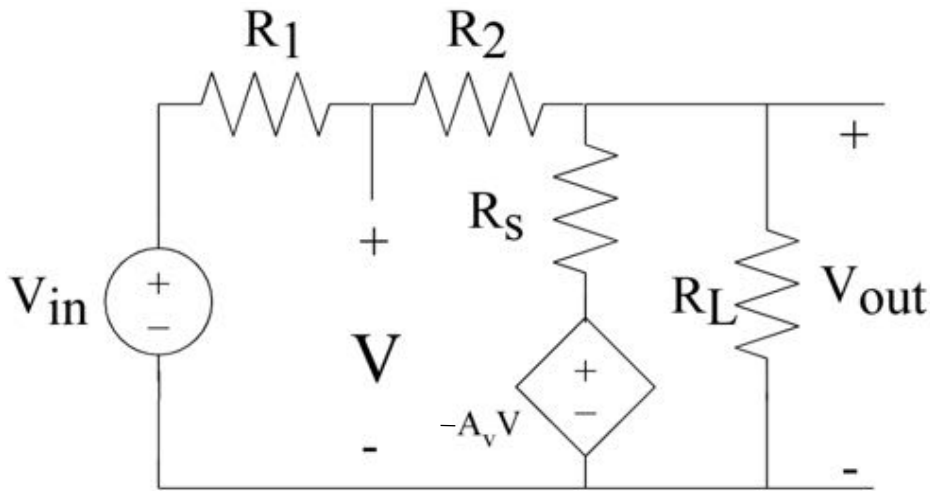

$$\frac{V_{in} - V}{R_1} = \frac{V - V_{out}}{R_2} = \frac{V_{out} + A_v V}{R_s} + \frac{V_{out}}{R_L}$$

If $R_s = 0$, $V_{out} = -A_v V$

$$\frac{R_2}{R_1} \left(V_{in} + \frac{V_{out}}{A_v} \right) = - \left(\frac{1}{A_v} + 1 \right) V_{out}$$

$$V_{out} \left(1 + \frac{1}{A_v} \left(1 + \frac{R_2}{R_1} \right) \right) = - \frac{R_2}{R_1} V_{in}$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1} \frac{1}{1 + \frac{1}{A_v} \left(1 + \frac{R_2}{R_1} \right)}$$

$$\begin{aligned} R_1 &= 10\text{k}\Omega & R_L &= 1\text{k}\Omega \\ R_2 &= 100\text{k}\Omega & A_v &= 100,000 \end{aligned}$$


$$V_{out} = -V_{in} (9.999) \sim -10V_{in}$$

$$V \left(-\frac{A_v}{R_s} + \frac{1}{R_2} \right) = \frac{V_{out}}{R_s // R_2 // R_L}$$


$$R_s \ll R_2, R_L$$

$$-V A_v / R_s = V_{out} / R_s$$

$$V_{out} = -A_v V$$

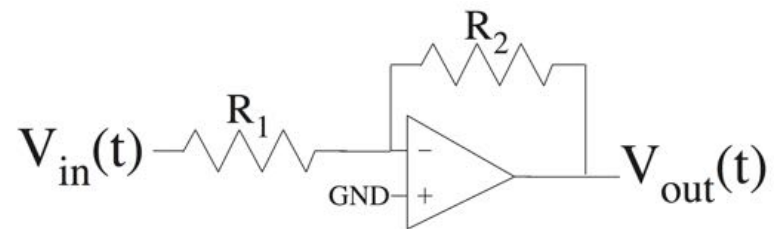

State Holding Divider Circuits

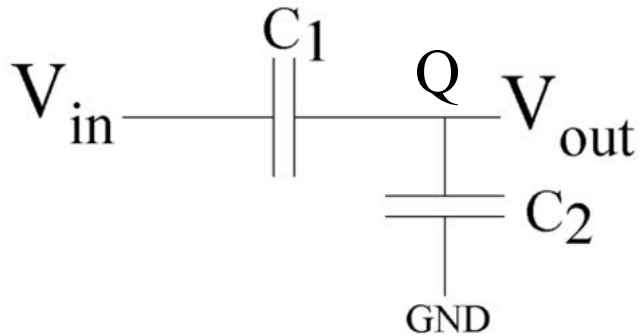

Maybe like
 Conductances: $V_{out} = V_{in} \frac{C_1}{C_1 + C_2}$?

$$V_{in} = 0, V_{out} = \frac{Q}{C_1 + C_2}$$


$$Q_1 = C_1(V_{in} - V_{out})$$

$$Q_2 = C_2 V_{out}$$

Total charge ($Q - \overbrace{Q_1}^{\text{Negative Plate}} + \overbrace{Q_2}^{\text{Positive Plate}}$) at V_{out} is fixed


$$V_{out} = V_{in} \frac{C_1}{C_1 + C_2} + V_{offset}$$

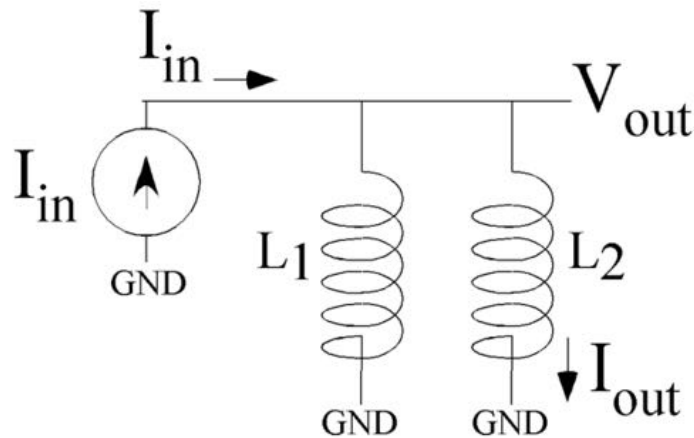Similar case with Inductors
 (current divider, offset I):



$$I_{out} = I_{in} \frac{L_1}{L_1 + L_2} + I_{offset}$$

Resistive Current Divider


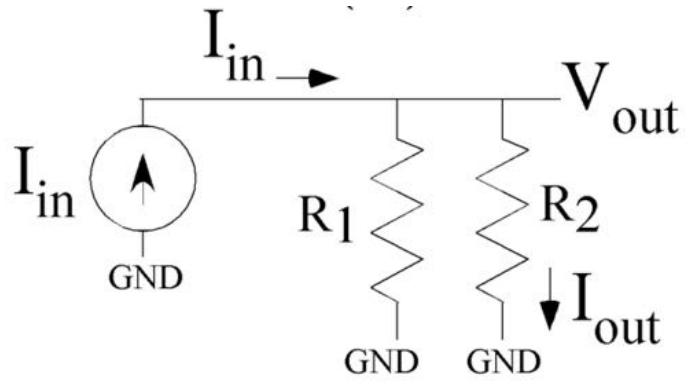


$$V_{out} = I_{in}(R_1 // R_2)$$


$$I_{out} = \frac{V_{out}}{R_2} = I_{in} \frac{R_1 // R_2}{R_2}$$

$$a // b = \frac{1}{\frac{1}{a} + \frac{1}{b}}$$

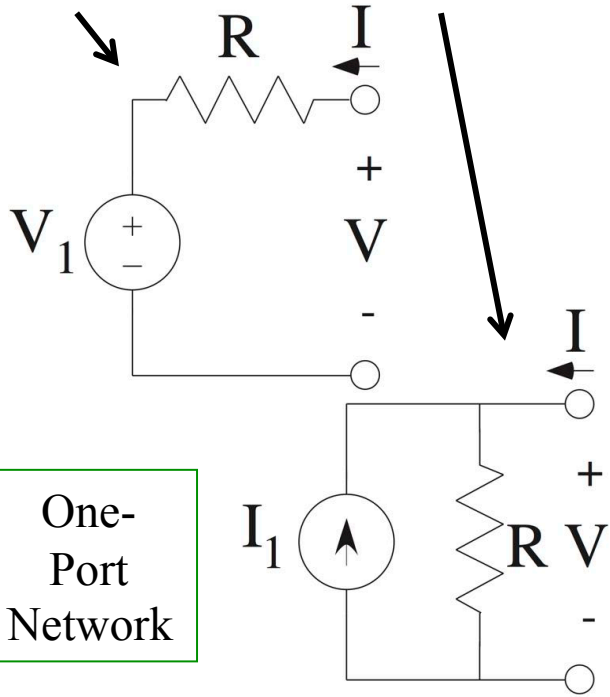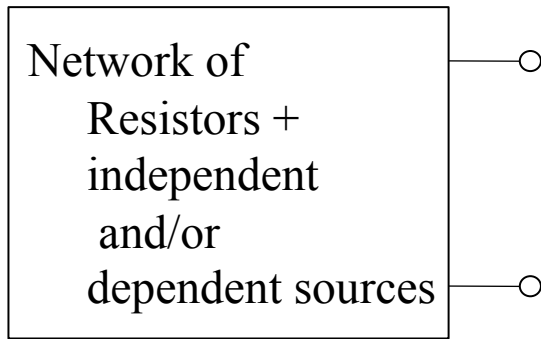
$$V_{out} = V_{in} \frac{R_1}{R_1 + R_2}$$



Thevenin One-Port

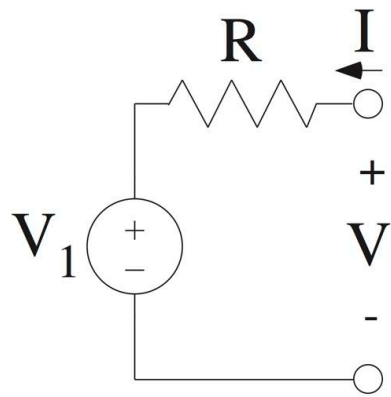






Norton One-Port

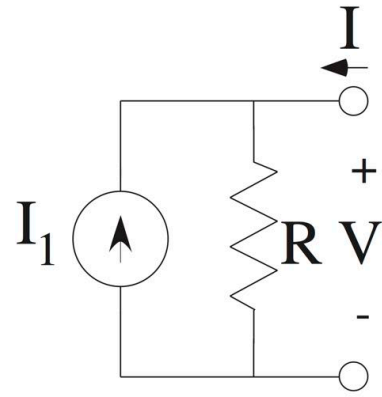


$$I_1 \rightarrow V_1/R$$

$$V_1 \rightarrow RI_1$$

Using Thevenin-Norton Equivalents

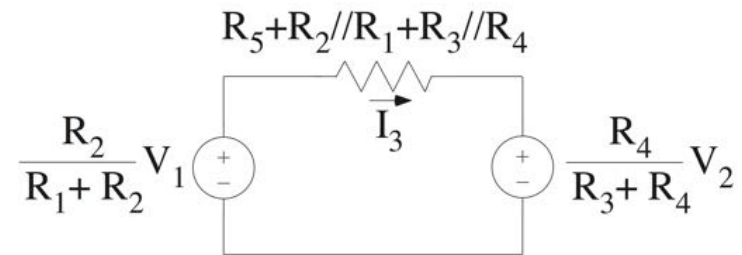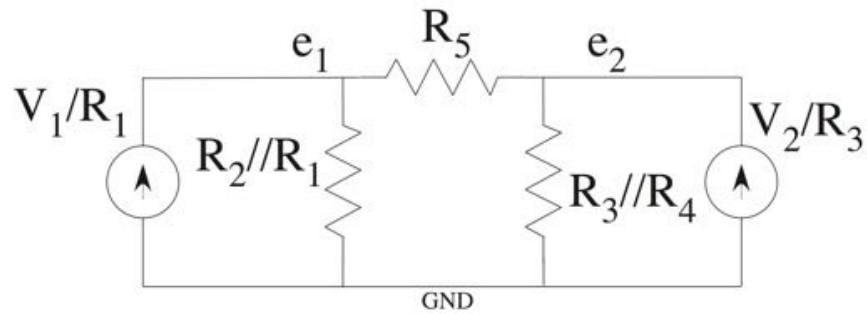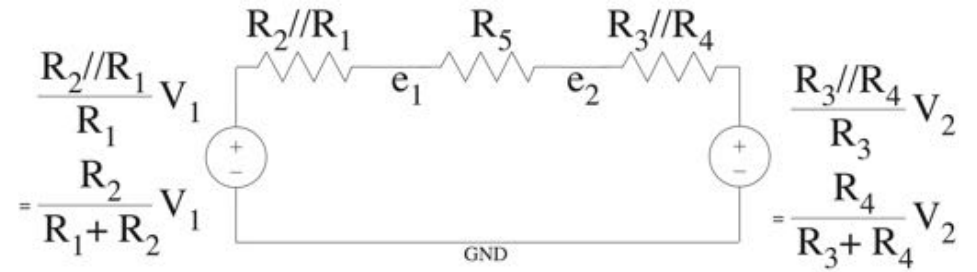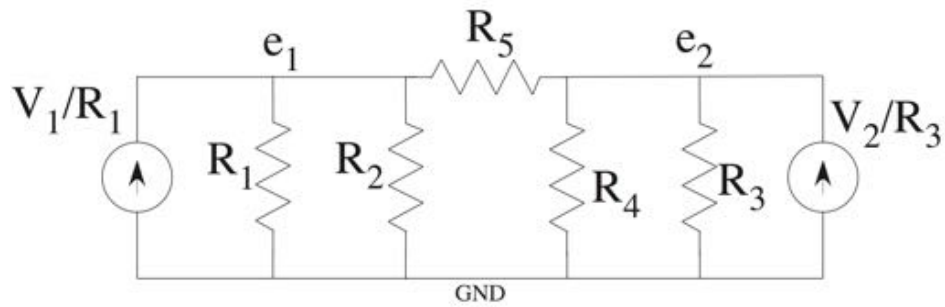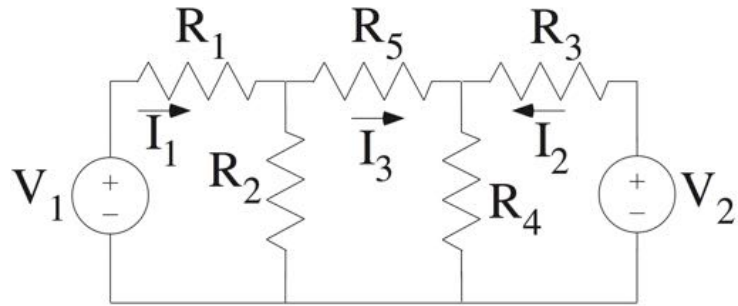


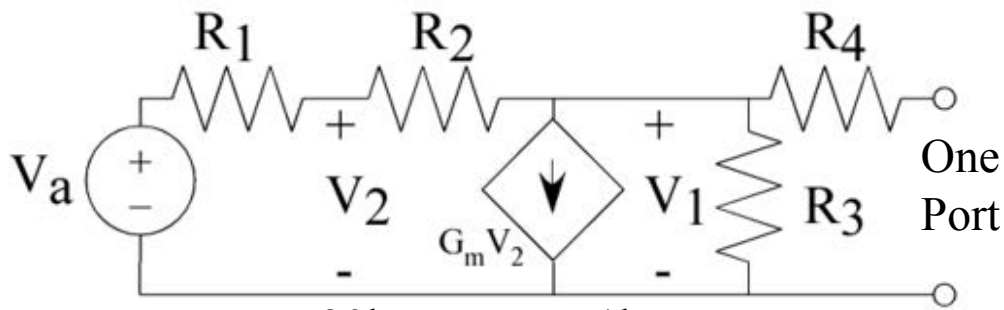



$$R_1 = 20\text{k}\Omega \quad R_3 = 1\text{k}\Omega$$

$$R_2 = 20\text{k}\Omega \quad R_4 = 1\text{k}\Omega \quad G_m = 1 / 500\Omega$$

Voltage Source = 0 (R out)

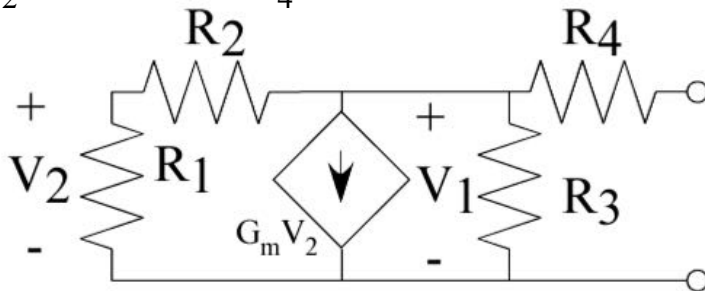

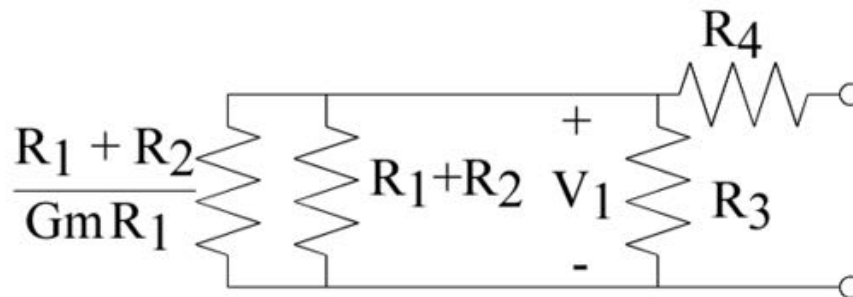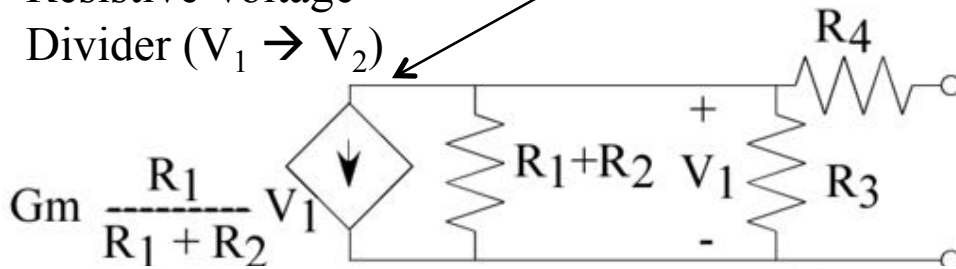Resistive Voltage Divider ($V_1 \rightarrow V_2$)



$$R_{eff} = R_4 + R_3 // \left(\frac{R_1 + R_2}{R_1} \frac{1}{G_m} \right) // (R_1 + R_2) \longrightarrow R_{eff} = 1.5\text{k}\Omega$$

V_{eff} : Measure output. No output I (R_4 has no effect)

KCL at V_2 & V_1

$$\frac{V_a - V_2}{R_1} = \frac{V_2 - V_1}{R_2} = \frac{V_1}{R_3} + G_m V_2$$


$$\frac{V_a}{R_1} + \frac{V_1}{R_2} = \frac{V_2}{R_1 // R_2}$$

$$\longrightarrow V_a + V_1 = 2V_2$$

$$V_2 \left(\frac{1}{R_2} - G_m \right) = \frac{V_1}{R_2 // R_3}$$

$$\longrightarrow -2V_2 = V_1$$

$$V_{eff} = V_1 = \frac{V_a}{2}$$

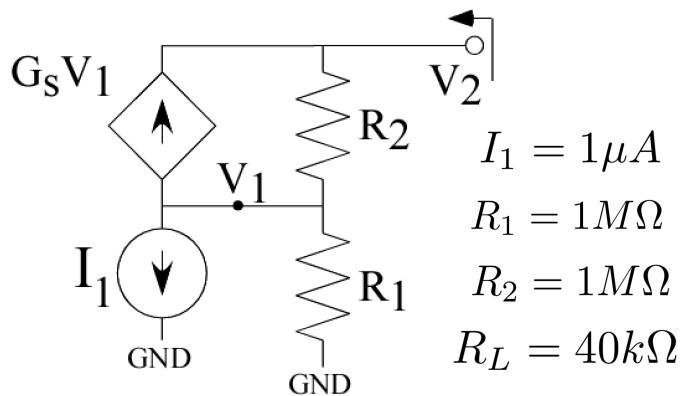

Two cases


$G_s = 0$

Norton-Thevenin at V_1

$V_{eff} = -I_1 R_1 = -1V$

$R_{eff} = R_1 + R_2 = 2M\Omega$

$I_{eff} = -0.5\mu A$

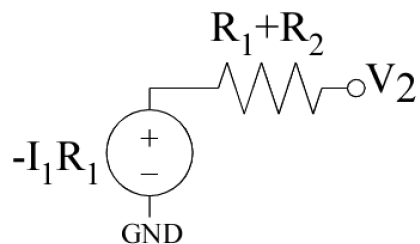

$G_s = 1/1k\Omega$

I_{eff} : $V_2 = GND$ (measure I @ V_2)

$I_1 + V_1 \left(G_s + \frac{1}{R_1 + R_2} \right) \approx I_1 + V_1 G_s = 0$

$V_1 = -I_1 / G_s = -1mV$

$I_{eff} \approx 1\mu A$



R_{eff} : $I_1 = 0$

$R = \frac{V_2}{I} = \frac{V_2 V_1}{V_1 I}$


$V_1 \left(G_s + \frac{1}{R_1 + R_2} \right) = \frac{V_2}{R_2}$

$V_1 = V_2 \frac{1}{G_s R_2}$

$R = (G_s R_2) R_1 \quad (1G\Omega)$

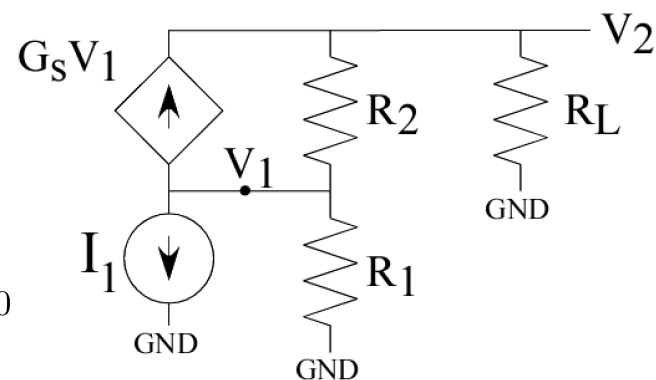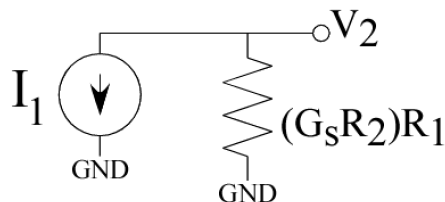


$G_s = 0$

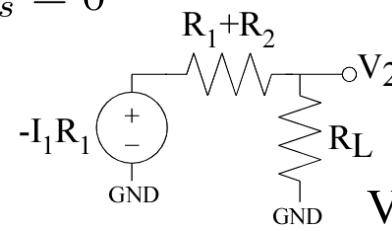


$V_2 = -20mV$

$G_s = 1/1k\Omega$

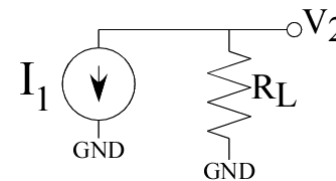

$V_2 = -40mV$

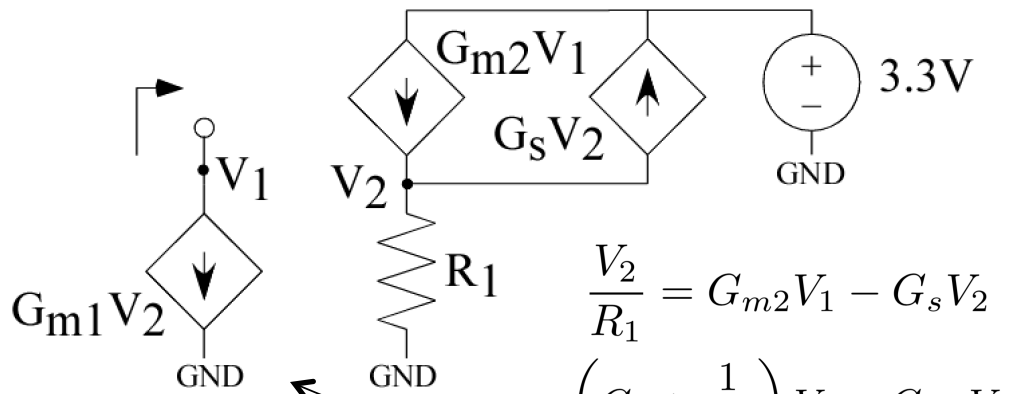

$$\frac{V_2}{R_1} = G_{m2}V_1 - G_sV_2$$

$$\left(G_s + \frac{1}{R_1}\right)V_2 = G_{m2}V_1$$

$$V_2 \approx \frac{G_{m2}}{G_s}V_1$$

Resistor: $\frac{1}{\frac{G_{m1}}{G_s}}$

no Thevenin voltage source

$$G_{m2} = 1/2k\Omega$$

$$G_s = 1/1k\Omega$$

$$G_{m1} = 1/200k\Omega$$

$$R_1 = 1M\Omega$$

Resistor: 400k Ω


$$G_{m2} = 1/20k\Omega$$

$$G_s = 1/10k\Omega$$

$$G_{m1} = 1/10M\Omega$$

$$R_1 = 10M\Omega$$

Resistor: 20M Ω

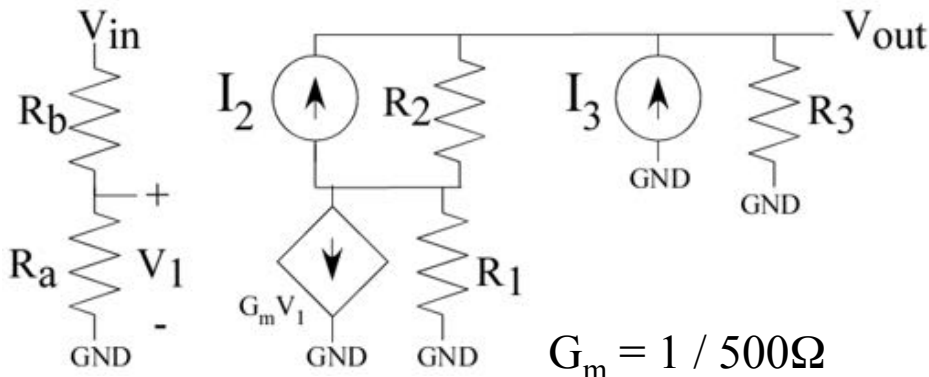

$$R_1 = 2\text{k}\Omega$$

$$R_a = 1\text{k}\Omega$$

$$I_2 = 2\text{mA}$$



$$R_2 = 2\text{k}\Omega$$

$$R_b = 1\text{k}\Omega$$

$$I_3 = 1\text{mA}$$

$$R_3 = 4\text{k}\Omega$$

$$G_m = 1 / 500\Omega$$

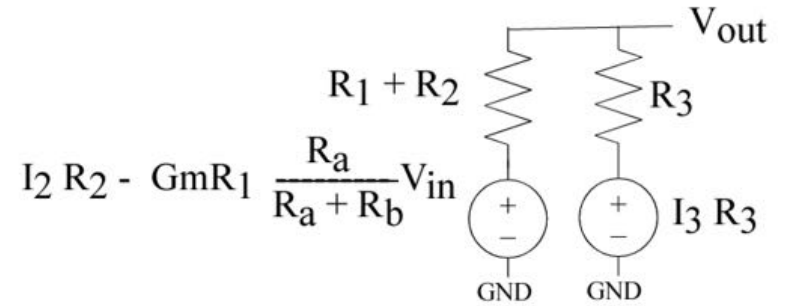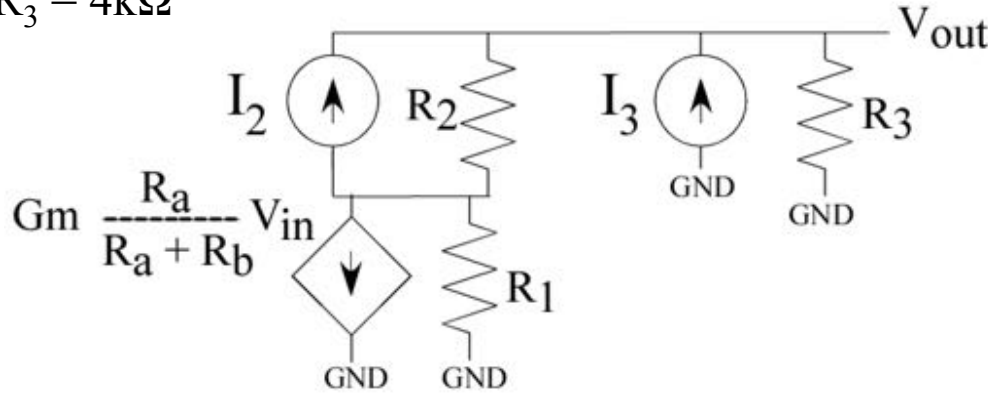

$$V_{out} = \left(I_2 R_2 - G_m R_1 \frac{R_a}{R_a + R_b} V_{in} \right) \left(\frac{R_3}{R_1 + R_2 + R_3} \right) + I_3 R_3 \left(\frac{R_1 + R_2}{R_1 + R_2 + R_3} \right)$$


$$G_m R_1 \frac{R_a}{R_a + R_b} = 4 \left(\frac{1}{2} \right) = 2 \quad I_2 R_2 = 4\text{V}$$


$$R_1 + R_2 + R_3 = 8\text{k}\Omega$$

$$I_3 R_3 = 4\text{V}$$

$$V_{out} = (4\text{V} - 2V_{in}) \left(\frac{1}{2} \right) + 4\text{V} \left(\frac{1}{2} \right)$$

$$V_{out} = 4\text{V} - V_{in}$$

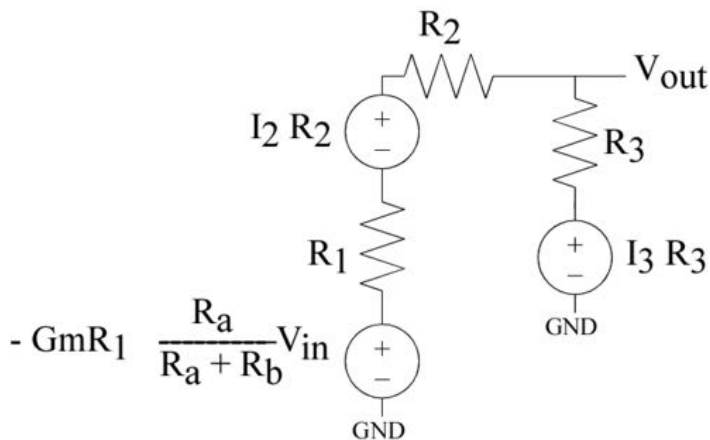

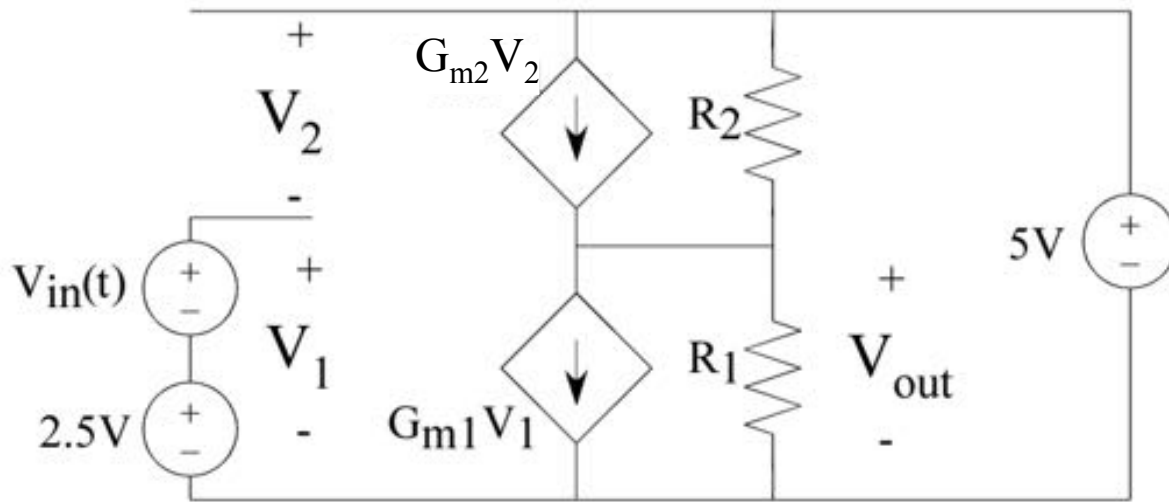

$$V_1 = V_{in} + 2.5, V_2 = 5 - V_1 = 2.5 - V_{in}$$

Solve using superposition:

Case I: 2.5V & 5V source, Case II: V_{in} source

Case I: $V_1 = V_2 = 2.5V$

$$\frac{V_{out}}{R_1} = (G_{m2} - G_{m1})2.5V + \frac{5V - V_{out}}{R_2}$$

$$V_{out} = (R_1 // R_2) ((G_{m2} - G_{m1})2.5V + 5V/R_2)$$

Case II: $V_1 = -V_2 = V_{in}$

$$-(G_{m1} + G_{m2})V_{in} = \frac{V_{out}}{R_1 // R_2}$$

$$\frac{V_{out}}{V_{in}} = -(G_{m1} + G_{m2})(R_1 // R_2)$$

$$R_1 = 100k\Omega$$

$$R_2 = 200k\Omega$$


$$G_{m1} = 1k\Omega$$


$$G_{m2} = 1k\Omega$$

Case I: $V_{out} = 1.67V$

Case II: $V_{out} = -133V_{in}$

CMOS Inverter

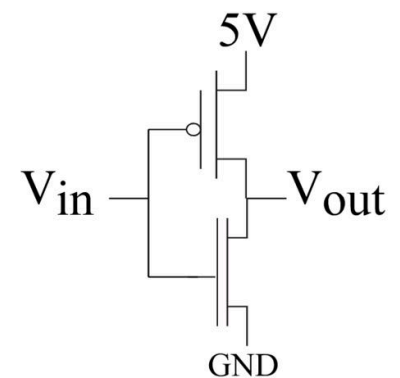

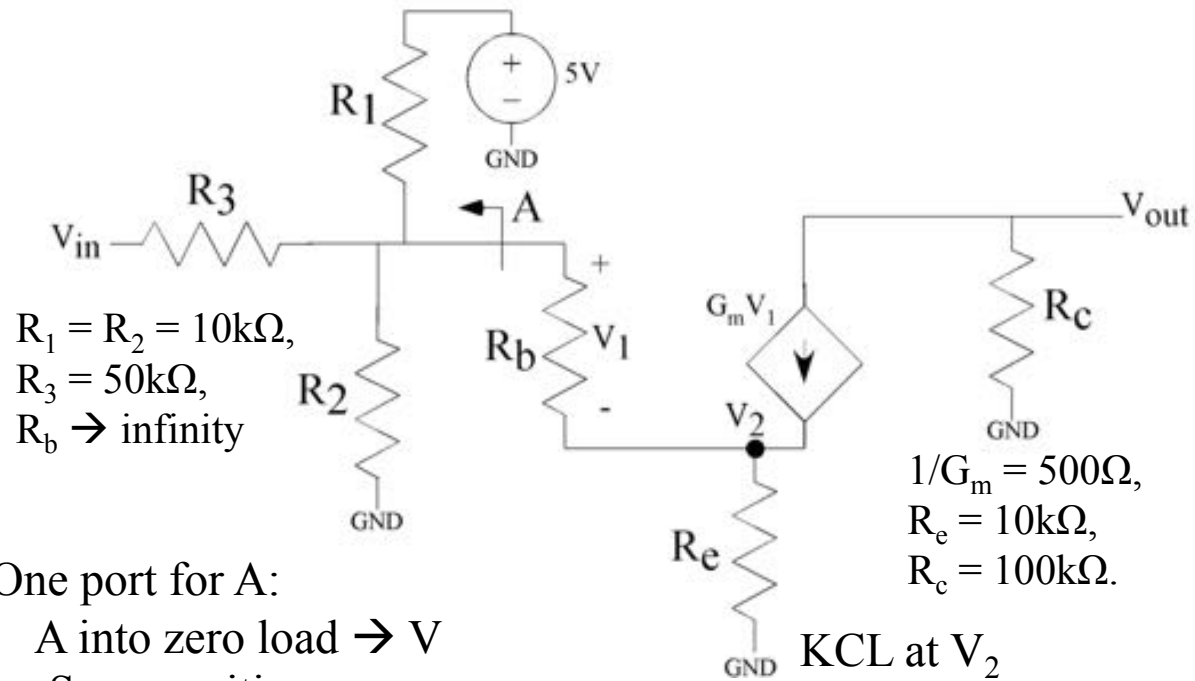

$R_1 = R_2 = 10\text{k}\Omega,$
 $R_3 = 50\text{k}\Omega,$
 $R_b \rightarrow \text{infinity}$

$1/G_m = 500\Omega,$
 $R_e = 10\text{k}\Omega,$
 $R_c = 100\text{k}\Omega.$

One port for A:

A into zero load $\rightarrow V$

Superposition:

$$V_A = \frac{R_1 // R_2 // R_3}{R_1} 5V$$

$$V_A = \frac{R_1 // R_2 // R_3}{R_3} V_{in}$$

$$V_{eq} = (R_1 // R_2 // R_3) \left(\frac{V_{in}}{R_3} + \frac{5V}{R_1} \right)$$

(= 0.091 V_{in} + 2.25V)

$$R_{eq} = R_1 // R_2 // R_3 \quad (4.5\text{k}\Omega)$$

KCL at V_2

$$G_m V_1 = \frac{V_A - V_1}{R_e}$$

$$(1 + G_m R_e) V_1 = V_A$$


$$(21 V_1 = V_A)$$

KCL at V_{out}

$$V_{out} = G_m R_c V_1$$

($V_{out} = 200 V_1$)

$$(V_{out} = 9.52 V_A)$$

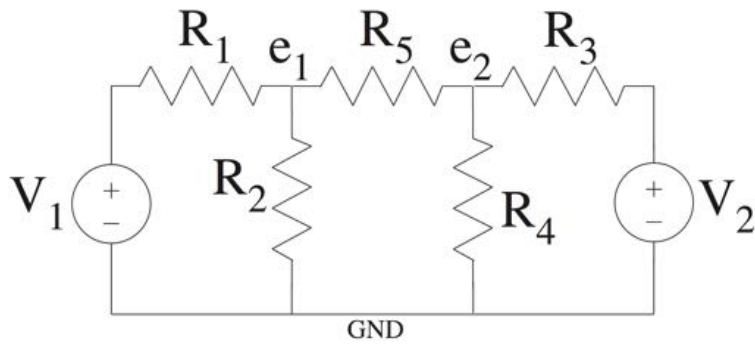

Superposition:

Can turn each source on separately,
add the results

A linear function, $f(\)$,

$$f(Ax + By) = A f(x) + B f(y)$$

V_1 on, $V_2 = 0$: (Resistive Divider)

$$e_1 = \frac{R_2 // (R_5 + R_3 // R_4)}{R_1 + R_2 // (R_5 + R_3 // R_4)} \quad V_1$$

$$e_2 = e_1 \frac{R_3 // R_4}{R_5 + R_3 // R_4}$$


V_2 on, $V_1 = 0$:

$$e_2 = \frac{R_4 // (R_5 + R_1 // R_2)}{R_3 + R_4 // (R_5 + R_1 // R_2)} \quad V_2$$

$$e_1 = e_2 \frac{R_1 // R_2}{R_5 + R_1 // R_2}$$

$$e_1 = \frac{R_2 // (R_5 + R_3 // R_4)}{R_1 + R_2 // (R_5 + R_3 // R_4)} V_1 + \frac{R_4 // (R_5 + R_1 // R_2)}{R_3 + R_4 // (R_5 + R_1 // R_2)} \frac{R_1 // R_2}{R_5 + R_1 // R_2} V_2$$
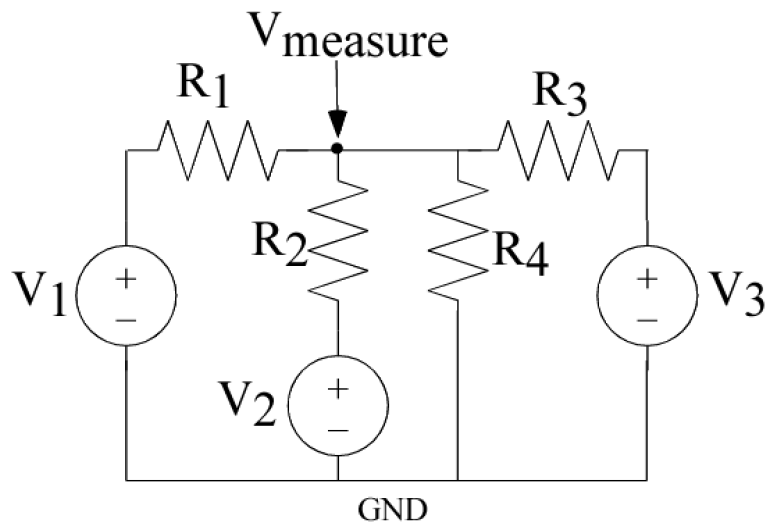
$$e_2 = \frac{R_4 // (R_5 + R_1 // R_2)}{R_3 + R_4 // (R_5 + R_1 // R_2)} V_2 + \frac{R_2 // (R_5 + R_3 // R_4)}{R_1 + R_2 // (R_5 + R_3 // R_4)} \frac{R_3 // R_4}{R_5 + R_3 // R_4} V_1$$




$$R_1 = 1k\Omega$$

$$R_2 = 2k\Omega$$


$$R_3 = 4k\Omega$$

$$R_4 = 4k\Omega$$

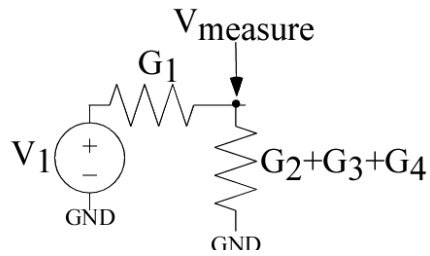
$$V_{measure} = \frac{G_1 V_1 + G_2 V_2 + G_3 V_3}{G_1 + G_2 + G_3 + G_4}$$


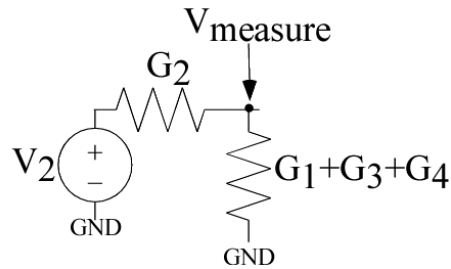
$$V_{measure} = \frac{G_1}{G_1 + G_2 + G_3 + G_4} V_1$$



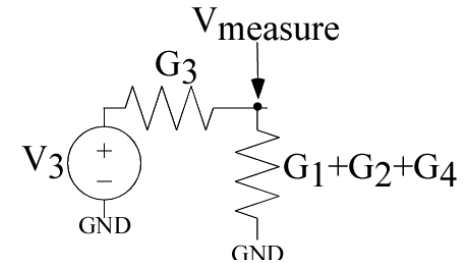
$$V_{measure} = \frac{G_2}{G_1 + G_2 + G_3 + G_4} V_2$$



$$V_{measure} = \frac{G_3}{G_1 + G_2 + G_3 + G_4} V_3$$

$$V_{measure} = \frac{1}{2} V_1 + \frac{1}{4} V_2 + \frac{1}{8} V_3$$
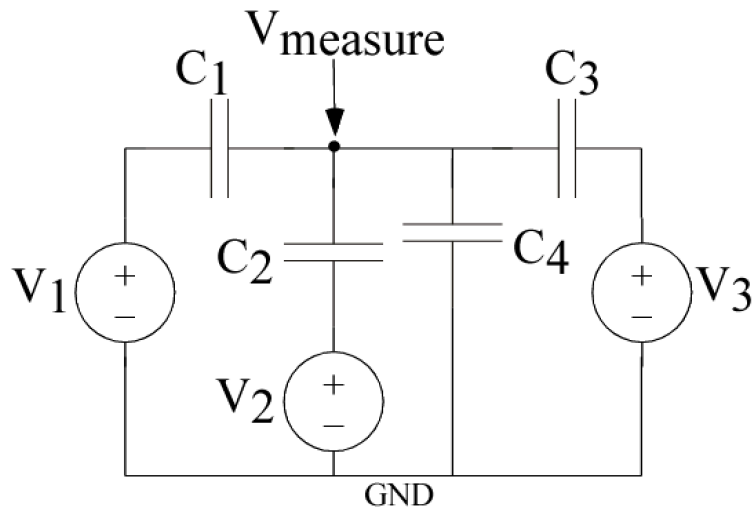
$$V_1 = V_2 = V_3 = 2V, \text{ what is } V_{measure} ? \quad 1.75V$$




$$C_1 = 4\text{pF}$$

$$C_2 = 2\text{pF}$$


$$C_3 = 1\text{pF}$$

$$C_4 = 1\text{pF}$$

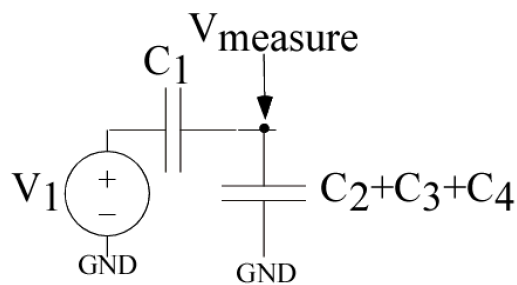
$$V_{measure} = \frac{C_1 V_1 + C_2 V_2 + C_3 V_3}{C_1 + C_2 + C_3 + C_4} + V_{offset}$$


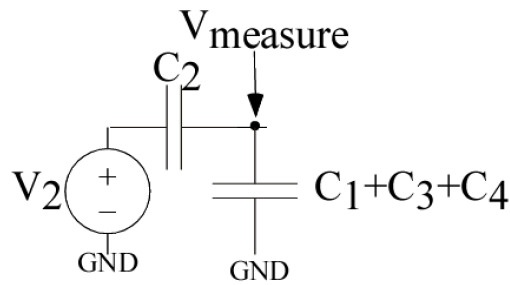
$$V_{measure} = \frac{C_1}{C_1 + C_2 + C_3 + C_4} V_1 + V_{offset}$$


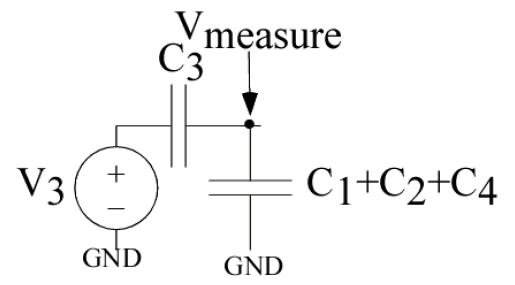
$$V_{measure} = \frac{C_2}{C_1 + C_2 + C_3 + C_4} V_2 + V_{offset}$$











$$V_{measure} = \frac{C_3}{C_1 + C_2 + C_3 + C_4} V_3 + V_{offset}$$

$$V_{measure} = \frac{1}{2} V_1 + \frac{1}{4} V_2 + \frac{1}{8} V_3 + V_{offset}$$





$$V_{measure} = 0.5\text{V when } V_1, V_2, V_3 = 0\text{V,}$$
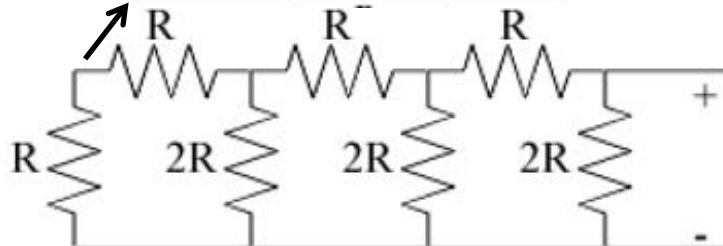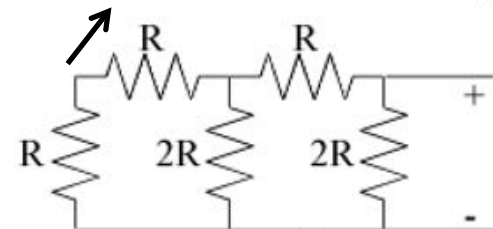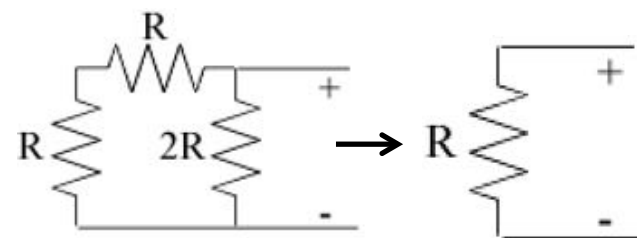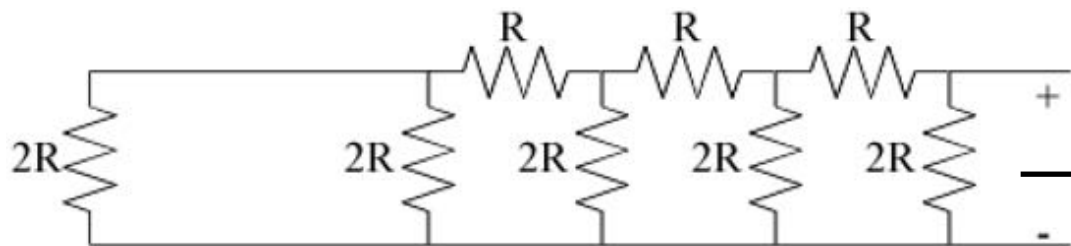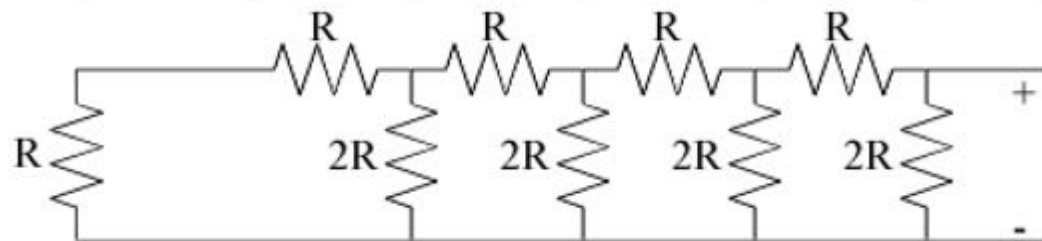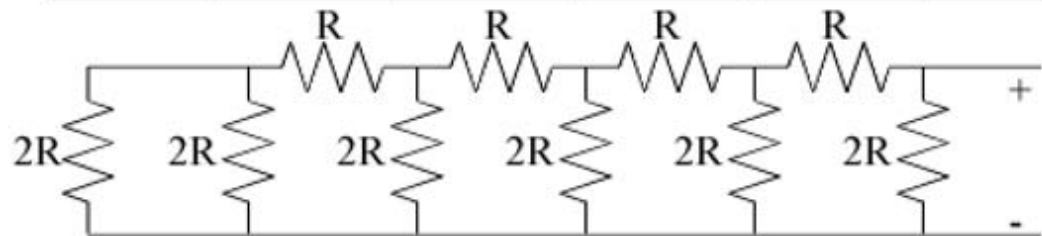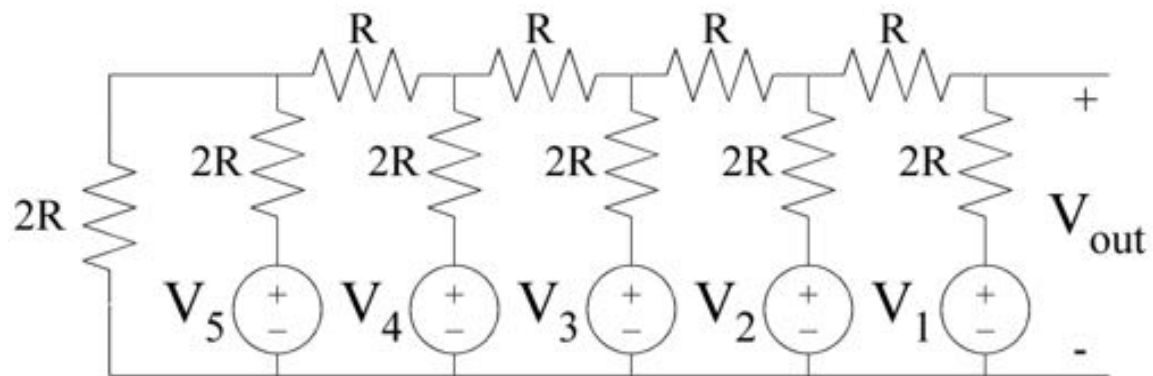
$$V_1 = V_2 = V_3 = 2\text{V, what is } V_{measure} ? \quad 2.25\text{V}$$





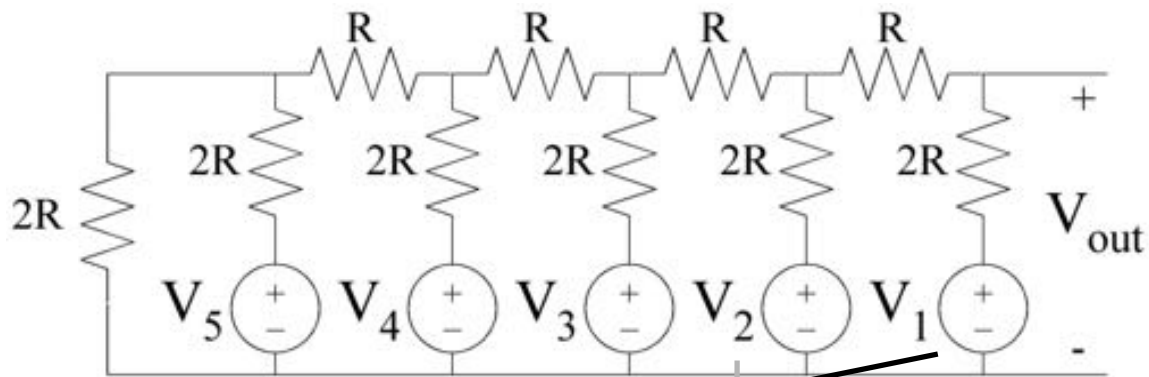


Superposition

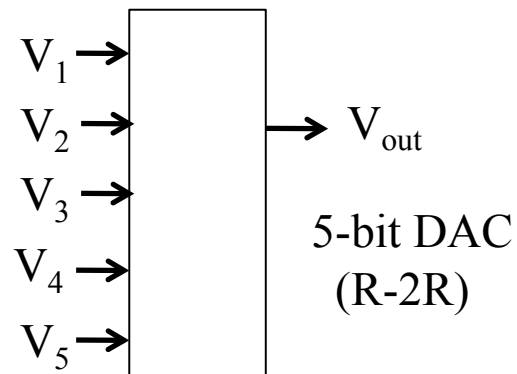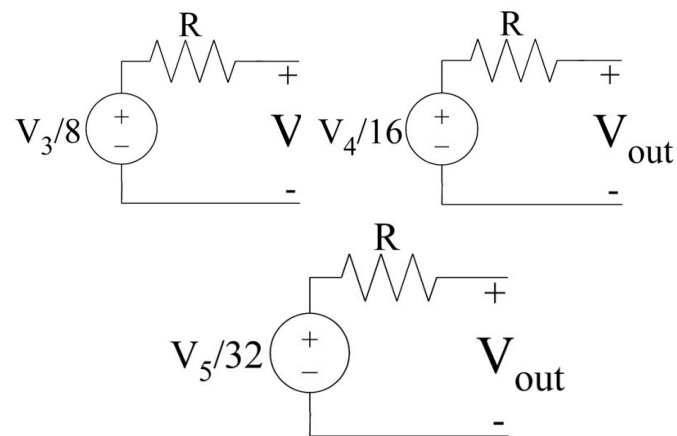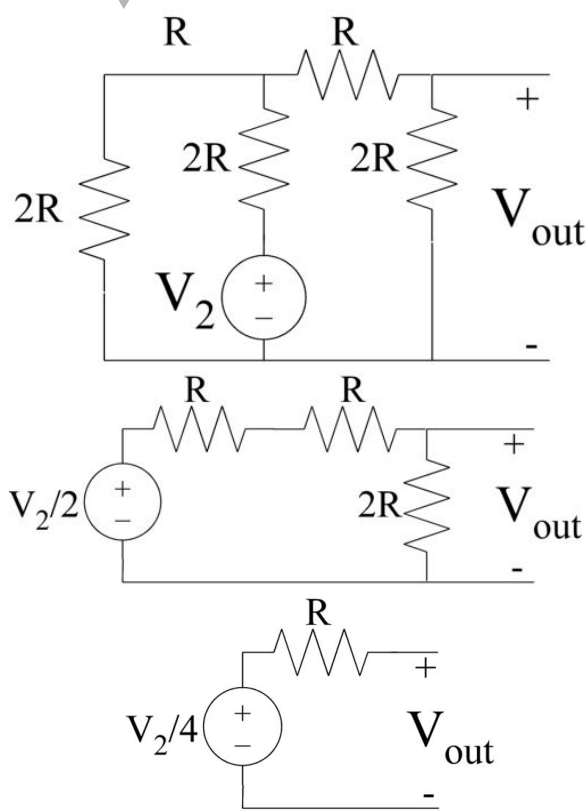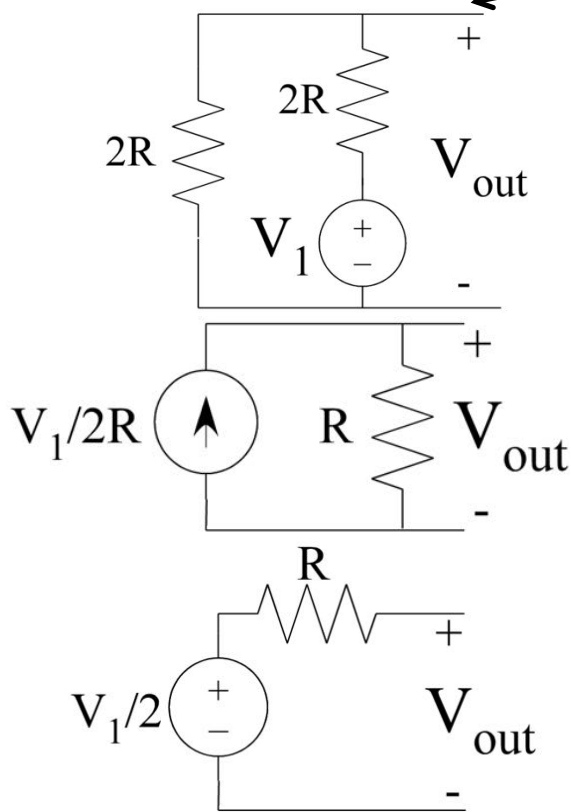

Symmetric Resistive Circuits

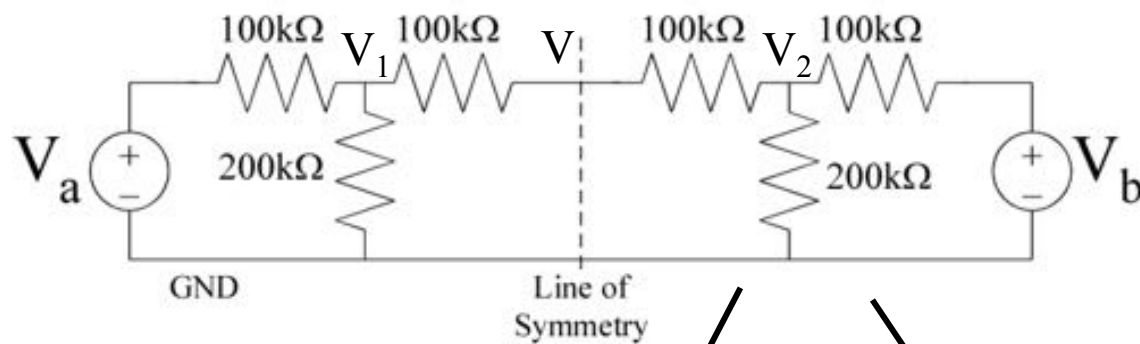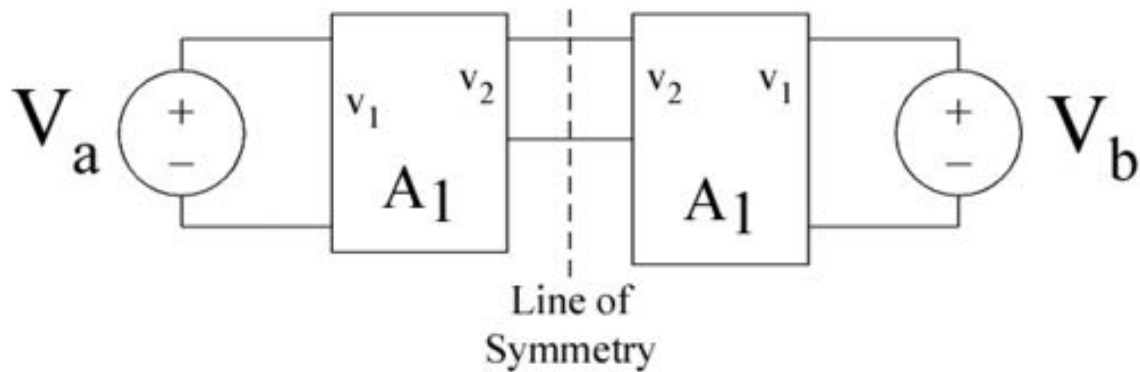


Common-Mode Circuit

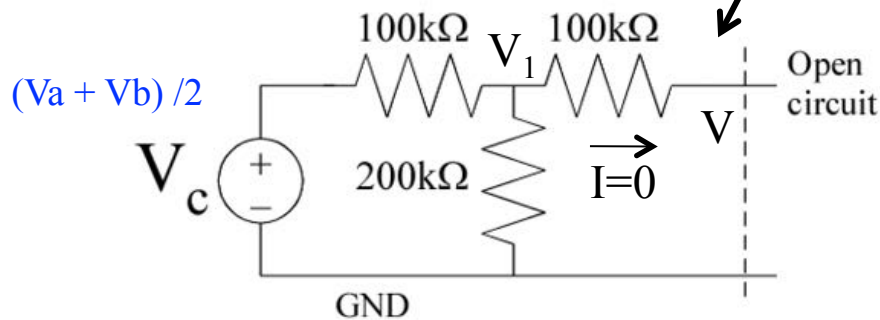

Voltage Divider: $V = V_1 = V_2 = (2/3) V_c$


$$V_c = \text{average}(V_1, V_2) = \frac{(V_1 + V_2)/2}{(V_a + V_b)/2}$$

Differential-Mode Circuit

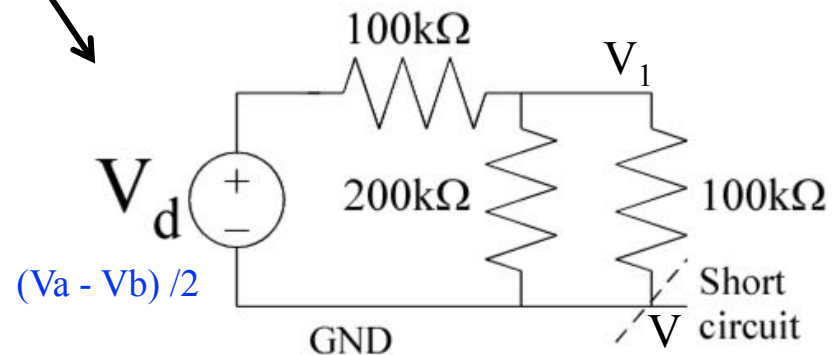

Voltage Divider: $V = V_1 = -V_2 = (2/5) V_d$

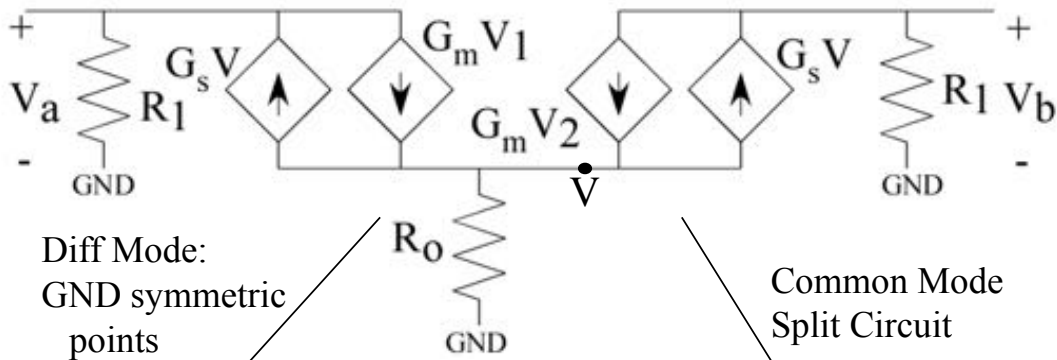
$$V_d = \frac{(V_1 - V_2)/2}{(V_a - V_b)/2}$$



Diff Mode:
GND symmetric
points

Common Mode
Split Circuit

Diff Mode Half Circuit

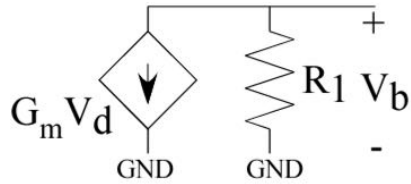


$$V_b = -G_m R_1 V_d$$

$$V_a = -5 V_d$$

$$V_d = (V_1 - V_2) / 2$$

Common Mode Half Circuit

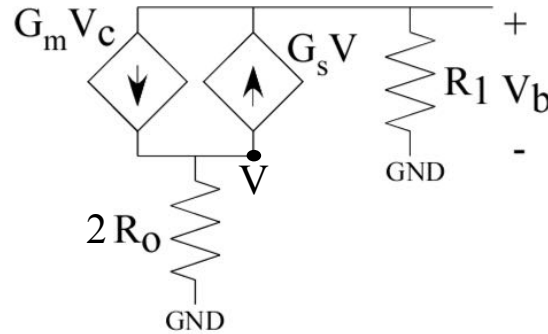

$$V_a = -0.00025 V_c - 5 V_d$$

$$V_b = -0.00025 V_c + 5 V_d$$


$$R_o = 10\text{M}\Omega \quad G_m = 1/2\text{k}\Omega$$

$$R_1 = 10\text{k}\Omega \quad G_s = 1/1\text{k}\Omega$$

$$\frac{V}{2R_o} = G_m V_c - G_s V = -\frac{V_b}{R_1}$$

$$V \left(G_s + \frac{1}{2R_o} \right) = G_m V_c \quad V = \frac{2R_o G_m}{2R_o G_s + 1} V_c$$
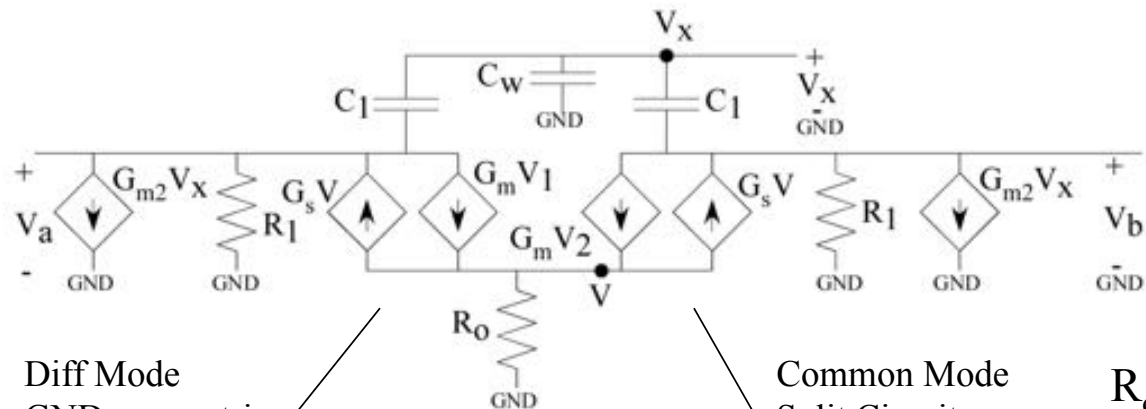
$$V_b = -\frac{R_1}{2R_o} \frac{2R_o G_m}{2R_o G_s + 1} V_c \sim -0.00025 V_c$$



Diff Mode
GND symmetric
points

Common Mode
Split Circuit


$$R_o = 10\text{M}\Omega \quad C_1 = 1\text{pF} \quad G_m = 1/2\text{k}\Omega$$

$$R_1 = 80\text{k}\Omega \quad C_w = 2\text{pF} \quad G_s = 1/1\text{k}\Omega$$

$$G_{m2} = 1/2\text{k}\Omega$$


Diff Mode Half Circuit

Common Mode Half Circuit

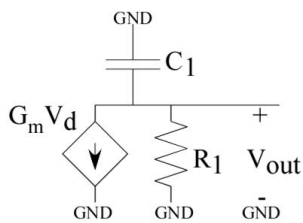

$$V_b = -G_m R_1 V_d$$

$$= -40 V_d$$

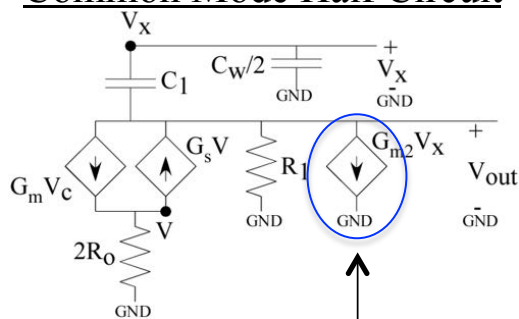

$$R: \frac{1}{G_m 2} \frac{C_w/2 + C_1}{C_1} \rightarrow 4\text{k}\Omega \ll R_1$$

$$\frac{V}{2R_o} = G_m V_c - G_s V$$

$$V \left(G_s + \frac{1}{2R_o} \right) = G_m V_c$$

$$V = \frac{2R_o G_m}{2R_o G_s + 1} V_c$$


$$\sim 0.5 V_c$$

$$\frac{V}{2R_o} = -\frac{V_b}{R}$$


$$V_b = -\frac{R}{2R_o} V$$

$$= -\frac{R}{4R_o} V_c$$

$$= -0.0001 V_c$$

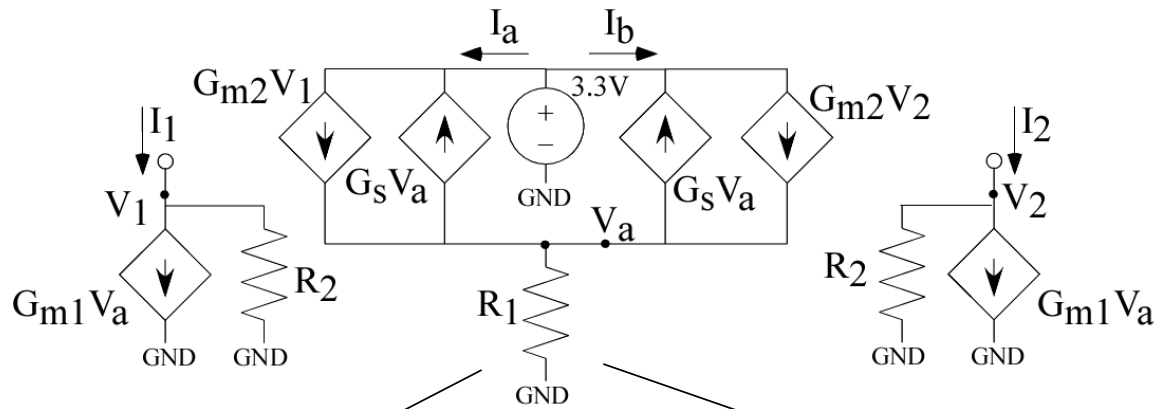


Diff Mode

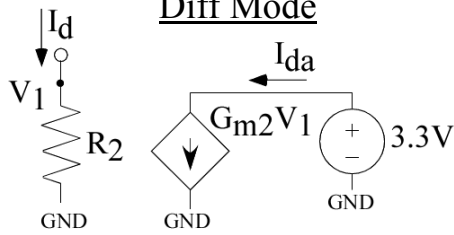

$$I_{da} = G_{m2}V_1 = (G_{m2}R_2)I_d$$

$$I_{da} = 100I_d$$

Common Mode

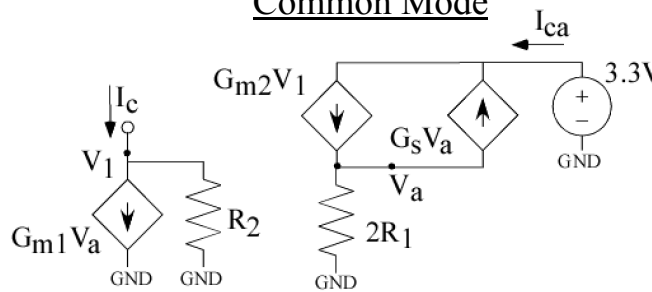

$$I_c = G_{m1}V_a + \frac{V_1}{R_2}$$

$$I_c = V_a \left(G_{m1} + \frac{G_s}{G_{m2}} \frac{1}{R_2} \right)$$

$$I_c \approx G_{m1}V_a$$

$$G_{m2}V_1 = \frac{V_a}{2R_1} + G_sV_a$$

$$G_{m2}V_1 = \left(\frac{1}{2R_1} + G_s \right) V_a$$

$$G_{m2}V_1 \approx G_sV_a$$

$$G_{m2} = 1/10k\Omega$$

$$G_s = 1/5k\Omega$$

$$R_1 = 5M\Omega$$

$$R_2 = 1M\Omega$$

$$G_{m1} = 1/1k\Omega$$


$$I_{ca} = \frac{V_a}{2R_1}$$

$$I_{ca} = \frac{I_c}{2G_{m1}R_1}$$

$$I_{ca} = 0.0001I_c$$

$I_1 = 20.1\mu\text{A}$ and $I_2 = 19.9\mu\text{A} \rightarrow I_c = 20\mu\text{A}$, $I_d = 100\text{nA} \rightarrow I_a = 10\mu\text{A} + 1\text{nA} \sim 10\mu\text{A}$

Curve Fitting Circuit Parameters

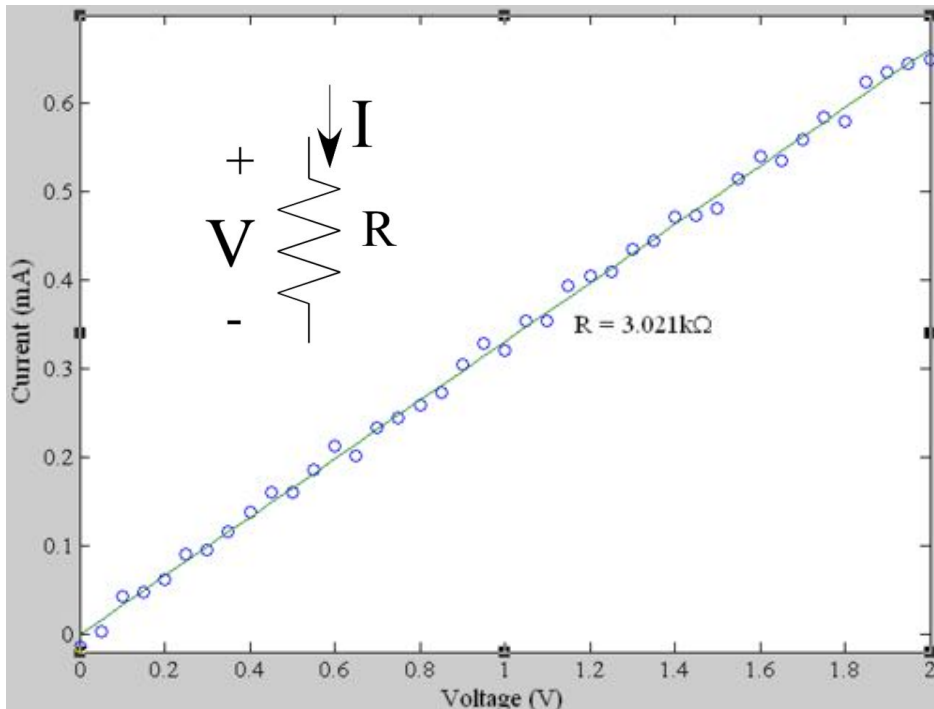

```
[A] = polyfit(V,I1,1);
I1 fit = polyval(A,V);
plot(V,I1,'o',V,I1 fit);
```

```
[A] = polyfit(V,V1,1);
V1 fit = polyval(A,V);
plot(V,V1,'o',V,V1 fit);
```

