


First-Order Dynamical Circuits

Typically an R + C or L

Need to find equivalent R, C, L

First order → one state variable
→ storage (e.g. Q) point.

R + C Prototype (lowpass)

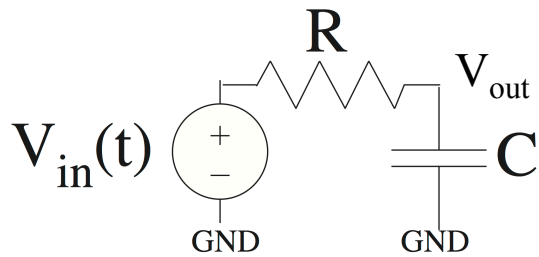


$$V_{in} = V_R + V_{out}$$

$$\frac{V_R}{R} = C \frac{dV_{out}}{dt}$$

$$\tau = RC \rightarrow V_1 = \tau \frac{dV_{out}}{dt}$$

$$\tau \frac{dV_{out}}{dt} + V_{out} = V_{in}$$

R + L Prototype (lowpass)

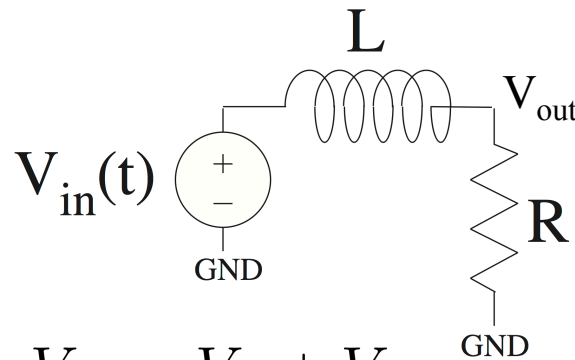

$$V_{in} = V_L + V_{out}$$

$$i = \frac{V_{out}}{R} \quad \tau = \frac{L}{R}$$

$$V_L = L \frac{di}{dt} = \frac{L}{R} \frac{dV_{out}}{dt}$$


1st-Order High-Pass Circuits

Typically an R + C or L

Need to find equivalent R, C, L

First order → one state variable
→ storage (e.g. Q) point.

R + C Prototype (lowpass)

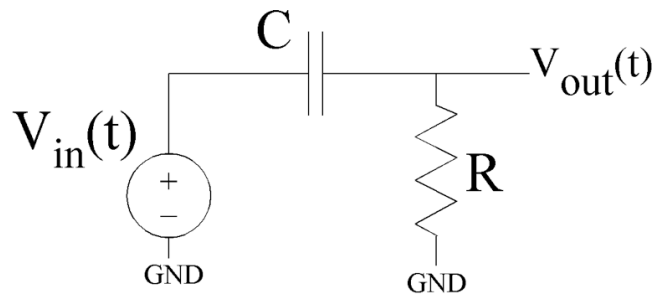


$$V_{in} = V_C + V_{out}$$

$$\frac{V_{out}}{R} = C \frac{d(V_{in} - V_{out})}{dt}$$

$$\tau = RC \rightarrow V_{out} = \tau \frac{d(V_{in} - V_{out})}{dt}$$

$$\tau \frac{dV_{out}}{dt} + V_{out} = \tau \frac{dV_{in}}{dt}$$



R + L Prototype (lowpass)

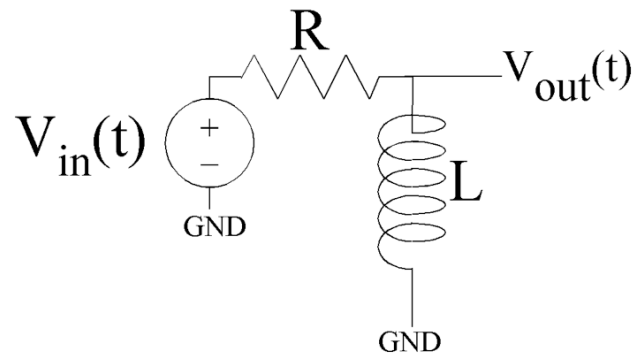

$$I = \frac{V_{in} - V_{out}}{R}$$


$$V_{out} = L \frac{dI}{dt} = \frac{L}{R} \frac{d(V_{in} - V_{out})}{dt}$$

$$\tau = \frac{L}{R}$$


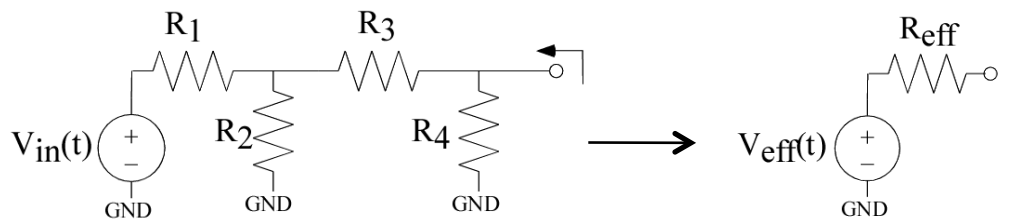
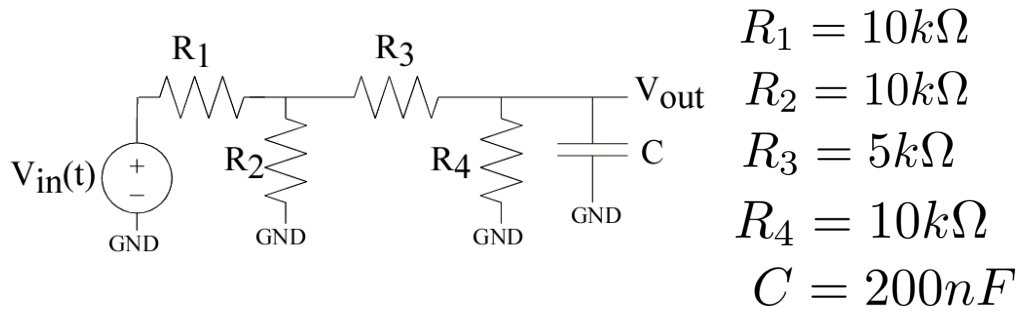


$$V_{eff} = \frac{1}{4}V_{in}(t)$$

$$R_{eff} = 5k\Omega$$

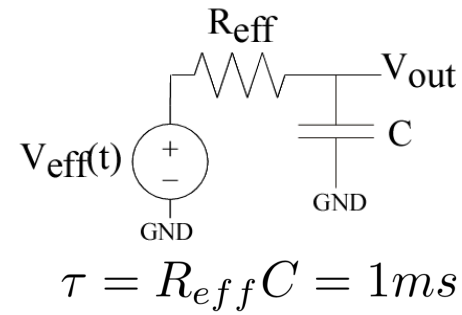
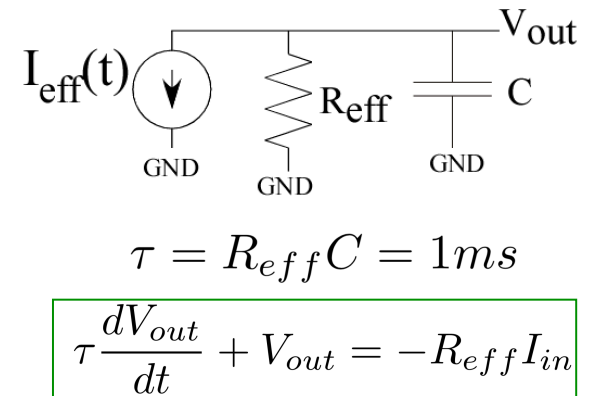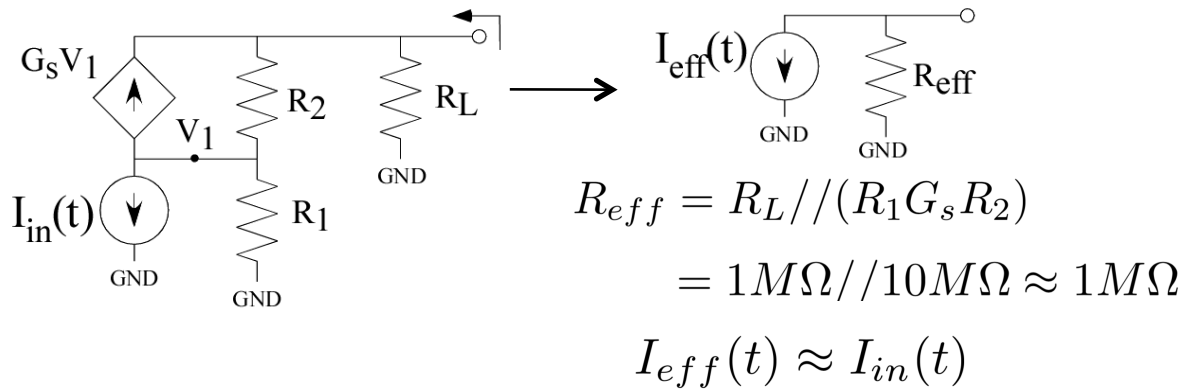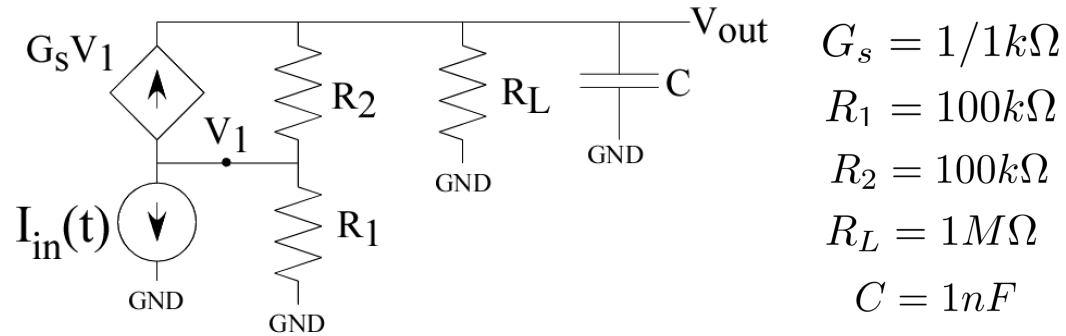
$$\tau \frac{dV_{out}}{dt} + V_{out} = \frac{1}{4}V_{in}$$






Op-Amp Basics

$$V_{\text{out}} = A_v(V^+ - V^-)$$

Typical A_v :


300 – 1000000 \rightarrow infinite

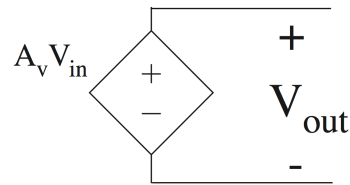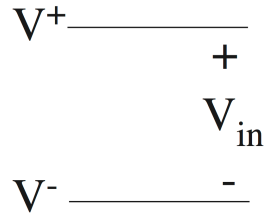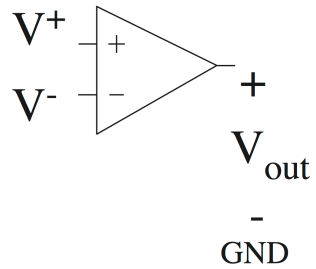


Inputs equal (V^+ , V^-), and no connection between them ????

Core Op-Amp Circuits


Voltage follower

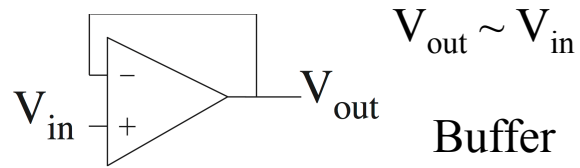


Non-Inverting Amplifier

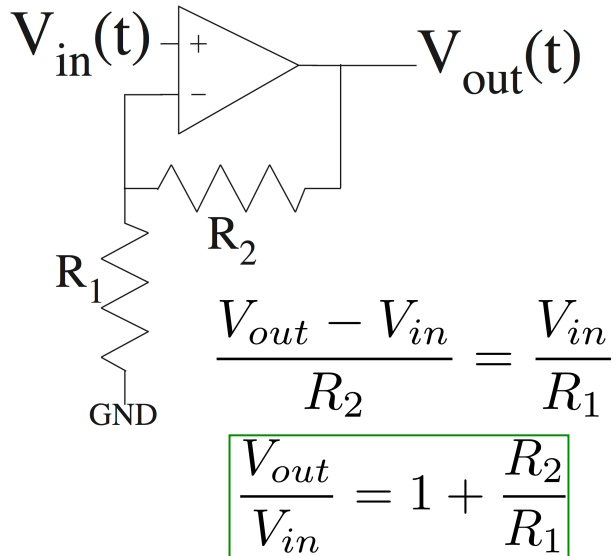

Inverting Amplifier Configuration

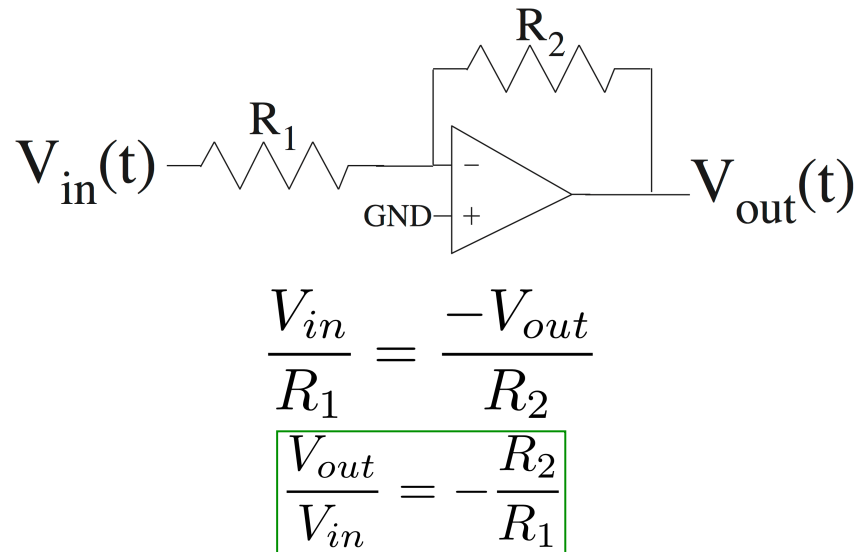

Difference Configuration

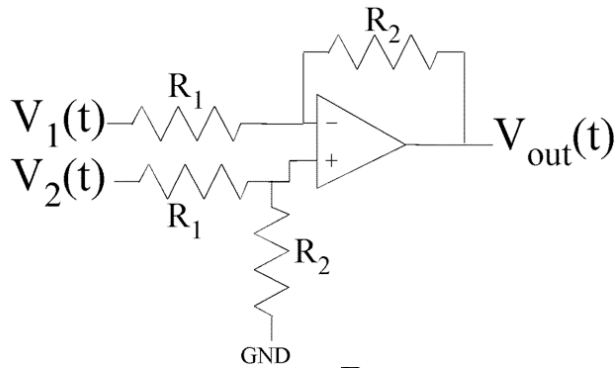


$$V_2(t) = 0V, V_{out} = -\frac{R_2}{R_1}V_1(t)$$

$$V_1(t) = 0V, V_{out} =$$

$$\left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2}{R_1 + R_2}\right) V_2(t) = \frac{R_2}{R_1}V_2(t)$$

$$\underline{V_{out} = \frac{R_2}{R_1}(V_2(t) - V_1(t))}$$

Instrumentation Amplifier

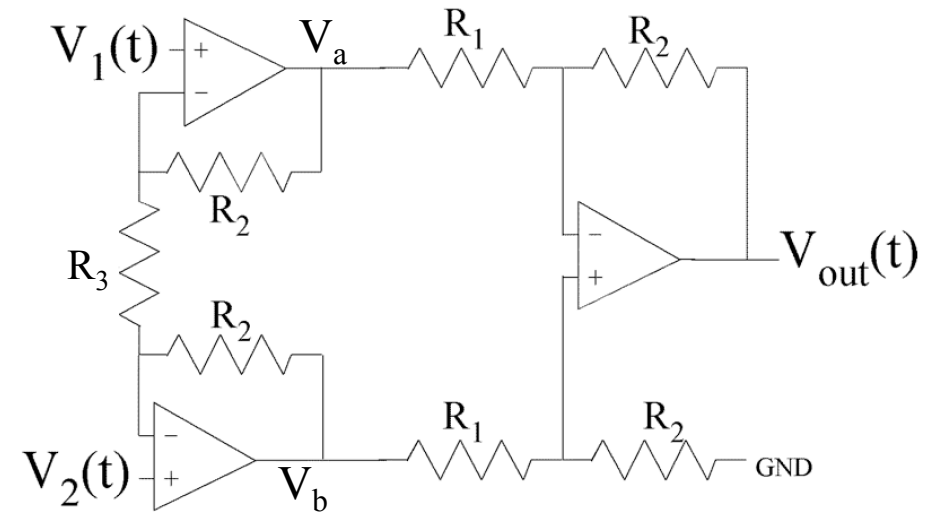

Symmetric Circuit Difference Configuration

($R_3 = R_3/2 + R_3/2$)



$$V_{out} = \frac{R_2}{R_1}(V_b(t) - V_a(t))$$

Symmetry Point = 0V

(diff circuit)

$$V_b - V_a = \left(1 + \frac{2R_2}{R_3}\right) (V_2 - V_1)$$
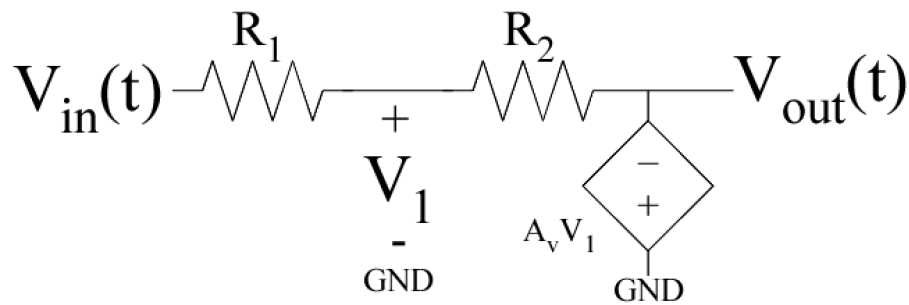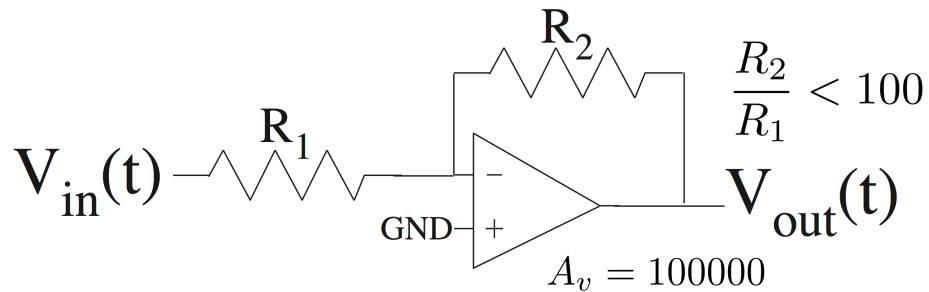
$$V_b - V_a = (V_2 - V_1) \cdot \frac{R_2}{R_1} \left(1 + \frac{2R_2}{R_3}\right)$$



$$V_{out} = -A_v V_1 \quad \frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_{out}}{R_2}$$



$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{A_v(R_1 // R_2)} - \frac{V_{out}}{R_2}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \frac{1}{1 + \frac{R_1}{A_v(R_1 + R_2)}}$$

Invert this term

$$\approx -\frac{R_2}{R_1}$$
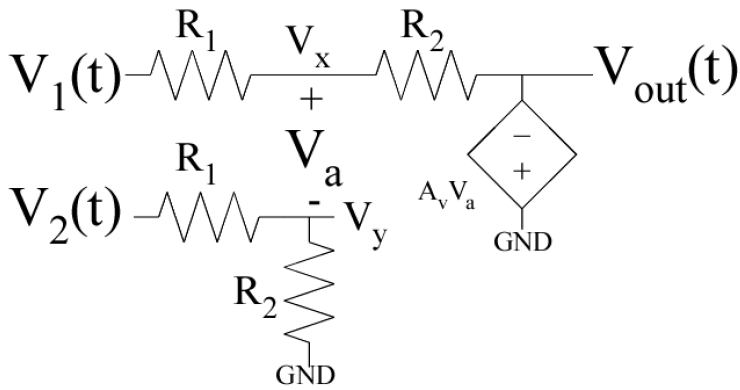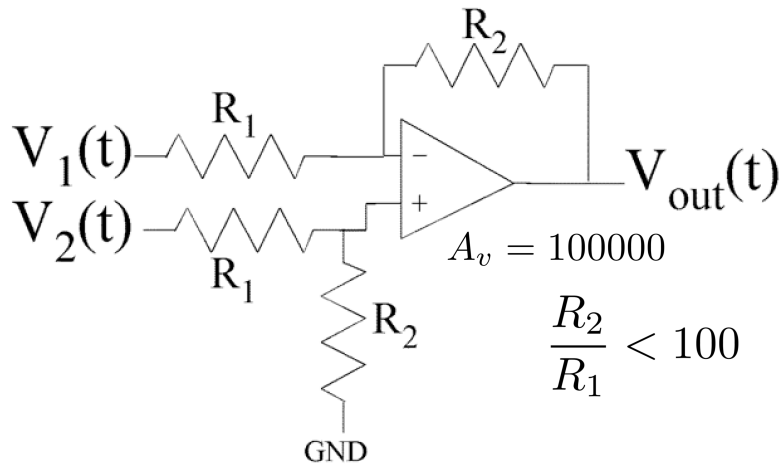
$$\begin{matrix} R_1 = 10k\Omega \\ R_2 = 100k\Omega \end{matrix} \longrightarrow \frac{V_{out}}{V_{in}} = -10$$



$$\frac{V_1 - V_x}{R_1} = \frac{V_x - V_{out}}{R_2} \longrightarrow \frac{V_1}{R_1} + \frac{V_{out}}{R_2} = \frac{V_x}{R_1 // R_2}$$

$$V_y = \frac{R_2}{(R_1 + R_2)} V_2 \quad V_x = (R_1 // R_2) \left(\frac{V_1}{R_1} + \frac{V_{out}}{R_2} \right)$$

$$V_{out} = -A_v V_a = A_v (V_y - V_x)$$

$$\frac{V_{out}}{A_v} = V_y - V_x = \frac{R_2}{R_1 + R_2} V_2 - \frac{R_2}{R_1 + R_2} V_1 - \frac{R_1}{R_1 + R_2} V_{out}$$



$$V_{out} \left(1 + \frac{R_1 + R_2}{A_v R_1} \right) = \frac{R_2}{R_1} (V_2 - V_1)$$

$$V_{out} \approx -\frac{R_2}{R_1} (V_2 - V_1)$$


$$R_1 = 10k\Omega$$

$$R_2 = 100k\Omega$$

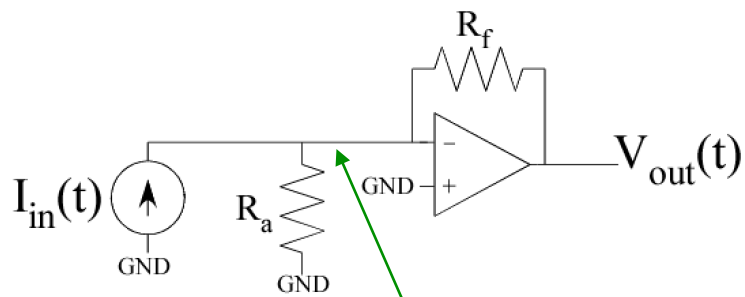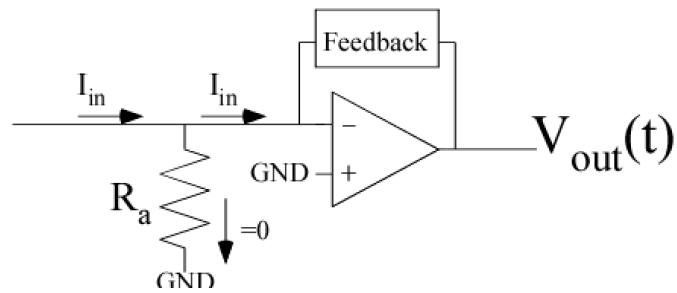
$$\longrightarrow V_{out} \approx -10(V_2 - V_1)$$



Norton Equivalent Circuit
Node ~ GND

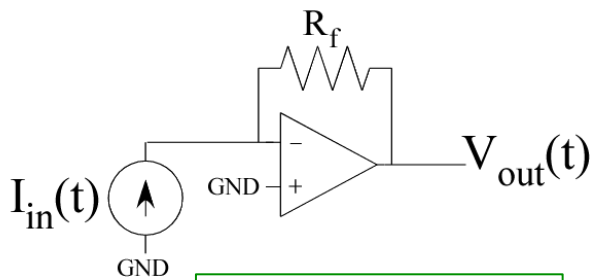


$$V_{out}(t) = -R_f I_{in}(t)$$

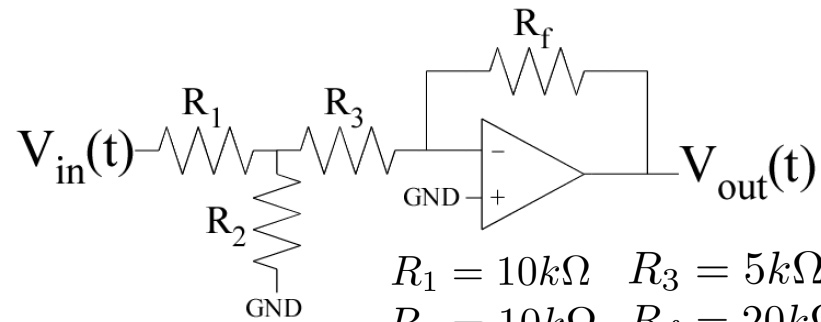

$$R_1 = 10k\Omega \quad R_3 = 5k\Omega$$
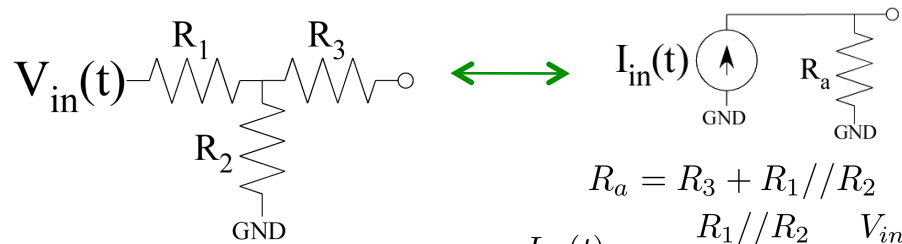
$$R_2 = 10k\Omega \quad R_f = 20k\Omega$$



$$R_a = R_3 + R_1 // R_2$$

$$I_{in}(t) = \frac{R_1 // R_2}{R_3 + R_1 // R_2} \frac{V_{in}}{R_1}$$

$$V_{out}(t) = -\frac{R_f}{R_1} \frac{R_1 // R_2}{R_3 + (R_1 // R_2)} V_{in}$$

$$R_a = 10k\Omega \quad I_{in}(t) = \frac{V_{in}}{20k\Omega} \quad V_{out}(t) = -V_{in}$$

Laplace Transform Table

Time Domain (t)	Laplace Domain (s)
$\frac{df(t)}{dt}$	$sF(s)$
$\int f(t)dt$	$\frac{1}{s}F(s)$
$u(t)$	$\frac{1}{s}$
$e^{-at}u(t)$	$\frac{1}{s+a}$
$\sin(\omega_1 t)u(t)$	$\frac{\omega_1}{s^2 + \omega_1^2}$
$\cos(\omega_1 t)u(t)$	$\frac{s}{s^2 + \omega_1^2}$
$f(t \rightarrow \infty)$	$\lim_{t \rightarrow 0} sF(s)$
$f(t \rightarrow 0)$	$\lim_{t \rightarrow \infty} sF(s)$

How to handle general linear differential equations with arbitrary inputs (e.g. signals)?

$$\frac{d^4 y}{dt^4} + 3\frac{d^3 y}{dt^3} + 7\frac{d^2 y}{dt^2} + 4\frac{dy}{dt} + 25y = x_{in}(t)$$

Change $d/dt \rightarrow s$ (Heavyside)

$$s^4 y + 3s^3 y + 7s^2 y + 4s y + 25y = x_{in}(t)$$

and solve in some different ways

Laplace Transform (should be Heavyside Transform)

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

$$s = \sigma + j\omega \quad \begin{array}{l} \text{Complex exponential} \\ \text{Basis functions} \end{array}$$

$$f(t) \rightarrow F(s) \quad F(s) \rightarrow f(t)$$

$$\tau \frac{dV}{dt} + V(t) = V_{in}(t)$$

$$s\tau V(s) + V(s) = V_{in}(s)$$

$$V(s) = \frac{1}{s\tau + 1} V_{in}(s)$$

$$V_{in}(t) = u(t) \rightarrow V_{in}(s) = \frac{1}{s}$$

$$V(s) = \frac{1}{s\tau + 1} \frac{1}{s} = \frac{1}{s} - \frac{\tau}{s\tau + 1}$$

$$V(s) = \frac{1}{s} - \frac{1}{s + 1/\tau}$$

$$V(t) = u(t) - e^{-t/\tau} u(t) = \left(1 - e^{-t/\tau}\right)$$

$$\begin{aligned} V(t \rightarrow 0^+) &= \lim_{s \rightarrow \infty} s \left(\frac{1}{s\tau + 1} \frac{1}{s} \right) \\ &= \lim_{s \rightarrow \infty} \frac{1}{s\tau + 1} = 0 \end{aligned}$$

$$\begin{aligned} V(t \rightarrow \infty) &= \lim_{s \rightarrow 0} s \left(\frac{1}{s\tau + 1} \frac{1}{s} \right) \\ &= \lim_{s \rightarrow 0} \frac{1}{s\tau + 1} = 1 \end{aligned}$$

$$V_{in}(t) = \sin(\omega t) \quad s = \sigma + j\omega \rightarrow j\omega$$

$$\frac{V(s)}{V_{in}(s)} = \frac{1}{s\tau + 1} \quad \frac{V(j\omega)}{V_{in}(j\omega)} = \frac{1}{j\omega\tau + 1}$$

$$V_{in}(t) = \frac{1}{\sqrt{1 + \omega^2\tau^2}} \sin(\omega t - \tan^{-1}(\tau\omega))$$

$$V_{in}(t) = e^{-at/\tau} u(t) \rightarrow V_{in}(s) = \frac{1}{s + a/\tau}$$

$$V(s) = \frac{1}{s\tau + 1} \frac{\tau}{s\tau + a}$$

$$V(s) = \frac{\tau}{a - 1} \frac{1}{s\tau + 1} - \frac{\tau}{a - 1} \frac{1}{\tau s + a}$$

$$V(s) = \frac{1}{a - 1} \frac{1}{s + 1/\tau} - \frac{1}{a - 1} \frac{1}{s + a/\tau}$$

$$V(t) = \frac{1}{a - 1} \left(e^{-t/\tau} - e^{-at/\tau} \right) u(t)$$

$$V_{in}(t) = u(t) \rightarrow V_{in}(s) = \frac{1}{s}$$

$$V(s) = \frac{1}{s\tau + 2} \frac{1}{s\tau + 1} \frac{1}{s}$$

$$V(s) = A \frac{\tau}{s\tau + 2} + B \frac{\tau}{s\tau + 1} + C \frac{1}{s}$$

$$V(s) = \frac{1}{2} \frac{1}{s + 2/\tau} - \frac{1}{s + 1/\tau} + \frac{1}{2} \frac{1}{s}$$

$$V_{out}(t) = \left(\frac{1}{2} \left(1 + e^{-2t/\tau} \right) - e^{-t/\tau} \right) u(t)$$

$$\tau^2 \frac{d^2V}{dt^2} + 3\tau \frac{dV}{dt} + 2V(t) = V_{in}(t)$$

$$s^2\tau^2 V(s) + 3s\tau V(s) + 2V(s) = V_{in}(s)$$

$$V(s) = \frac{1}{s^2\tau^2 + 3s\tau + 2} V_{in}(s)$$

$$V(s) = \frac{1}{(s\tau + 2)(s\tau + 1)} V_{in}(s)$$

$$\frac{V(s)}{V_{in}(s)} = \frac{1}{s^2\tau^2 + 3s\tau + 2}$$


$$V_{in}(t) = \sin(\omega t)$$


$$s = \sigma + j\omega \rightarrow j\omega$$


$$\frac{V(j\omega)}{V_{in}(j\omega)} = \frac{1}{(j\omega)^2\tau^2 + 3(j\omega)\tau + 2}$$


$$V_{in}(t) = \frac{1}{((2 - \omega^2\tau^2)^2 + 9\omega^2\tau^2)^{1/2}} \sin \left(\omega t - \tan^{-1} \left(\frac{3\omega\tau}{2 - \omega^2\tau^2} \right) \right)$$

Laplace form of Circuit elements

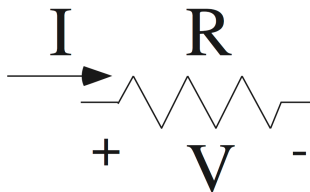
Resistor
 $V = RI \longrightarrow V(s) = R I(s)$

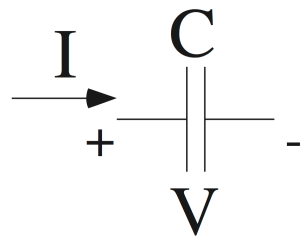
Capacitor
 $I = C \frac{dV}{dt} \longrightarrow I(s) = s C V(s)$

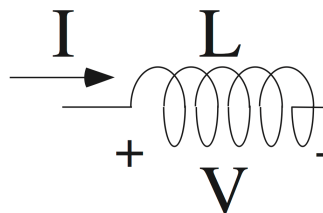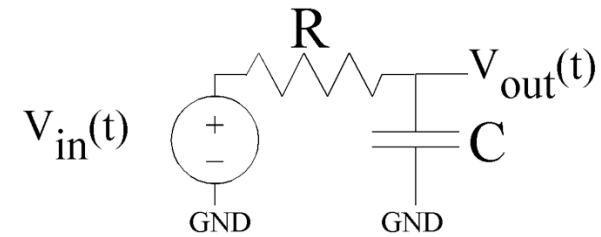
Inductor
 $V = L \frac{dI}{dt} \longrightarrow V(s) = s L I(s)$




Voltage Divider:

$$\begin{aligned}
 V_{out}(s) &= V_{in}(s) \frac{1/sC}{R + 1/sC} \\
 &= V_{in}(s) \frac{1}{1 + sRC} \\
 &= V_{in}(s) \frac{1}{1 + s\tau}
 \end{aligned}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + s\tau}$$

Heavyside Step Function

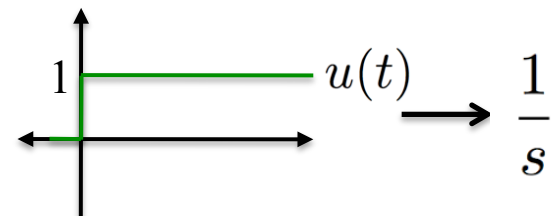

$$V_{out}(t) = (1 - e^{-t/\tau})u(t)$$

Laplace Transform \rightarrow Fourier Transform

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad F(j\omega) = \int_{-\infty}^{\infty} f(t)e^{-j\omega t} dt$$


$$s = \sigma + j\omega \quad \sigma = 0, s \rightarrow j\omega \quad j = \sqrt{-1}$$

$$f(t) \rightarrow F(s) \quad F(s) \rightarrow f(t)$$

Transform: reversible

Quantum Physics:
Momentum relates to
Fourier Transform of
position

1st order example

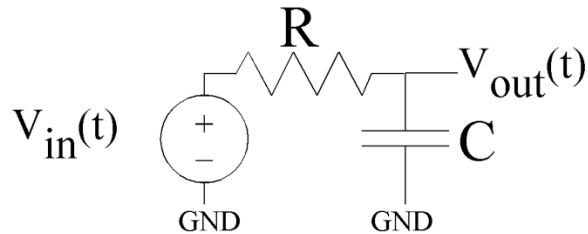

$$s \rightarrow j\omega \quad \omega = 2\pi f$$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{1 + j\omega\tau}$$

$$|a + jb| = \sqrt{a^2 + b^2}$$



$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + s\tau}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2\tau^2}}$$

$$\text{Phase} = \tan^{-1}(\omega\tau)$$



First-Order Low-Pass Filter

$$H(s) = \frac{1}{1 + s\tau}$$

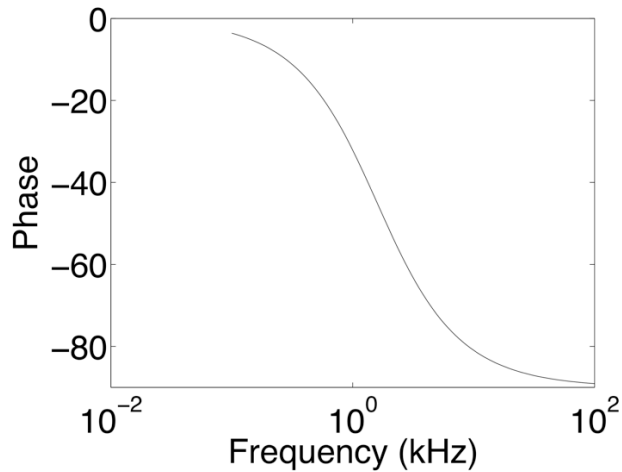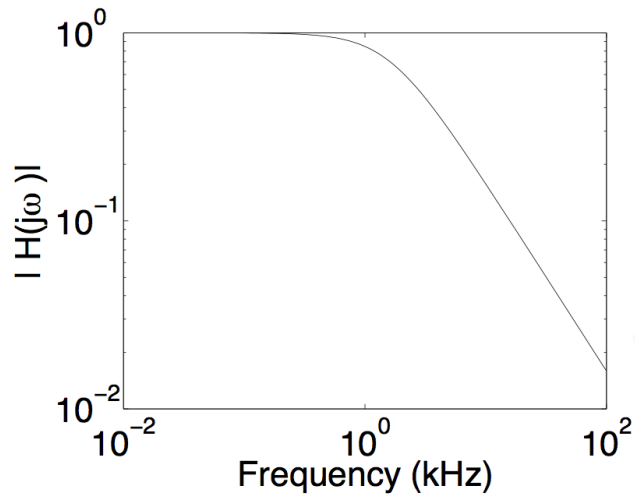


First-Order High-Pass Filter





$$H(s) = \frac{s\tau}{1 + s\tau}$$

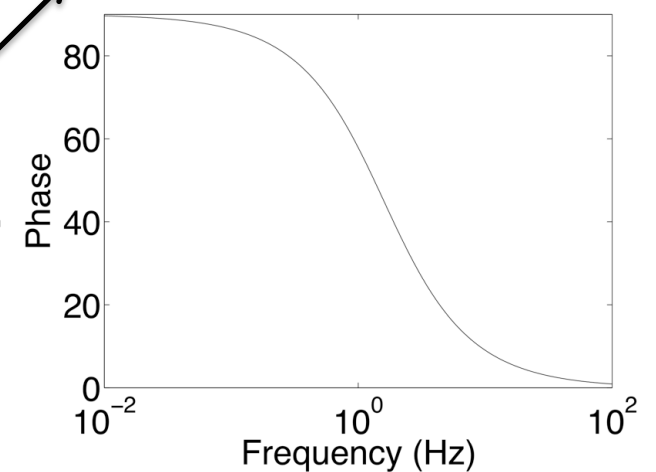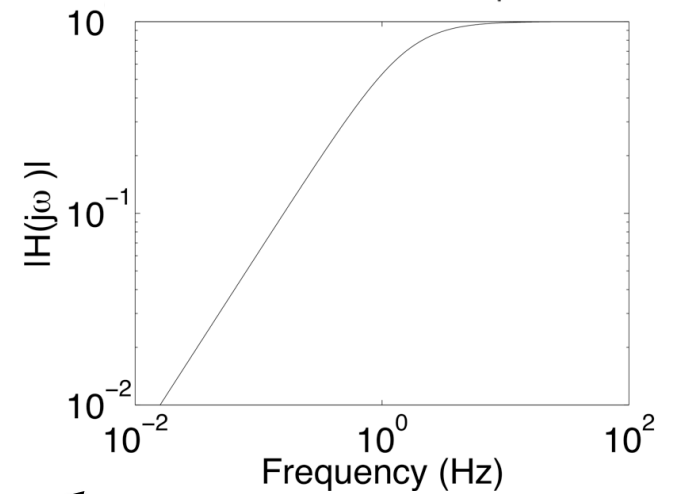



First-Order ODE:
Frequency Response

$$\sigma = 0, s \rightarrow j\omega$$

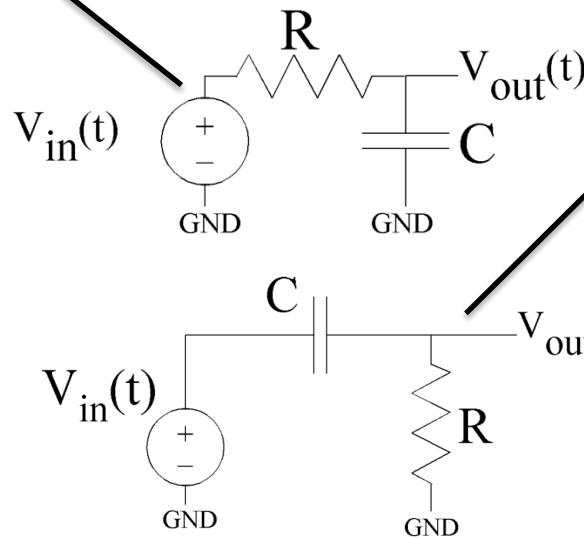

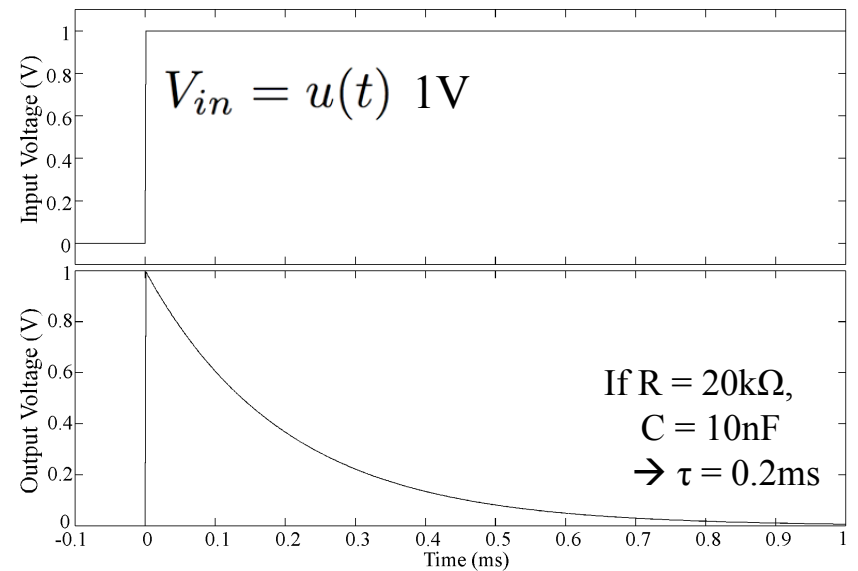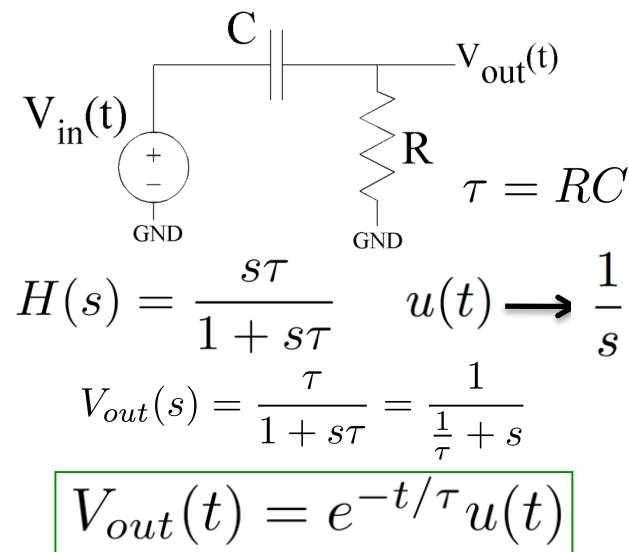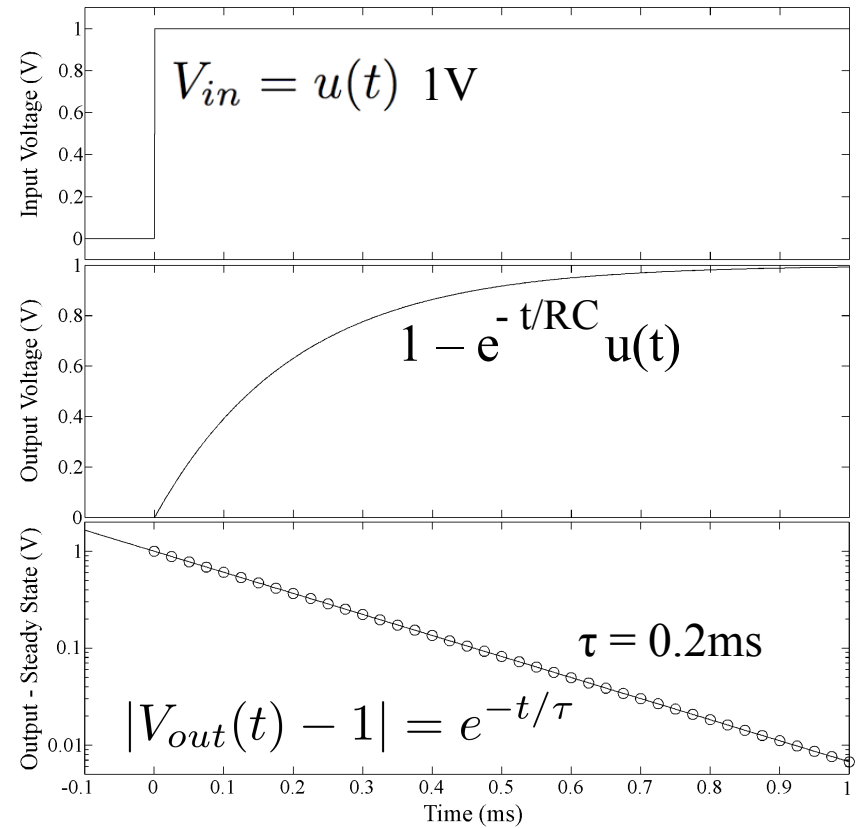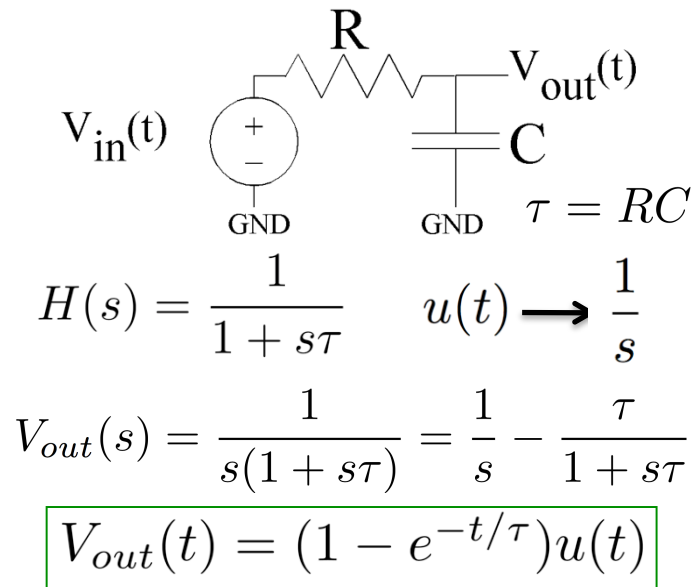

1st Order Step Response (Op-Amp)

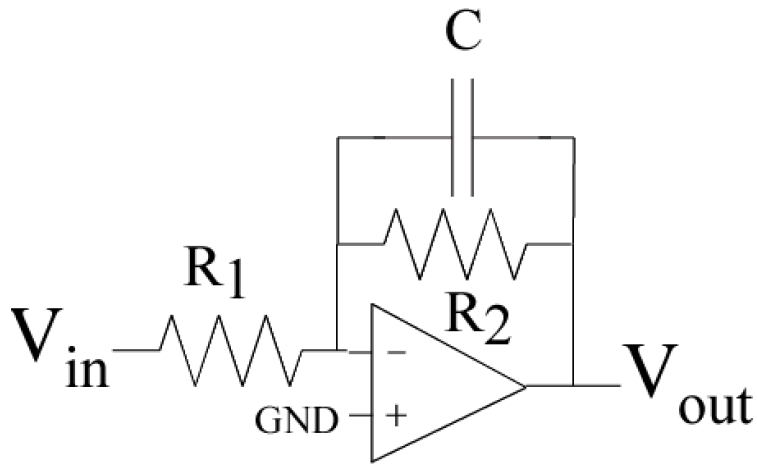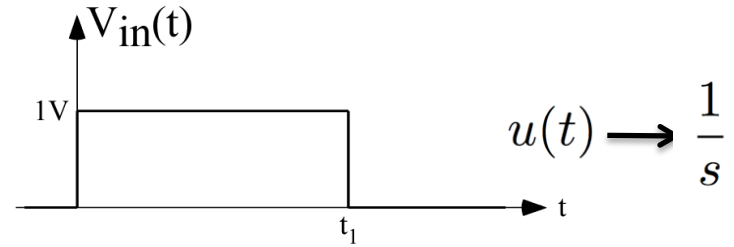


$$V_{in}/R_1 = -V_{out}(sC + 1/R_2)$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \frac{1}{1 + s\tau} \quad \tau = R_2C$$

$$V_{out}(s) = -\frac{R_2}{R_1} \frac{1}{s(1 + s\tau)} = \frac{1}{s} - \frac{\tau}{1 + s\tau}$$
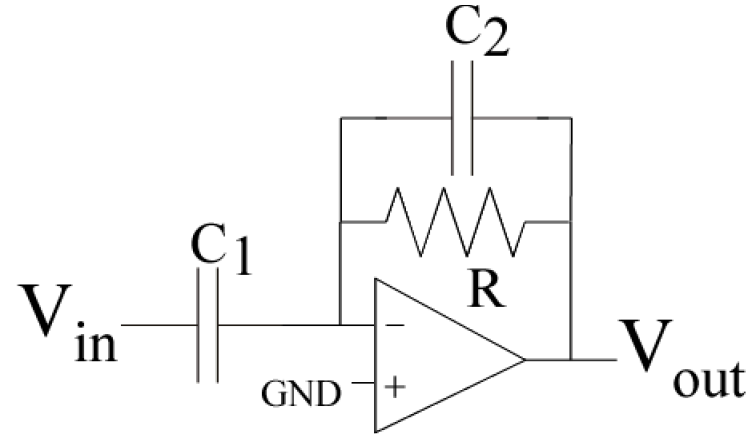
$$V_{out}(t) = -\frac{R_2}{R_1} (1 - e^{-t/\tau}) u(t)$$




$$sC_1V_{in} = -V_{out}(sC_2 + 1/R)$$

$$\frac{V_{out}}{V_{in}} = -\frac{C_1}{C_2} \frac{s\tau}{1 + s\tau} \quad \tau = RC_2$$

$$V_{out}(s) = -\frac{C_1}{C_2} \frac{\tau}{1 + s\tau} = \frac{1}{\frac{1}{\tau} + s}$$
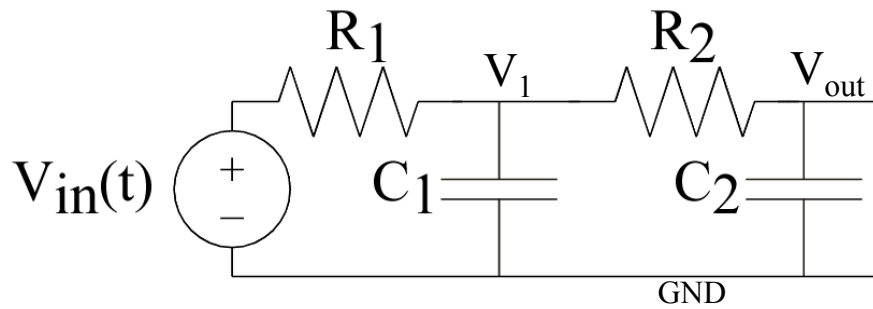
$$V_{out}(t) = -\frac{C_1}{C_2} e^{-t/\tau} u(t)$$



$$\begin{aligned}
 V_1: \frac{V_{in} - V_1}{R_1} + \frac{V_{out} - V_1}{R_2} &= sC_1 V_1 & \rightarrow & sC_1(sR_2C_2V_{out} + V_{out}) + \frac{sR_2C_2V_{out} + V_{out}}{R_1 // R_2} = \frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} \\
 sC_1 V_1 + \frac{V_1}{R_1 // R_2} &= \frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} & & sC_1 R_1 (sR_2 C_2 V_{out} + V_{out}) + s(R_1 + R_2) C_2 V_{out} + V_{out} = V_{in} \\
 V_{out}: \frac{V_{out} - V_1}{R_2} + sC_2 V_{out} &= 0 & & \frac{V_{out}}{V_{in}} = \frac{1}{s^2 R_1 C_1 R_2 C_2 + s(R_1 C_1 + R_1 C_2 + R_2 C_2) + 1} \\
 sR_2 C_2 V_{out} + V_{out} &= V_1 & & \tau = \sqrt{R_1 C_1 R_2 C_2} \quad Q \leq 1/2
 \end{aligned}$$

Specific case: $R = R_1 = R_2, C = C_1 = C_2$ ($Q = 1/3$)

$$\frac{V_{out}}{V_{in}} = \frac{1}{s^2 \tau^2 + 3s\tau + 1} = \frac{1}{(s\tau + 0.382)(s\tau + 2.618)} \quad \tau = RC$$

1V step input ($0 \rightarrow 1V$)


$$u(t) \rightarrow \frac{1}{s} \quad V_{in}(s) = \frac{1V}{s}$$

$$V_{out} = \frac{1}{s(s\tau + 0.382)(s\tau + 2.618)} = \frac{1V}{s} + \frac{B}{s\tau + 0.382} + \frac{C}{s\tau + 2.618}$$

$$B = \frac{1}{s(s\tau + 2.618)} \text{ for } s\tau = -0.382 \quad C = \frac{1}{s(s\tau + 0.382)} \text{ for } s\tau = -2.618$$

$$V_{out}(s) = \frac{1V}{s} - \frac{1.171\tau}{s\tau + 0.382} + \frac{0.171\tau}{s\tau + 2.618}$$
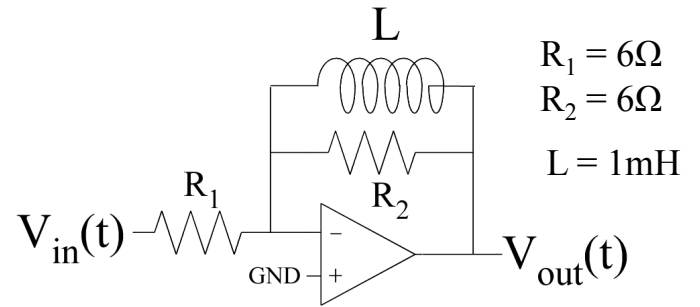
$$V_{out}(t) = \left(1 - 1.171e^{-0.382t/\tau} + 0.171e^{-2.618t/\tau} \right) u(t)$$




$$\frac{V_{in}}{R_1 + sL} = -\frac{V_{out}}{R_2}$$




$$\frac{V_{out}}{V_{in}} = -\frac{R_2 // (sL)}{R_1}$$


$$= -\frac{R_2 \frac{s(L/R_2)}{1 + s(L/R_2)}}{R_1}$$
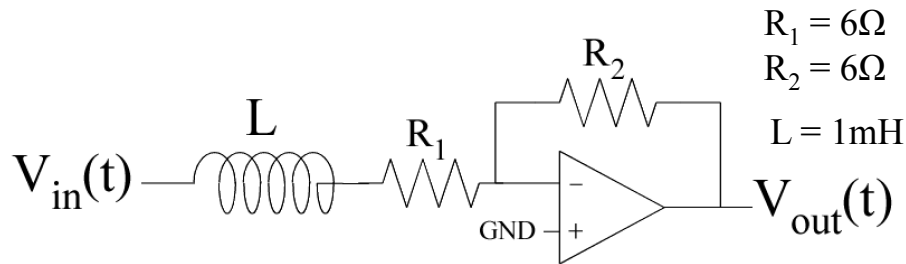
$$= -\frac{R_2}{R_1} \frac{s\tau}{1 + s\tau} \quad \tau = L/R_2 \quad \tau = 1/6 \text{ ms}$$


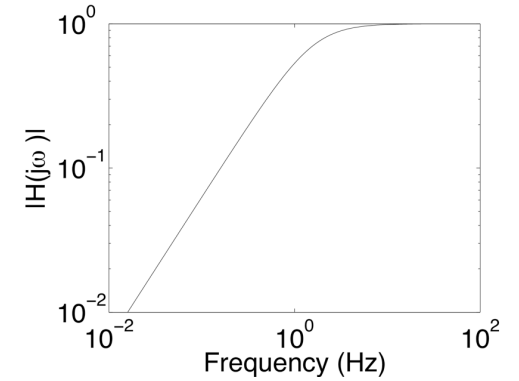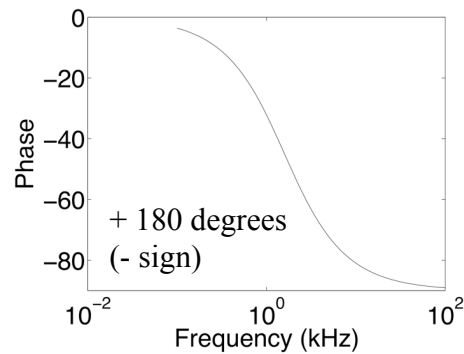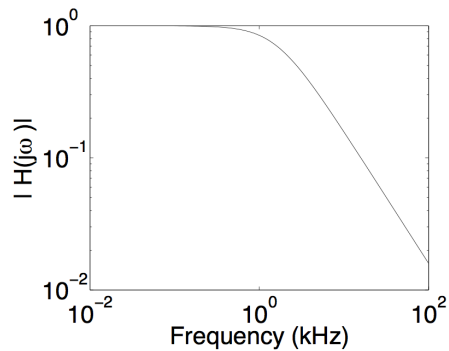
$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1 + sL} = -\frac{R_2}{R_1} \frac{1}{1 + s\tau} \quad \tau = L/R_1 \quad \tau = 1/6 \text{ ms}$$



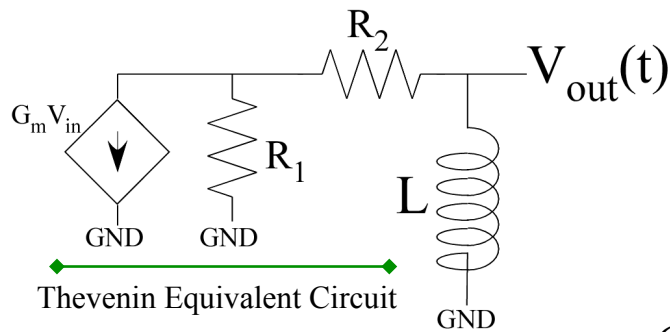

$$R_1 = 100\text{k}\Omega \quad G_m = 1/10\text{k}\Omega$$

$$R_2 = 100\text{k}\Omega \quad L = 6\text{mH}$$

Becomes an R-L Circuit


$$R_1 + R_2 \rightarrow R$$

$$(200\text{k}\Omega)$$

$$G_m R_1 V_{in}(t) \rightarrow V_{in}(t)$$

$$(-10 V_{in})$$
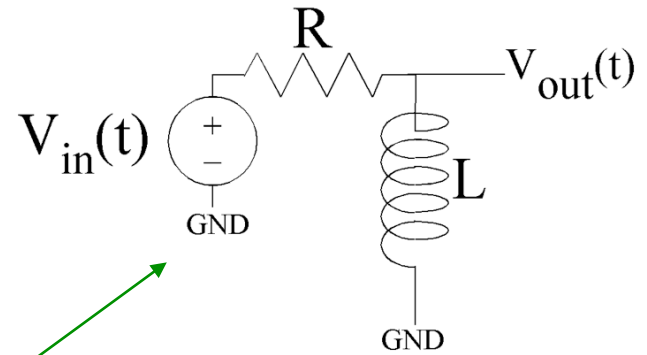
$$V_{in} = 1V u(t) \rightarrow -10V u(t)$$




$$V_{out} = L \frac{dI}{dt} = \frac{L}{R} \frac{d(V_{in} - V_{out})}{dt}$$

$$\tau \frac{dV_{out}}{dt} + V_{out} = \tau \frac{dV_{in}}{dt} \quad \tau = \frac{L}{R}$$

$$\tau = 30\text{ns}$$

$$V_{out}(s) = -\frac{10}{s + 1/\tau}$$

$$V_{out}(t) = -10e^{-t/\tau} u(t)$$

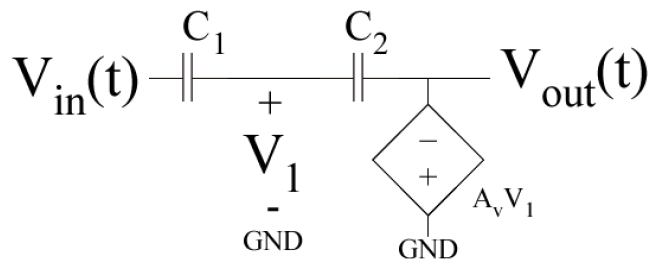



$$sC_1(V_{in} - V_1) = sC_2(V_1 - V_{out})$$

$$V_{out} = -A_v V_1$$

$$sC_1 V_{in} = -\left(sC_2 + s\frac{C_1 + C_2}{A_v}\right) V_{out}$$

$$\frac{V_{out}}{V_{in}} = -\frac{sC_2 + s\frac{C_1 + C_2}{A_v}}{sC_1}$$
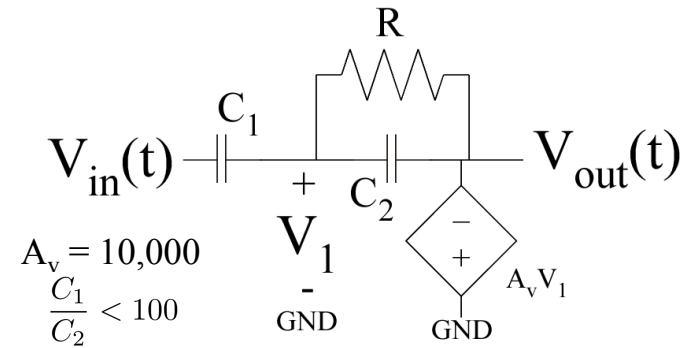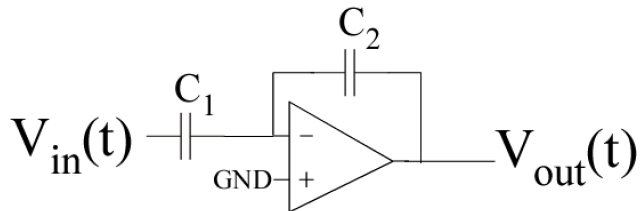
$$\frac{V_{out}(s)}{V_{in}(s)} = -\frac{C_2 + \frac{C_1 + C_2}{A_v}}{C_1} \quad \text{unless } s = 0.$$




$$sC_1(V_{in} - V_1) = \frac{V_1 - V_{out}}{R} + sC_2(V_1 - V_{out})$$


$$sC_1 V_{in} = -V_{out} \left(sC_2 + \frac{1}{R} + \frac{s(C_1 + C_2) + \frac{1}{R}}{A_v} \right)$$

$$sC_1 V_{in} = -V_{out} \left(s \left(C_2 + \frac{C_1 + C_2}{A_v} \right) + \frac{1}{R} \left(1 + \frac{1}{A_v} \right) \right)$$
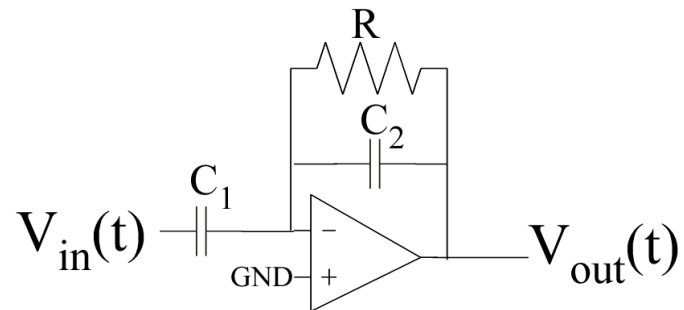
$$\frac{C_1}{C_2} < 100 \quad \frac{V_{out}}{V_{in}} = \frac{sC_1 R}{sC_2 R + 1} \quad \begin{matrix} 1^{\text{st}}\text{-order} \\ \text{HPF} \end{matrix}$$





Op-Amp with Capacitive Feedback

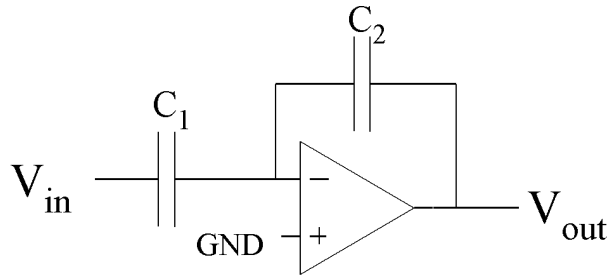

$$C_1 \frac{dV_{in}}{dt} = -C_2 \frac{dV_{out}}{dt}$$

$$V_{out}(t) = -\frac{C_1}{C_2} V_{in}(t) + V_{offset}$$

Heavyside Step Function

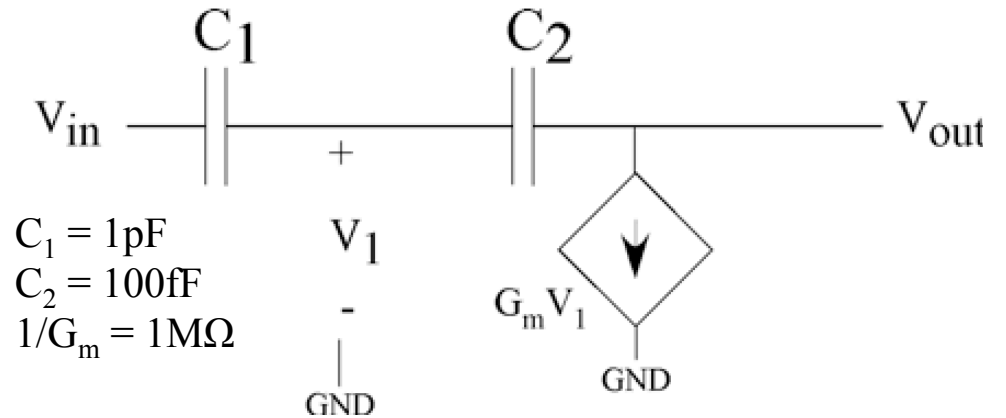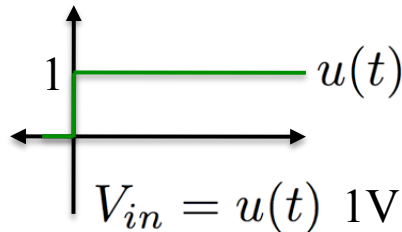

$$C_1 = 1\text{pF}$$

$$C_2 = 100\text{fF}$$

$$1/G_m = 1\text{M}\Omega$$

$$C_1 \frac{d(V_{in} - V_1)}{dt} = C_2 \frac{d(V_1 - V_{out})}{dt} = G_m V_1$$

$$sC_1(V_{in} - V_1) = sC_2(V_1 - V_{out}) = G_m V_1$$

$$\left(1 + s\frac{C_1}{G_m}\right) V_1 = s\frac{C_1}{G_m} V_{in} - \left(1 - s\frac{C_2}{G_m}\right) V_1 = s\frac{C_2}{G_m} V_{out}$$


$$-s\frac{C_1}{G_m} \left(1 - s\frac{C_2}{G_m}\right) V_{in} = s\frac{C_2}{G_m} \left(1 + s\frac{C_1}{G_m}\right) V_{out}$$

$$\frac{V_{out}}{V_{in}} = -\frac{s C_1}{s C_2} \frac{1 - s\frac{C_2}{G_m}}{1 + s\frac{C_1}{G_m}} \quad A_v = -\frac{C_1}{C_2} \quad \tau = \frac{C_1}{G_m}$$

$$\frac{V_{out}}{V_{in}} = -\frac{s}{s} A_v \frac{1 - s\frac{\tau}{A_v}}{1 + s\tau}$$

1st Order Transfer Function

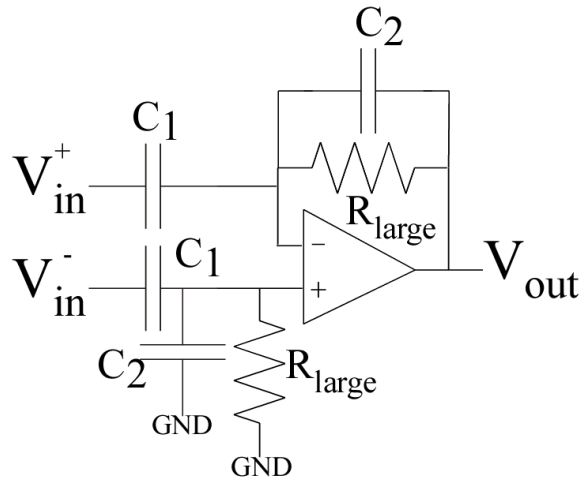Differential inverting capacitor-based amplifier (R. Harrison: Front-End Neural Amplifier)



$$Z_1 = 1/sC_1 \quad Z_2 = R_{\text{large}} // (1/sC_1)$$

(input) (feedback)

$$V_{out} = -\frac{C_1}{C_2} \frac{s\tau}{1 + s\tau} (V_{in}^+ - V_{in}^-)$$

$$\tau = R_{\text{large}}C_2 \quad (< 1\text{Hz})$$

R_{large} sets biasing (no Q issues)

For higher frequencies: $V_{out} = -\frac{C_1}{C_2} (V_{in}^+ - V_{in}^-)$