

Laplace Transform Table

Time Domain (t)	Laplace Domain (s)
$\frac{df(t)}{dt}$	$sF(s)$
$\int f(t)dt$	$\frac{1}{s}F(s)$
$u(t)$	$\frac{1}{s}$
$e^{-at}u(t)$	$\frac{1}{s+a}$
$\sin(\omega_1 t)u(t)$	$\frac{\omega_1}{s^2 + \omega_1^2}$
$\cos(\omega_1 t)u(t)$	$\frac{s}{s^2 + \omega_1^2}$
$f(t \rightarrow \infty)$	$\lim_{t \rightarrow 0} sF(s)$
$f(t \rightarrow 0)$	$\lim_{t \rightarrow \infty} sF(s)$

How to handle general linear differential equations with arbitrary inputs (e.g. signals)?

$$\frac{d^4 y}{dt^4} + 3\frac{d^3 y}{dt^3} + 7\frac{d^2 y}{dt^2} + 4\frac{dy}{dt} + 25y = x_{in}(t)$$

Change $d/dt \rightarrow s$ (Heavyside)

$$s^4 y + 3s^3 y + 7s^2 y + 4s y + 25y = x_{in}(t)$$

and solve in some different ways

Laplace Transform (should be Heavyside Transform)

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

$$s = \sigma + j\omega \quad \begin{array}{l} \text{Complex exponential} \\ \text{Basis functions} \end{array}$$

$$f(t) \rightarrow F(s) \quad F(s) \rightarrow f(t)$$

$$V_{in}(t) = u(t) \rightarrow V_{in}(s) = \frac{1}{s}$$

$$V(s) = \frac{1}{s\tau + 2} \frac{1}{s\tau + 1} \frac{1}{s}$$

$$V(s) = A \frac{\tau}{s\tau + 2} + B \frac{\tau}{s\tau + 1} + C \frac{1}{s}$$

$$V(s) = \frac{1}{2} \frac{1}{s + 2/\tau} - \frac{1}{s + 1/\tau} + \frac{1}{2} \frac{1}{s}$$

$$V_{out}(t) = \left(\frac{1}{2} \left(1 + e^{-2t/\tau} \right) - e^{-t/\tau} \right) u(t)$$

$$\tau^2 \frac{d^2V}{dt^2} + 3\tau \frac{dV}{dt} + 2V(t) = V_{in}(t)$$

$$s^2\tau^2V(s) + 3s\tau V(s) + 2V(s) = V_{in}(s)$$

$$V(s) = \frac{1}{s^2\tau^2 + 3s\tau + 2} V_{in}(s)$$

$$V(s) = \frac{1}{(s\tau + 2)(s\tau + 1)} V_{in}(s)$$

$$\frac{V(s)}{V_{in}(s)} = \frac{1}{s^2\tau^2 + 3s\tau + 2}$$


$$V_{in}(t) = \sin(\omega t)$$


$$s = \sigma + j\omega \rightarrow j\omega$$


$$\frac{V(j\omega)}{V_{in}(j\omega)} = \frac{1}{(j\omega)^2\tau^2 + 3(j\omega)\tau + 2}$$


$$V_{in}(t) = \frac{1}{(2 - \omega^2\tau^2)^2 + 9\omega^2\tau^2} \sin \left(\omega t - \tan^{-1} \left(\frac{3\omega\tau}{2 - \omega^2\tau^2} \right) \right)$$

Laplace form of Circuit elements

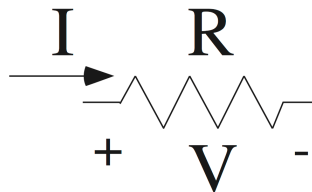
Resistor
 $V = RI \longrightarrow V(s) = R I(s)$

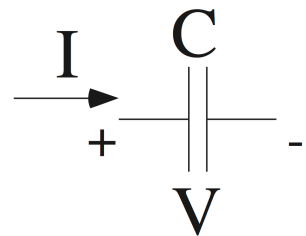
Capacitor
 $I = C \frac{dV}{dt} \longrightarrow I(s) = s C V(s)$

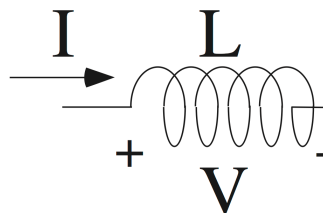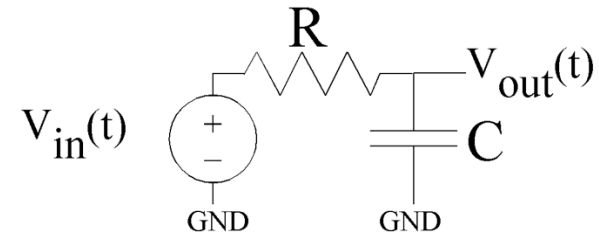
Inductor
 $V = L \frac{dI}{dt} \longrightarrow V(s) = s L I(s)$




Voltage Divider:

$$\begin{aligned}
 V_{out}(s) &= V_{in}(s) \frac{1/sC}{R + 1/sC} \\
 &= V_{in}(s) \frac{1}{1 + sRC} \\
 &= V_{in}(s) \frac{1}{1 + s\tau}
 \end{aligned}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + s\tau}$$

Heavyside Step Function

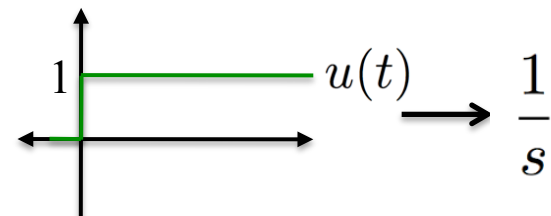

$$V_{out}(t) = (1 - e^{-t/\tau})u(t)$$

Laplace Transform \rightarrow Fourier Transform

$$F(s) = \int_0^{\infty} f(t)e^{-st} dt \quad F(j\omega) = \int_{-\infty}^{\infty} f(t)e^{-j\omega t} dt$$


$$s = \sigma + j\omega \quad \sigma = 0, s \rightarrow j\omega \quad j = \sqrt{-1}$$

$$f(t) \rightarrow F(s) \quad F(s) \rightarrow f(t)$$

Transform: reversible

Quantum Physics:
Momentum relates to
Fourier Transform of
position

1st order example

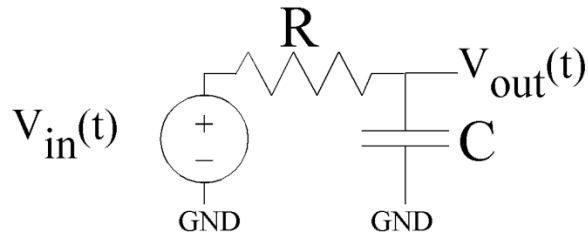

$$s \rightarrow j\omega \quad \omega = 2\pi f$$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{1 + j\omega\tau}$$


$$|a + jb| = \sqrt{a^2 + b^2}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + s\tau}$$




$$|H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2\tau^2}}$$

$$\text{Phase} = \tan^{-1}(\omega\tau)$$

2nd-Order
Low-Pass




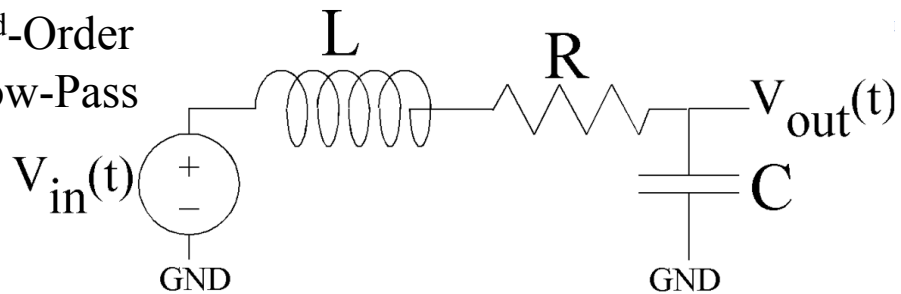

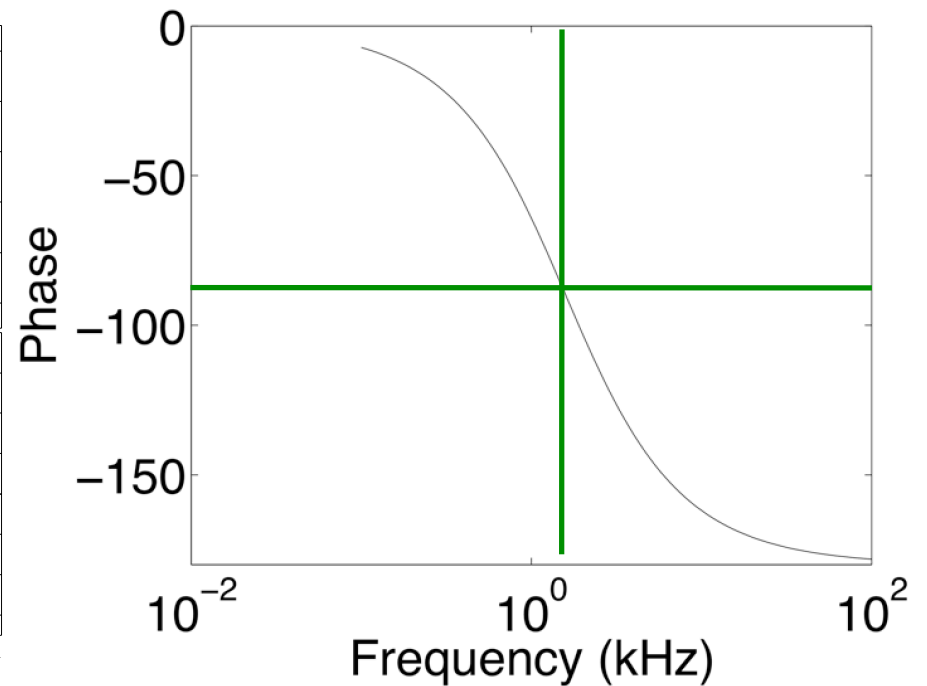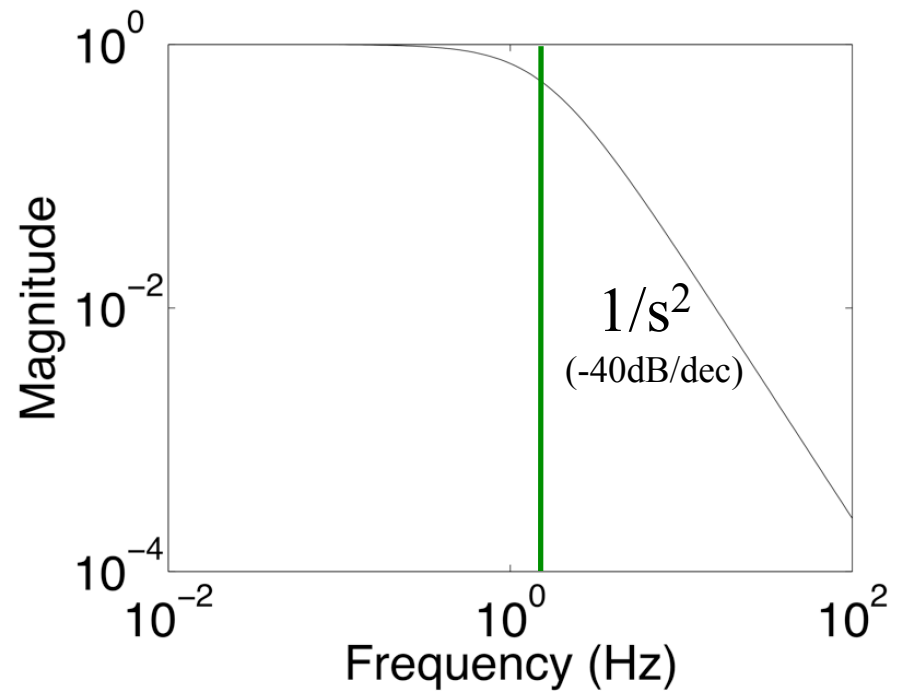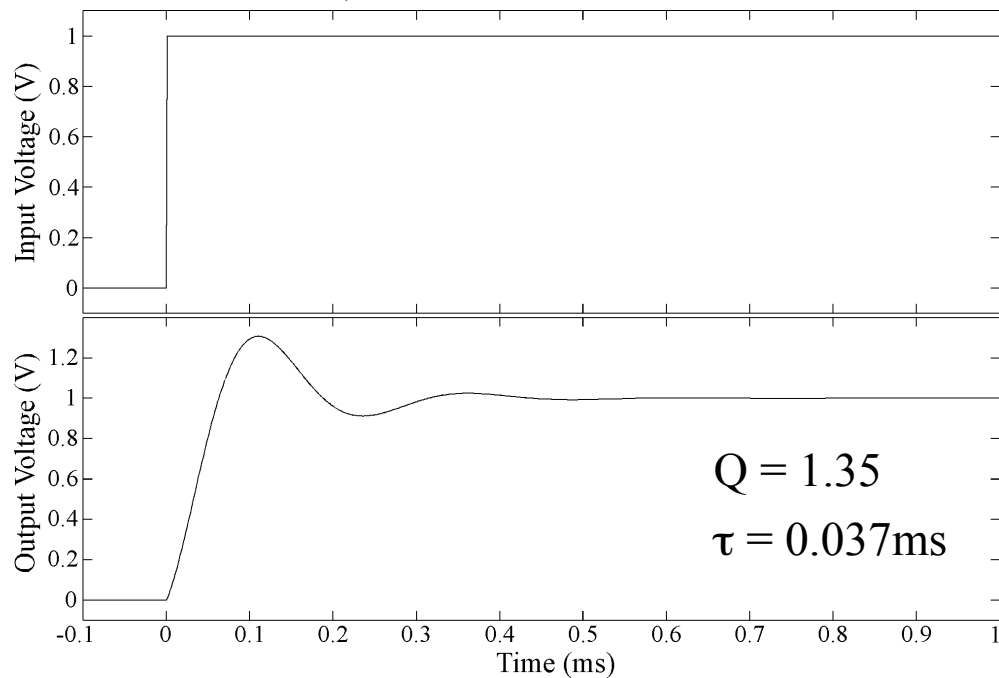
$$H(s) = \frac{1}{1 + s\tau/Q + s^2\tau^2} = \frac{1}{s^2LC + sRC + 1}$$




2nd-Order
Band-Pass

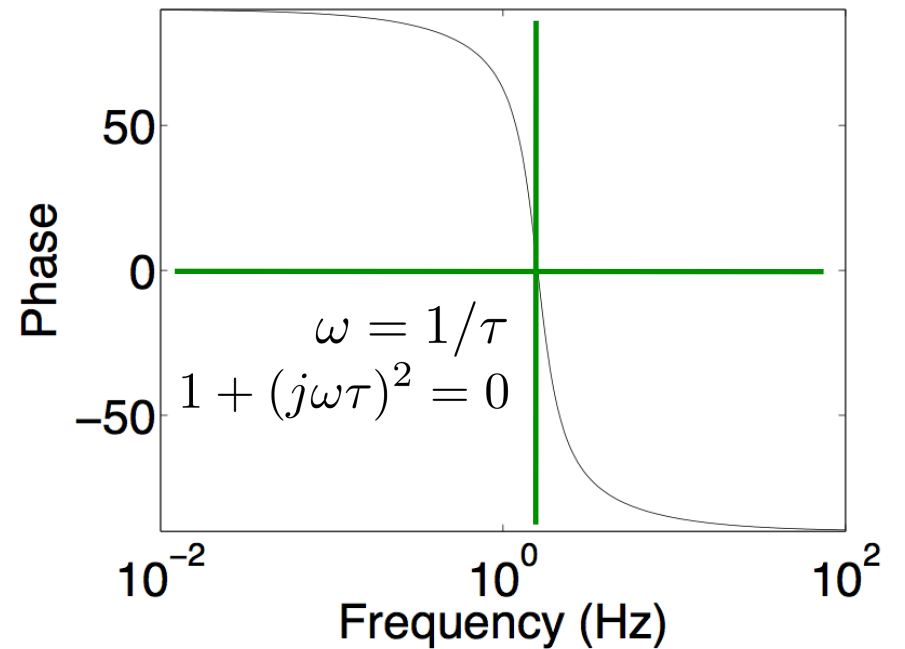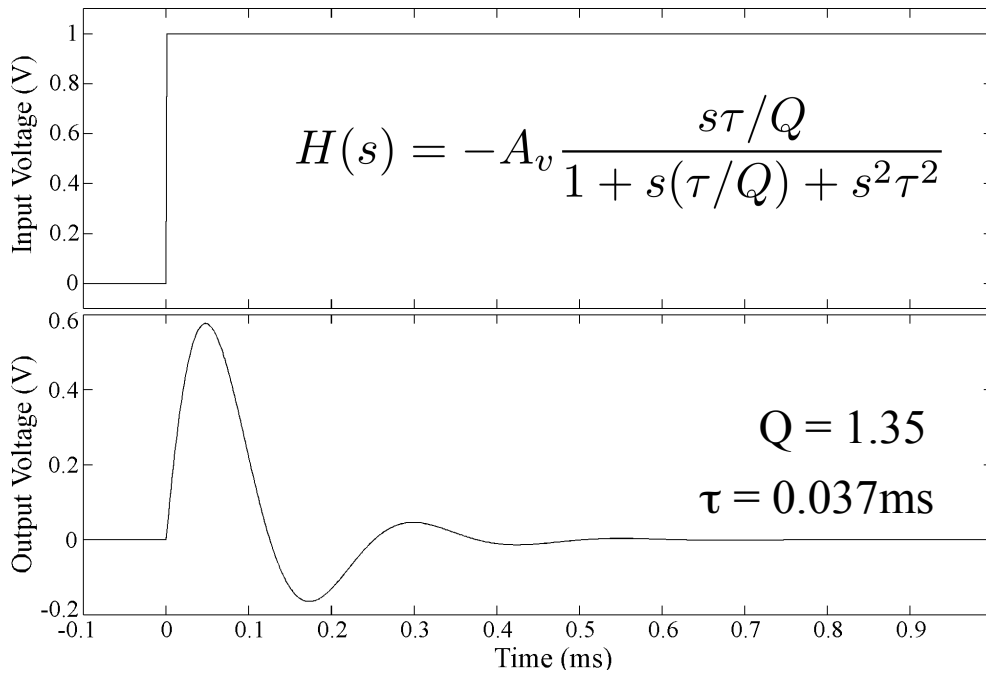
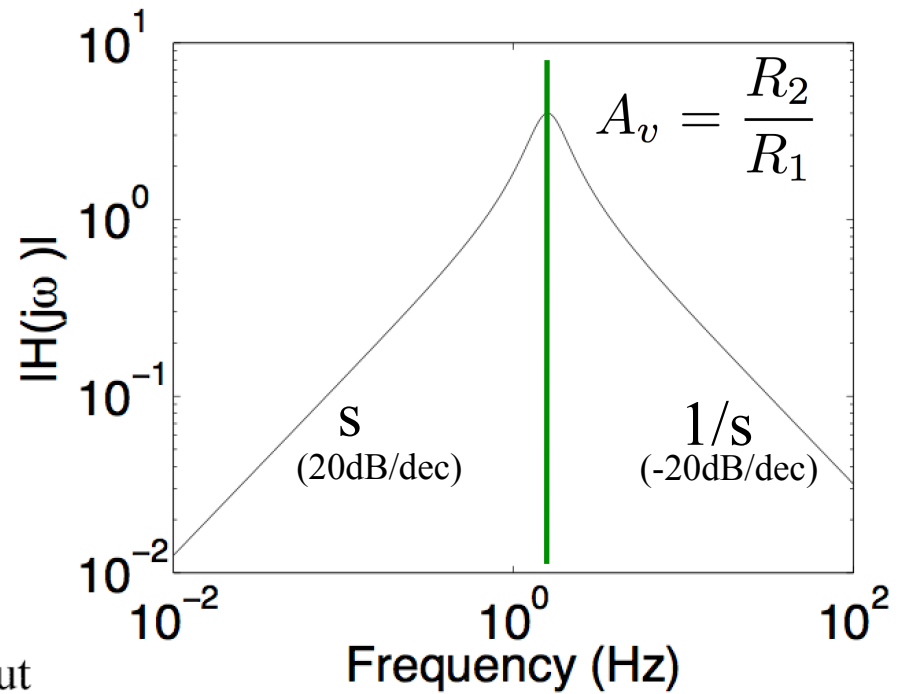
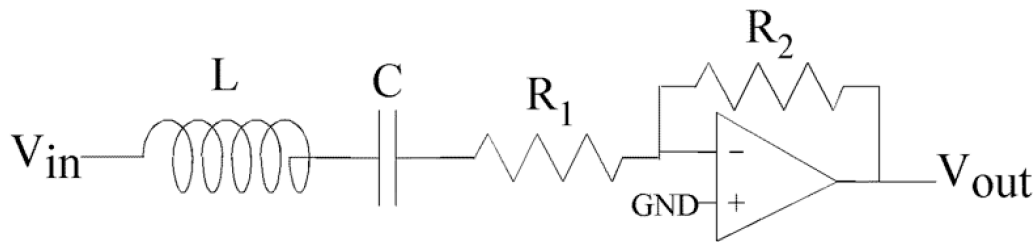
$$H(s) = -\frac{sR_2C}{1 + sR_1C + s^2LC}$$






2nd-Order High-Pass

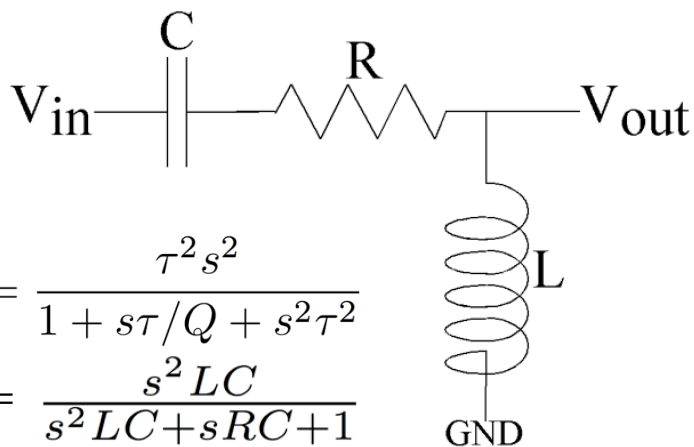
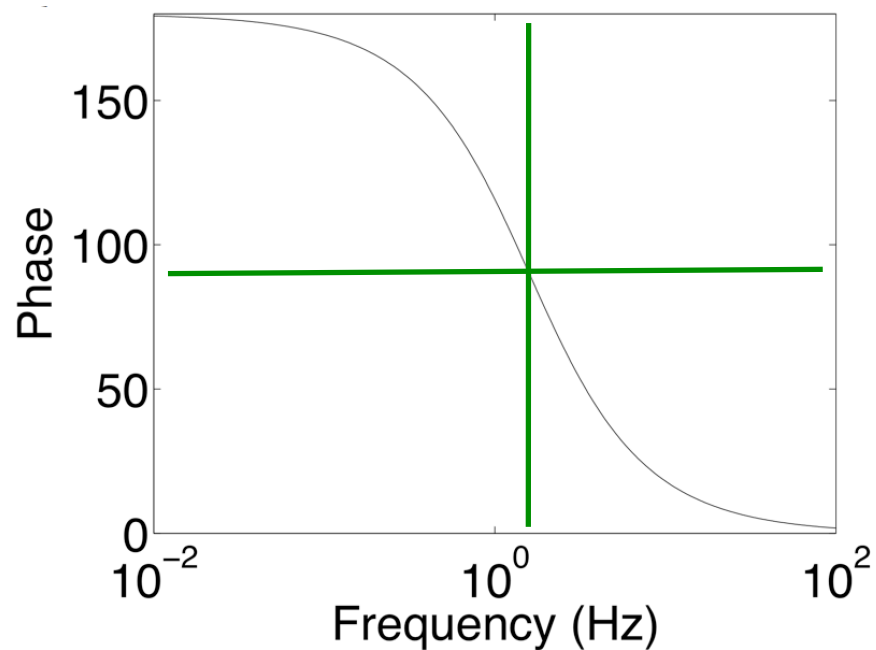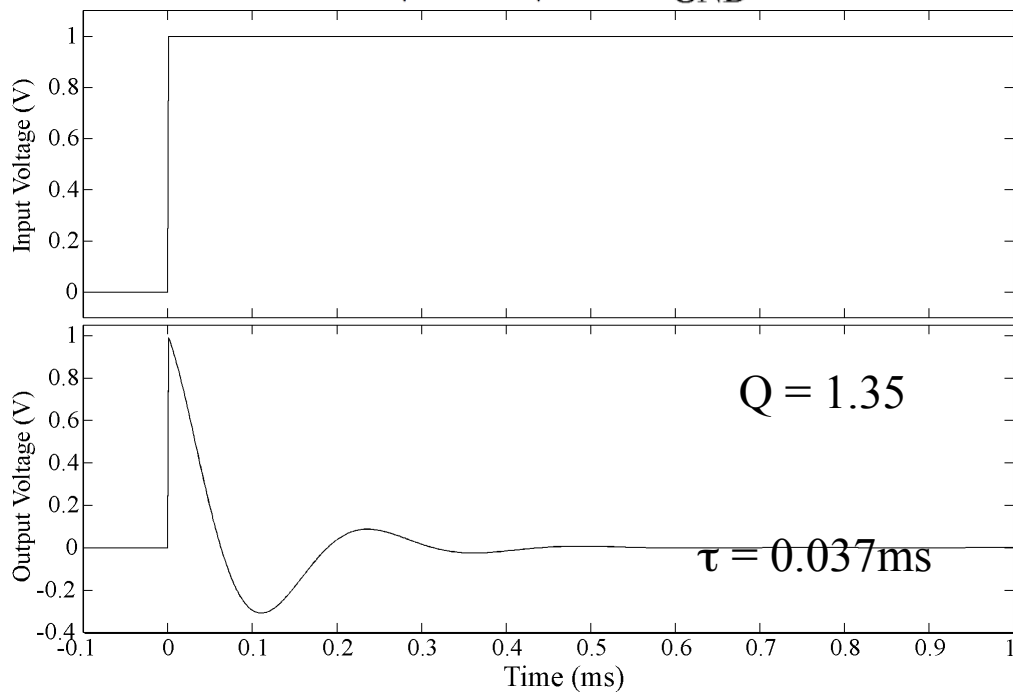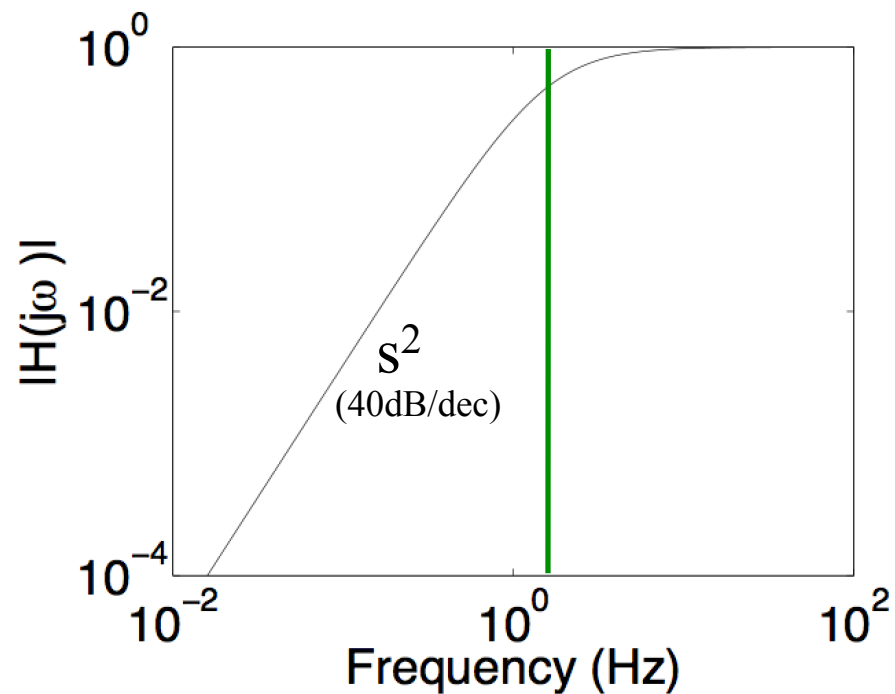
$$H(s) = \frac{\tau^2 s^2}{1 + s\tau/Q + s^2\tau^2}$$
$$= \frac{s^2 LC}{s^2 LC + sRC + 1}$$



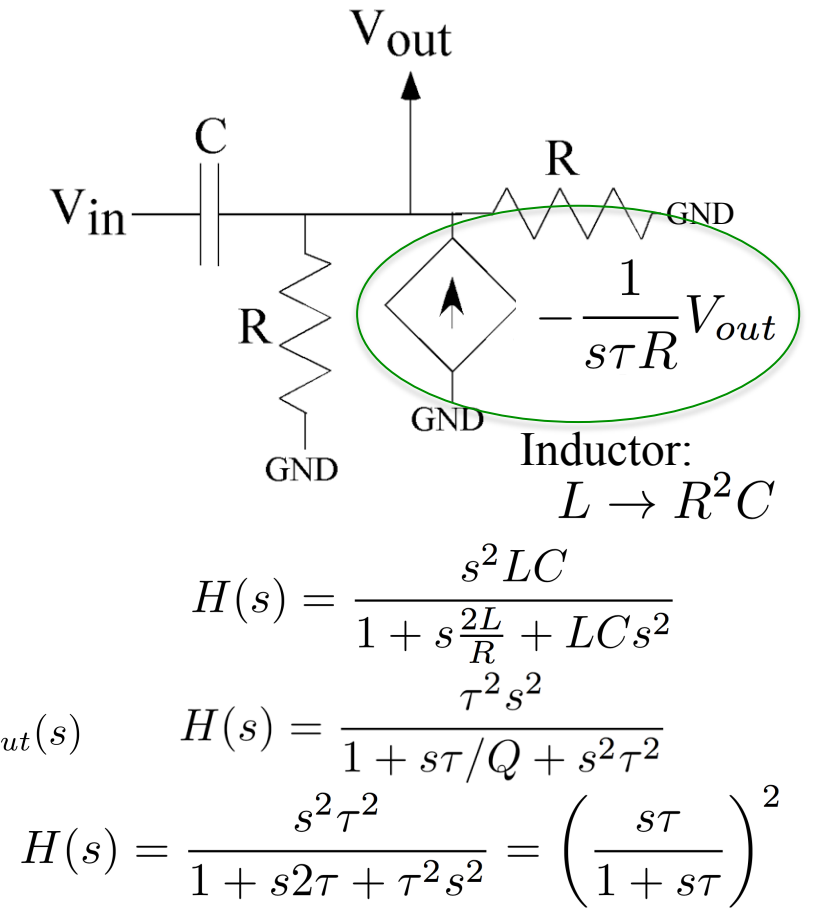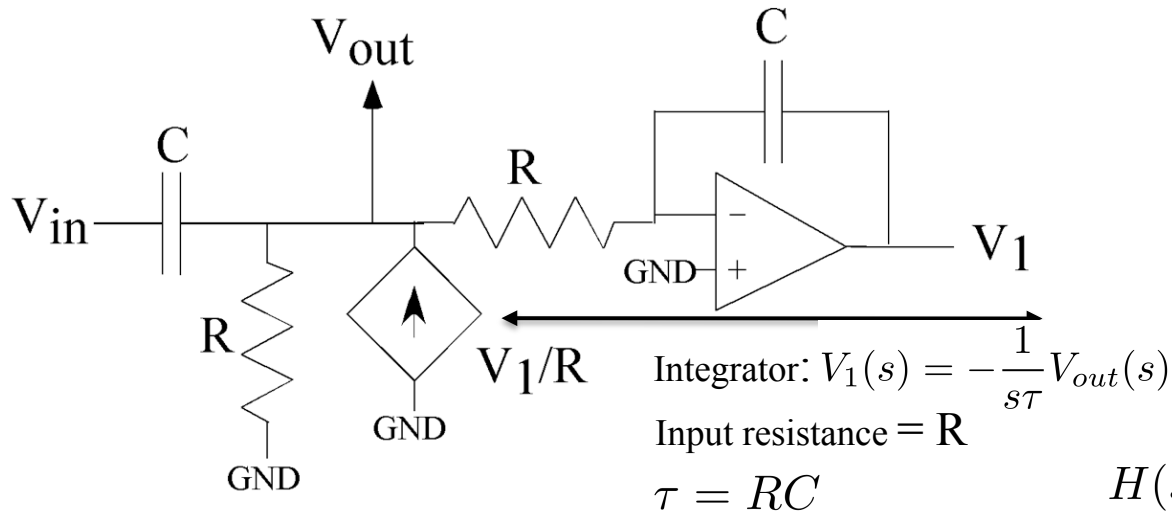

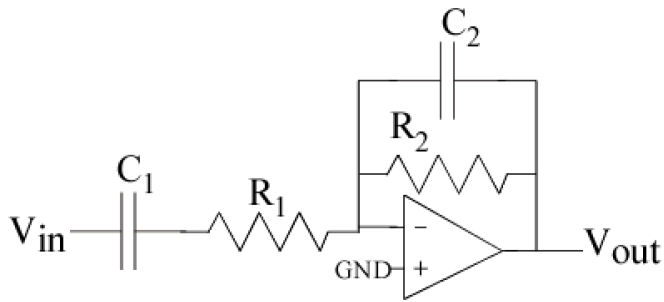

$$R_1 = 10\text{k}\Omega$$

$$R_2 = 100\text{k}\Omega$$

$$C_2 = 10\text{pF}$$

$$C_1 = 1\text{nF}$$

$$\begin{aligned}
 H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2 // \frac{1}{sC_2}}{R_1 + \frac{1}{sC_1}} \\
 &= -\frac{1}{\left(R_1 + \frac{1}{sC_1}\right)\left(\frac{1}{R_2} + sC_2\right)} \\
 &= -\frac{sR_2C_1}{(1 + sR_1C_1)(1 + sR_2C_2)} \\
 &= -\frac{R_2}{R_1} \frac{s\tau_1}{(1 + s\tau_1)(1 + s\tau_2)} \\
 &= -\frac{R_2}{R_1} \frac{s\tau_1}{(1 + s\tau_1)} \frac{1}{(1 + s\tau_2)}
 \end{aligned}$$

10
HPF
LPF

$$\tau_1 = R_1C_1$$

$$\tau_2 = R_2C_2$$

$$R_1C_1 > R_2C_2$$

$$\tau_1 = 10\mu\text{s}$$


$$(f_1 = 16\text{kHz})$$


$$\tau_2 = 1\mu\text{s}$$

$$(f_2 = 160\text{kHz})$$

$$H(j\omega) = -\frac{R_2}{R_1} \frac{j\omega\tau_1}{(1 + j\omega\tau_1)} \frac{1}{(1 + j\omega\tau_2)}$$

HPF
L.PF

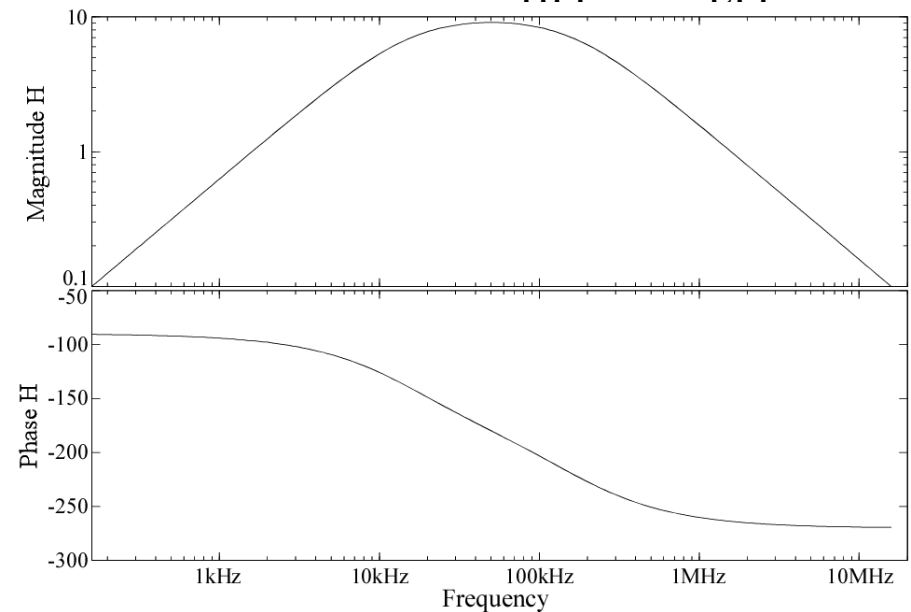

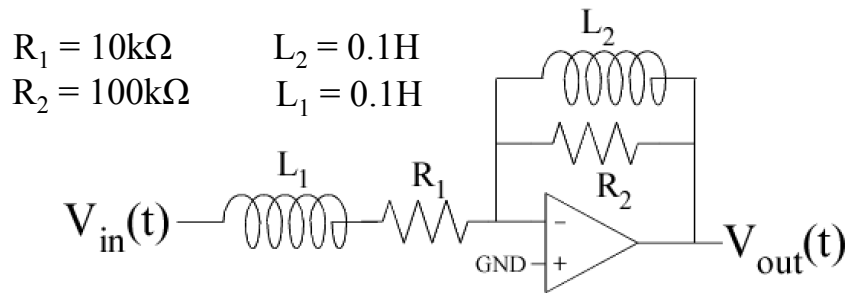

$$\begin{aligned}
 H(s) &= -\frac{R_2 // sL_2}{R_1 + sL_1} \\
 &= -\frac{R_2}{R_1} \frac{s(L_2/R_2)}{1 + s(L_2/R_2)} \frac{1}{R_1 + sL_1} \\
 &= -\frac{R_2}{R_1} \frac{sL_2}{R_2 + sL_2} \frac{1}{1 + s(L_1/R_1)}
 \end{aligned}$$

$\tau_2 = L_1/R_1 = 10\mu\text{s}$ $(f_1 = 16\text{kHz})$
 $\tau_1 = L_2/R_2 = 1\mu\text{s}$ $(f_1 = 160\text{kHz})$
 $L_1/R_1 > L_2/R_2$


HPF LPF


$$= -\frac{R_2}{R_1} \frac{s\tau_1}{(1 + s\tau_1)} \frac{1}{(1 + s\tau_2)}$$

HPF LPF

$$H(j\omega) = -\frac{R_2}{R_1} \frac{j\omega\tau_1}{(1 + j\omega\tau_1)} \frac{1}{(1 + j\omega\tau_2)}$$



10 HPF LPF

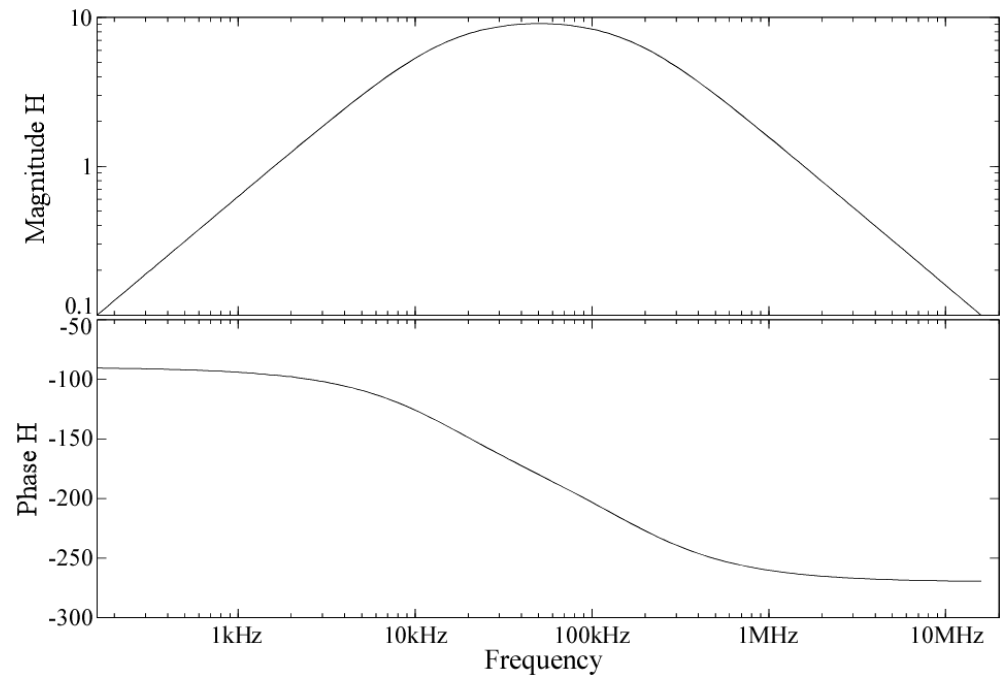


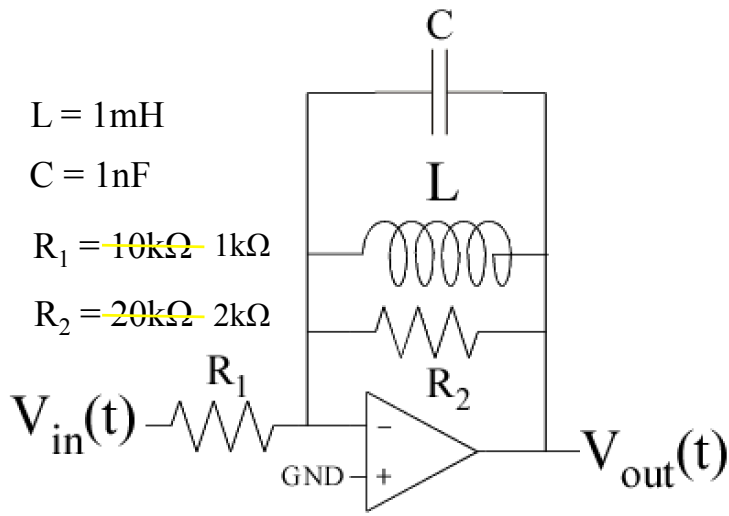


$$\begin{aligned}
 H(s) &= \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2 // sL // \frac{1}{sC}}{R_1} \\
 &= -\frac{\frac{1}{sC + \frac{1}{R_2} + \frac{1}{sL}}}{R_1} \\
 &= -\frac{R_2}{R_1} \frac{sL}{s^2 CLR_2 + sL + R_2} \\
 &= -\frac{R_2}{R_1} \frac{s(L/R_2)}{s^2 LC + s(L/R_2) + 1} \\
 &= -\frac{R_2}{R_1} \frac{s(\tau/Q)}{s^2 \tau^2 + s(\tau/Q) + 1}
 \end{aligned}$$

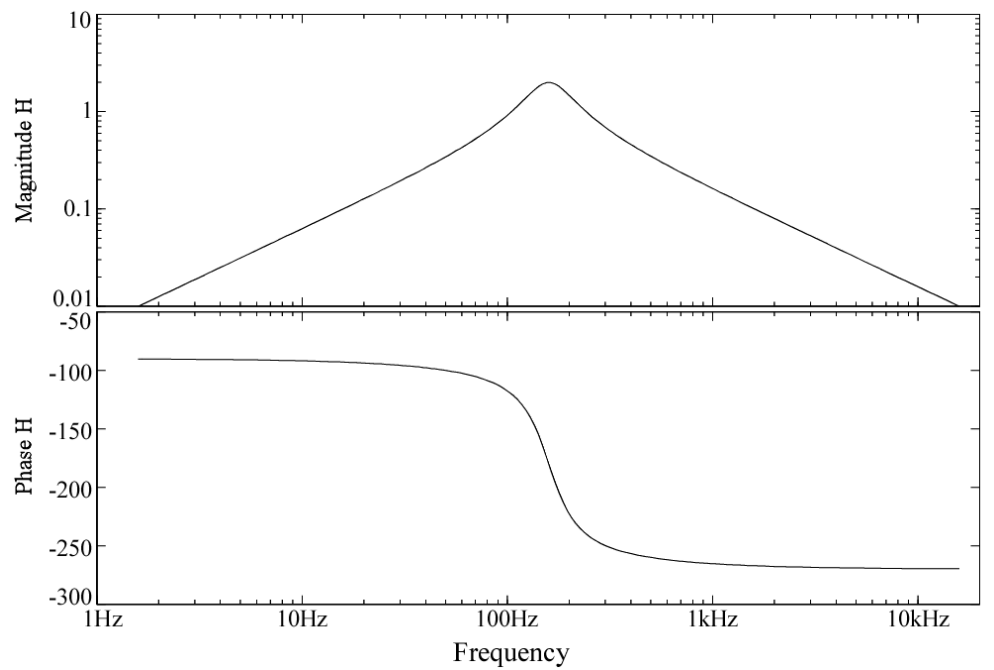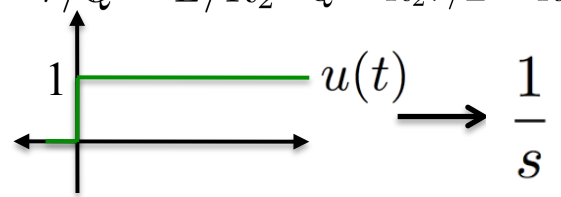$\tau^2 = LC, \tau = 1\mu\text{s} \quad R_{LC} = \sqrt{L/C} = 1\text{k}\Omega$
 $\tau/Q = L/R_2 \quad Q = R_2\tau/L = R_2\sqrt{\frac{C}{L}} = 2$


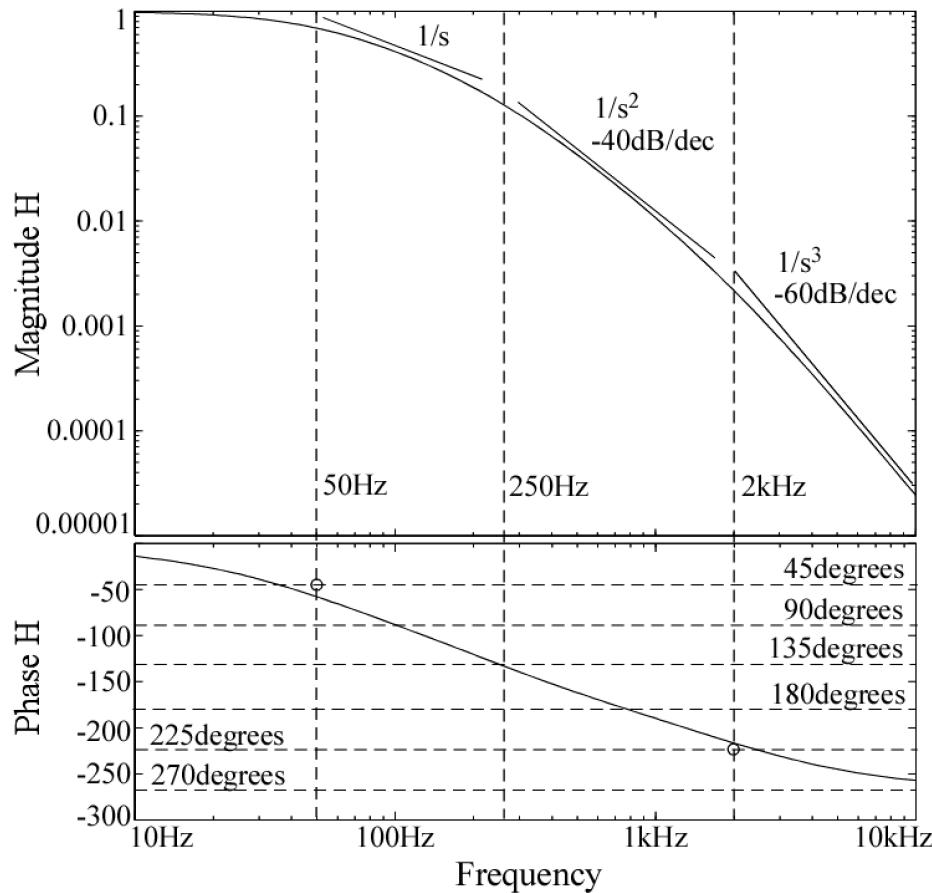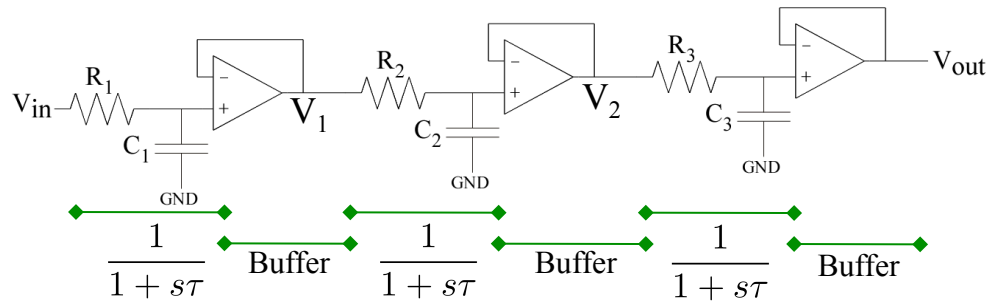
$$\begin{aligned}
 V_{out}(s) &= -\frac{R_2}{R_1} \frac{1}{Q\tau} \frac{1}{s^2 + s\frac{1}{Q\tau} + \frac{1}{\tau^2}} \\
 e^{-at} \sin(\omega_1 t) u(t) &\longleftrightarrow \frac{\omega_1}{(s+a)^2 + \omega_1^2} \\
 V_{out}(t) &= -\frac{R_2}{R_1} \frac{1}{\sqrt{1 - \frac{1}{4Q^2}}} e^{-t/(2Q\tau)} \sin\left(\frac{t}{\tau} \sqrt{1 - \frac{1}{4Q^2}}\right)
 \end{aligned}$$



$$R_1=1\text{k}\Omega \quad R_2=3\text{k}\Omega \quad R_3=4\text{k}\Omega$$

$$C_1=3\mu\text{F} \quad C_2=210\text{nF} \quad C_3=20\text{nF}$$

$$\text{Define: } \tau_1 = R_1 C_1, \tau_2 = R_2 C_2, \tau_3 = R_3 C_3$$

$$\tau_1=3.2\text{ms} \quad \tau_2=637\mu\text{s} \quad \tau_3=79.6\mu\text{s}$$


$$H(s) = \frac{1}{(1 + s\tau_1)(1 + s\tau_2)(1 + s\tau_3)}$$

$$H(j\omega) = \frac{1}{(1 + j\omega\tau_1)(1 + j\omega\tau_2)(1 + j\omega\tau_3)}$$


$$\text{dB of amplitude (x): } 20 \log_{10} x$$

$$\begin{aligned} \text{of power } (\rightarrow x^2): & 10 \log_{10} x^2 \\ & = 20 \log_{10} x \end{aligned}$$

(e.g. $P = V^2/R$ for a Resistor)

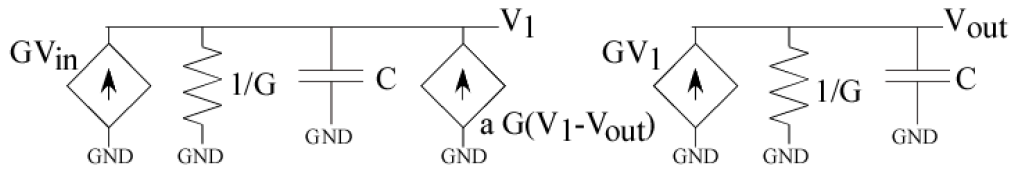

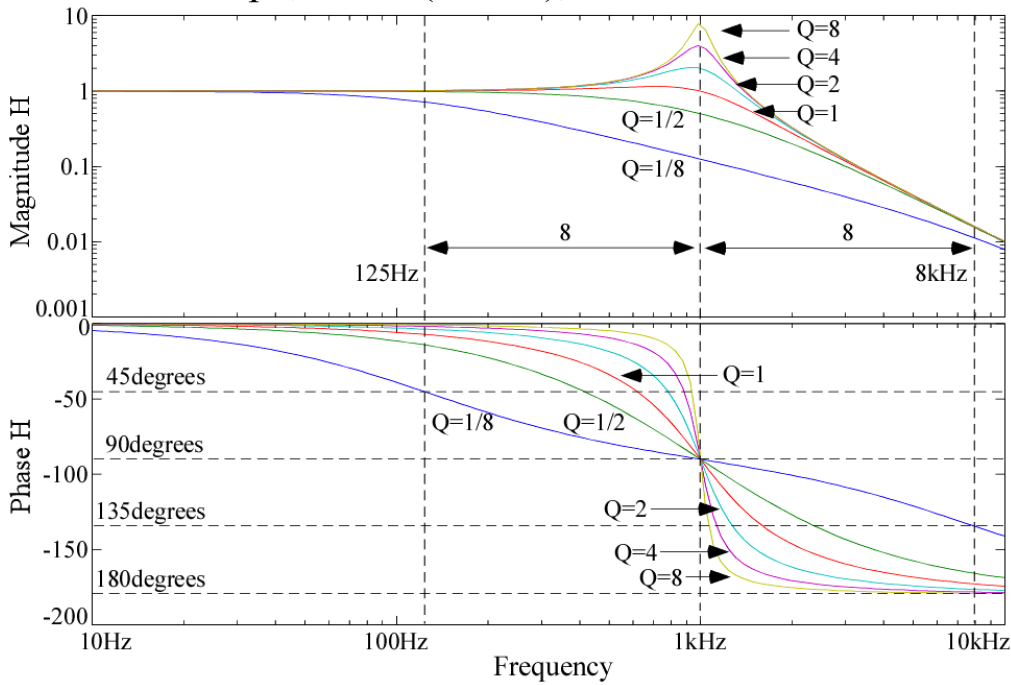$C = 4\text{pF}$, $G = 1/(40\text{M}\Omega)$, $C/G = 0.16\text{ms}$



$$sCV_1 + GV_1 = GV_{in} + aG(V_1 - V_{out})$$

$$sCV_{out} + GV_{out} = GV_1$$

$$\tau = C/G$$

$$(1 - a + s\tau)V_1 = V_{in} - aV_{out}$$


$$(1 + s\tau)V_{out} = V_1$$

$$(1 - a + s\tau)(1 + s\tau)V_{out} = V_{in} - aV_{out}$$

$$[(1 - a + s\tau)(1 + s\tau) + a]V_{out} = V_{in}$$


$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + s\tau(2 - a) + s^2\tau^2}$$
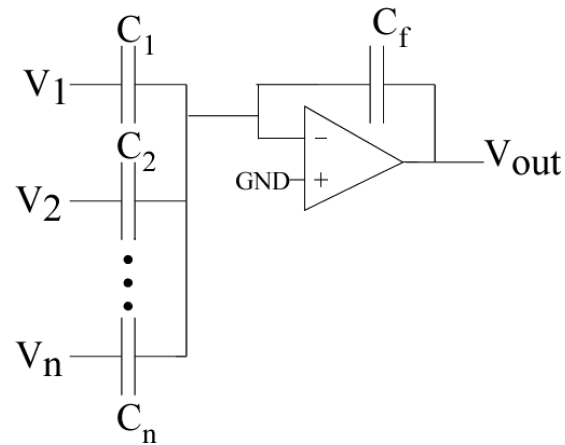
$$f_c = \frac{1}{2\pi\tau} \quad Q = \frac{1}{2 - a}$$



$$sC_1V_1 + sC_2V_2 + \dots + sC_nV_n = -sC_fV_{out}$$
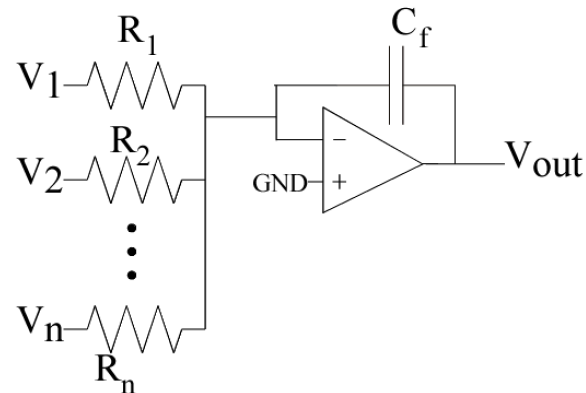
$$V_{out} = V_{offset} - \sum_{k=1}^n \frac{C_k}{C_f} V_k$$




$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = -sC_fV_{out}$$

$$V_{out} = - \sum_{k=1}^n \frac{1}{sC_f R_k} V_k$$

Summation by Current / Charge

KCL: Sum of currents in = current out

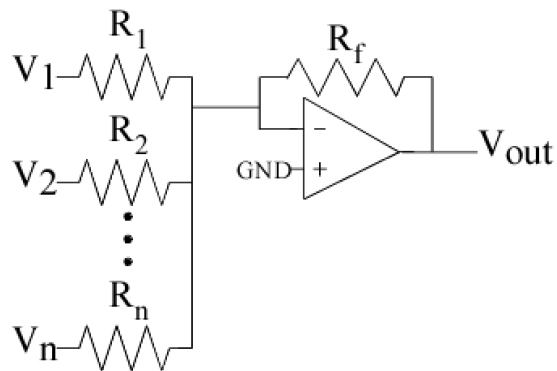


KCL at - Terminal:

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} = -\frac{V_{out}}{R_f}$$



$$V_{out} = - \sum_{k=1}^n \frac{R_f}{R_k} V_k$$

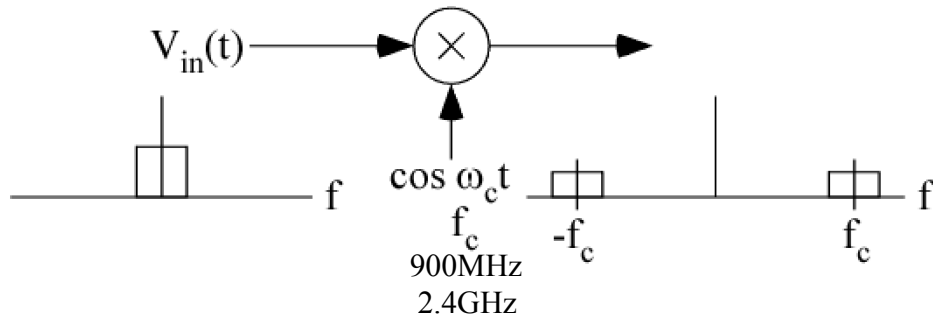Some circuits operate at a single or near single frequency:
 Communications, modulated signals




Another key application: Power Transmission (e.g. 60Hz US)

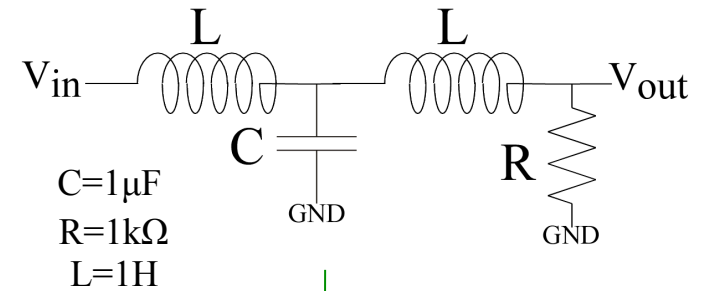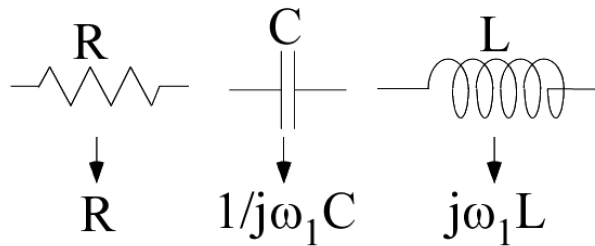→ circuit elements: Resistance at a single frequency (f_1, ω_1)



$\omega_1 \sim 1 \text{krad/s}$

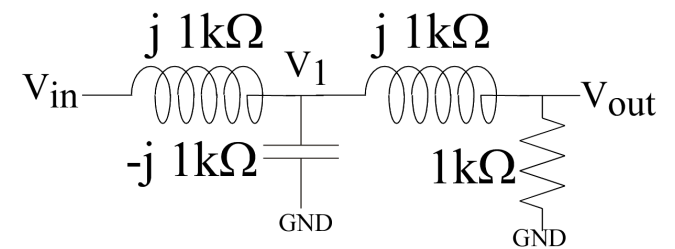

$$\frac{V_{in} - V_1}{j1k\Omega} + \frac{V_{out} - V_1}{j1k\Omega} = \frac{V_1}{-j1k\Omega}$$



$$V_{in} - V_1 + V_{out} - V_1 + V_1 = 0 \rightarrow V_1 = V_{in} + V_{out}$$

$$\frac{V_1 - V_{out}}{j1k\Omega} = \frac{V_{out}}{1k\Omega}$$


$$V_1 = V_{out}(1 + j)$$

$$V_{in} + V_{out} = V_{out}(1 + j) \rightarrow V_{out} = -jV_{in}$$

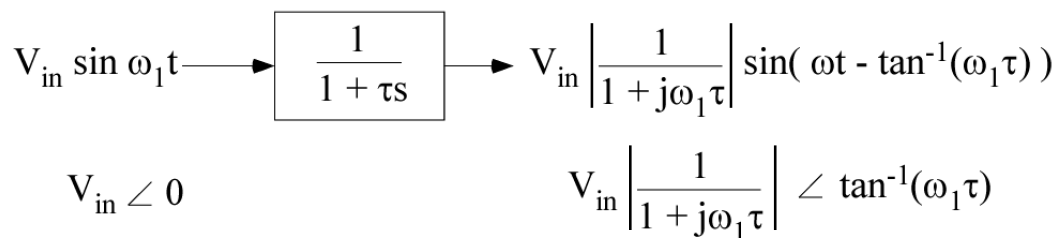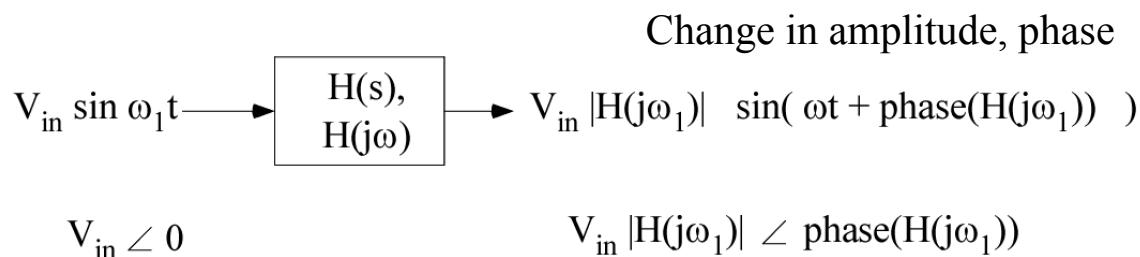Sinusoidal input \rightarrow Linear System \rightarrow Output Sinusoid
 freq f_1 freq f_1



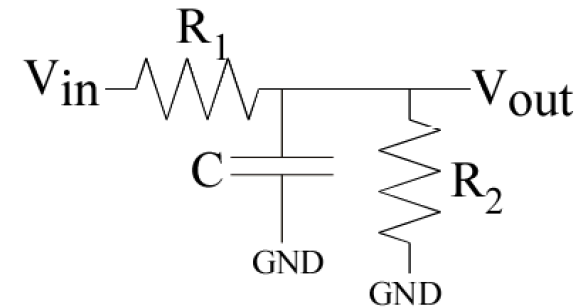Phasors: Frequency assumed; just amplitude and phase



$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_1 // \frac{1}{sC}}{R_1 + R_1 // \frac{1}{sC}} = \frac{R_2}{R_1 + R_2} \frac{1}{1 + s\tau}$$

$$\tau = (R_1 // R_2)C$$

$$|H(j\omega)| = \frac{R_2}{R_1 + R_2} \frac{1}{\sqrt{1 + (\omega\tau)^2}} \quad \text{Phase: } \tan^{-1}(\omega\tau)$$

Input: $V_{in} \sin \omega_1 t \rightarrow V_{in} \angle 0$

Output: $V_{in} |H(j\omega_1)| \angle -\tan^{-1} \omega_1 \tau$

Input is 1V sinusoid, 0 phase


$C = 1\mu\text{F} \quad R_1 = 2\text{k}\Omega \quad R_2 = 2\text{k}\Omega$

$\tau = 1\text{ms} \quad |H(j\omega)| = \frac{1}{2} \frac{1}{\sqrt{1 + (\omega\tau)^2}}$


At 160Hz ($\sim 1\text{krad/s}$):

$1\text{V} \angle 0 \rightarrow 0.354\text{V} \angle -45^\circ$


Low-Pass Filter

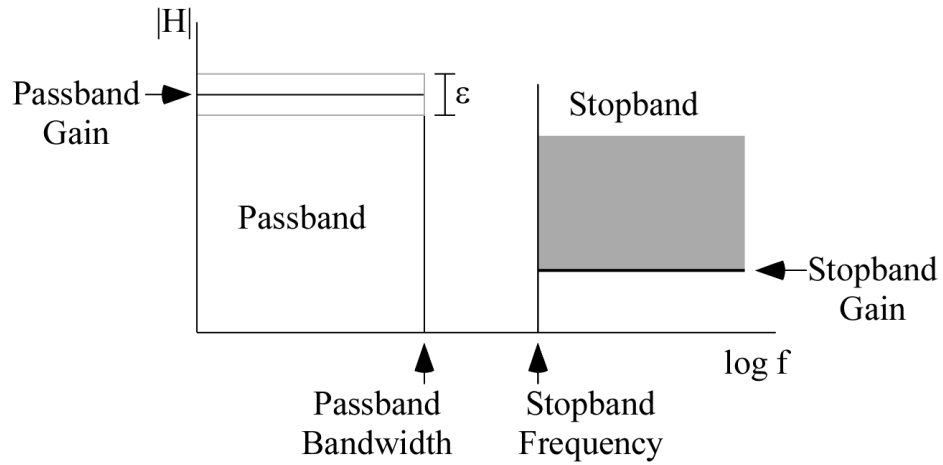


High-Pass Filter

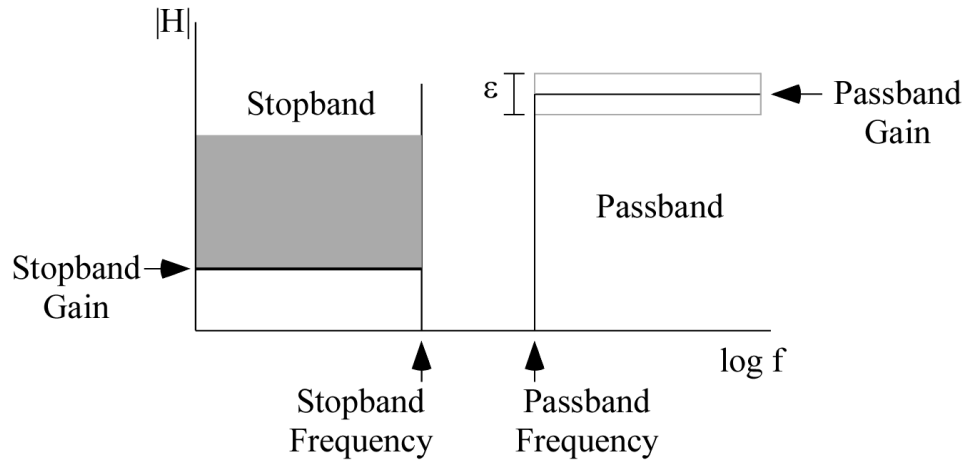

BandPass Filter

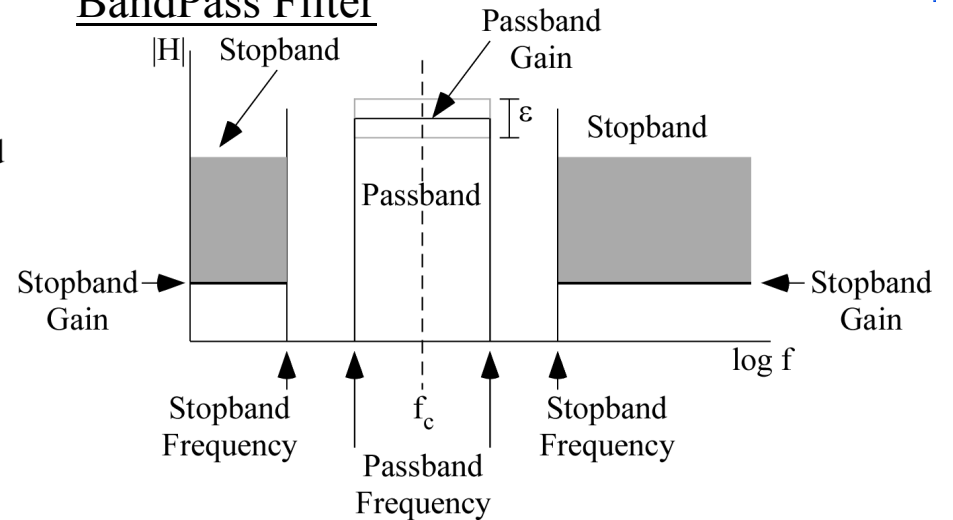

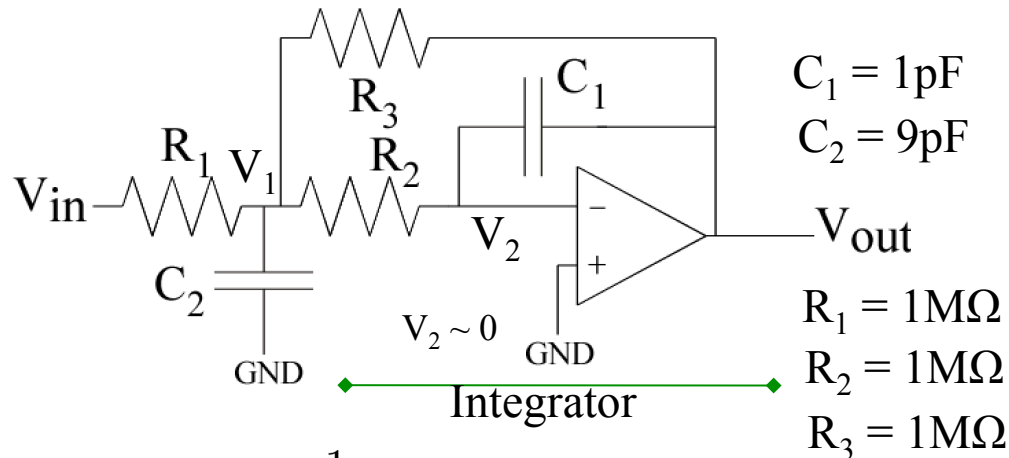

$$V_{out} = -V_1 \frac{1}{sR_2C_1} \rightarrow -sR_2C_1V_{out} = V_1$$

$$sC_2V_1 = \frac{V_{in} - V_1}{R_1} + \frac{V_{out} - V_1}{R_3} - \frac{V_1}{R_2}$$

$$\left(sC_2 + \frac{1}{R_1 // R_2 // R_3}\right)V_1 = \frac{V_{in}}{R_1} + \frac{V_{out}}{R_3}$$

$$-\left(sC_2 + \frac{1}{R_1 // R_2 // R_3}\right)sR_2C_1V_{out} = \frac{V_{in}}{R_1} + \frac{V_{out}}{R_3}$$

$$\left(s^2R_2R_3C_1C_2 + s\frac{R_3R_2}{R_1 // R_2 // R_3}C_1 + 1\right)V_{out} = -\frac{R_3}{R_1}V_{in}$$

$$\left(s^2R_2R_3C_1C_2 + s\left(R_2 + R_3 + \frac{R_2R_3}{R_1}\right)C_1 + 1\right)V_{out} = -\frac{R_3}{R_1}V_{in}$$

$$\tau^2 = R_2R_3C_1C_2 \quad \text{gain} = -\frac{R_3}{R_1}$$


$$\frac{\tau}{Q} = \left(R_2 + R_3 + \frac{R_2R_3}{R_1}\right)C_1$$

$$Q = \frac{\tau}{\left(R_2 + R_3 + \frac{R_2R_3}{R_1}\right)C_1}$$

$$= \sqrt{\frac{C_2}{C_1}} \frac{\sqrt{R_2R_3}}{\left(R_2 + R_3 + \frac{R_2R_3}{R_1}\right)}$$

$$\tau = 3\mu\text{s} \quad \text{gain} = -1 \quad Q = 1$$

Rauch Biquadratic cell

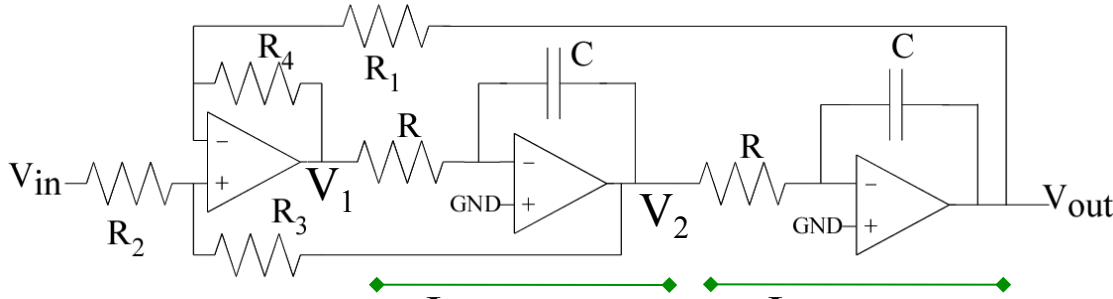

$$C_2 = 1\text{nF}$$

Integrator
Integrator

$$V_2 = -V_1 \frac{1}{sRC} \quad V_{out} = -V_2 \frac{1}{sRC}$$

$$V_1 = -\frac{R_4}{R_1} V_{out} + \frac{R_4 + R_1}{R_1} \left(\frac{R_3 V_{in}}{R_3 + R_2} + \frac{R_2 V_2}{R_2 + R_3} \right)$$

$$s^2 (RC)^2 V_{out} = -\frac{R_4}{R_1} V_{out} + \frac{R_4 + R_1}{R_1} \left(\frac{R_3 V_{in}}{R_3 + R_2} - \frac{R_2 s(RC) V_{out}}{R_2 + R_3} \right)$$

$$\left(s^2 (RC)^2 + \frac{R_4 + R_1}{R_1} \frac{s(RC) R_2}{R_2 + R_3} + \frac{R_4}{R_1} \right) V_{out} = \frac{R_4 + R_1}{R_1} \left(\frac{R_3 V_{in}}{R_3 + R_2} \right)$$

$$(s^2 (RC)^2 R_1 (R_2 + R_3) + s(RC) R_2 (R_4 + R_1) + R_4 (R_2 + R_3)) V_{out} = (R_4 + R_1) R_3 V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{(R_4 + R_1) R_3}{s^2 (RC)^2 R_1 (R_2 + R_3) + s(RC) R_2 (R_4 + R_1) + R_4 (R_2 + R_3)}$$

(LPF)

$$\tau = RC \sqrt{\frac{R_1}{R_4}} \quad \text{Gain} = \frac{R_4 + R_1}{R_4} \frac{R_3}{R_2 + R_3}$$



Kerwin-Huelsman-Newcomb Circuit

$$V_2 \rightarrow \text{BPF} \quad V_1 \rightarrow \text{HPF}$$


$$\frac{\tau}{Q} = RC \frac{R_2}{R_2 + R_3} \frac{R_4 + R_1}{R_4}$$

$$Q = \frac{RC \sqrt{\frac{R_1}{R_f}}}{RC \frac{R_2}{R_2 + R_3} \frac{R_4 + R_1}{R_4}} = \frac{R_2 + R_3}{R_2} \frac{\sqrt{R_4 R_1}}{R_4 + R_1}$$

R_1	R_2	R_3	R_4	R	τ	Q
1k Ω	1k Ω	1k Ω	1k Ω	1k Ω	1 μ s	1
4k Ω	1k Ω	1k Ω	4k Ω	1k Ω	1 μ s	1
1k Ω	4k Ω	4k Ω	1k Ω	1k Ω	1 μ s	1
1k Ω	1k Ω	1k Ω	1k Ω	4k Ω	4 μ s	1
4k Ω	1k Ω	1k Ω	1k Ω	1k Ω	2 μ s	4/5
1k Ω	1k Ω	1k Ω	4k Ω	1k Ω	0.5 μ s	4/5

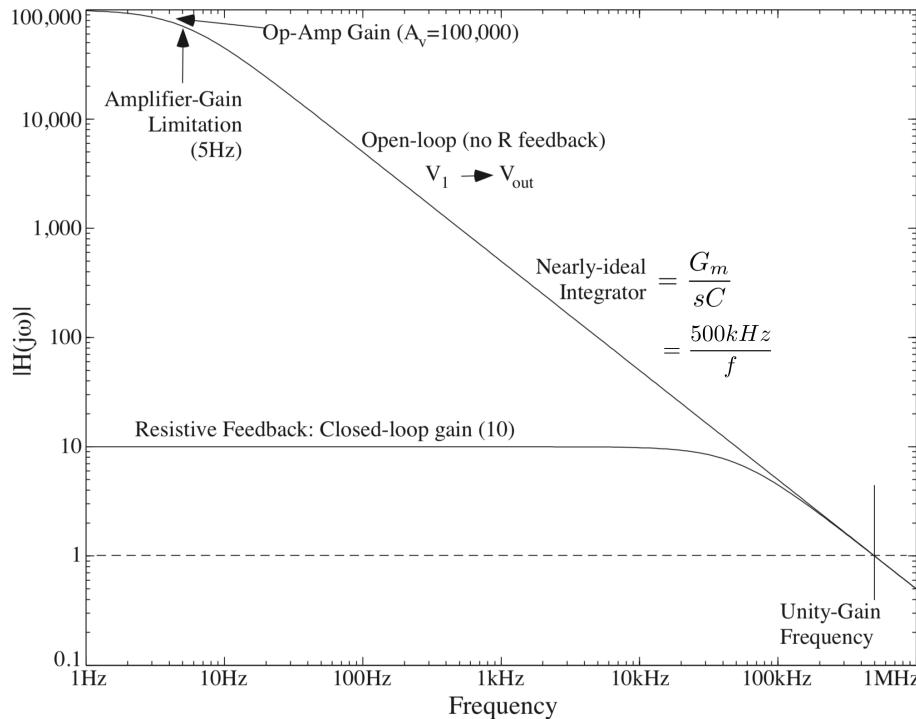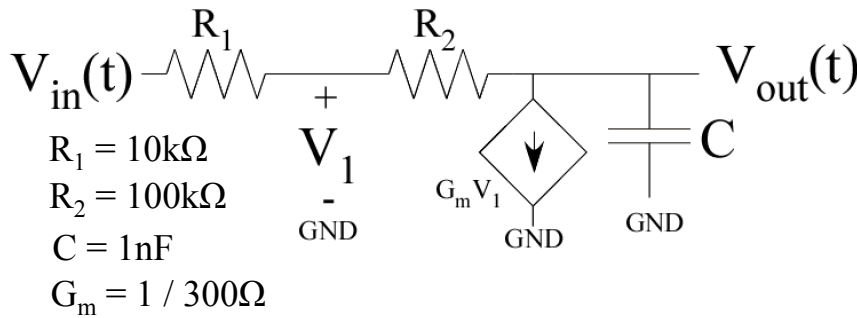

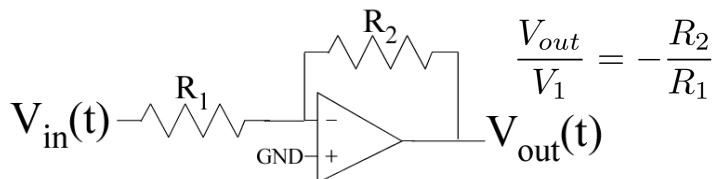Ideal Op-Amp: Output capacitance has no effect



Real Op-Amps can have a frequency response

$$\frac{V_{in} - V_1}{R_1} = \frac{V_1 - V_{out}}{R_2} = G_m V_1 + sC V_{out}$$

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = \frac{V_1}{R_1 // R_2}$$

$$R_2 V_{in} + R_1 V_{out} = (R_1 + R_2) V_1$$

$$\left(G_m - \frac{1}{R_2}\right) V_1 + \left(sC + \frac{1}{R_2}\right) V_{out} = 0$$

As $G_m \gg \frac{1}{R_2}$,


$$G_m V_1 + \left(sC + \frac{1}{R_2}\right) V_{out} = 0$$

$$G_m R_2 V_1 + (sC R_2 + 1) V_{out} = 0$$

$$V_{out} = -\frac{G_m R_2}{1 + sC R_2} V_1 \rightarrow = -\frac{G_m}{sC} V_1$$

$$\frac{V_{out}}{V_1} = -\frac{R_2}{R_1} \frac{1}{1 + \frac{1}{G_m} \frac{R_1 + R_2}{R_2 R_1} + s \frac{C}{G_m} \frac{R_1 + R_2}{R_1}}$$

10 0.033 (small) ~50kHz

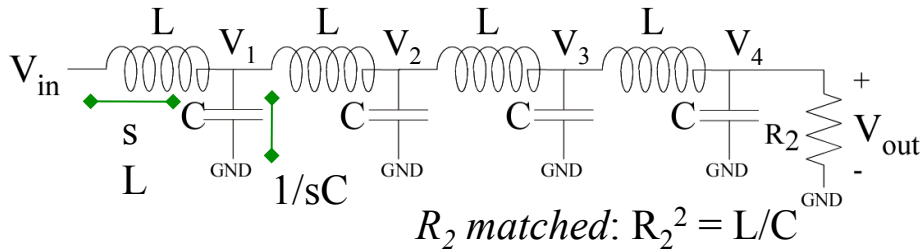

$$sCV_1 = \frac{V_{in} - V_1}{sL} + \frac{V_2 - V_1}{sL}$$

$$s^2LCV_1 = V_{in} - 2V_1 + V_2$$

$$\tau^2 = LC$$

$$s^2\tau^2 V_1 = V_{in} - 2V_1 + V_2$$

$$sCV_4 + \frac{V_4}{R_2} = \frac{V_3 - V_4}{sL}$$

$$(s^2\tau^2 + 2)V_1 = V_{in} + V_2$$

$$(s^2LC + s\frac{L}{R_2} + 1)V_4 = V_3$$

$$(s^2\tau^2 + 2)V_2 = V_1 + V_3$$

from matching:

$$(s^2\tau^2 + 2)V_3 = V_2 + V_4$$

$$(s^2\tau^2 + s\tau + 1)V_4 = V_3$$

$$(s^2\tau^2 + 2)^2 V_2 = (s^2\tau^2 + 2)V_1 + (s^2\tau^2 + 2)V_3$$

$$= V_{in} + 2V_2 + V_4$$



$$[(s^2\tau^2 + 2)^2 - 2] V_2 = V_{in} + V_4$$


$$(s^2\tau^2 + 2)(s^2\tau^2 + s\tau + 1)V_4 = V_2 + V_4$$

$$[(s^2\tau^2 + 2)(s^2\tau^2 + s\tau + 1) - 1] V_4 = V_2$$

$$([(s^2\tau^2 + 2)^2 - 2] [(s^2\tau^2 + 2)(s^2\tau^2 + s\tau + 1) - 1] - 1) V_4 = V_{in}$$
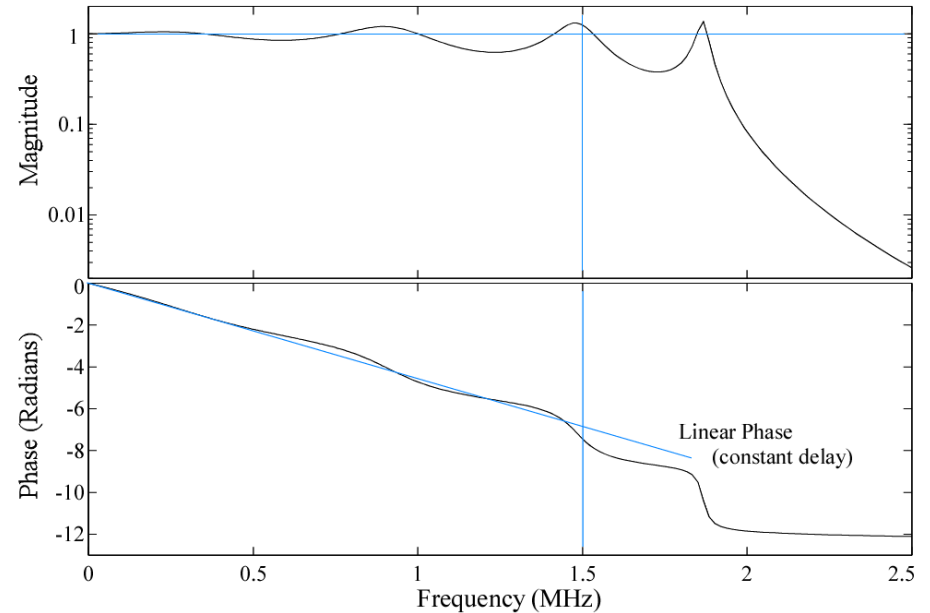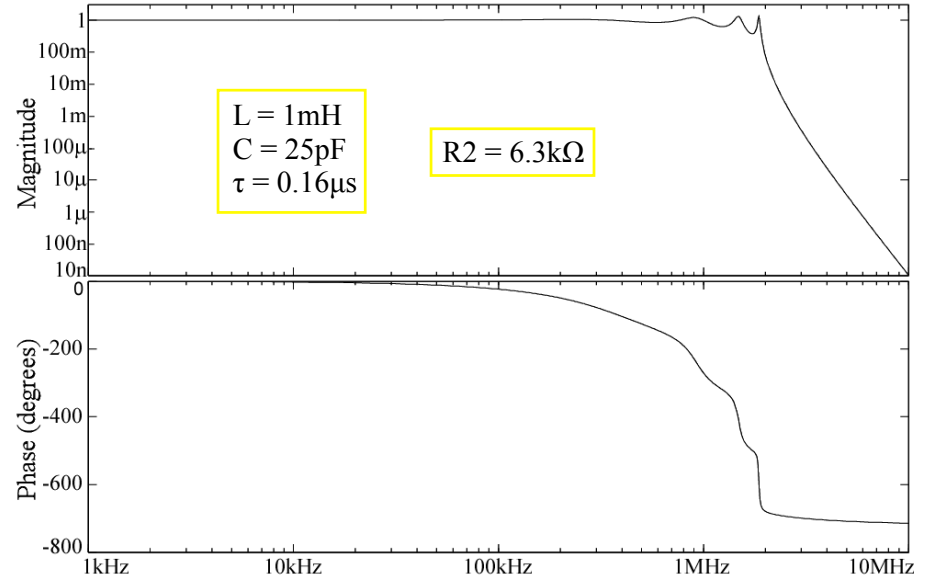
$$\frac{V_4}{V_{in}} = \frac{1}{s^8\tau^8 + s^7\tau^7 + 7s^6\tau^6 + 6s^5\tau^5 + 15s^4\tau^4 + 10s^3\tau^3 + 10s^2\tau^2 + 4s\tau + 1}$$



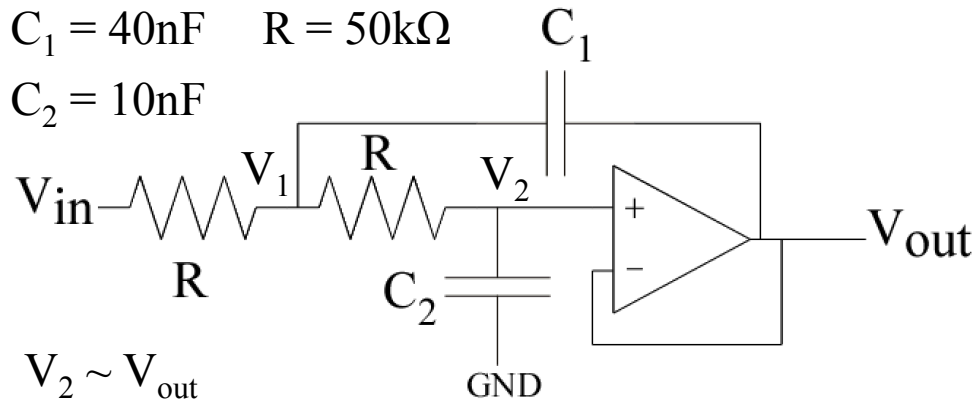

$$\frac{V_1 - V_{out}}{R} = sC_2 V_2 \rightarrow \tau_2 = RC_2, (1 + s\tau_2)V_{out} = V_1$$

$$\frac{V_{in} - V_1}{R} + \frac{V_{out} - V_1}{R} = sC_1(V_1 - V_{out})$$

$$\tau_1 = RC_1, V_{in} + (1 + s\tau_1)V_{out} = (2 + s\tau_1)V_1$$

$$V_{in} = ((2 + s\tau_1)(1 + s\tau_2) - (1 + s\tau_1)) V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{s^2\tau_1\tau_2 + 2s\tau_2 + s\tau_1 + 2 - 1 - s\tau_1}$$

$$= \frac{1}{s^2\tau_1\tau_2 + 2s\tau_2 + 1}$$

$$\tau^2 = \tau_1\tau_2 \quad \frac{\tau}{Q} = 2\tau_2, Q = \frac{\tau}{2\tau_2} = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$

$$= R\sqrt{C_1C_2}$$

$$\tau_1 = 2\text{ms}$$


$$\tau = 1\text{ms}$$

$$\tau_2 = 0.5\text{ms}$$

$$Q = 1$$

Sallen & Key 2nd Order Circuit

C_1	C_2	R	τ	Q
40nF	10nF	50k Ω	1ms	1
80nF	5nF	50k Ω	1ms	2
40nF	10nF	100k Ω	2ms	1
80nF	20nF	50k Ω	2ms	1

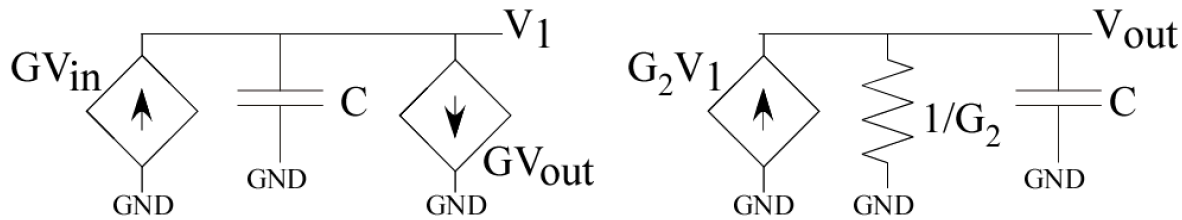

$$sCV_1 = G(V_{in} - V_{out}) \rightarrow \tau_1 = \frac{C}{G}, s\tau_1 V_1 = V_{in} - V_{out}$$

$$sCV_{out} + G_2V_{out} = G_2V_1 \rightarrow \tau_2 = \frac{C}{G_2}, (1 + s\tau_2)V_{out} = V_1$$

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + s\tau_1 + s^2\tau_1\tau_2}$$

$$\tau^2 = \tau_1\tau_2 \quad \tau_1 = \frac{\tau}{Q} \quad Q = \frac{\tau}{\tau_1} = \sqrt{\frac{\tau_2}{\tau_1}} = \text{sqrt}(G/G_2)$$

$$C = 1\text{pF}$$

$$G = 1 / 4\text{M}\Omega$$

$$G_2 = 1 / 1\text{M}\Omega$$


$$\tau_1 = 4\mu\text{s}$$

$$\tau = 2\mu\text{s}$$


$$\tau_2 = 1\mu\text{s}$$

$$Q = \underline{1/2}$$

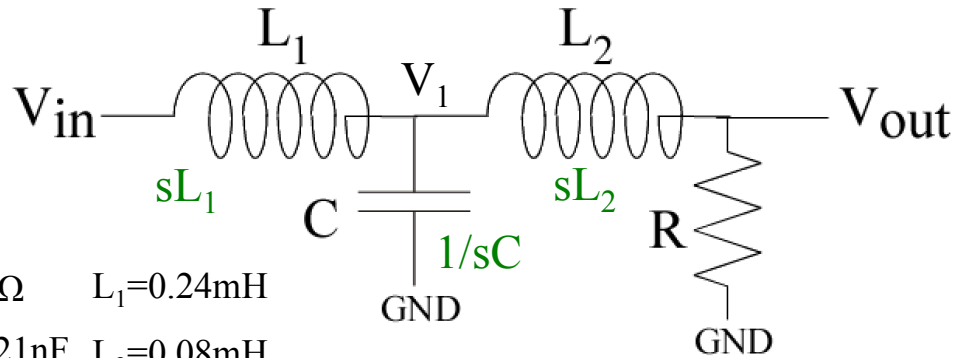Circuit: One form of Tau-Thomas;
also called Diff2 structure



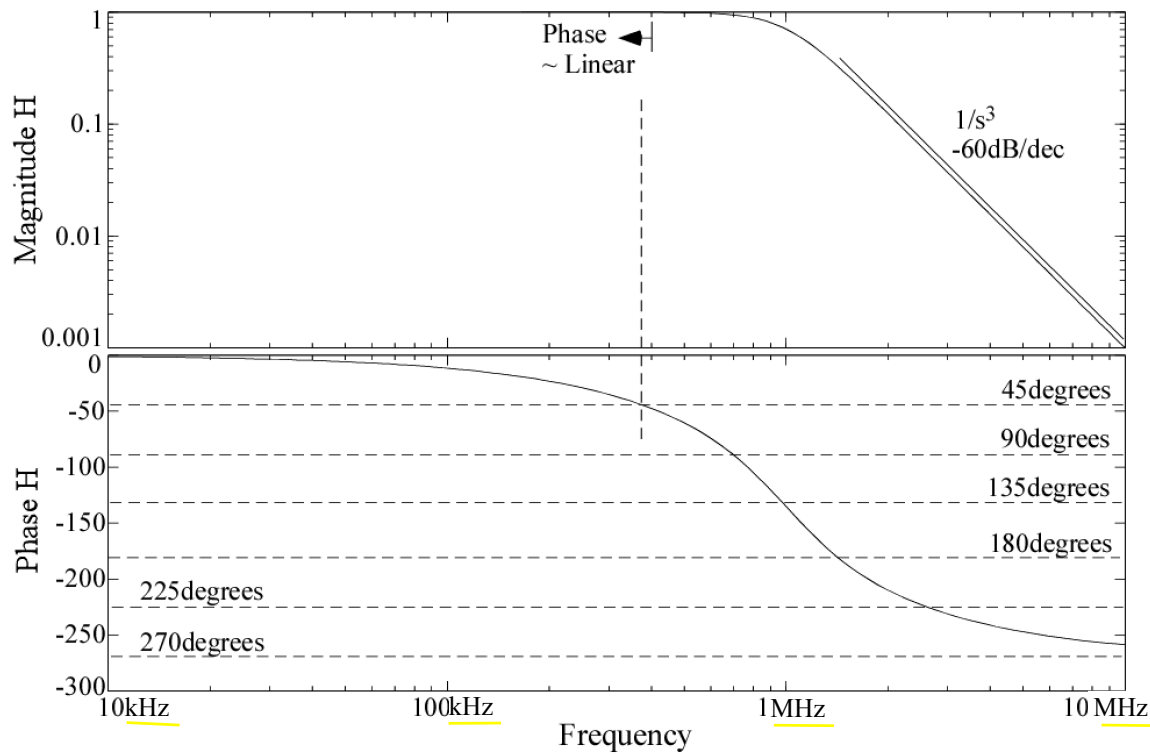$R=1\text{k}\Omega$ $L_1=0.24\text{mH}$
 $C=0.21\text{nF}$ $L_2=0.08\text{mH}$



$$\frac{V_1 - V_{out}}{sL_2} = V_{out}/R \quad \rightarrow V_1 = V_{out}\left(1 + s\frac{L_2}{R}\right)$$

$$\frac{V_{in} - V_1}{sL_1} + \frac{V_{out} - V_1}{sL_2} = sCV_1$$

$$\frac{V_{in}}{sL_1} + \frac{V_{out}}{sL_2} = \left(sC + \frac{1}{sL_1} + \frac{1}{sL_2}\right) V_1$$

$$V_{in} = sL_1 \left(\left(sC + \frac{1}{sL_1} + \frac{1}{sL_2}\right) \left(1 + s\frac{L_2}{R}\right) - \frac{1}{sL_2} \right) V_{out}$$

$$V_{in} = \frac{1}{R} (s^3 L_1 L_2 C + s^2 L_1 R C + s(L_1 + L_2) + R) V_{out}$$


With values: $\tau \sim 0.16\mu\text{s}$

$$\frac{V_{out}}{V_{in}} = \frac{1}{s^3 \tau^3 + 2s^2 \tau^2 + 2s\tau + 1}$$

$$= \frac{1}{(s\tau + 1)(s^2 \tau^2 + s\tau + 1)}$$

$Q=1$

3rd Order Butterworth Filter

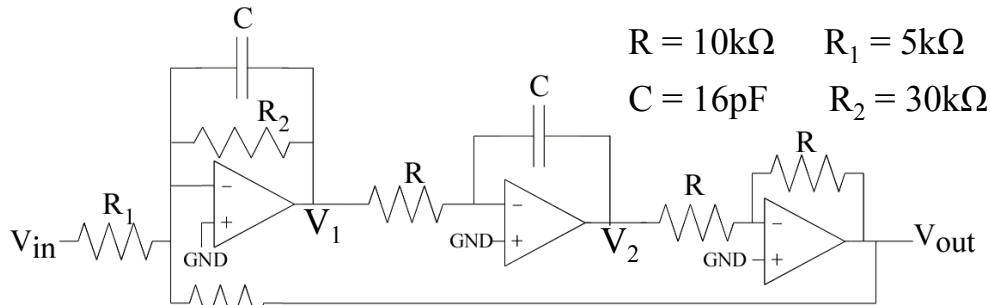

$R = 10\text{k}\Omega$ $R_1 = 5\text{k}\Omega$
 $C = 16\text{pF}$ $R_2 = 30\text{k}\Omega$

LPF block Integrator gain = -1
 $\frac{V_{in}}{R_1} + \frac{V_{out}}{R} = -(sC + \frac{1}{R_2})V_1$ $V_2 = -V_1 \frac{1}{sRC}$ $V_{out} = -V_2$

$$\frac{1}{R_1} V_{in} = -V_{out} \left(\frac{1}{R} + (sC + \frac{1}{R_2})sRC \right)$$

$$\frac{R}{R_1} V_{in} = -V_{out} \left(1 + s\tau \frac{R}{R_2} + s^2\tau^2 \right) \quad \tau = RC$$

$$Q = \frac{R_2}{R}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R}{R_1} \frac{1}{1 + s\tau \frac{R}{R_2} + s^2\tau^2}$$

$V_1 \rightarrow$ BPF

$V_{out} \rightarrow$ LPF

Tow-Thomas Second-Order Configuration

