

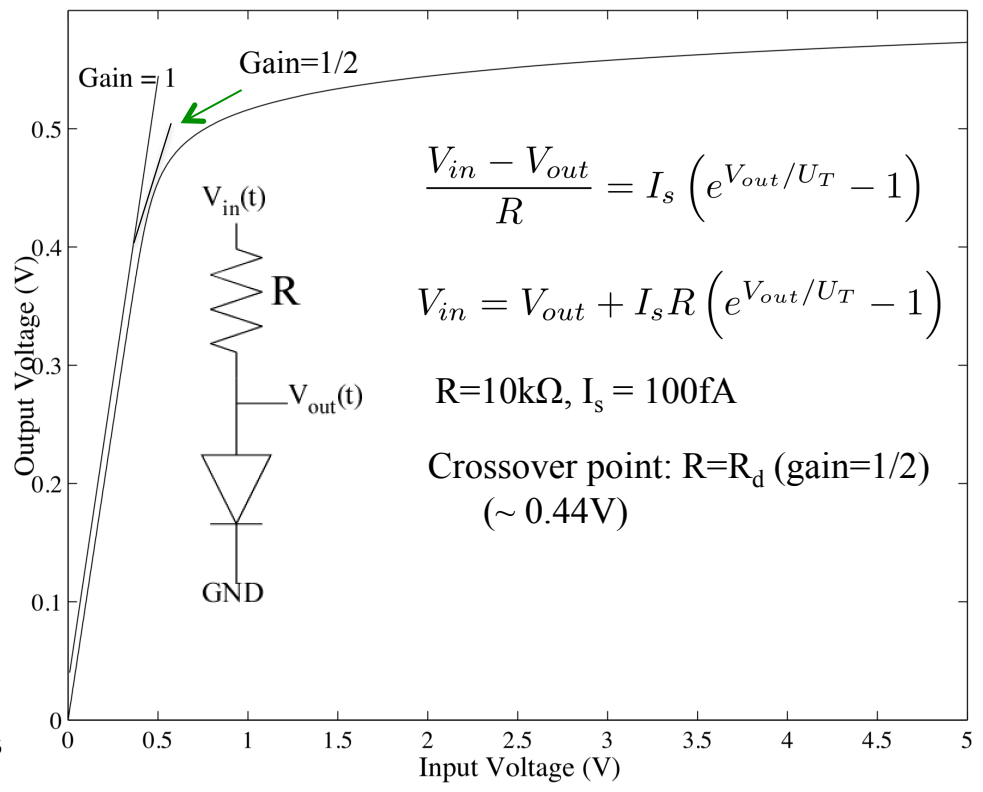
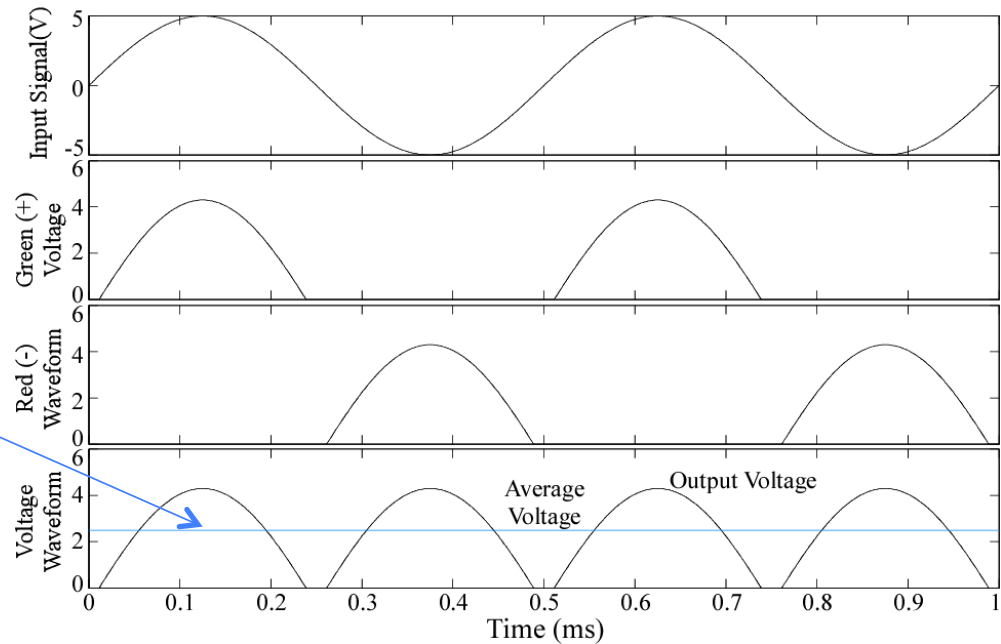

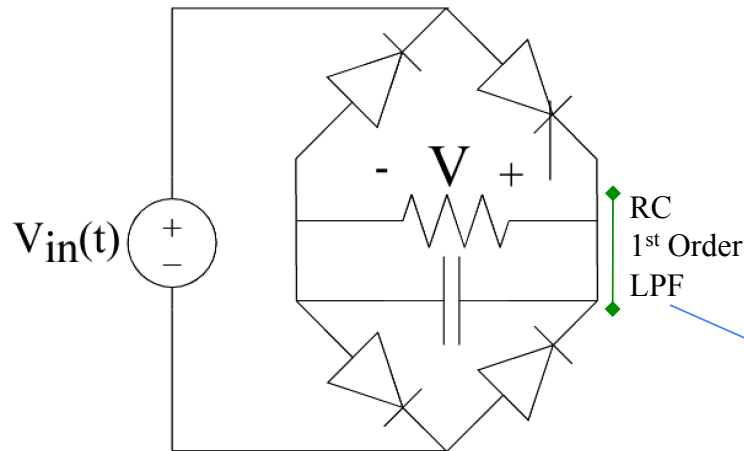
### P-N Junction Diode → Nonlinear Element





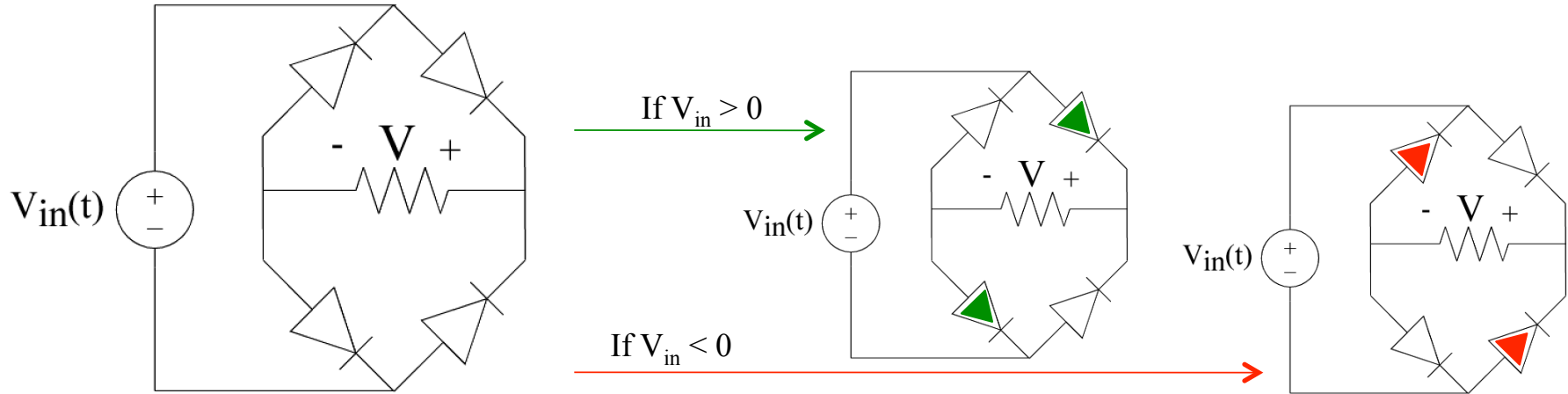
## Application of Diodes:

- Full Wave Rectification
- AC to DC supply Conversion





## P-N Junction Device

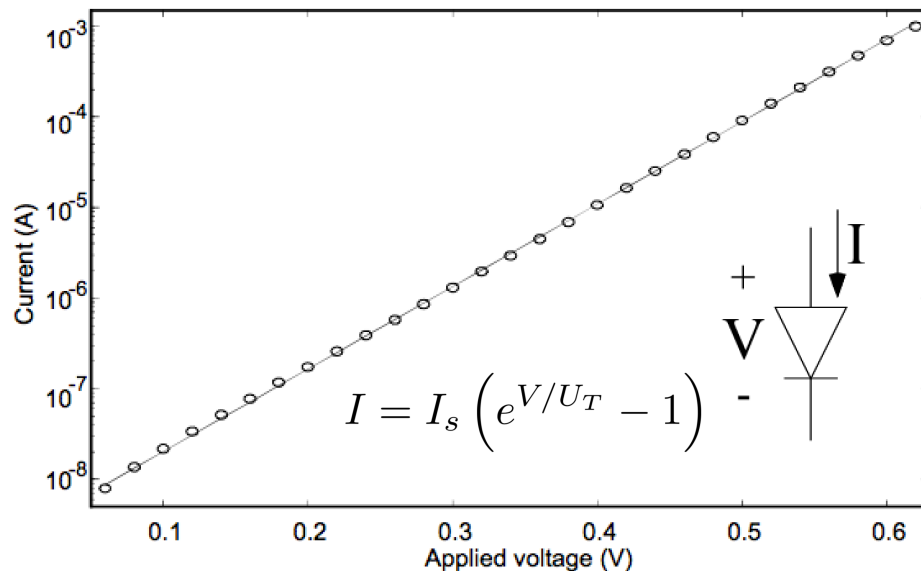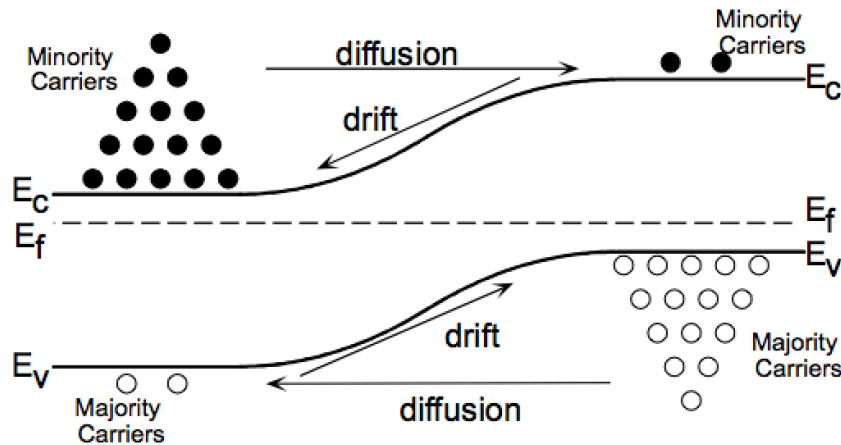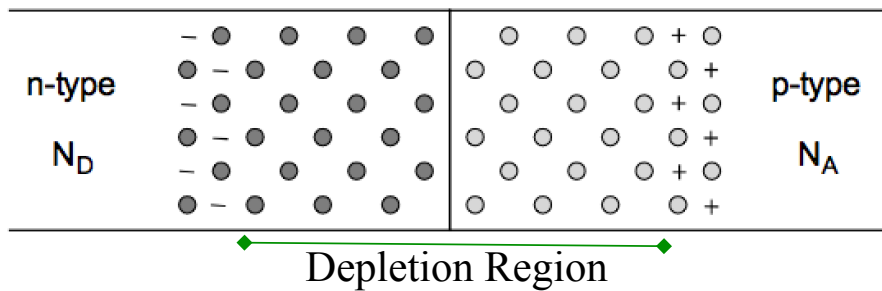
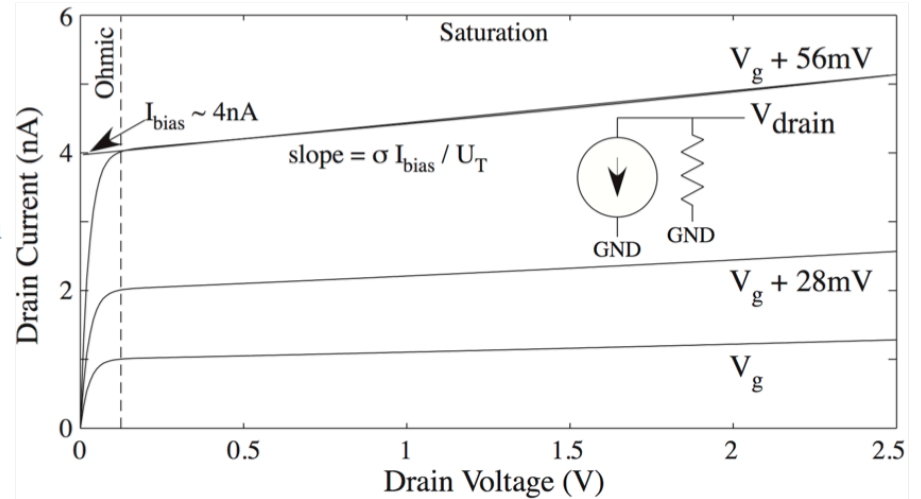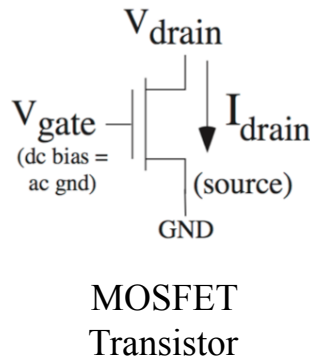
## P-N Junction Diode → Semiconductor Physics


- Bandgap (Si ~ 1.1 eV): free carrier concentrations
  - Electron (- charge)
  - Holes (+ charge)
  - Movement through available states
  - Doping changes electron, hole concentration (free ions)
- Drift current: Electric field moving charge particles
 
$$J = q\mu_n n \mathcal{E} \quad (\text{Ohm's law})$$
- Diffusion current: High-concentration to low region
 
$$J = qD_n \frac{\partial n}{\partial x}$$
- Exponential distribution of carriers (Fermi-Dirac)
 
$$f(E) = \frac{1}{1 + e^{(E-E_f)/kT}} \approx e^{-(E-E_f)/kT} \quad E > E_f$$
- Voltage-Controlled Barrier  $U_T = kT/q$   
Enables carriers above barrier energy








How to get independent and *dependent* sources?

*Fixed Gate Voltage*: Current Source

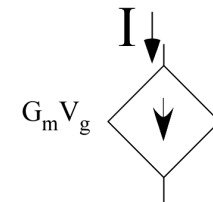*Input Gate Voltage*: Voltage Controlled, Current Sources



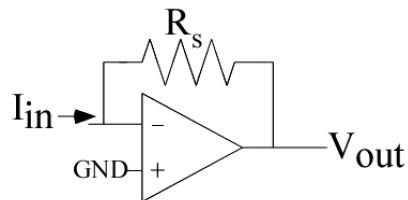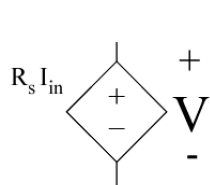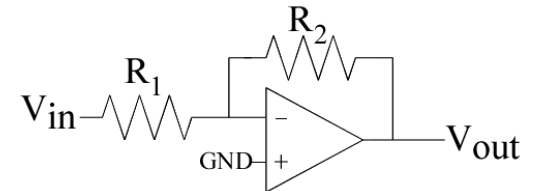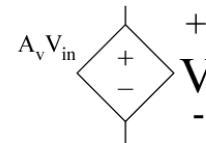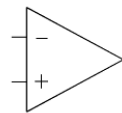*Voltage Amplifiers*: Voltage Controlled, Voltage Sources



*Transimpedance Amps*: Current Controlled, Voltage Sources

*Current Amplifiers*: Current Controlled, Current Sources (Norton Amplifier)