

EE247

Lecture 8

- Continuous-time filters continued
 - Various Gm-C filter implementations
 - Comparison of continuous-time filter topologies
- Switched-Capacitor Filters
 - “Analog” sampled-data filters:
 - Continuous amplitude
 - Quantized time
 - Applications:
 - First commercial product: Intel 2912 voice-band CODEC chip, 1979
 - Oversampled A/D and D/A converters
 - Stand-alone filters
E.g. National Semiconductor LMF100 (x2 biquads)

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 1

Summary Last Lecture

- Automatic on-chip filter tuning (continued from previous lecture)
 - Continuous tuning
 - Reference integrator locked to a reference frequency
 - DC tuning of resistive timing element
 - Periodic digitally assisted tuning
 - Systems where filter is followed by ADC & DSP, existing hardware can be used to periodically update filter freq. response
- Continuous-time filters
 - Highpass filters- 1st order → integrator in the feedback path
 - Bandpass filters
 - Cascade of LP and HP for $Q_{filter} < 5$
 - Direct implementation for narrow-band filter via LP to BP transformation

EECS 247 Lecture 8:

Filters: Gm-C & S.C.


© 2007 H.K. Page 2

Simplest Form of CMOS Gm-Cell Nonidealities

- DC gain (integrator Q)

$$a = \frac{g_m^{M1,2}}{g_0^{M1,2} + g_{load}}$$
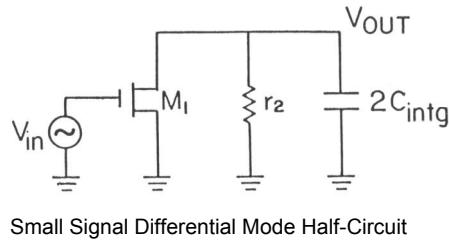
$$a = \frac{2L}{\theta(V_{gs} - V_{th})_{M1,2}}$$



Small Signal Differential Mode Half-Circuit


- Where a denotes DC gain & θ is related to channel length modulation by:

$$\lambda = \frac{\theta}{L}$$

- Seems no extra poles!

CMOS Gm-Cell High-Frequency Poles

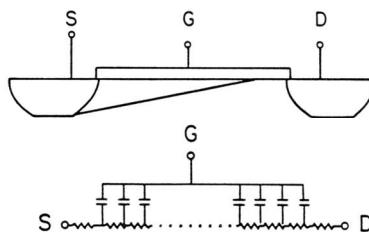Cross section view of a MOS transistor operating in saturation




Distributed channel resistance & gate capacitance

- Distributed nature of gate capacitance & channel resistance results in infinite no. of high-frequency poles

CMOS Gm-Cell High-Frequency Poles
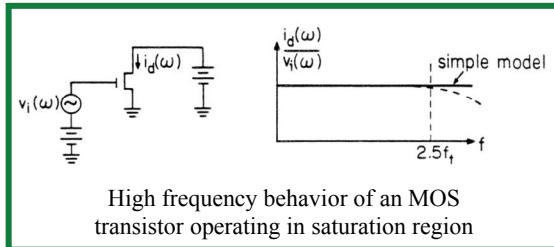
$$P_2^{\text{effective}} \approx \frac{I}{\sum_{i=2}^{\infty} \frac{I}{P_i}}$$



$$P_2^{\text{effective}} \approx 2.5\omega_t^{M1,2}$$

$$\omega_t^{M1,2} = \frac{g_m^{M1,2}}{2/3C_{ox}WL} = \frac{3}{2} \frac{\mu(V_{gs} - V_{th})_{M1,2}}{L^2}$$

- Distributed nature of gate capacitance & channel resistance results in an effective pole at 2.5 times input device cut-off frequency

Simple Gm-Cell Quality Factor

$$a = \frac{2L}{\theta(V_{gs} - V_{th})_{M1,2}}$$

$$P_2^{\text{effective}} = \frac{15}{4} \frac{\mu(V_{gs} - V_{th})_{M1,2}}{L^2}$$


$$Q_{\text{real}}^{\text{intg.}} \approx \frac{I}{\frac{I}{a} - \omega_b \sum_{i=2}^{\infty} \frac{I}{P_i}}$$

$$\frac{I}{Q^{\text{intg.}}} \approx \frac{\theta(V_{gs} - V_{th})_{M1,2}}{2L} - \frac{4}{15} \frac{\omega_b L^2}{\mu(V_{gs} - V_{th})_{M1,2}}$$

- Note that phase lead associated with DC gain is inversely prop. to L
 - Phase lag due to high-freq. poles directly prop. to L
- For a given ω_o there exists an optimum L which cancel the lead/lag phase error resulting in high integrator Q

Simple Gm-Cell Channel Length for Optimum Integrator Quality Factor
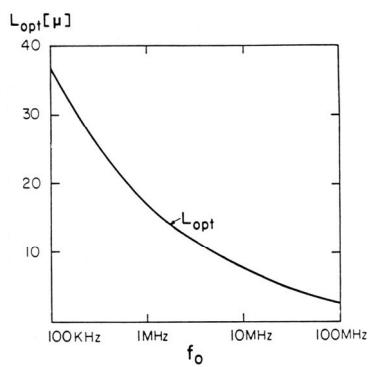
$$L_{opt} \approx \left[\frac{I_5}{4} \frac{\theta \mu (V_{gs} - V_{th})^2 M_{l,2}}{\omega_b} \right]^{1/3}$$



- Optimum channel length computed based on process parameters (could vary from process to process)

Source-Coupled Pair CMOS Gm-Cell Transconductance

For a source-coupled pair the differential output current (ΔI_d) as a function of the input voltage (Δv_i):

$$\Delta I_d = I_{ss} \left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M_{l,2}}} \right] \left\{ 1 - \frac{1}{4} \left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M_{l,2}}} \right]^2 \right\}^{1/2}$$



Note: For small $\left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M_{l,2}}} \right] \rightarrow \frac{\Delta I_d}{\Delta v_i} = g_m^{M_{l,M2}}$

Note: As Δv_i increases $\frac{\Delta I_d}{\Delta v_i}$ or the effective transconductance decreases

$$\Delta v_i = V_{il} - V_{i2}$$

$$\Delta I_d = I_{d1} - I_{d2}$$

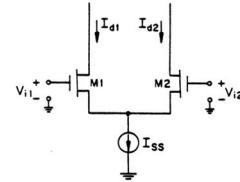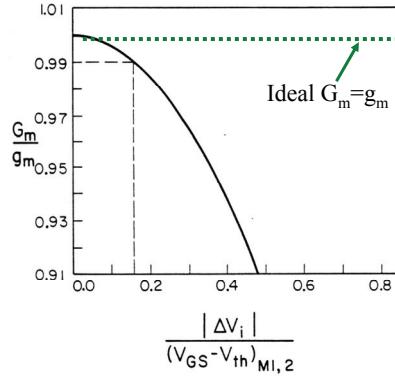Source-Coupled Pair CMOS Gm-Cell Linearity



- Large signal G_m drops as input voltage increases
→ Gives rise to nonlinearity

Measure of Linearity

$$V_{out} = \alpha_1 V_{in} + \alpha_2 V_{in}^2 + \alpha_3 V_{in}^3 + \dots$$
$$HD3 = \frac{\text{amplitude 3rd harmonic dist. comp.}}{\text{amplitude fundamental}}$$

$$= \frac{1}{4} \frac{\alpha_3}{\alpha_1} V_{in}^2 + \dots$$

$$IM_3 = \frac{\text{amplitude 3rd order IM comp.}}{\text{amplitude fundamental}}$$

$$= \frac{3}{4} \frac{\alpha_3}{\alpha_1} V_{in}^2 + \frac{25}{8} \frac{\alpha_5}{\alpha_1} V_{in}^4 + \dots$$

Source-Coupled Pair Gm-Cell Linearity

$$\Delta I_d = I_{ss} \left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M1,2}} \right] \left\{ 1 - \frac{I}{4} \left[\frac{\Delta v_i}{(V_{gs} - V_{th})_{M1,2}} \right]^2 \right\}^{1/2} \quad (1)$$


$$\Delta I_d = a_1 \times \Delta v_i + a_2 \times \Delta v_i^2 + a_3 \times \Delta v_i^3 + \dots$$

Series expansion used in (1)

$$a_1 = \frac{I_{ss}}{(V_{gs} - V_{th})_{M1,2}} \quad \& \quad a_2 = 0$$

$$a_3 = -\frac{I_{ss}}{8(V_{gs} - V_{th})_{M1,2}^3} \quad \& \quad a_4 = 0$$
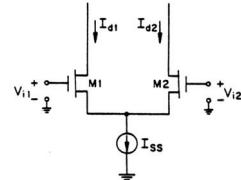
$$a_5 = -\frac{I_{ss}}{128(V_{gs} - V_{th})_{M1,2}^5} \quad \& \quad a_6 = 0$$




Linearity of the Source-Coupled Pair CMOS Gm-Cell

$$IM3 \approx \frac{3a_3}{4a_1} \hat{v}_i^2 + \frac{25a_5}{8a_1} \hat{v}_i^4 \dots$$

Substituting for a_1, a_3, \dots
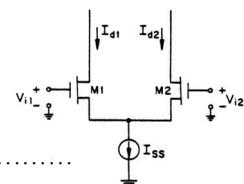
$$IM3 \approx \frac{3}{32} \left(\frac{\hat{v}_i}{(V_{GS} - V_{th})} \right)^2 + \frac{25}{1024} \left(\frac{\hat{v}_i}{(V_{GS} - V_{th})} \right)^4 \dots$$



$$\hat{v}_{i \max} \approx 4(V_{GS} - V_{th}) \times \sqrt{\frac{2}{3} \times IM3}$$

$$IM3 = 1\% \quad \& \quad (V_{GS} - V_{th}) = IV \Rightarrow \hat{V}_{in}^{rms} \approx 230mV$$

- Key point: Max. signal handling capability function of gate-overdrive voltage

Simplest Form of CMOS Gm Cell Disadvantages

- Max. signal handling capability function of gate-overdrive


$$IM_3 \propto (V_{GS} - V_{th})^{-2}$$

- Critical freq. is also a function of gate-overdrive

$$\omega_o = \frac{g_m M_{1,2}}{2 \times C_{intg}}$$

$$\text{since } g_m = \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th})$$

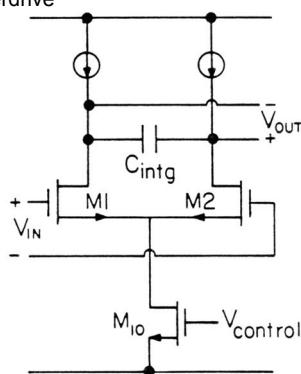
$$\text{then } \omega_o \propto (V_{gs} - V_{th})$$



→ Filter tuning affects max. signal handling capability!

Simplest Form of CMOS Gm Cell Removing Dependence of Maximum Signal Handling Capability on Tuning

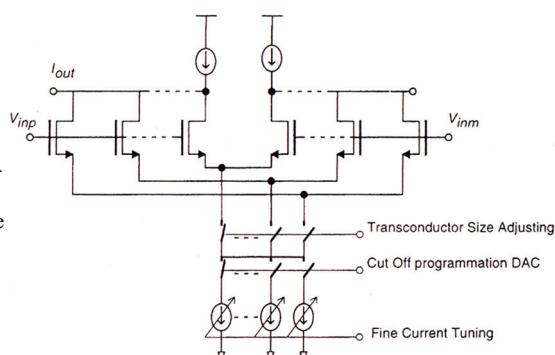- Can overcome problem of max. signal handling capability being a function of tuning by providing tuning through :
 - Coarse tuning via switching in/out binary-weighted cross-coupled pairs → Try to keep gate overdrive voltage constant
 - Fine tuning through varying current sources



→ Dynamic range dependence on tuning removed (to 1st order)

Dynamic Range for Source-Coupled Pair Based Filter

$$IM_3 = 1\% \quad \& \quad (V_{GS} - V_{th}) = 1V \Rightarrow V_{in}^{rms} \approx 230mV$$

- Minimum detectable signal determined by total noise voltage
- It can be shown for the **6th** order Butterworth bandpass filter fundamental noise contribution is given by:

$$\sqrt{v_o^2} \approx \sqrt{3Q \frac{kT}{C_{intg}}}$$

Assuming $Q = 10 \quad C_{intg} = 5pF$

$$v_{noise}^{rms} \approx 160\mu V$$

$$\text{since } v_{max}^{rms} = 230mV$$


$$\text{Dynamic Range} = 20 \log \frac{230 \times 10^{-3}}{160 \times 10^{-6}} \approx 63dB$$

Improving the Max. Signal Handling Capability of the Source-Coupled Pair Gm-Cell


- 2nd source-coupled pair added to subtract current proportional to nonlinear component associated with the main SCP

$$\frac{I_{ssl}}{I_{ss3}} = b \quad \& \quad \frac{(V_{GS} - V_{th})_{M1,2}}{(V_{GS} - V_{th})_{M3,4}} = a \quad \text{and thus}$$

$$\frac{(W)}{L}_{M1,2} = \frac{b}{a^2}$$

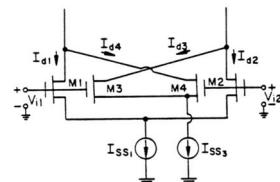


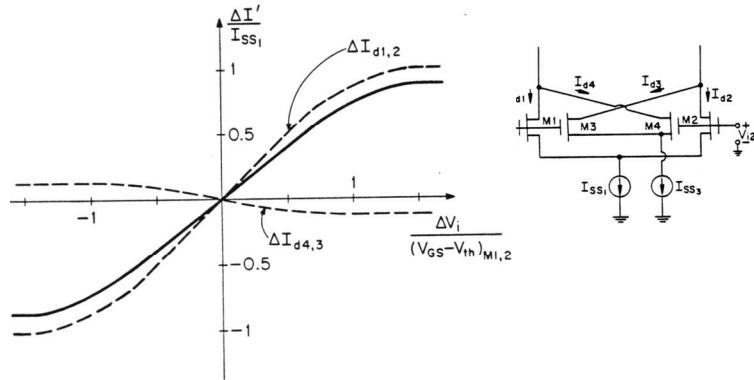Improving the Max. Signal Handling Capability of the Source-Coupled Pair Gm



Ref: H. Khorramabadi, "High-Frequency CMOS Continuous-Time Filters," U. C. Berkeley, Department of Electrical Engineering, Ph.D. Thesis, February 1985 (ERL Memorandum No. UCB/ERL M85/19).

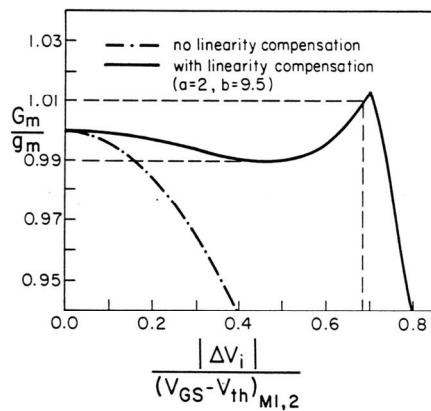
Improving the Max. Signal Handling Capability of the Source-Coupled Pair Gm



- Improves maximum signal handling capability by about 12dB
→ Dynamic range theoretically improved to $63+12=75$ dB

Simplest Form of CMOS Gm-Cell

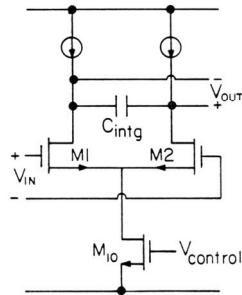- Pros
 - Capable of very high frequency performance (highest?)
 - Simple design
- Cons
 - Tuning affects power dissipation
 - Tuning affects max. signal handling capability (can overcome)
 - Limited linearity (possible to improve)



Ref: H. Khorramabadi and P.R. Gray, "High Frequency CMOS continuous-time filters," *IEEE Journal of Solid-State Circuits*, Vol.-SC-19, No. 6, pp.939-948, Dec. 1984.

Gm-Cell Source-Coupled Pair with Degeneration


$$I_d = \frac{\mu C_{ox}}{2} \frac{W}{L} \left[2(V_{gs} - V_{th})V_{ds} - V_{ds}^2 \right]$$

$$g_{ds} = \frac{\partial I_d}{\partial V_{ds}} \approx \mu C_{ox} \frac{W}{L} (V_{gs} - V_{th}) \Big|_{V_{ds} \text{ small}}$$

$$g_{eff} = \frac{I}{\frac{1}{g_{ds}^{M3}} + \frac{2}{g_m^{M1,2}}}$$


for $g_m^{M1,2} \gg g_{ds}^{M3}$

$$g_{eff} \approx g_{ds}^{M3}$$

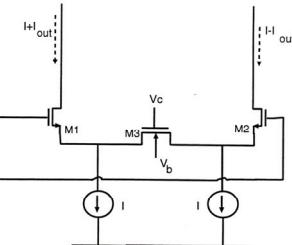

M3 operating in triode mode → source degeneration → determines overall gm
Provides tuning through varing Vc

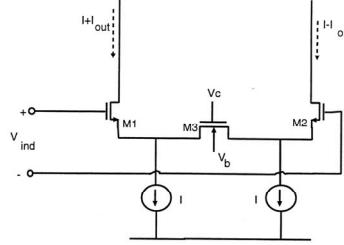Gm-Cell Source-Coupled Pair with Degeneration



- Pros

- Moderate linearity
- Continuous tuning provided by V_c
- Tuning does not affect power dissipation

- Cons

- Extra poles associated with the source of M1,2,3
→ Low frequency applications only

Ref: Y. Tsividis, Z. Czarnul and S.C. Fang, "MOS transconductors and integrators with high linearity," *Electronics Letters*, vol. 22, pp. 245-246, Feb. 27, 1986

BiCMOS Gm-Cell Example

- MOSFET in triode mode:

$$I_d = \frac{\mu C_{ox}}{2} \frac{W}{L} \left[2(V_{gs} - V_{th})V_{ds} - V_{ds}^2 \right]$$


- Note that if V_{ds} is kept constant:

$$g_m^{MI} = \frac{\partial I_d}{\partial V_{gs}} = \mu C_{ox} \frac{W}{L} V_{ds}$$

- Linearity performance → keep gm constant → function of how constant V_{ds} can be held
 - Need to minimize Gain @ Node X

$$A_x = g_m^{MI} / g_m^{BI}$$

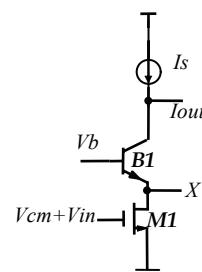
- Since for a given current, gm of BJT is larger compared to MOS- preferable to use BJT
- Extra pole at node X



gm can be varied by changing V_b and thus V_{ds}

Alternative Fully CMOS Gm-Cell Example

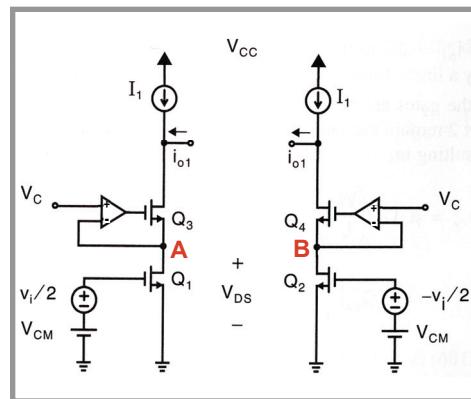- BJT replaced by a MOS transistor with boosted gm
- Lower frequency of operation compared to the BiCMOS version due to more parasitic capacitance at nodes A & B




EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 23

BiCMOS Gm-C Integrator

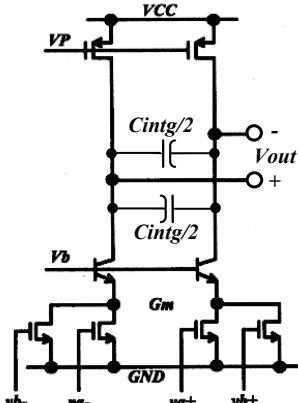- Differential- needs common-mode feedback ckt
- Freq.tuned by varying Vb
- Design tradeoffs:
 - Extra poles at the input device drain junctions
 - Input devices have to be small to minimize parasitic poles
 - Results in high input-referred offset voltage → could drive ckt into non-linear region
 - Small devices → high 1/f noise




EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 24

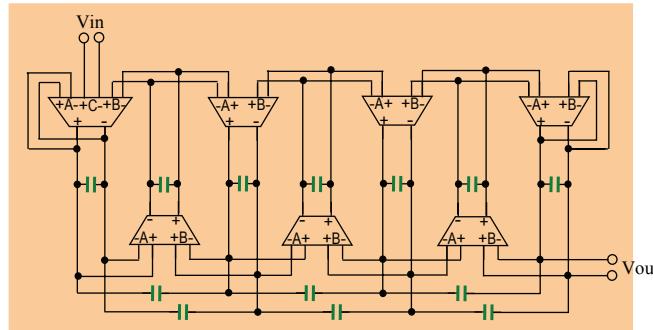7th Order Elliptic Gm-C LPF For CDMA RX Baseband Application



- Gm-Cell in previous page used to build a 7th order elliptic filter for CDMA baseband applications (650kHz corner frequency)
- In-band dynamic range of <50dB achieved


EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 25

Comparison of 7th Order Gm-C versus Opamp-RC LPF

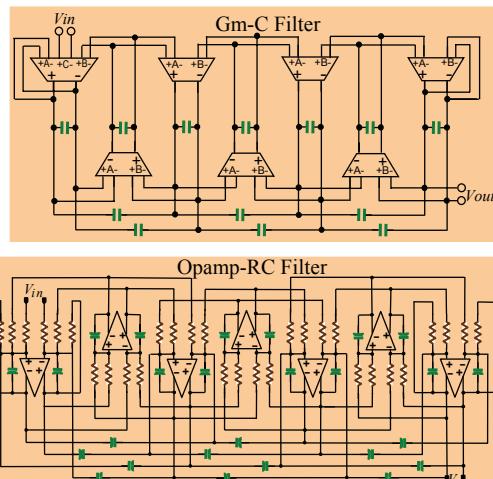- Gm-C filter requires 4 times less intg. cap. area compared to Opamp-RC
→ For low-noise applications where filter area is dominated by C_s , could make a significant difference in the total area
- Opamp-RC linearity superior compared to Gm-C
- Power dissipation tends to be lower for Gm-C since OTA load is C and thus no need for buffering




EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 26

BiCMOS Gm-OTA-C Integrator

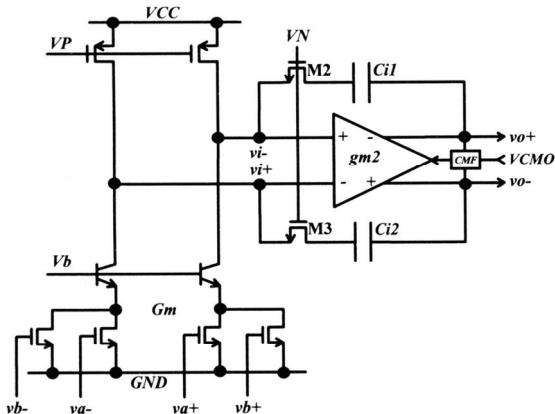- Used to build filter for disk-drive applications
- Since high frequency of operation, time-constant sensitivity to parasitic caps significant.
→ Opamp used
- M2 & M3 added to compensate for phase lag (provides phase lead)




Ref: C. Laber and P.Gray, "A 20MHz 6th Order BiCMOS Parasitic Insensitive Continuous-time Filter & Second Order Equalizer Optimized for Disk Drive Read Channels," *IEEE Journal of Solid State Circuits*, Vol. 28, pp. 462-470, April 1993.

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 27

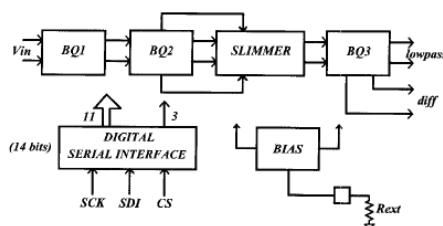6th Order BiCMOS Continuous-time Filter & Second Order Equalizer for Disk Drive Read Channels



- Gm-C-opamp of the previous page used to build a 6th order filter for Disk Drive
- Filter consists of 3 Biquad with max. Q of 2 each
- Performance in the order of 40dB SNDR achieved for up to 20MHz corner frequency


Ref: C. Laber and P.Gray, "A 20MHz 6th Order BiCMOS Parasitic Insensitive Continuous-time Filter & Second Order Equalizer Optimized for Disk Drive Read Channels," *IEEE Journal of Solid State Circuits*, Vol. 28, pp. 462-470, April 1993.

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 28

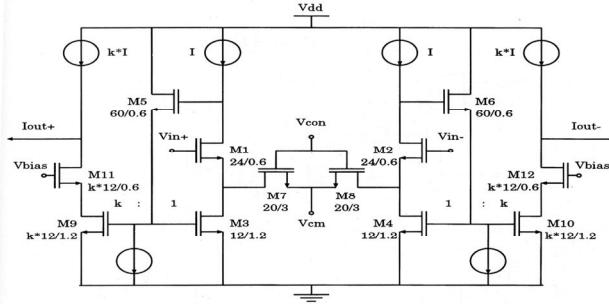
Gm-Cell Source-Coupled Pair with Degeneration



- Gm-cell intended for low Q disk drive filter

Ref: I.Mehr and D.R.Welland, "A CMOS Continuous-Time Gm-C Filter for PRML Read Channel Applications at 150 Mb/s and Beyond", IEEE Journal of Solid-State Circuits, April 1997, Vol.32, No.4, pp. 499-513.

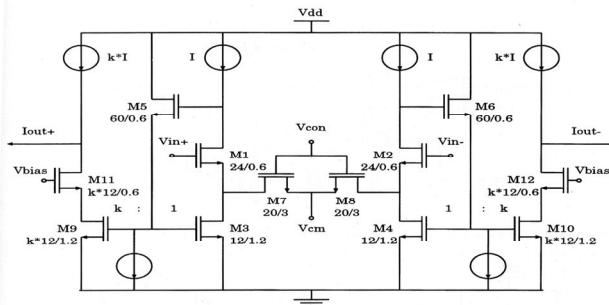
Gm-Cell Source-Coupled Pair with Degeneration



- M7,8 operating in triode mode determine the overall gm of the cell
- Feedback provided by M5,6 maintains the gate-source voltage of M1,2 constant by forcing their current to be constant → helps linearize *rds* of M7,8
- Current mirrored to the output via M9,10 with a factor of *k*
- Performance level of about 50dB SNDR at fcorner of 25MHz achieved

BiCMOS Gm-C Integrator

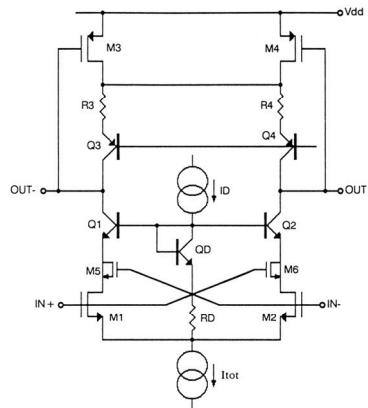
- Needs higher supply voltage compared to the previous design since quite a few devices are stacked vertically
- M1,2 → triode mode
- Q1,2 → hold V_{ds} of M1,2 constant
- Current ID used to tune filter critical frequency by varying V_{ds} of M1,2 and thus controlling gm of M1,2
- M3, M4 operate in triode mode and added to provide common-mode feedback



Ref: R. Alini, A. Baschirotto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.


BiCMOS Gm-C Integrator

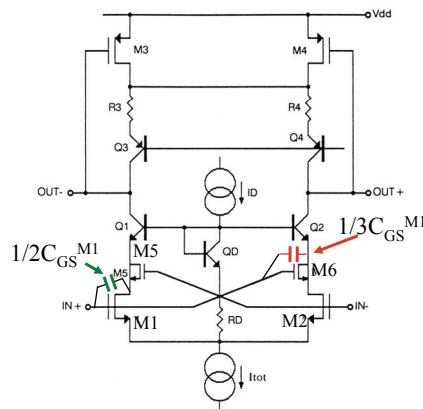- M5 & M6 configured as capacitors- added to compensate for RHP zero due to C_{gd} of M1,2 (moves it to LHP) size of M5,6 → $1/3$ of M1,2



Ref: R. Alini, A. Baschirotto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.

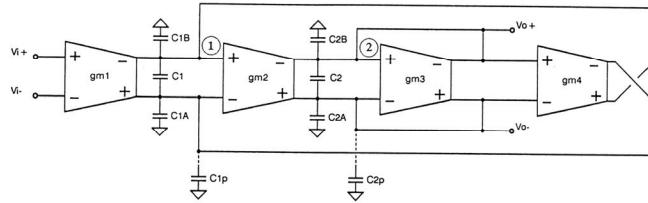BiCMOS Gm-C Filter For Disk-Drive Application



- Using the integrators shown in the previous page
- Biquad filter for disk drives
- $gm1=gm2=gm4=2gm3$
- $Q=2$
- Tunable from 8MHz to 32MHz

Ref: R. Alini, A. Baschirotto, and R. Castello, "Tunable BiCMOS Continuous-Time Filter for High-Frequency Applications," *IEEE Journal of Solid State Circuits*, Vol. 27, No. 12, pp. 1905-1915, Dec. 1992.

Summary Continuous-Time Filters



- Opamp RC filters
 - Good linearity → High dynamic range (60-90dB)
 - Only discrete tuning possible
 - Medium usable signal bandwidth (<10MHz)
- Opamp MOSFET-C
 - Linearity compromised (typical dynamic range 40-60dB)
 - Continuous tuning possible
 - Low usable signal bandwidth (<5MHz)
- Opamp MOSFET-RC
 - Improved linearity compared to Opamp MOSFET-C (D.R. 50-90dB)
 - Continuous tuning possible
 - Low usable signal bandwidth (<5MHz)
- Gm-C
 - Highest frequency performance (at least an order of magnitude higher compared to the rest <100MHz)
 - Dynamic range not as high as Opamp RC but better than Opamp MOSFET-C (40-70dB)

Switched-Capacitor Filters Today

- Emulating resistor via switched-capacitor network
- 1st order switched-capacitor filter
- Switch-capacitor filter considerations:
 - Issue of aliasing and how to avoid it
 - Tradeoffs in choosing sampling rate
 - Effect of sample and hold
 - Switched-capacitor filter electronic noise

Switched-Capacitor Resistor

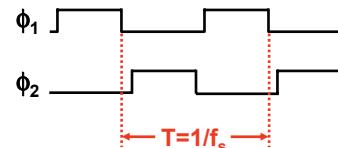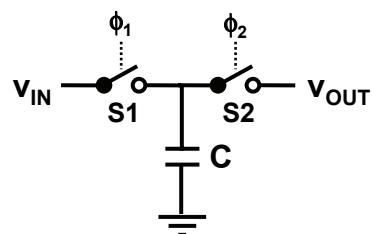
- Capacitor C is the “switched capacitor”
- Non-overlapping clocks ϕ_1 and ϕ_2 control switches S1 and S2, respectively
- v_{IN} is sampled at the falling edge of ϕ_1
 - Sampling frequency f_s
- Next, ϕ_2 rises and the voltage across C is transferred to v_{OUT}
- Why does this behave as a resistor?



Switched-Capacitor Resistors

- Charge transferred from v_{IN} to v_{OUT} during each clock cycle is:

$$Q = C(v_{IN} - v_{OUT})$$

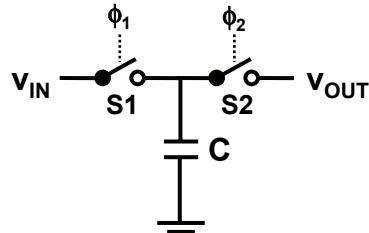


- Average current flowing from v_{IN} to v_{OUT} is:

$$i = Q/t = Q \cdot f_s$$

Substituting for Q :

$$i = f_s C(v_{IN} - v_{OUT})$$

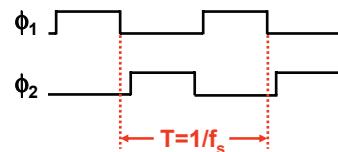


Switched-Capacitor Resistors

$$i = f_s C(v_{IN} - v_{OUT})$$

With the current through the switched-capacitor resistor proportional to the voltage across it, the equivalent "switched capacitor resistance" is:

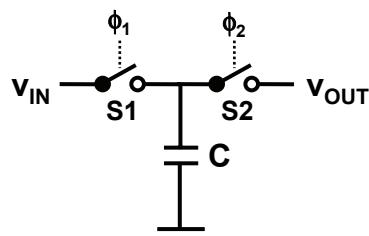
$$R_{eq} = \frac{V_{IN} - V_{OUT}}{i} = \frac{1}{f_s C}$$



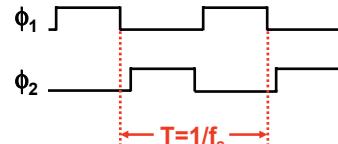Example:

$$\begin{aligned} f_s &= 100\text{KHz}, C = 0.1\text{pF} \\ \rightarrow R_{eq} &= 100\text{Mega}\Omega \end{aligned}$$

Note: Can build large time-constant in small area





Switched-Capacitor Filter

- Let's build a "switched- capacitor " filter ...
- Start with a simple RC LPF
- Replace the physical resistor by an equivalent switched-capacitor resistor
- 3-dB bandwidth:

$$\omega_{-3dB} = \frac{1}{R_{eq}C_2} = f_s \times \frac{C_1}{C_2}$$
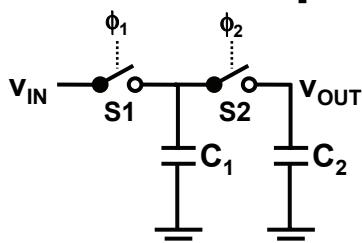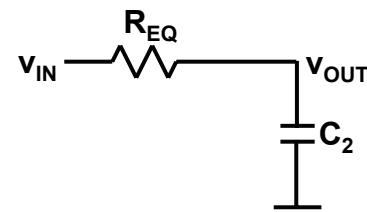
$$f_{-3dB} = \frac{1}{2\pi} f_s \times \frac{C_1}{C_2}$$




EECS 247 Lecture 8:


Filters: Gm-C & S.C.

© 2007 H.K. Page 39

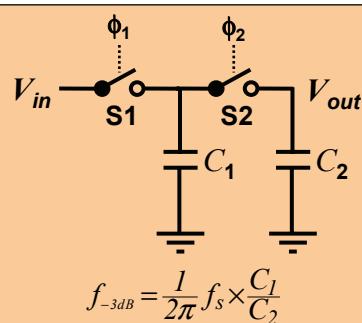Switched-Capacitor Filter Advantage versus Continuous-Time Filter



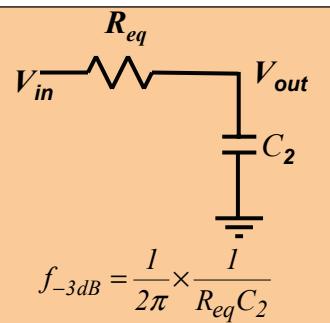- Corner freq. proportional to:
System clock (accurate to few ppm)
C ratio accurate $\rightarrow < 0.1\%$



- Corner freq. proportional to:
Absolute value of Rs & Cs
Poor accuracy $\rightarrow 20$ to 50%

Main advantage of SC filters \rightarrow inherent corner frequency accuracy


EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 40

Typical Sampling Process

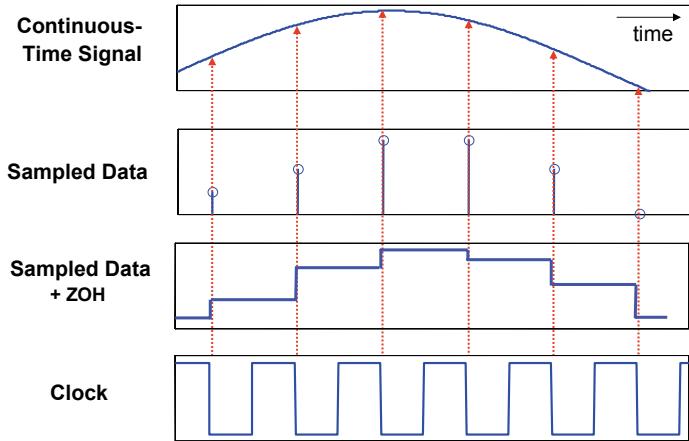Continuous-Time(CT) \Rightarrow Sampled Data (SD)



EECS 247 Lecture 8:

Filters: Gm-C & S.C.


© 2007 H.K. Page 41

Uniform Sampling

Nomenclature:

Continuous time signal	$x_c(t)$
Sampling interval	T
Sampling frequency	$f_s = 1/T$
Sampled signal	$x_d(kT) = x/k$

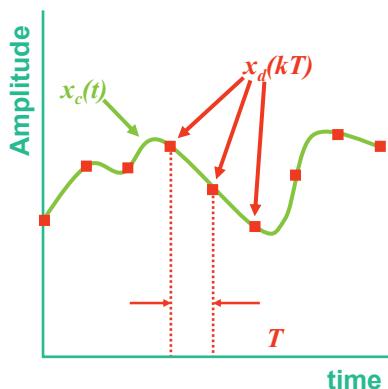- Problem: Multiple continuous time signals can yield exactly the same discrete time signal
- Let's look at samples taken at $1\mu s$ intervals of several sinusoidal waveforms ...




Note: Samples are the waveform values at kT instances and undefined in between

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 42

Sampling Sine Waves

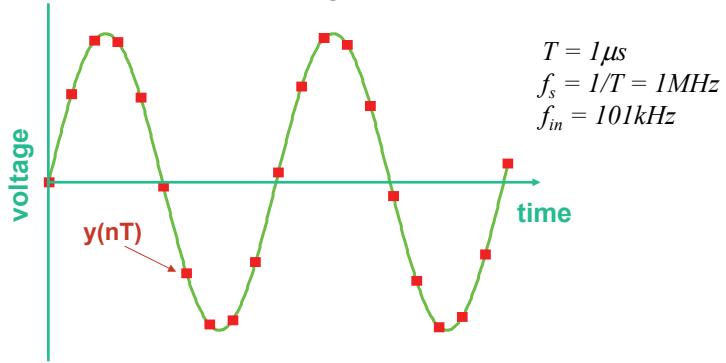

$$v(t) = \cos(2\pi f_{in} t)$$

Sampled-data domain $\rightarrow t \rightarrow n \cdot T$ or $t \rightarrow n/f_s$

$$v(n) = \cos\left(2\pi \frac{f_{in}}{f_s} \cdot n\right) = \cos\left(2\pi \frac{101kHz}{1MHz} \cdot n\right)$$


EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 43

Sampling Sine Waves

Aliasing

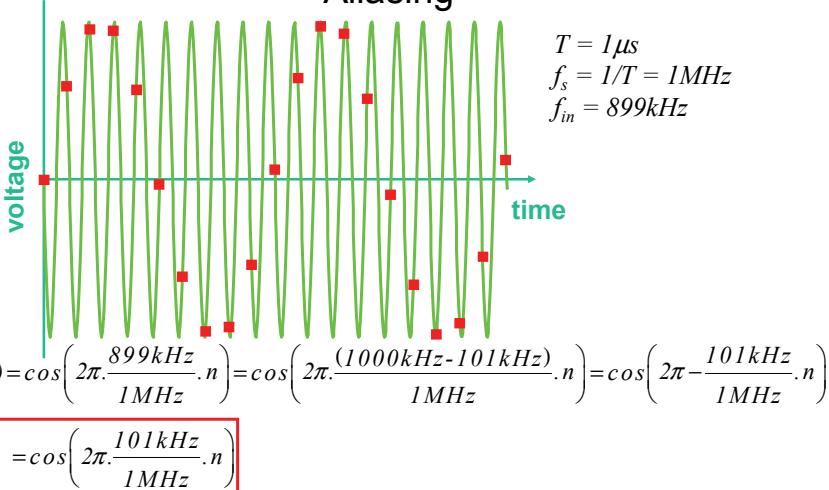


EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 44

Sampling Sine Waves Aliasing

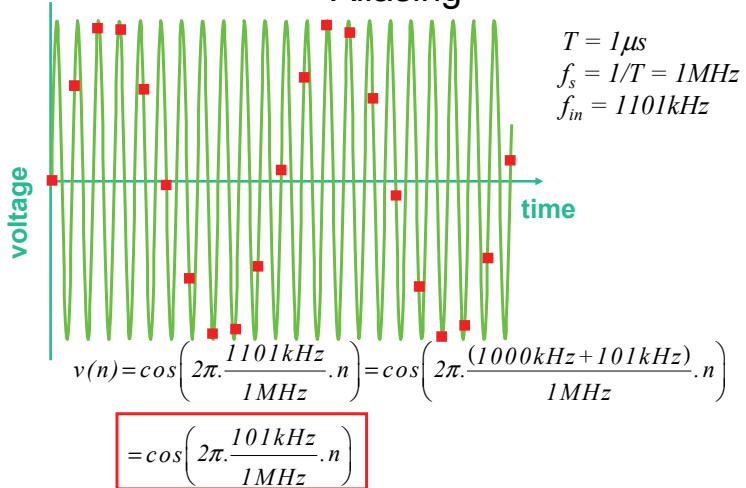

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 45

Sampling Sine Waves

Problem:

Identical samples for:

$$v(t) = \cos [2\pi f_{int} t]$$

$$v(t) = \cos [2\pi(f_{in} + n.f_s)t]$$

$$v(t) = \cos [2\pi(f_{in} - n.f_s)t]$$


* (n-integer)

→ Multiple continuous time signals can yield exactly the same discrete time signal

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 46

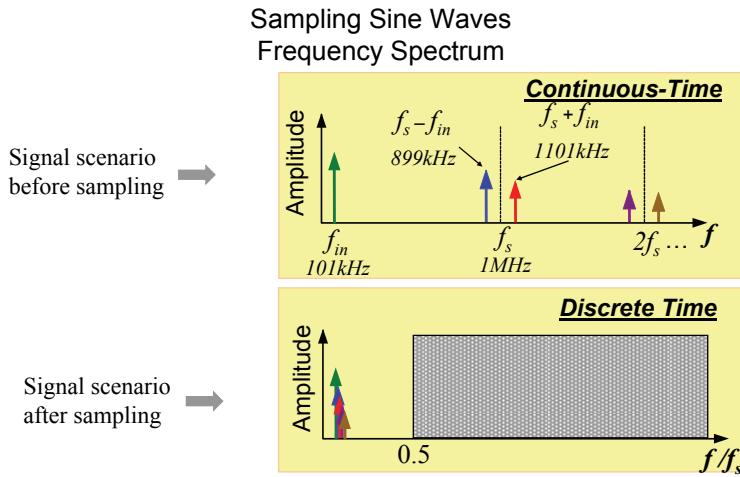

Key point: Signals @ $nf_s \pm f_{max_signal}$ fold back into band of interest → Aliasing

Aliasing

- Multiple continuous time signals can produce identical series of samples
- The folding back of signals from $nf_s \pm f_{sig}$ (n integer) down to f_{fin} is called aliasing
 - Sampling theorem: $f_s > 2f_{max_Signal}$
- If aliasing occurs, no signal processing operation downstream of the sampling process can recover the original continuous time signal

How to Avoid Aliasing?

- Must obey sampling theorem:

$$f_{\text{max-Signal}} < f_s / 2$$

*Note:


Minimum sampling rate of $f_s = 2f_{\text{max-Signal}}$ is called Nyquist rate

- Two possibilities:

1. Sample fast enough to cover all spectral components, including "parasitic" ones outside band of interest
2. Limit $f_{\text{max-Signal}}$ through filtering → attenuate out-of-band components prior to sampling

How to Avoid Aliasing?


1-Sample Fast

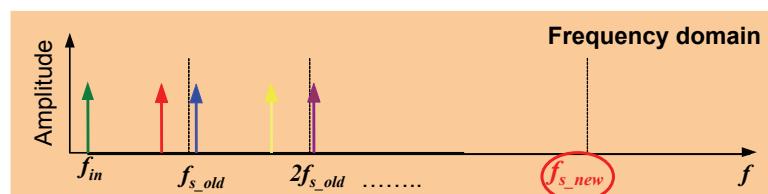

Push sampling frequency to $\times 2$ of the highest frequency signal to cover all unwanted signals as well as wanted signals

→ In vast majority of cases not practical

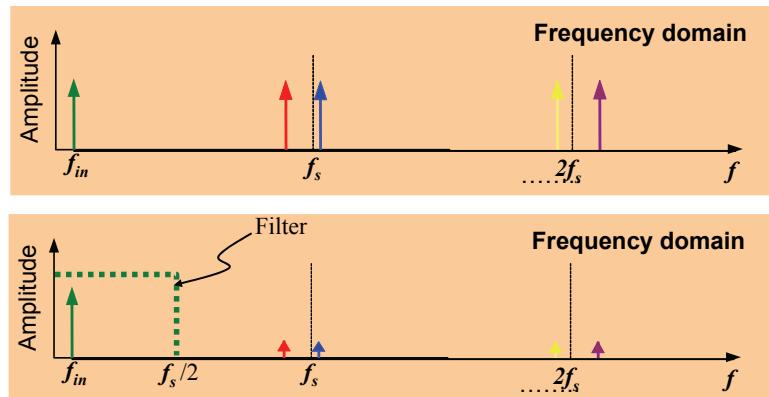How to Avoid Aliasing? 2-Filter Out-of-Band Signal Prior to Sampling




Pre-filter signal to eliminate/attenuate signals above $f_s/2$ - then sample

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 51

Anti-Aliasing Filter Considerations

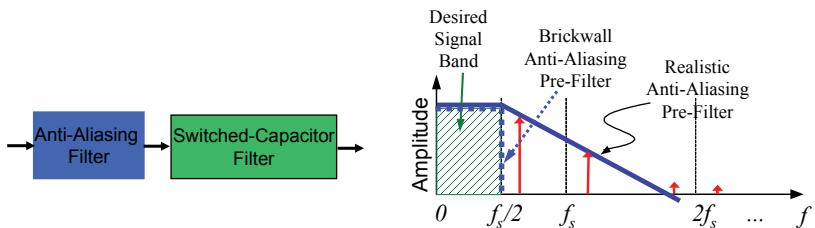

Case1- $B = f_{sig}^{max} = f_s/2$


- Non-practical since an extremely high order anti-aliasing filter (close to an ideal brickwall filter) is required
- Practical anti-aliasing filter → Non-zero filter "transition band"
- In order to make this work, we need to sample much faster than 2x the signal bandwidth
→ "Oversampling"

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 52

Practical Anti-Aliasing Filter

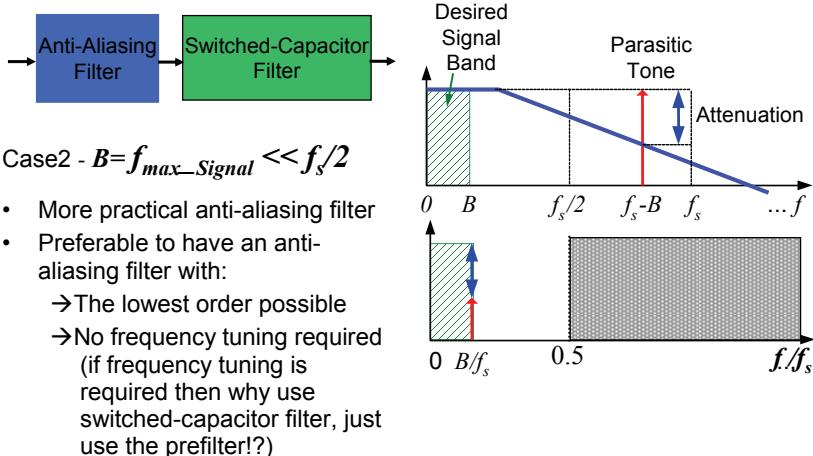


EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 53

Tradeoff

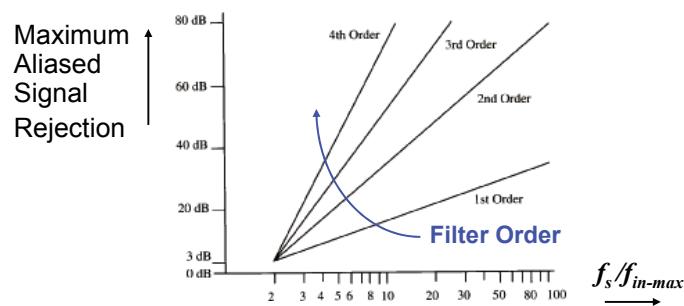Oversampling Ratio versus Anti-Aliasing Filter Order



* Assumption → anti-aliasing filter is Butterworth type (not a necessary requirement)

→ Tradeoff: Sampling speed versus anti-aliasing filter order


Ref: R. v. d. Plassche, *CMOS Integrated Analog-to-Digital and Digital-to-Analog Converters*, 2nd ed., Kluwer publishing, 2003, p.41

EECS 247 Lecture 8:

Filters: Gm-C & S.C.

© 2007 H.K. Page 54


Effect of Sample & Hold

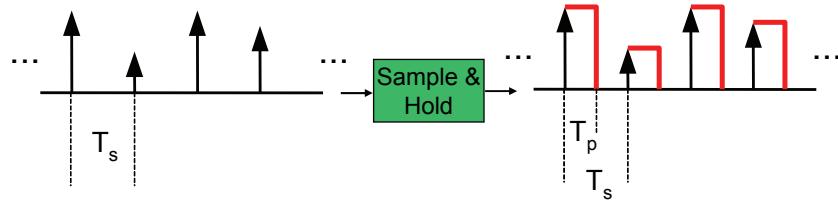


- Using the Fourier transform of a rectangular impulse:

$$|H(f)| = \frac{T_p}{T_s} \frac{\sin(\pi f T_p)}{\pi f T_p}$$

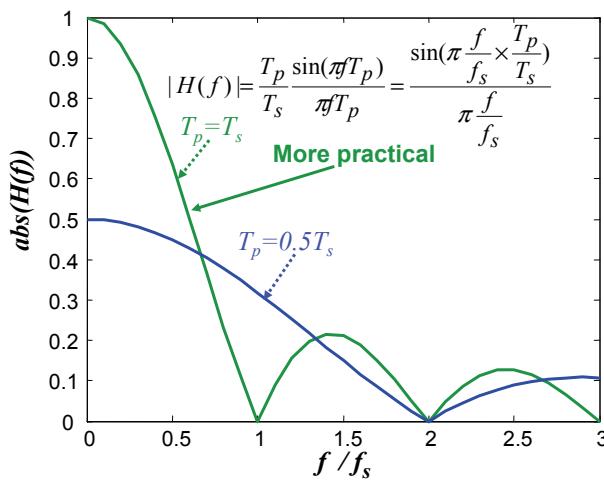
Effect of Sample & Hold on Frequency Response



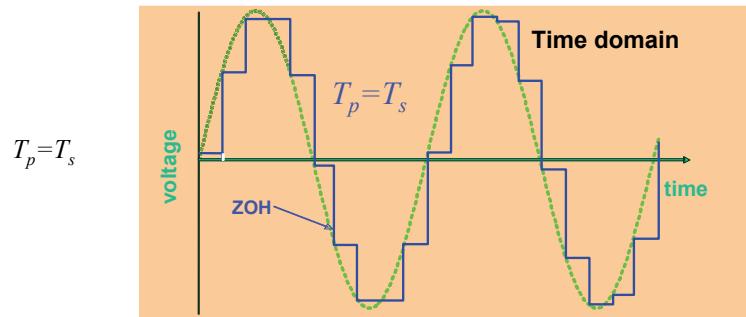Sample & Hold Effect (Reconstruction of Analog Signals)




Magnitude droop due to $\sin x/x$ effect

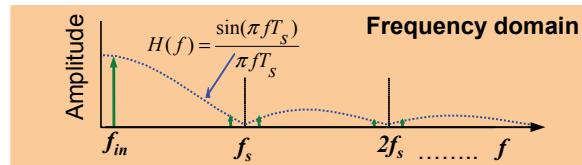


Sample & Hold Effect (Reconstruction of Analog Signals)

Magnitude droop due to $\sin x/x$ effect:

Case 1) $f_{sig} = f_s / 4$

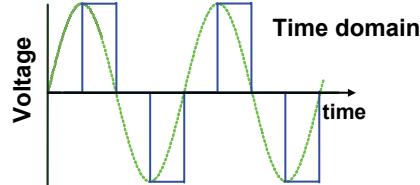

Droop = -1dB

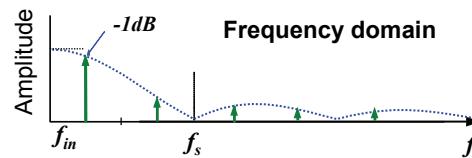


Sample & Hold Effect (Reconstruction of Analog Signals)

Magnitude droop due to $\sin x/x$ effect:

Case 2)
 $f_{sig} = f_s/32$


Time domain

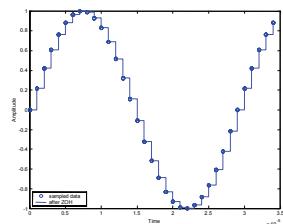

Droop = -0.0035dB

→ High
oversampling ratio
desirable

Frequency domain

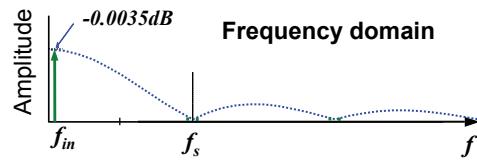

Sampling Process Including S/H

