
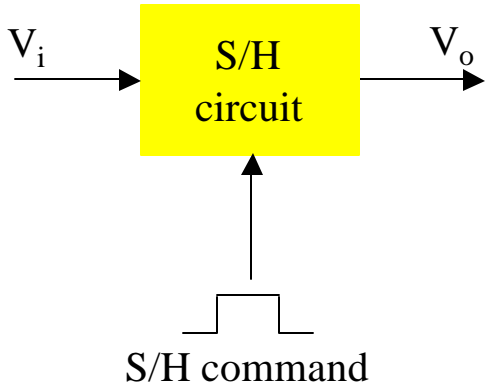


Track & Hold: Architectures and Circuits

Sample-and-Hold Circuit

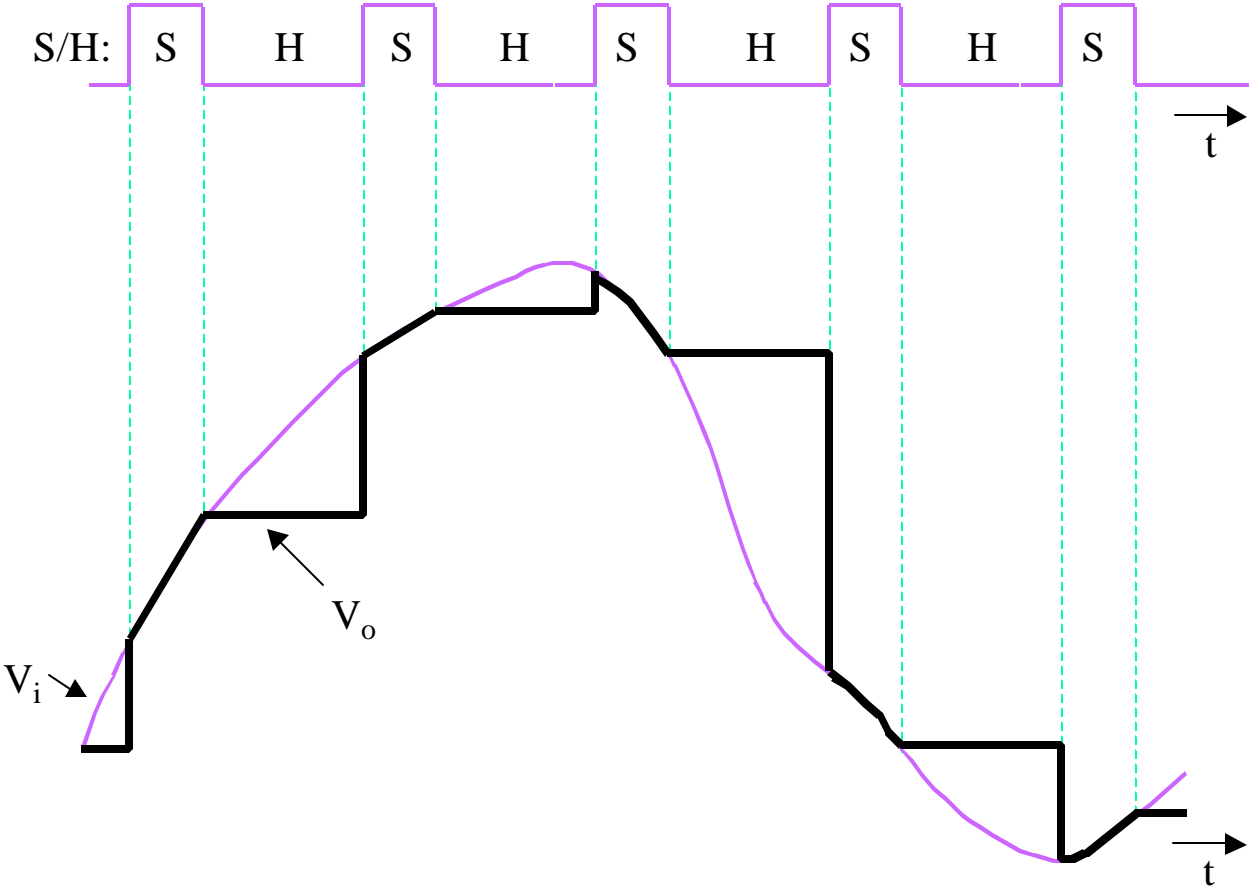


Block Diagram




I dealized Response

Performances of S & H

➔ Realistic Transient Response:

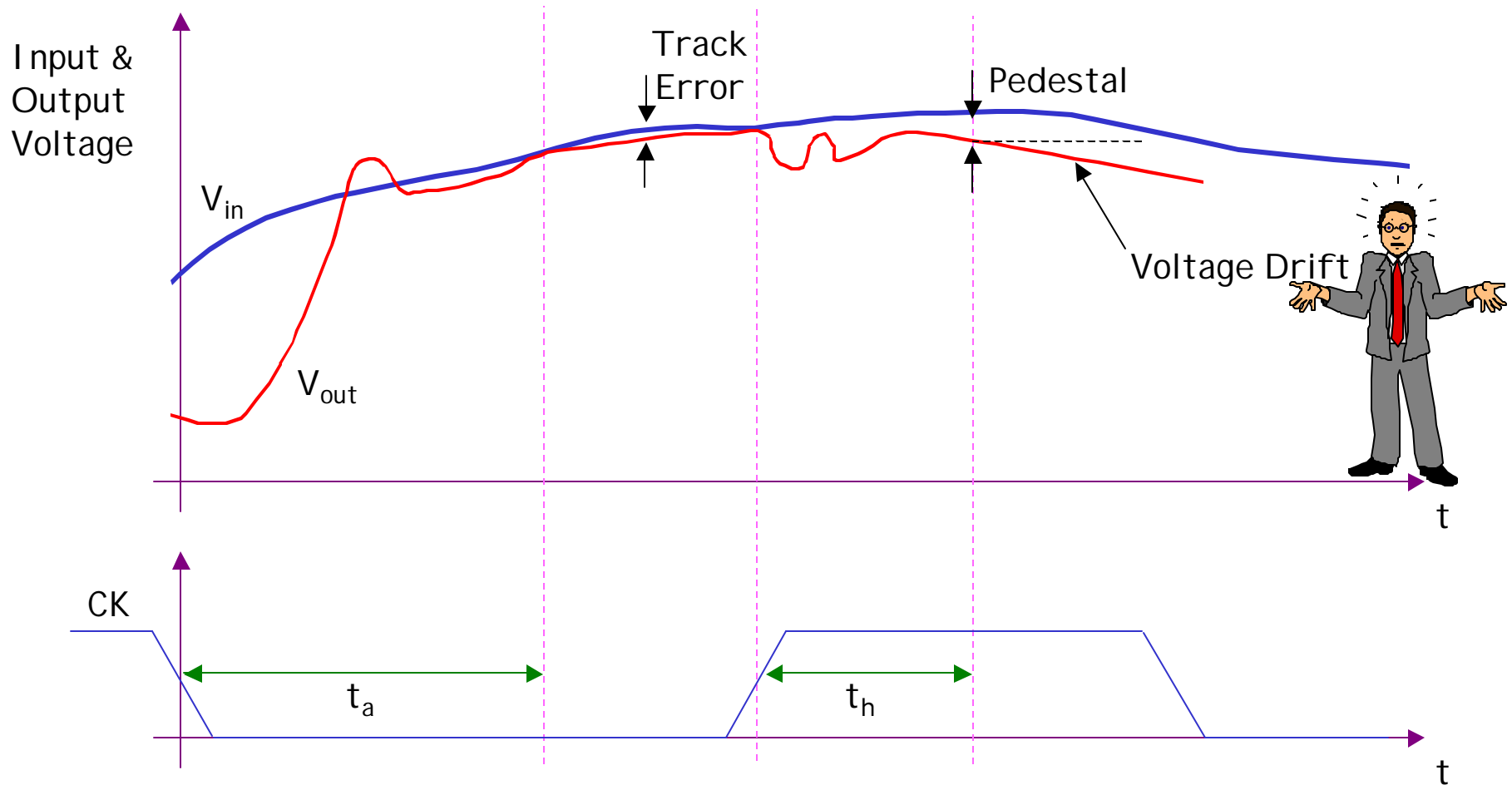

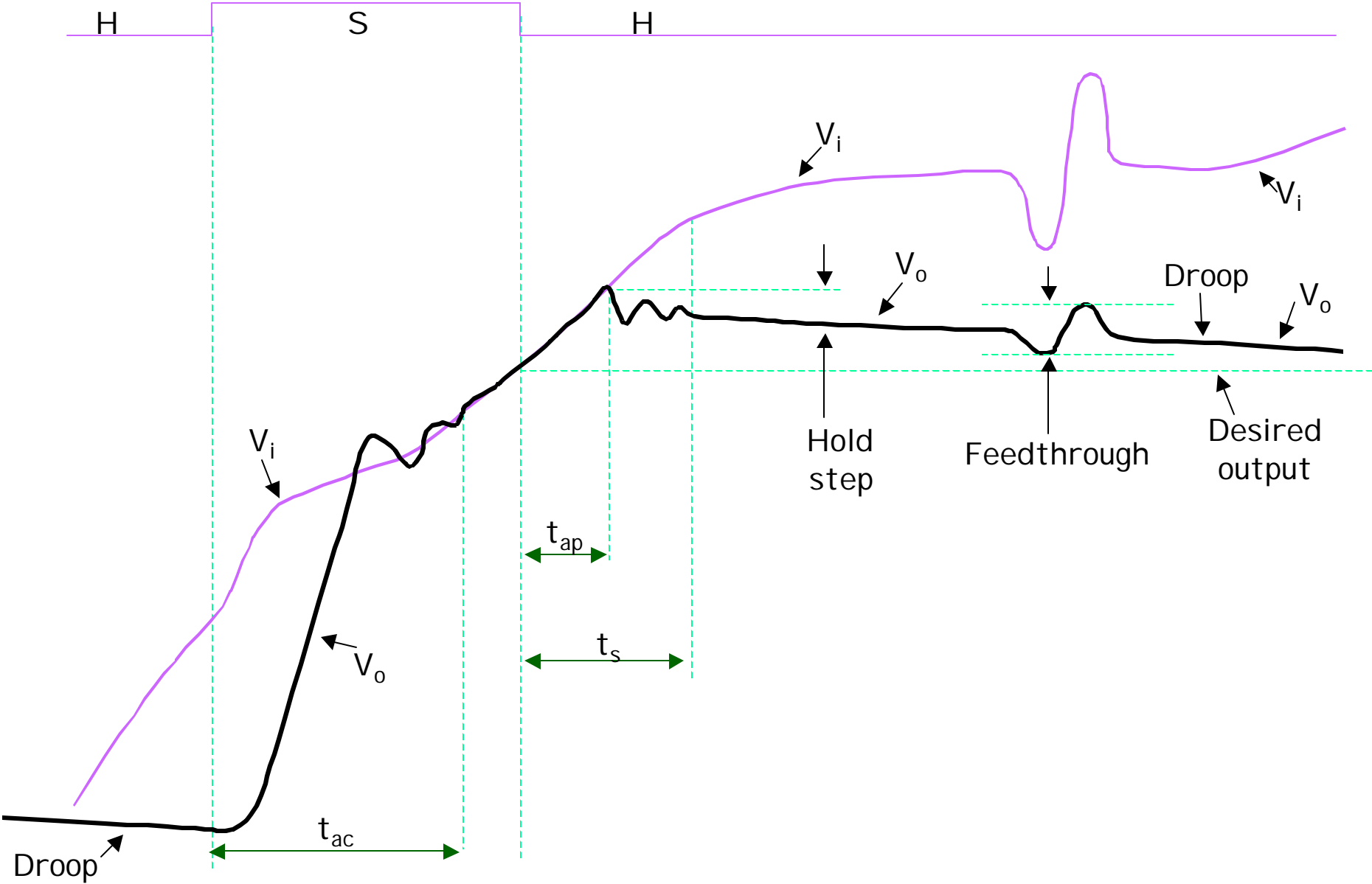S/H Circuit Waveforms and Performance Parameters




Performance Definition

- **Acquisition Time:** the required time for the output transient after the sampling signal.
- **Hold Settling Time:** the time after the hold signal required for the output to settle within an acceptable error.
- **Pedestal Error:** due to the transition of sample to hold mode.
- **Voltage Drift:** the rate of discharge of the sampling capacitor during the hold mode.
- **Dynamic Range:** the ratio of the maximum and minimum input level, which can be sampled with a given resolution.

Performance Definition

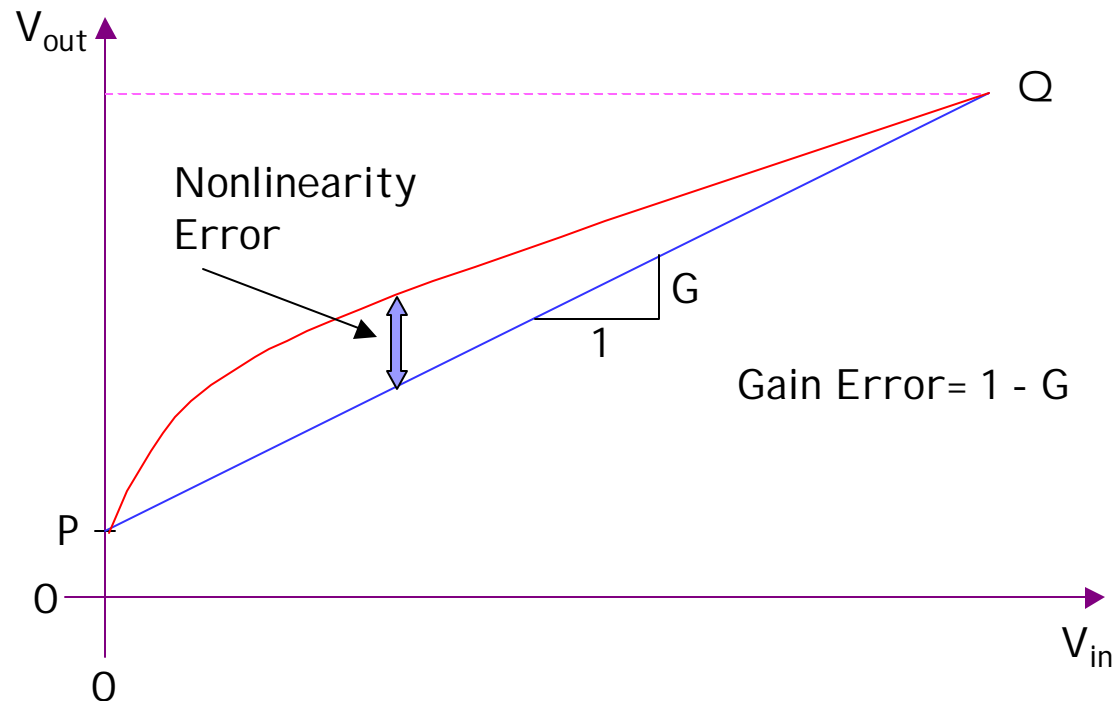
- **Nonlinearity Error:** the maximum deviation of the $V_{\text{out}}/V_{\text{in}}$ characteristic from the straight line passed through the end points.
- **Gain Error:** the deviation of the slope of the straight line from unity.



Track and hold

Performance Definition

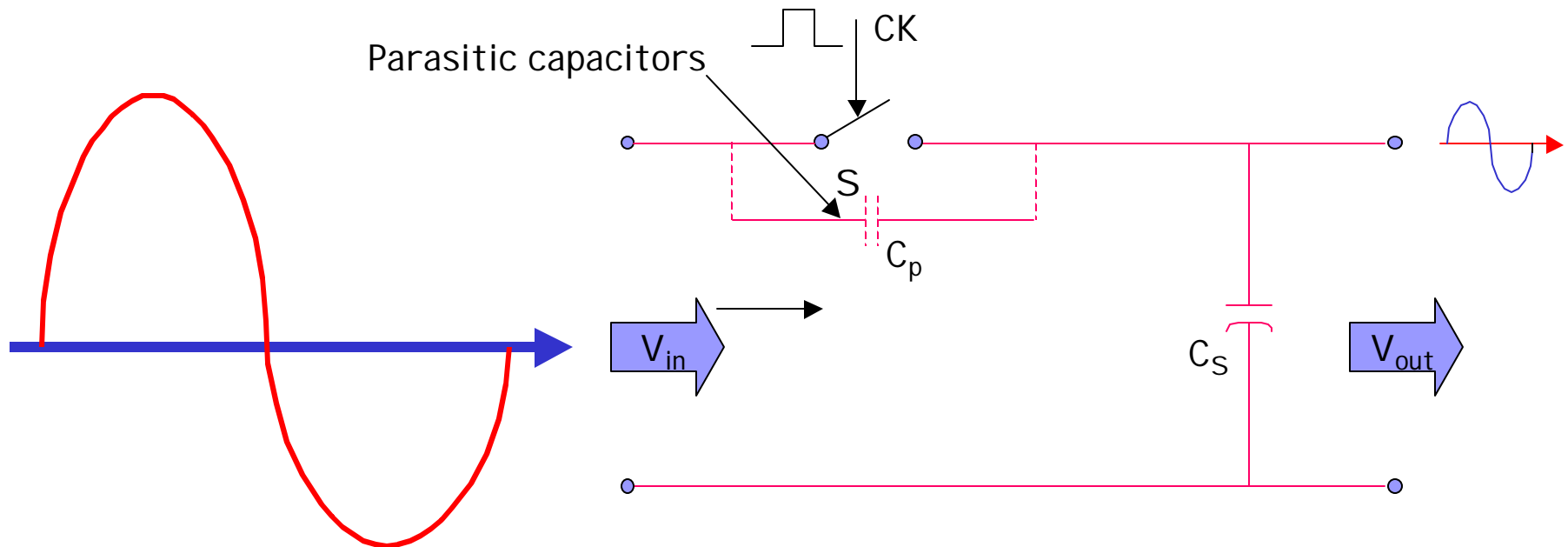- **Hold Mode Feedthrough:** the percentage of the input signal that appears at the output during the hold mode.





Performance Definition

- Aperture Error:** the random variation of the turn off time of the switch results in an uncertain sampling time.




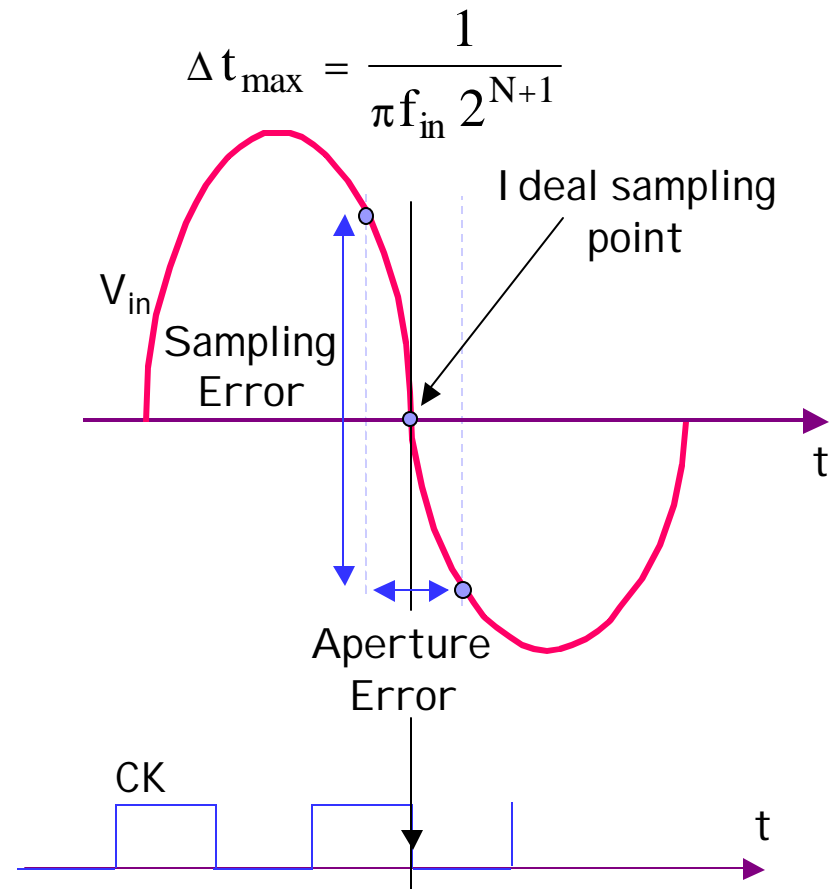 Maximum Allowable
Aperture Error for 1/2 LSB:



Performance Definition

 - **Signal-to-Noise Ratio (SNR):** the ration of the signal power to the noise power at the output. The sources of noise are the input and output buffer, switch, and clock jitter.
- **Signal to Noise + Distortion Ratio (SNDR):** the ration of signal power to the total noise and harmonic power at the output. The source of harmonics are the nonlinearity of the buffers and the switch.



Sample-and-Hold Basic Architectures

 


Fig. 1 An open-loop track and hold realized using MOS technology.

Analysis

$$\Delta Q_{C_{hld}} = \frac{Q_{CH}}{2} = \frac{C_{OX}WL V_{eff-1}}{2}$$

where V_{eff-1} is given by

$$V_{eff-1} = V_{GS1} - V_{tn} = V_{DD} - V_{tn} - V_{in}$$

$$\Delta V' = \frac{\Delta Q_{C-hld}}{C_{hld}} = -\frac{C_{OX}WL V_{eff-1}}{2C_{hld}} = -\frac{C_{OX}WL(V_{DD} - V_{tn} - V_{in})}{2C_{hld}}$$

$$\Delta V' \cong -\frac{C_{OX}WL_{OV}(V_{DD} - V_{SS})}{C_{hld}}$$

 


Fig. 2 An open-loop track and hold realized using a CMOS transmission gate.


 



Fig. 3 An open-loop track and hold realized using an n-channel switch along with a dummy switch for clock-feedthrough cancellation.

 

Buffered Sample & Hold Circuit


➔ Input and Output Buffer:

 The capacitor voltage during the hold mode can be affected by the current drawn by the following circuit. Therefore, the output voltage is buffered.




Unity Gain Buffer Circuit: BJT and CMOS implementations

Bipolar Technology

 



CMOS Technology

 

Track & Hold (T&H) Circuit

➔ Simple Closed-Loop Architecture:

 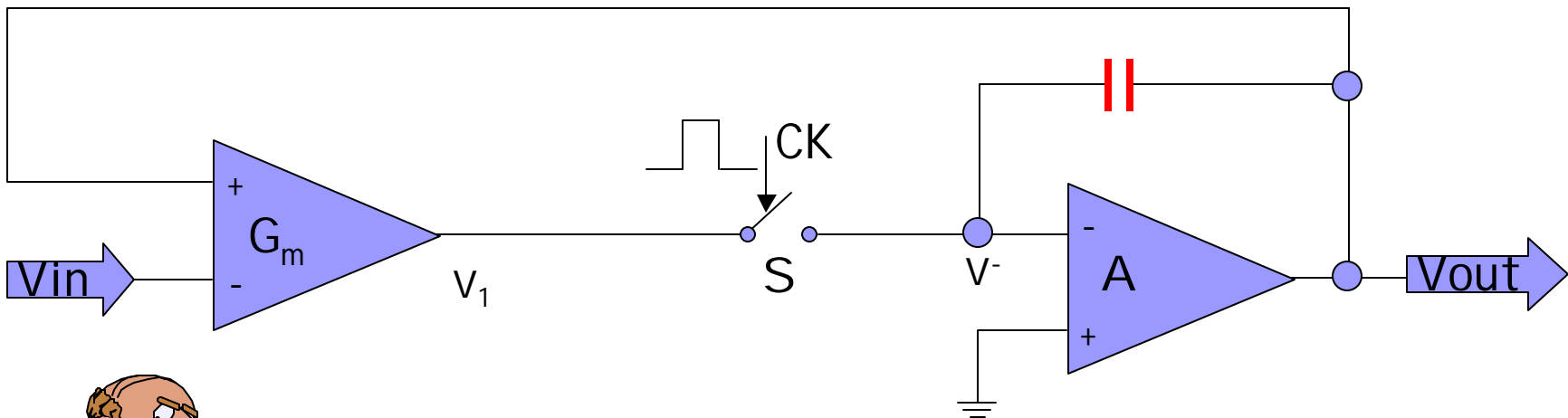During the sampling time, the drain and source voltage of MOS switch are closed to ground. Thus the charge injection and clock feedthrough introduce an offset voltage at the output and is independent of the input voltage.




Disadvantage: stability problems and low speed.

T&H Circuit: Closed-Loop Architecture

➔ Offset Voltage Cancellation:



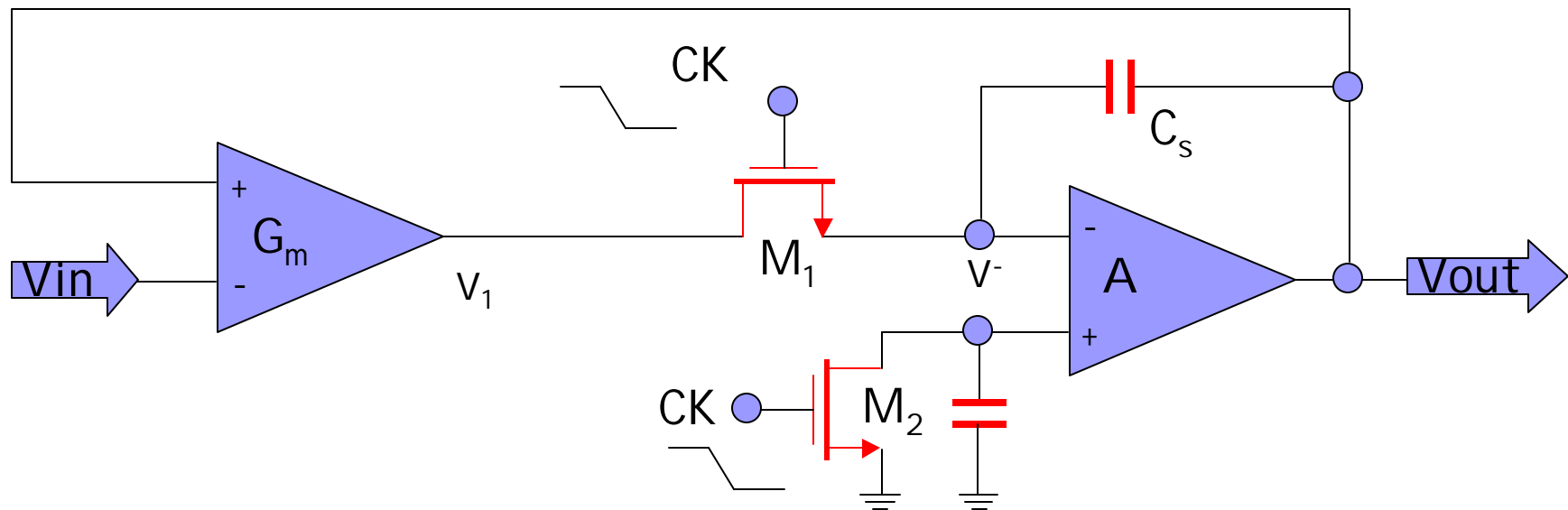
The charge injection and clock feedthrough can be cancelled out by applying a replica of the offset voltage to the positive terminal of the second amplifier (common-mode voltage).



T&H Circuit: Switched Capacitor

➔ Switched-Capacitor Architecture:

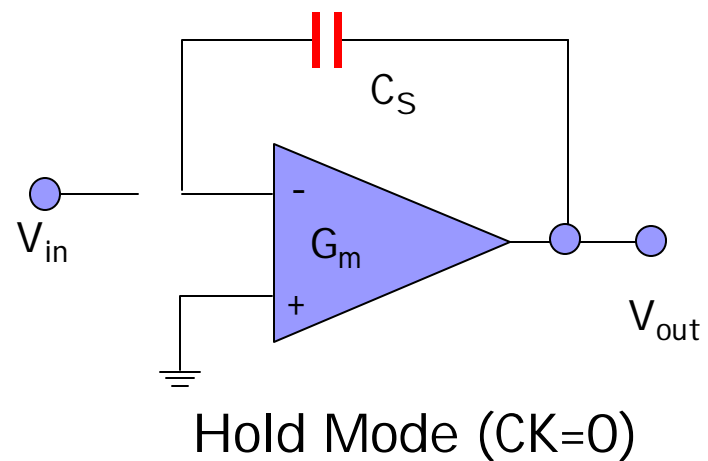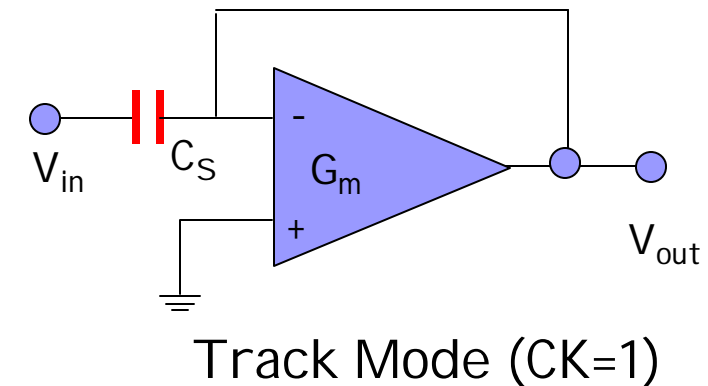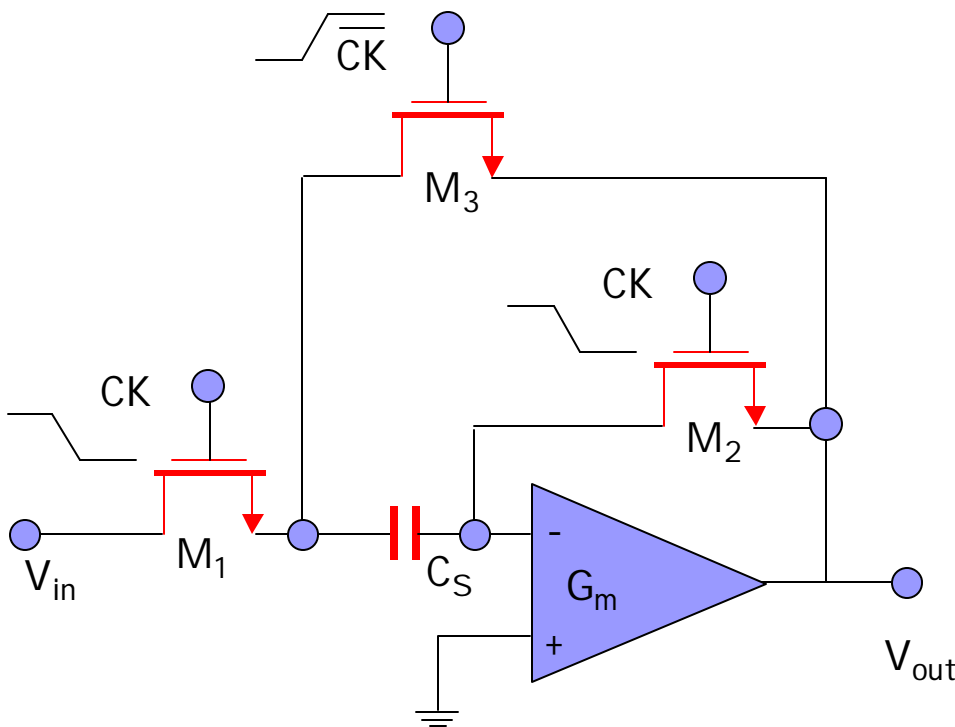This architecture consists of sampling capacitor C_S , amplifier G_m , and MOS switches.



Evolution of S/H Architectures

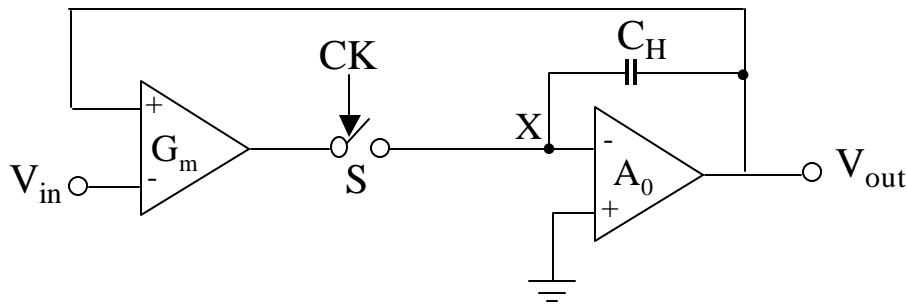


Fig A. Closed-loop sample-and-hold architecture.


 


Fig B. Including an opamp in a feedback loop of a sample and hold to increase the input impedance.

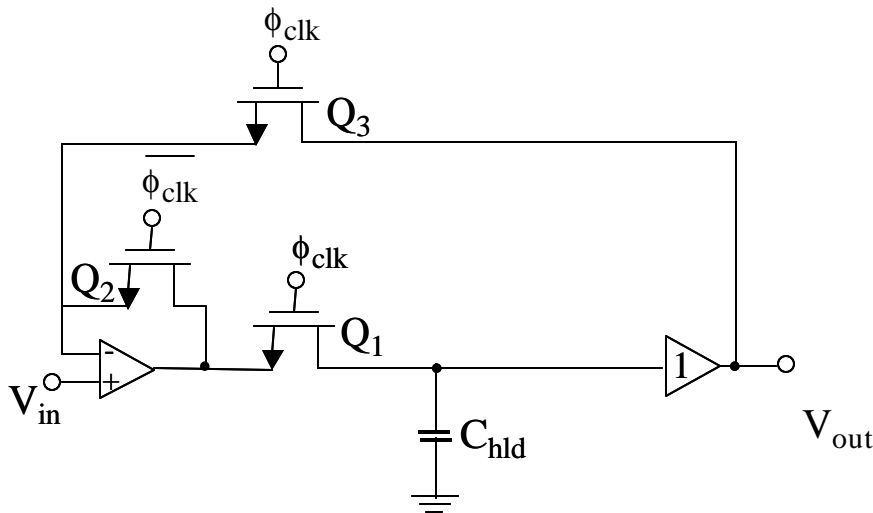

C. Adding on additional switch to the S/H of Fig B to minimize slewing time.


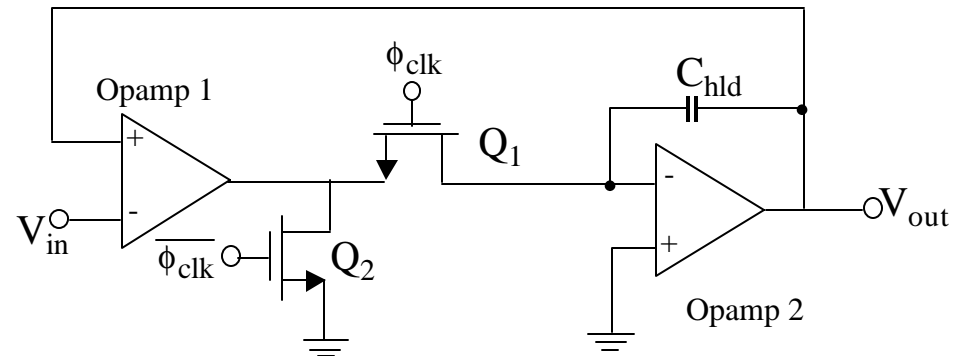
 


Fig D An improved configuration for an S/H as compared to that of Fig C

T&H Circuit: Current-Mode

➔ Current-Mode Architecture:

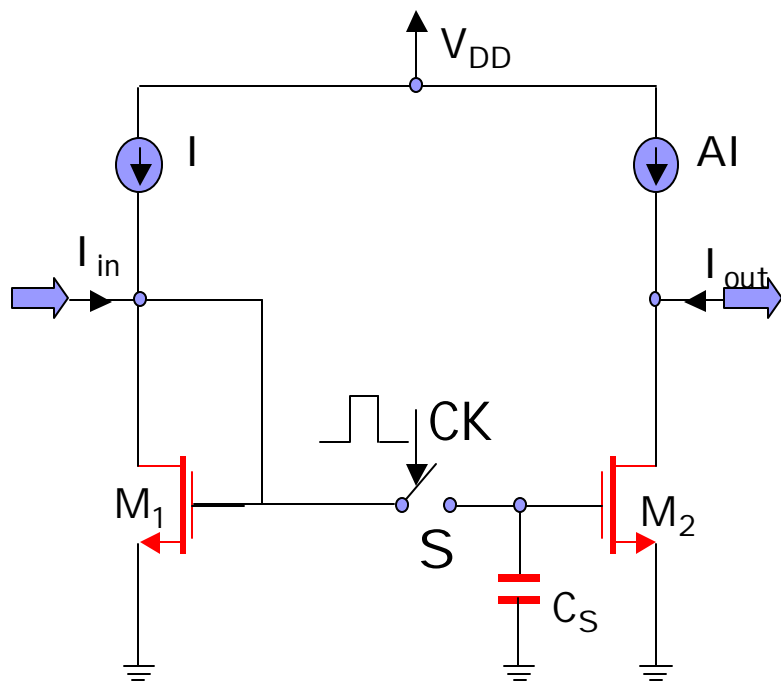Advantages: high-speed (over 100MHz) and low voltage (<1.2).
The speed depends on the time constant given by:





$$\tau = \frac{C_S}{g_{m1}}$$

$$C_S = \frac{2}{3} C_{ox} (1 + A) W_1 \cdot L_1$$

$$g_{m1} = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{Th})$$

Two Op Amps S/H Circuit

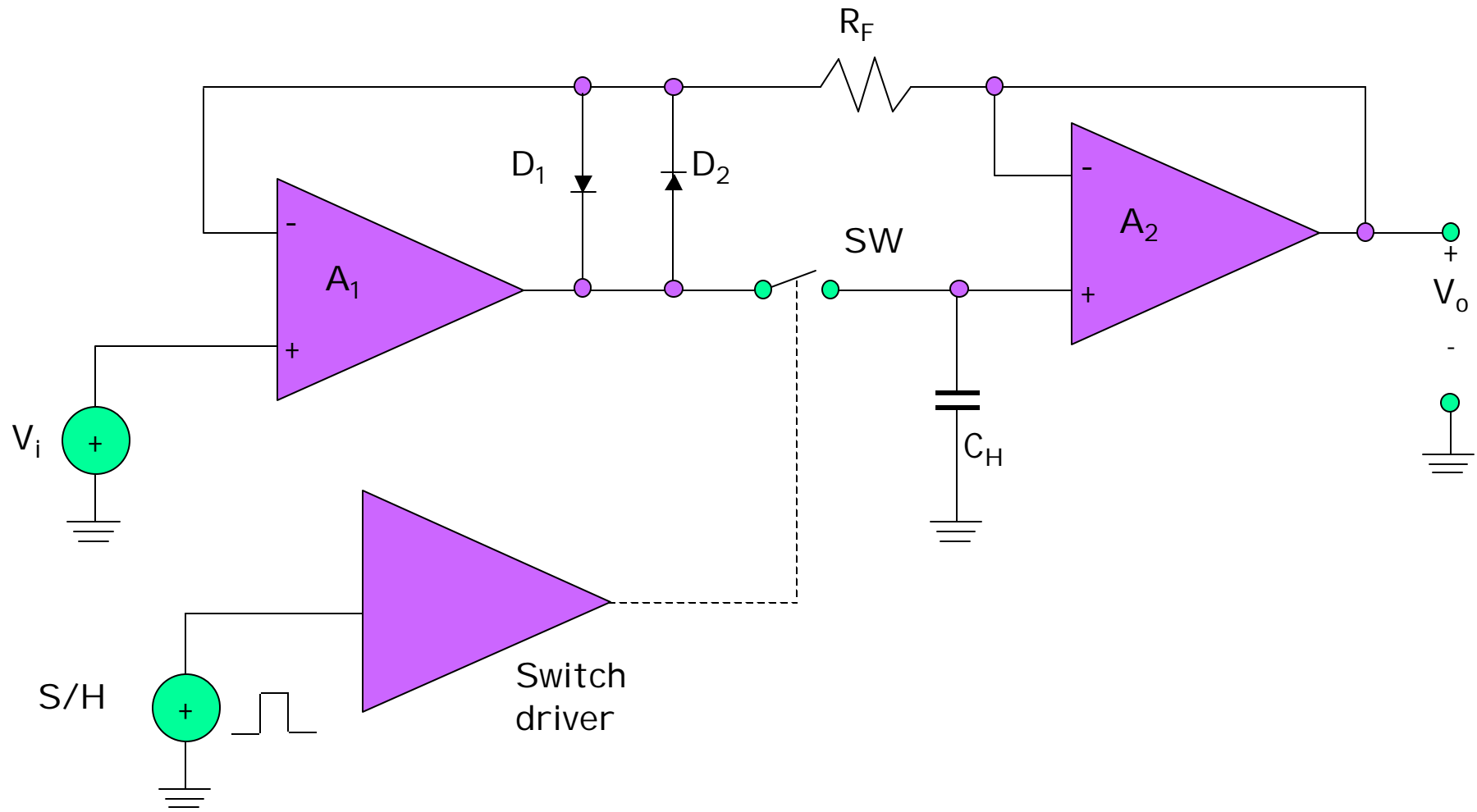

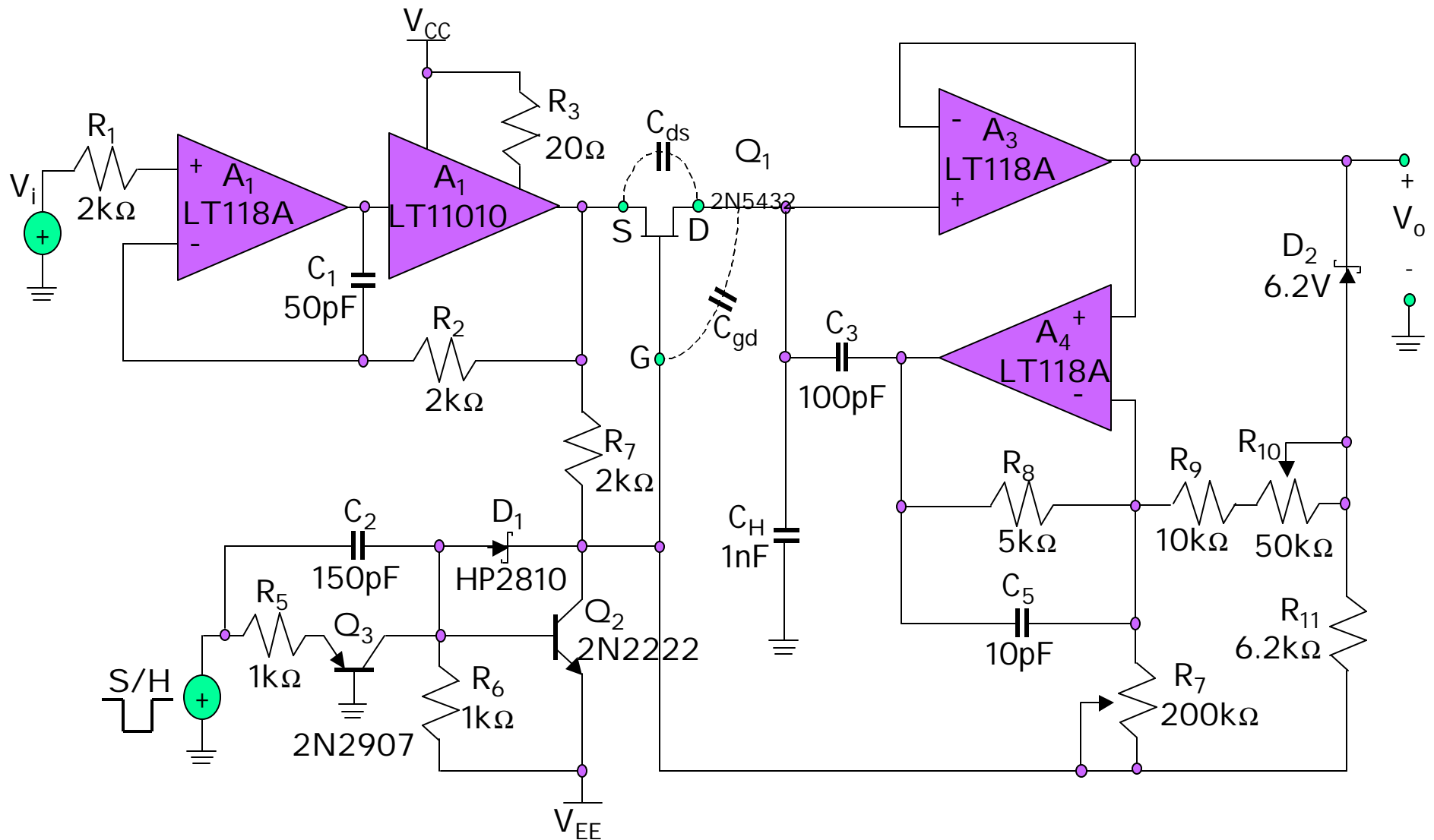

A 5 MHz track-and-hold circuit, using discrete components, with charge compensation to minimize the hold step.

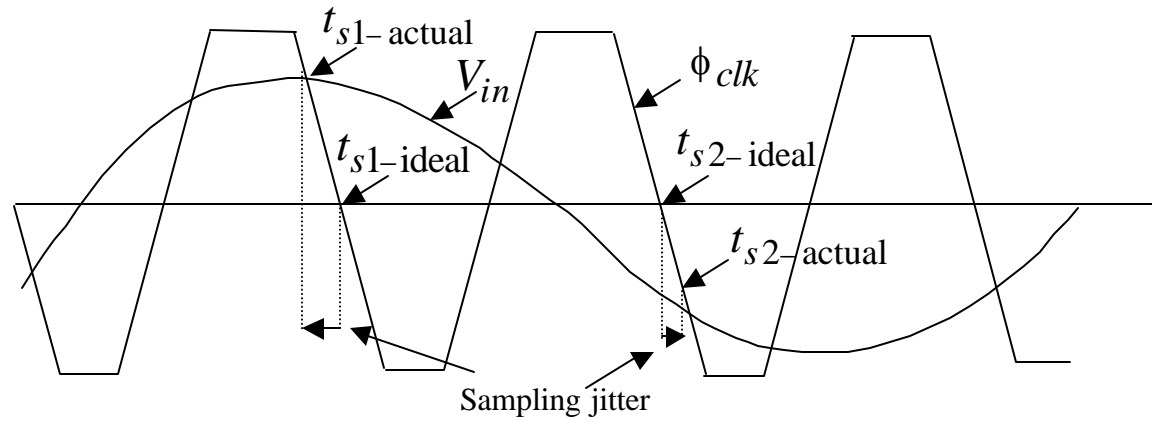


Fig. The clock waveforms for V_{in} and ϕ_{clk} used to illustrate how a finite slope for the sampling clock introduces sampling-time jitter.

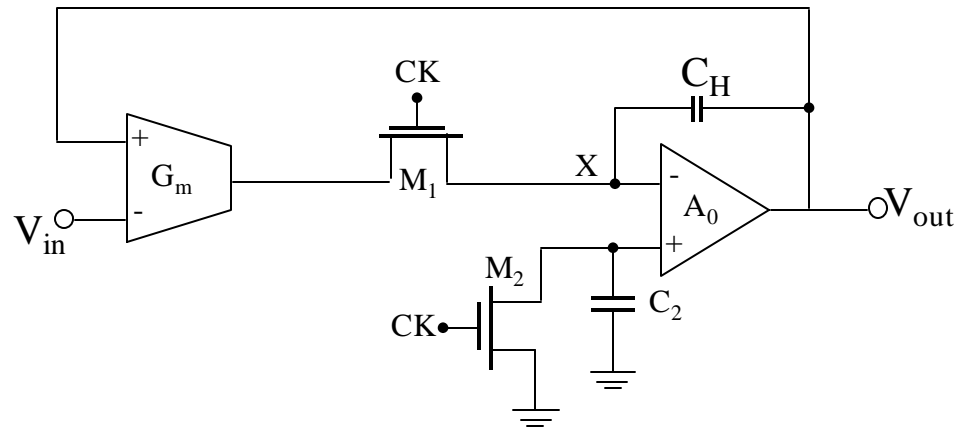


Fig. Closed-loop sample-and-hold architecture with pedestal cancellation.

S/H Open Loop Architecture with Miller Capacitance


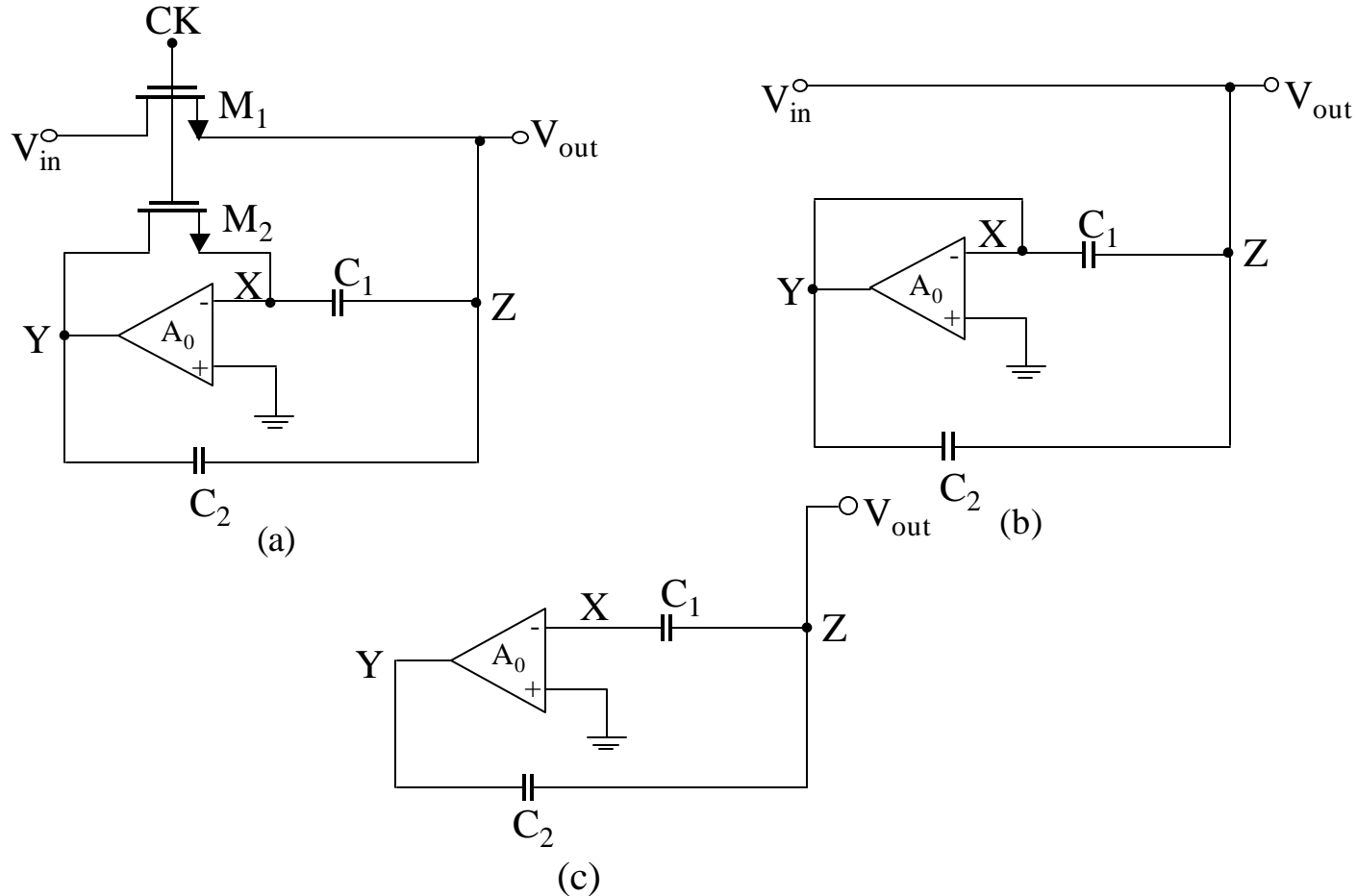



Fig. Open-loop architecture with Miller capacitance. (a) Basic circuit; (b) equivalent circuit in the acquisition mode; (c) equivalent circuit in the hold mode.

The open-loop architecture with Miller capacitance employs two different values of capacitance in the acquisition and hold modes to achieve high speed and small pedestal error. This is accomplished using a Miller amplifier that multiplies the effective value of the sampling capacitor by a large number when the SHA enters the hold mode.

Switched-Capacitor S/H Implementations


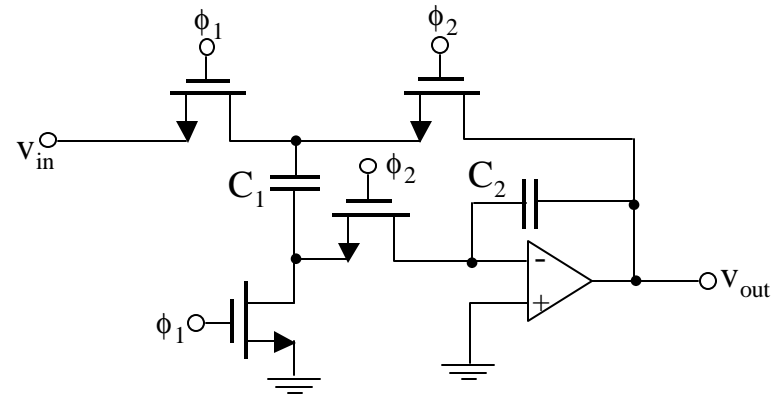


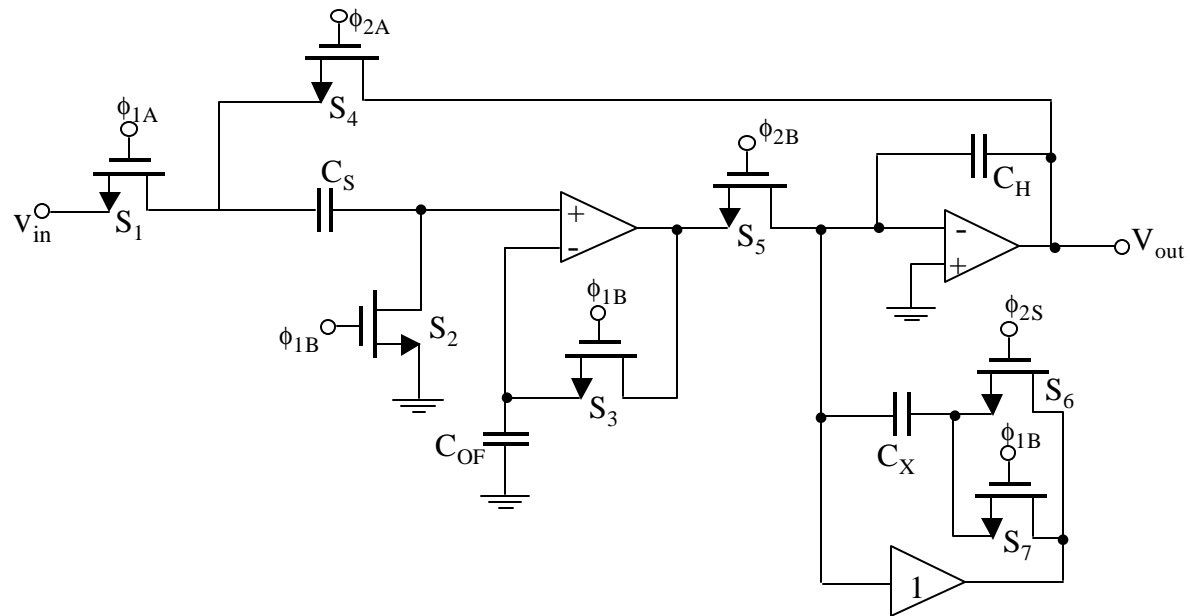A switched-capacitor sample and hold and low-pass filter.



A switched-capacitor S/H.

MULTIPLEXED-INPUT ARCHITECTURES

 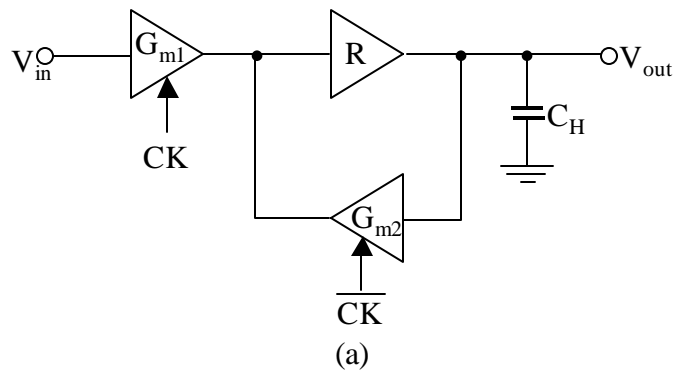

Multiplexed-input architecture. (a) Basic (single-ended) circuit; (b) equivalent circuit in the hold mode.


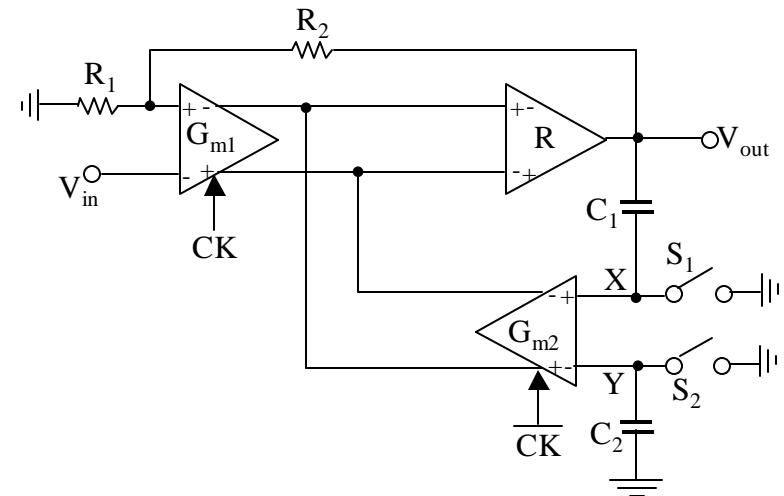
 


Fig. 15(a) Dual-loop multiplexed architecture.

 


Equivalent circuits of dual-loop multiplexed-input architecture. (b) Acquisition mode; (c) hold mode.

T&H Circuit: Current-Mode

➔ Closed-Loop Current-Mode Architecture:

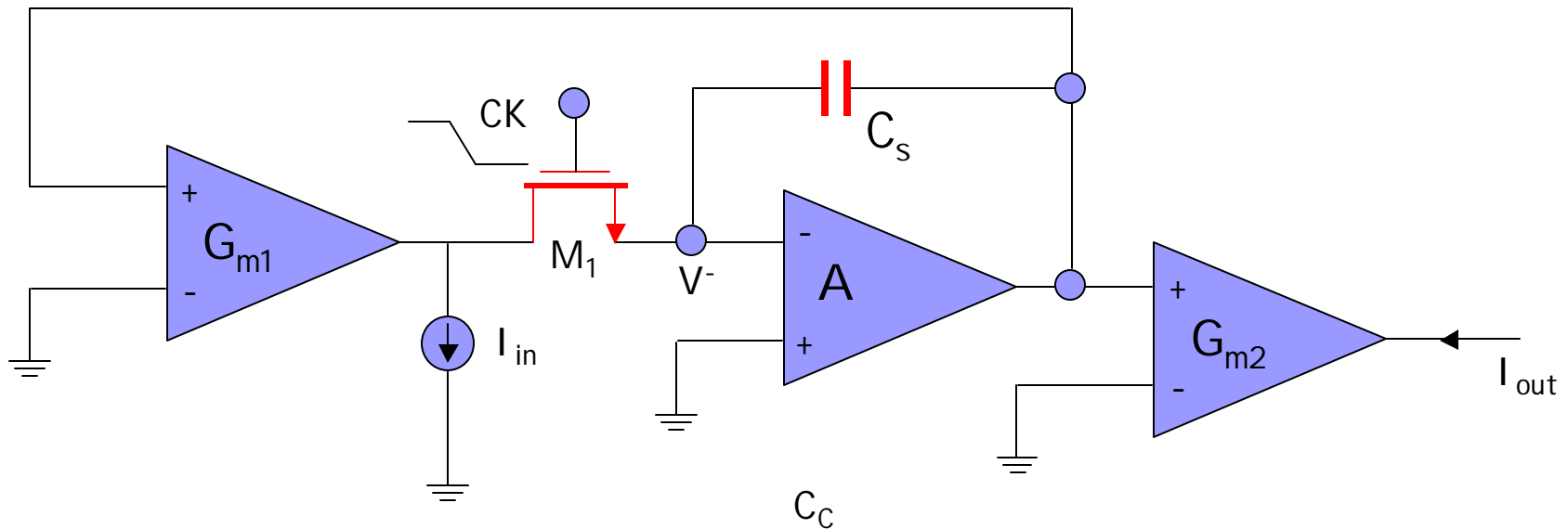
This architecture needs stability and speed considerations.
The distortion of G_{m2} affects directly the output current [21].




T&H Circuit: Example

➔ BiCMOS Track & Hold Amplifier (12-Bit & 50MSPs):

 This circuit consists of input buffer, hold section, and output buffer [3].



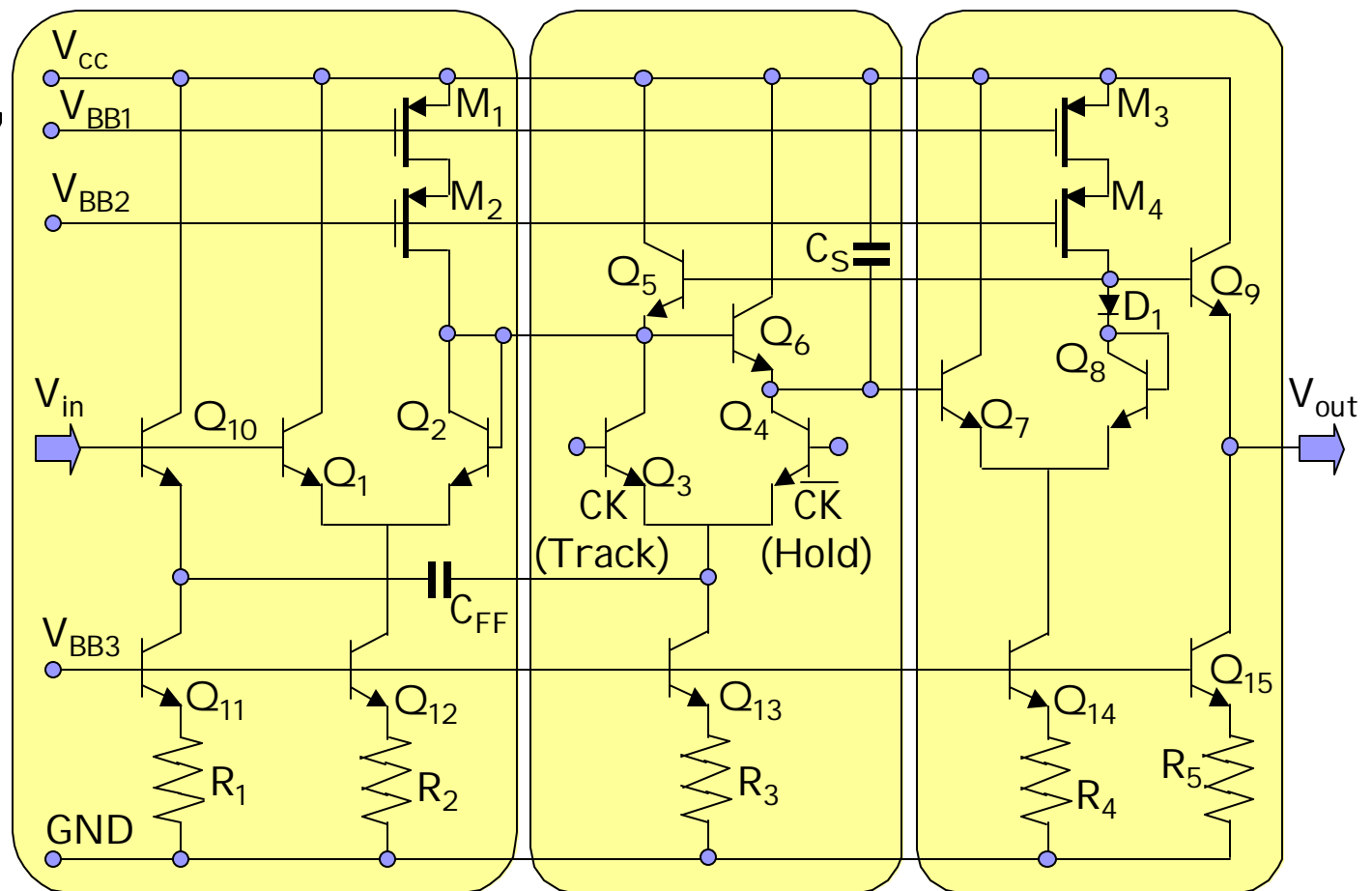$C_S = 3\text{pF}$
 C_{FF} is a feed-forward compensation capacitor for the charge injection of Q_4



RECYCLING S/H ARCHITECTURE

 


Fig. 16 Recycling architecture.



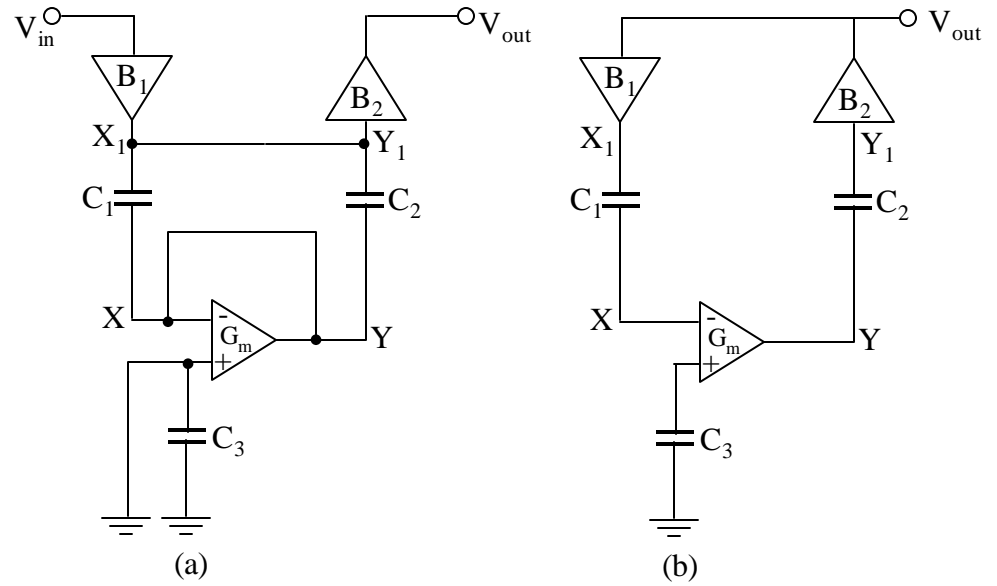


Fig. 17 Equivalent circuits of recycling architecture.
(a) Sampling mode; (b) hold mode.

Integrating Amplifier S/H Circuit

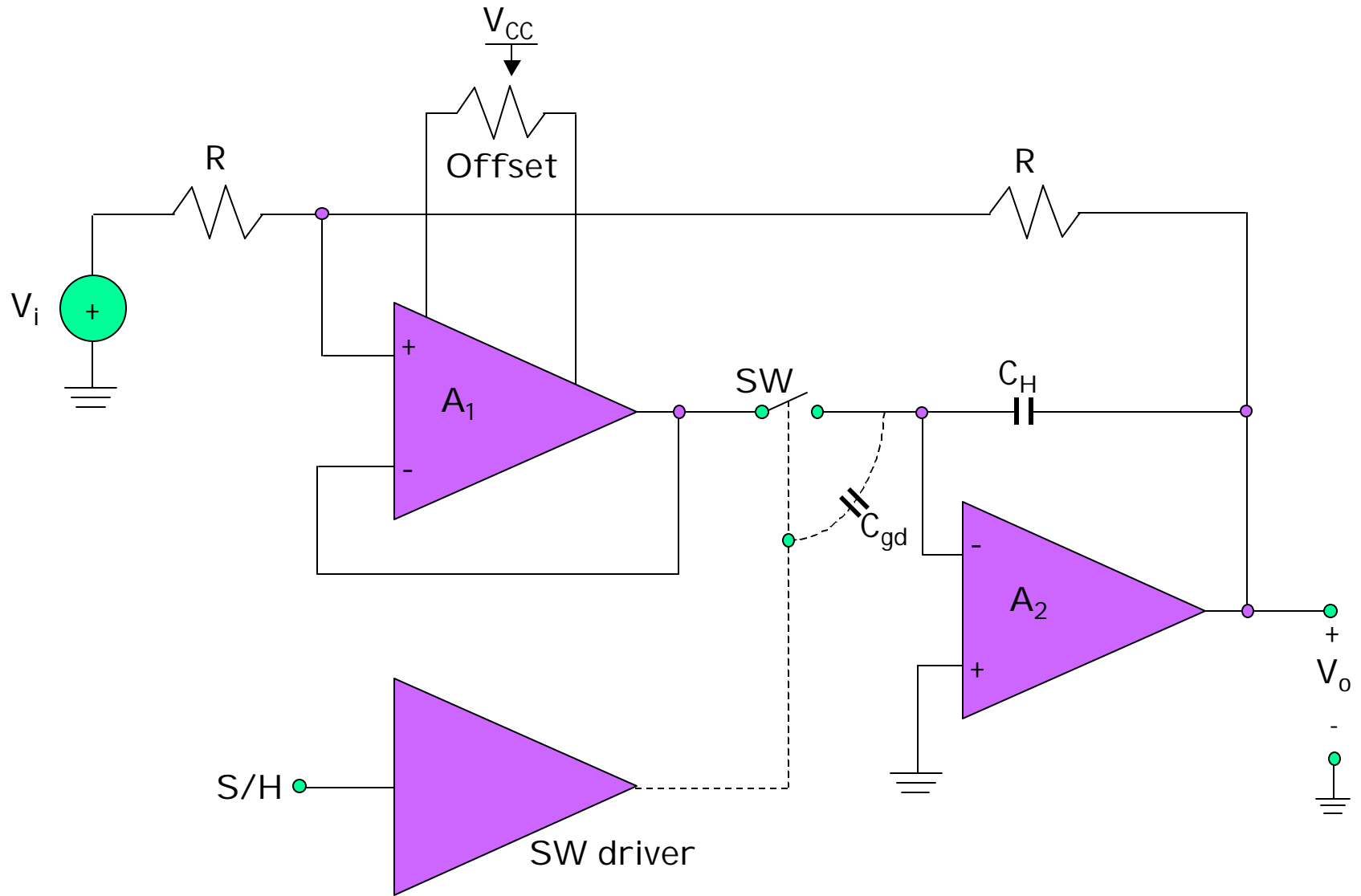


Improved S/H Circuit

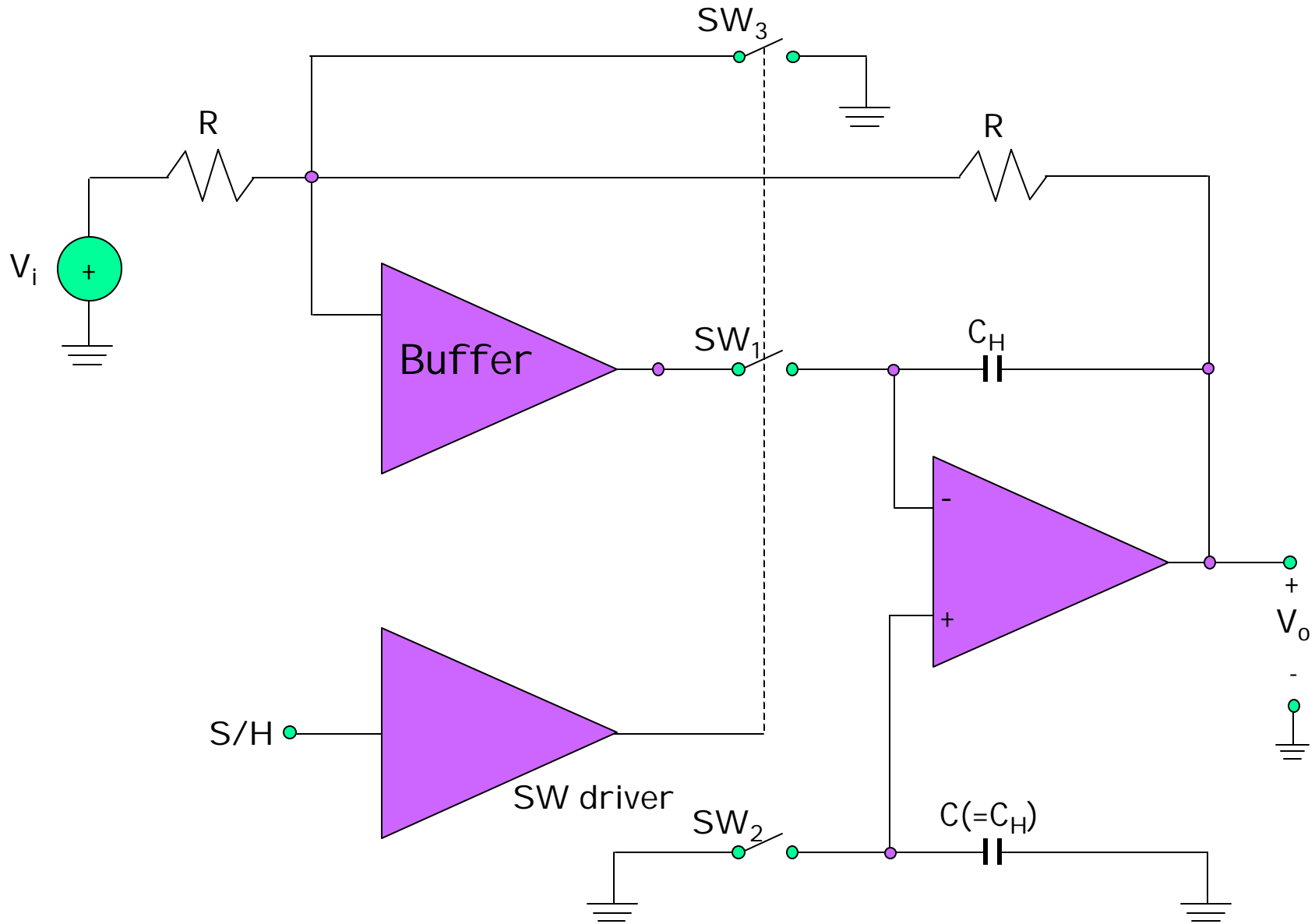

Sample and Hold based on a Switched Op Amp

L.Dai and R. Harjani," CMOS Switched-Op-Amp Based Sample and Hold Circuit, IEEE JSSC, January 2000, pp 109-113

 Charge injection and clock feedthrough mechanism





$$Q_{ch} = -WLC_{ox}(V_{GS} - V_T)$$

$$\Delta V' = \frac{k \cdot Q_{ch}}{C_h} = -\frac{kWLC_{ox}(V_{GS} - V_T)}{C_h}$$


$$\Delta V'' = -\frac{(V_{DD} - V_{SS})C_{para}}{C_{para} + C_h}$$

 Channel charge in (top) triode and (bottom) saturation



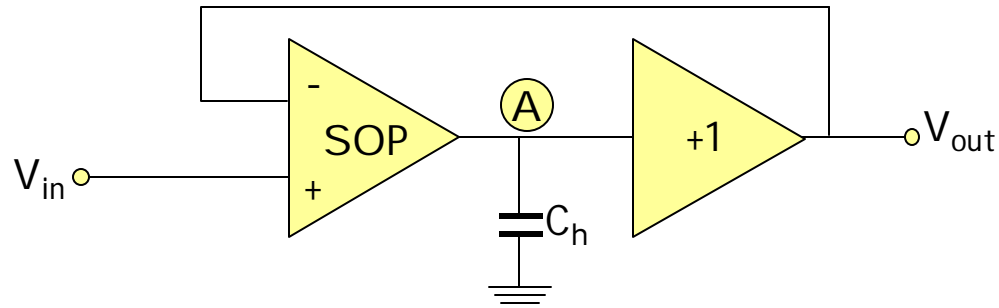


Switched-Op-Amp-Based S/H Circuit

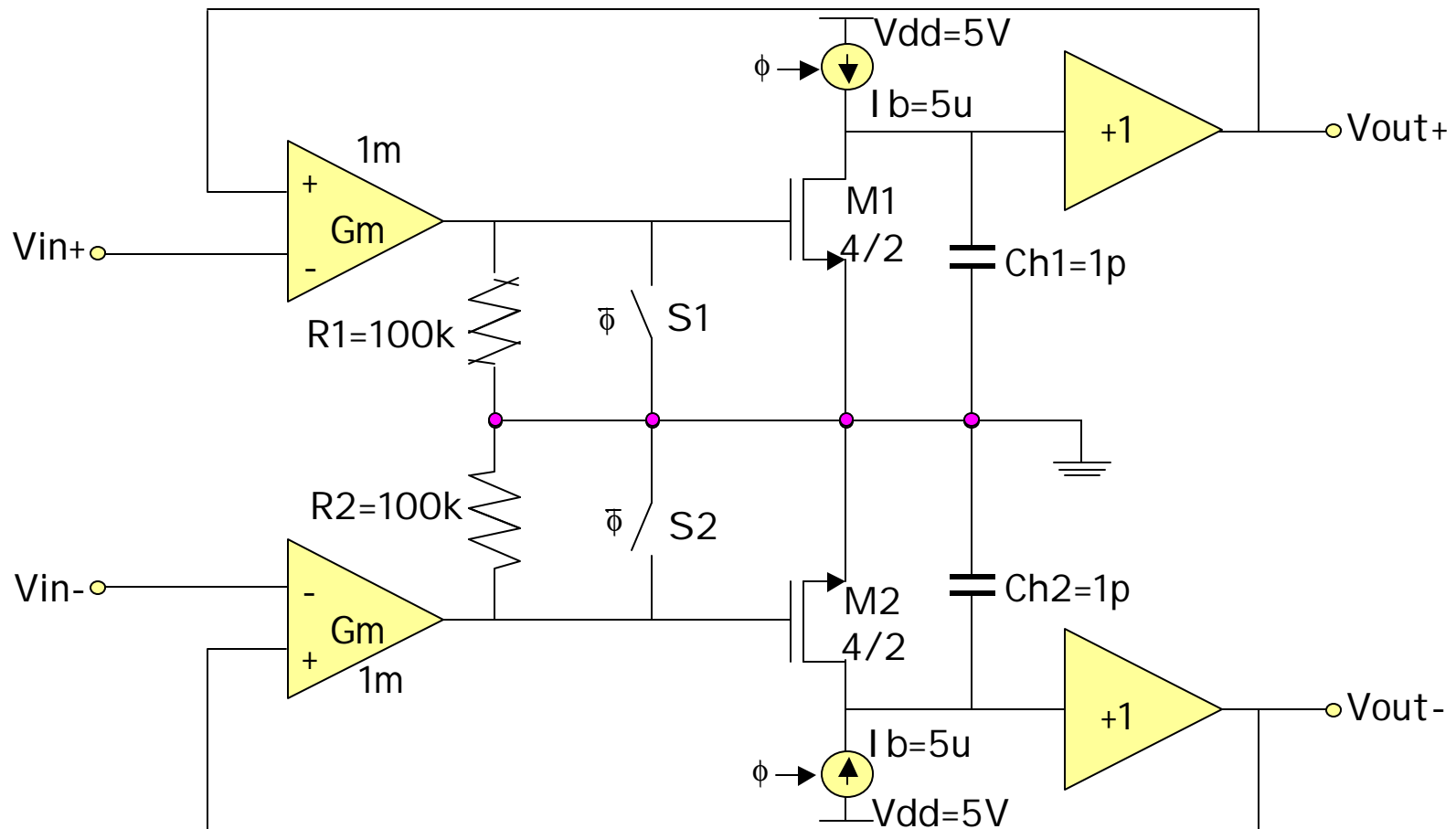

Simplified model of the pseudo-differential SOP-based S/H

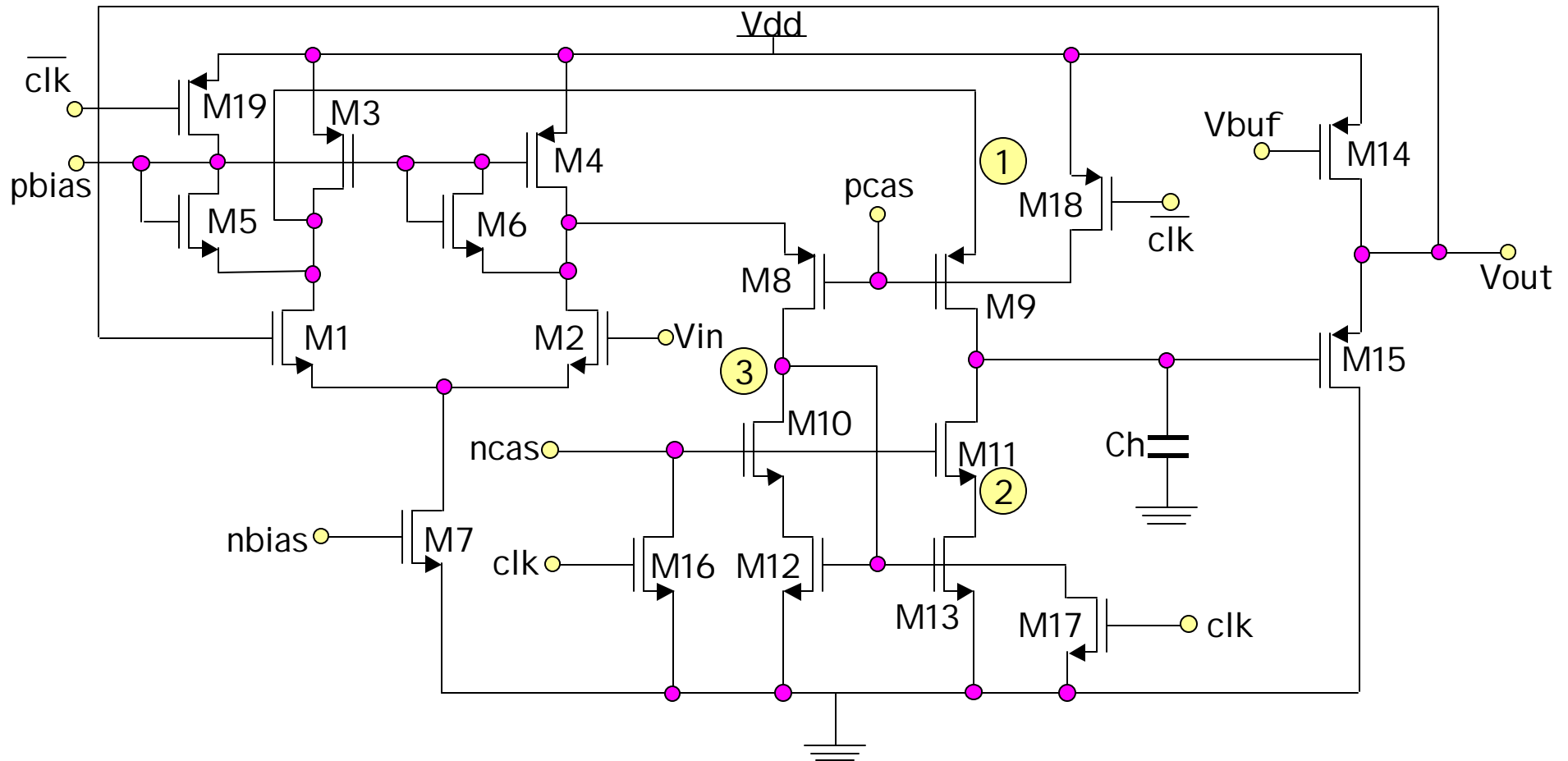
Folded cascode switched op-amp in the unity-gain feedback configuration




$$V_{Nerr} = -\frac{C_{Npara}}{C_h + C_{Npara}} V_{NGS}$$

$$V_{Perr} = -\frac{C_{Ppara}}{C_h + C_{Ppara}} |V_{PGS}|$$

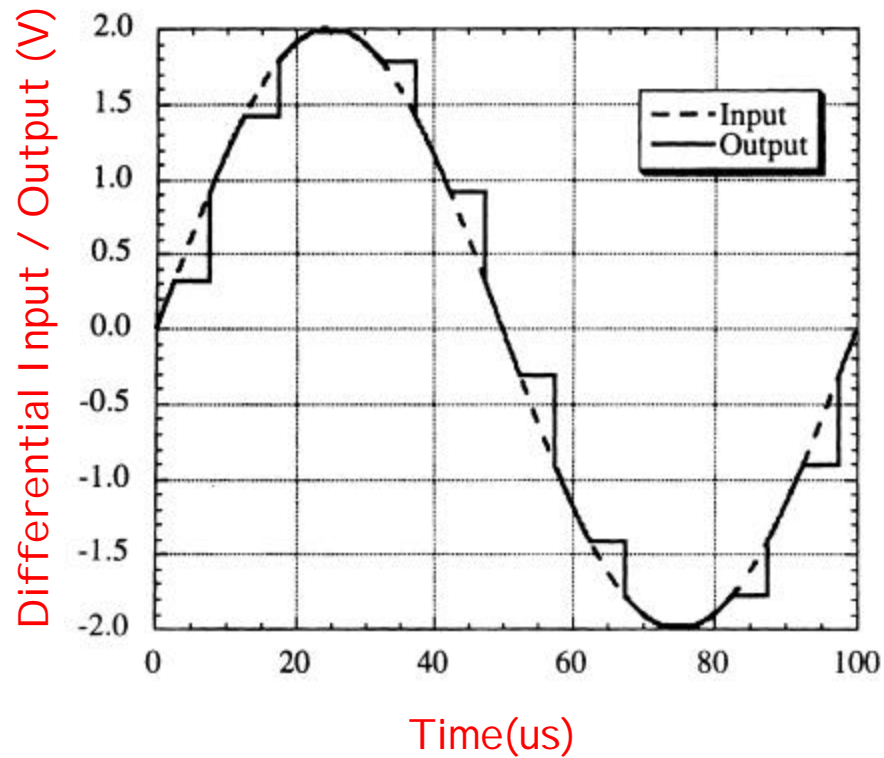Simulation results for a complete cycle of sampled-and-held waveform



 Simulation results of the spectrum of the sampled-and-held waveform



References

- [1] U.L. McCreary and P.R. Gray, "All-MOS charge redistribution analog-to-digital conversion techniques," *IEEE J. Solid-State Circuits*, vol. SC-10, pp. 371-379, Dec. 1975.
- [2] P. Van Peteghem and W. Sanaen, "Single versus complementary switches: A discussion of clock feedthrough in SC circuits," in *Proc. 12th Eur. Solid-State Circuits Conf. (ESSCIRC '86)*, Delft, the Netherlands, Sept. 1986, pp. 16-18.
- [3] C. Eichenberger and W. Guggenbuhl, "Dummy transistor compensation of analog MOS switches," *IEEE J. Solid-State Circuits*, vol. 24, pp. 1143-1146, Aug. 1991.
- [4] M. Nayebi and B.A. Wooley, "A 10-bit video BiCMOS track-and-hold amplifier," *IEEE J. Solid-State Circuits*, vol. 24, pp. 1507-1516, Dec. 1989.
- [5] P.J. Lim and B.A. Wooley, "A high-speed sample-and-hold technique using a miller hold capacitance," *IEEE Solid-State Circuits*, vol. 26, pp. 643-651, Apr. 1991.
- [6] G.C. Temes, Y. Huang, and P.F. Ferguson Jr., "A high-frequency track-and-hold stage with offset and gain compensation," *IEEE Trans. Circuits Syst. II*, vol. 42, pp. 559-560. Aug. 1995.
- [7] S. Brigati, F. Maloberti, and G. Torelli, "A CMOS sample and hold for high-speed ADC's," in *Proc. IEEE Int. Symp. Circuits and Systems Circuits and Systems Connecting the World*, vol. 1, May 1996, pp. 163-166.
- [8] J.H. Shieh, M. Patil, and B.J. Sheu, "Measurement and analysis of charge injection in MOS switches," *IEEE J. Solid-State Circuits*, vol. SC-22, pp. 277-281, Apr. 1986.
- [9] G. Wegman, E.A. Vittoz, and F. Rahali, "Charge injection in analog MOS switches," *IEEE J. Solid-State Circuits*, vol. SC-22, pp. 1091-1097, Dec. 1987.
- [10] D. Jons and K. Martin, *Analog Integrated Circuit Design*. New York: Wiley, 1997.
- [11] J. Crols and M. Steyaert, "Switched-opamp: An approach to realize full CMOS switched-capacitor circuits at very low power supply voltages," *IEEE J. Solid-State Circuits*, vol. 29, no. 8, Aug. 1994.