

Switched Capacitor Circuits I

Prof. Paul Hasler

Georgia Institute of Technology


Switched Capacitor Circuits

- Making a resistor using a capacitor and switches;
therefore resistance is set by a digital clock and the capacitor.
- Filters built in this technology are set by external clocks,
and ratio of capacitors (matching of 0.1% to 1%)

The precision of the frequency response is realized by ratios of capacitors
(1% to 0.1%...better matching, larger caps; therefore more power/area),
and a clock signal (which can be set precisely with a crystal reference)


Capacitor Circuits

Capacitive Voltage Divider

 


$$V_{\text{out}}(t) = \frac{C_1}{C_T} V_1(t) + \frac{Q}{C_T}$$

Multiple Input Voltage Divider

 


$$V_{\text{out}}(t) = \frac{C_1}{C_T} V_1(t) + \frac{C_2}{C_T} V_2(t) + \frac{Q}{C_T}$$

Capacitive Feedback

 

 
$$V_{\text{out}}(t) = -\frac{C_1}{C_2} V_1(t) - \frac{Q}{C_2}$$



$$V_{\text{out}}(t) = \left(1 + \frac{C_1}{C_2}\right) V_1(t) - \frac{Q}{C_2}$$

Non-Overlapping Clocks

 
We will always be using non-overlapping clocks; therefore, we want a waveform like



We effectively have
four phases.

Non-Overlapping Clocks

 We will always be using non-overlapping clocks; therefore, we want a waveform like




We effectively have four phases.

Would want t_d as small as possible
for proper operation

We will also assume that the input
is held constant through
the entire $[n]^{\text{th}}$ cycle

Non-Overlapping Clocks

 We will always be using non-overlapping clocks; therefore, we want a waveform like




We effectively have four phases.


Circuit to generate waveform

Would want t_d as small as possible for proper operation

 
We will also assume that the input is held constant through the entire $[n]^{\text{th}}$ cycle




Basic Switched Capacitors

 


Basic Switched Capacitors

 

Basic Switched Capacitors

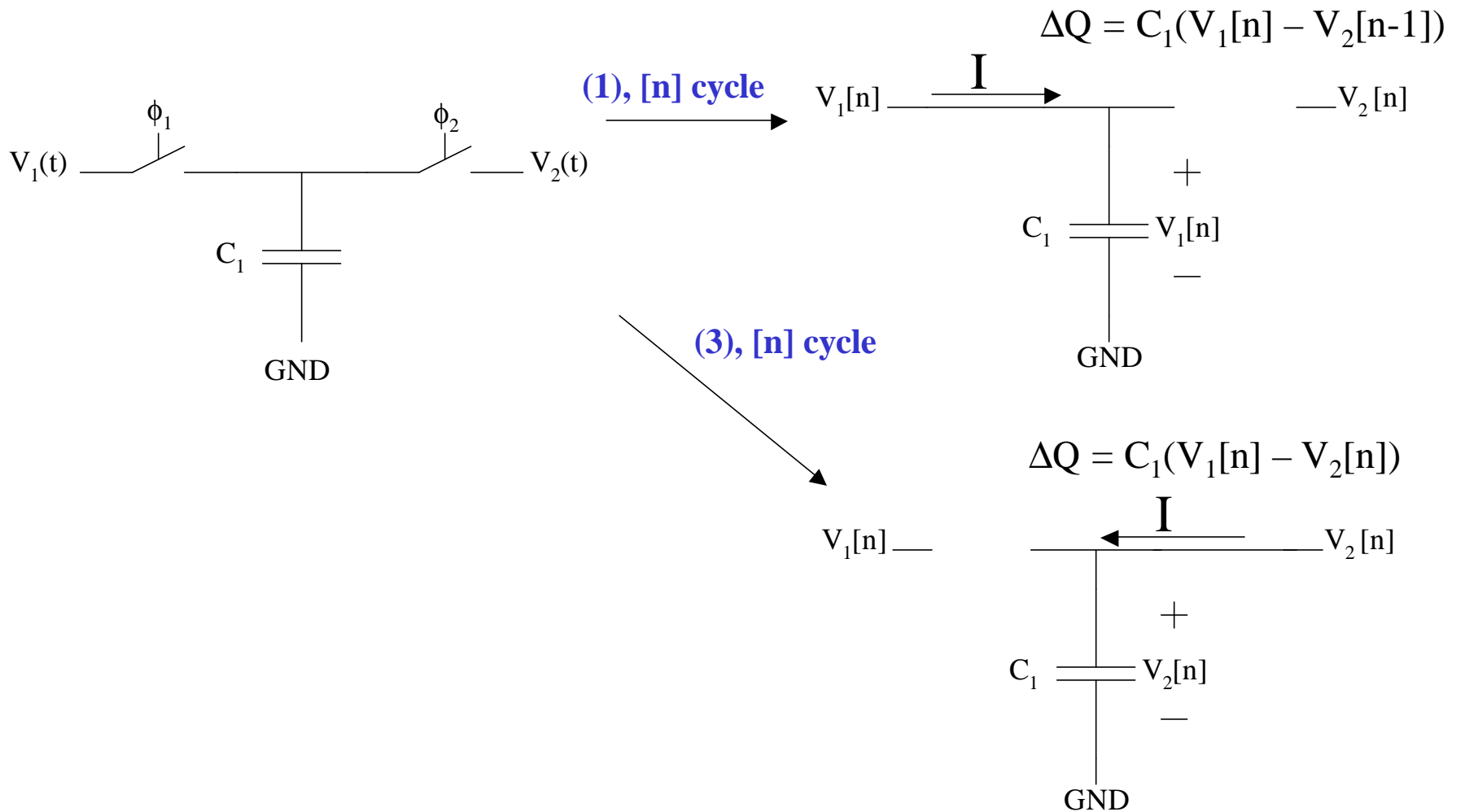

Basic Switched Capacitors


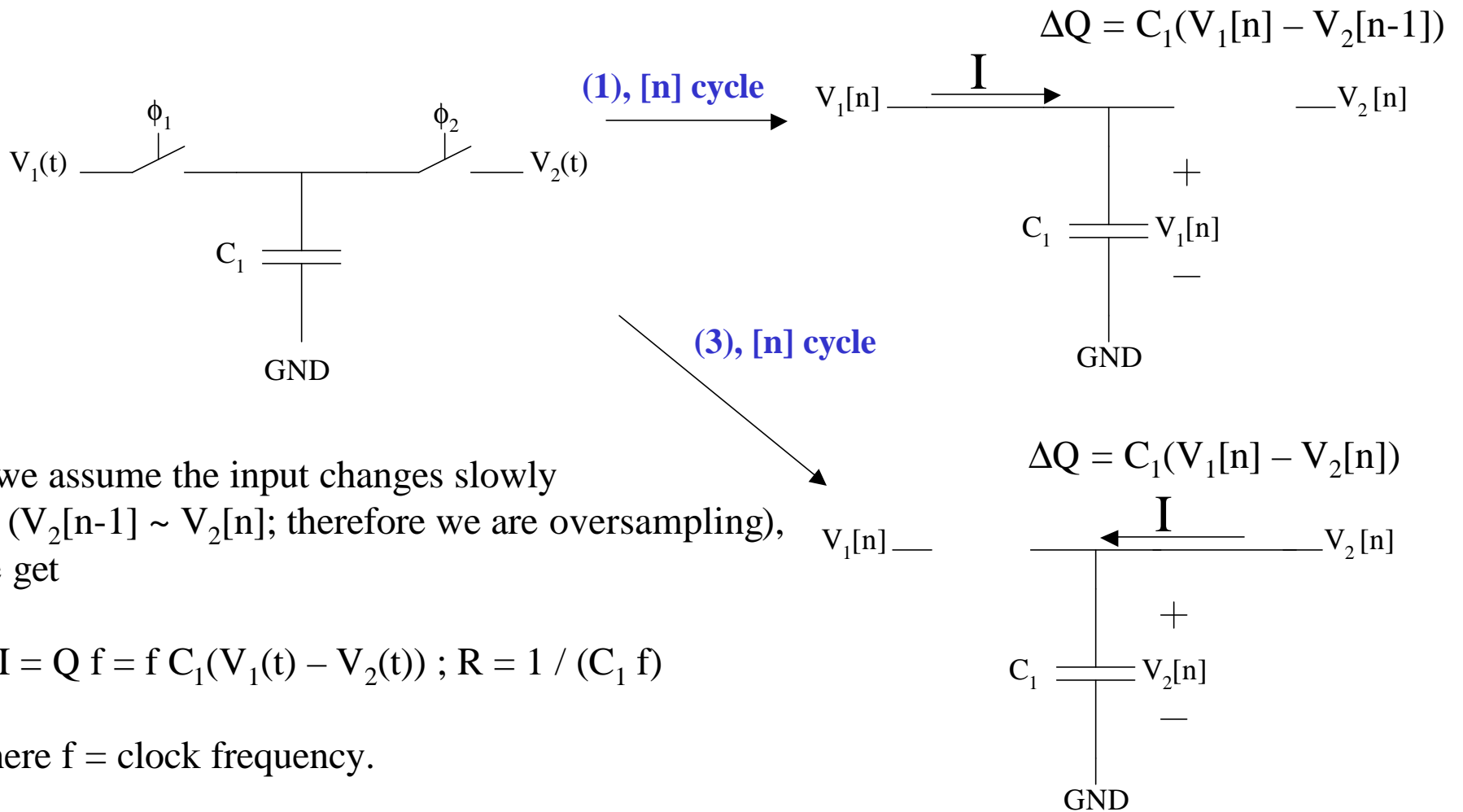


If we assume the input changes slowly
 ($V_2[n-1] \sim V_2[n]$; therefore we are oversampling),
 we get

$$I = Q f = f C_1(V_1(t) - V_2(t)) ; R = 1 / (C_1 f)$$


where f = clock frequency.

Basic Switched Capacitors

  


where f = clock frequency.

Basic Switched Capacitors

 



~

 

where f = clock frequency.

For 0.1pF capacitor,
and a 10kHz clock,
we get a resistance of 1GOhm

Basic Switched Capacitors

  


where f = clock frequency.


For 0.1pF capacitor,
and a 10kHz clock,
we get a resistance of 1GOhm

Rule of thumb: slow moving means
we oversample the Nyquist frequency of the
input signal by a factor of **20 or more**.

Basic Switch-Cap Integrator

 


Basic Switch-Cap Integrator

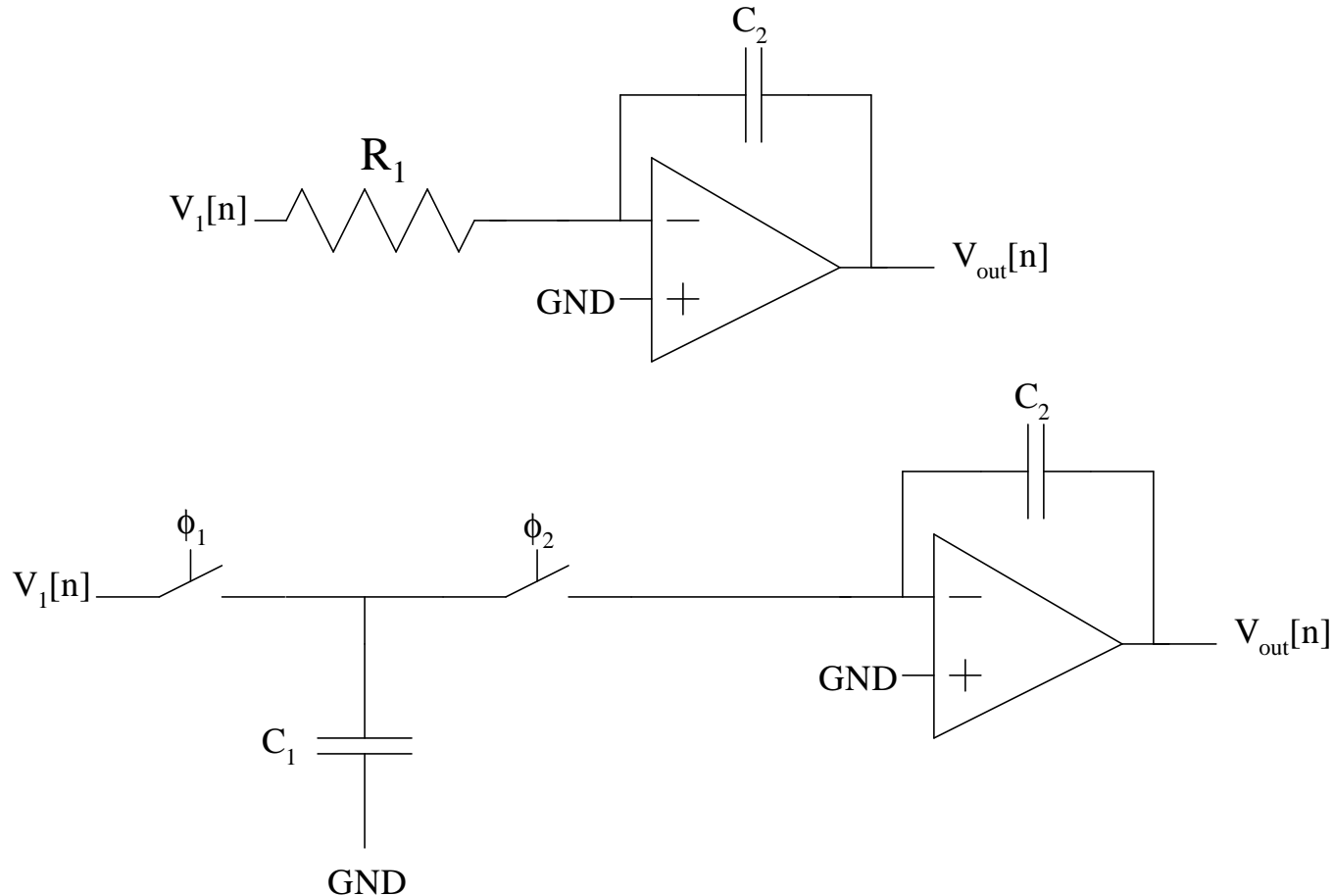

- We will step through all four phases, to get the proper result.

Basic Switch-Cap Integrator


(4), [n-1] cycle

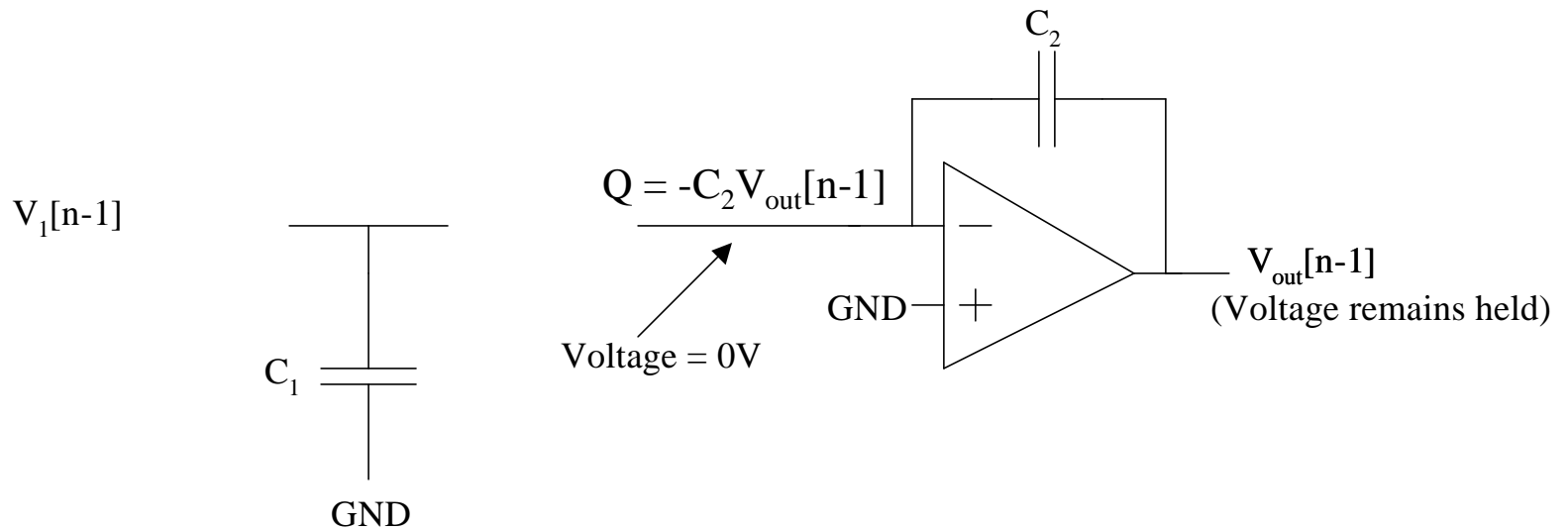

- This case is important to understand our starting point
charge is stored on a capacitor ; therefore we need to know the initial state

Basic Switch-Cap Integrator


(1), [n] cycle: ϕ_1

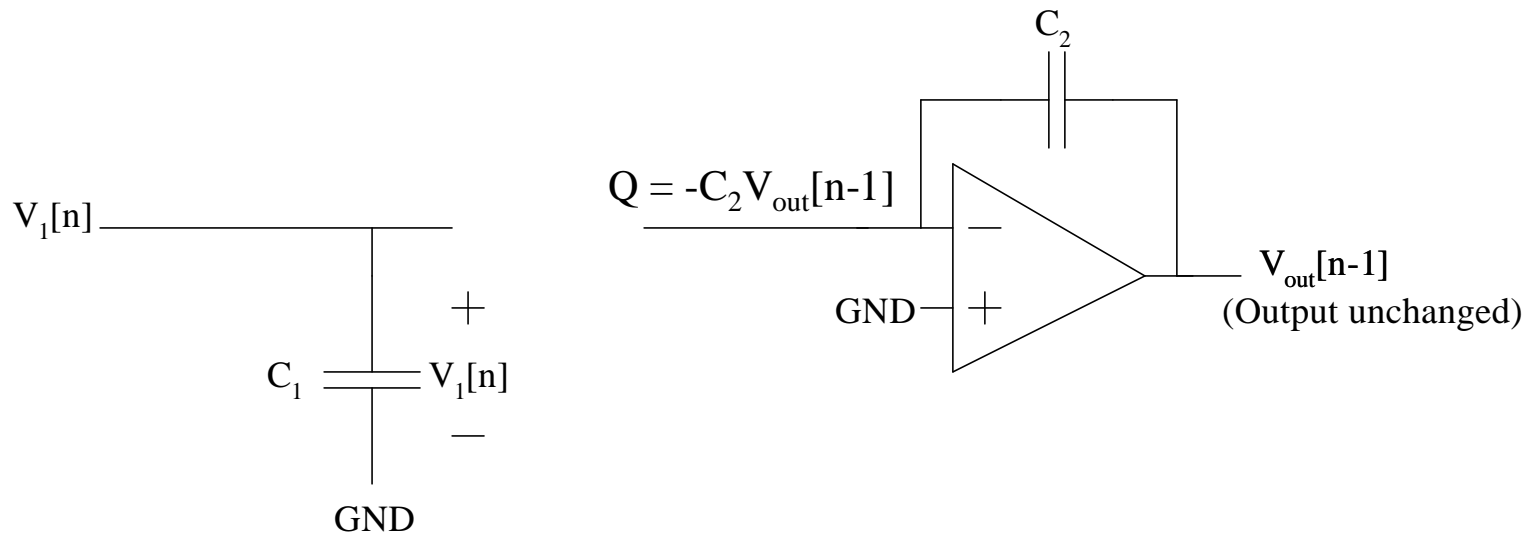

- Charge up the capacitor with voltage $V_1[n]$

Basic Switch-Cap Integrator


(2), [n] cycle

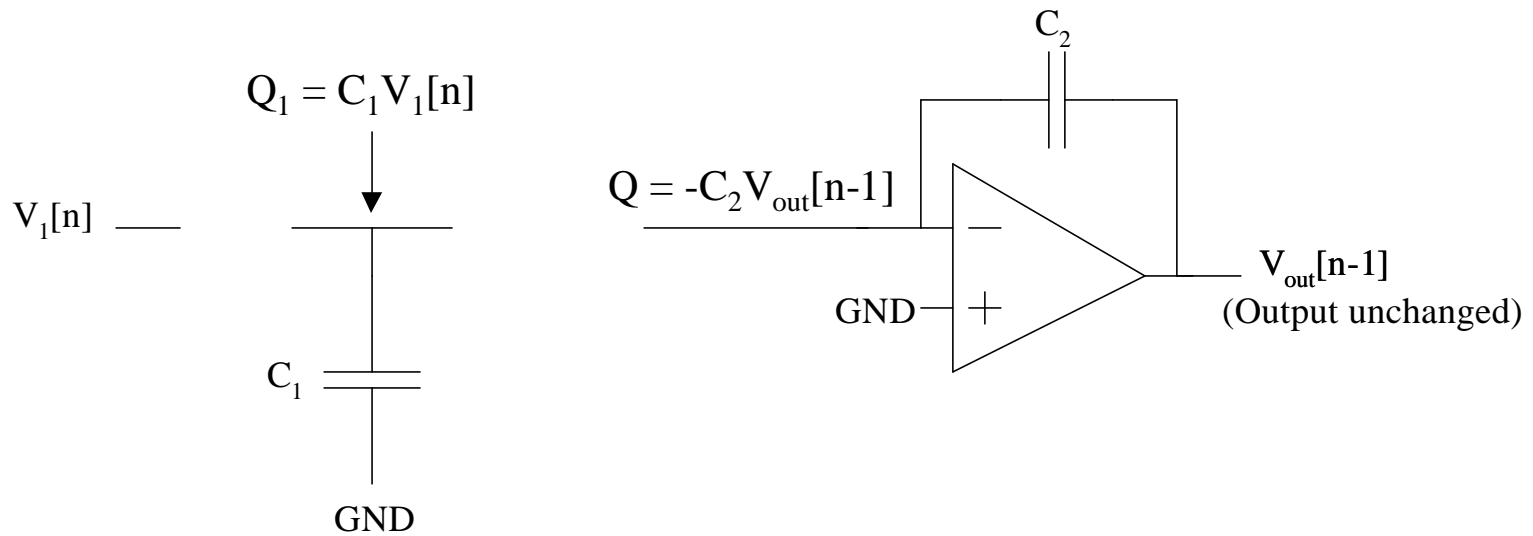

- We remove the capacitor from the input voltage.
- The voltage is stored across the capacitor

Basic Switch-Cap Integrator


(3), [n] cycle: ϕ_2

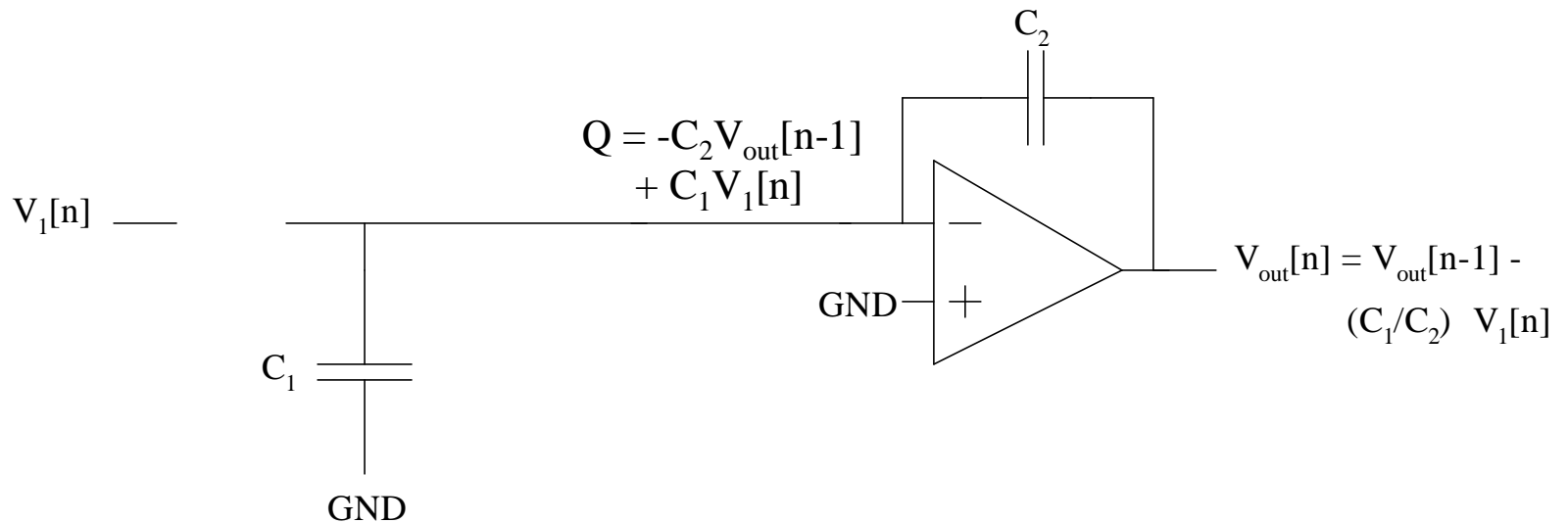

- We connect the capacitor to the charge summing node
- The charge initially stored on the capacitor as well as the resulting charge from the second input ($V_2[n]$) contributes to the total charge

Basic Switch-Cap Integrator


(4), [n] cycle

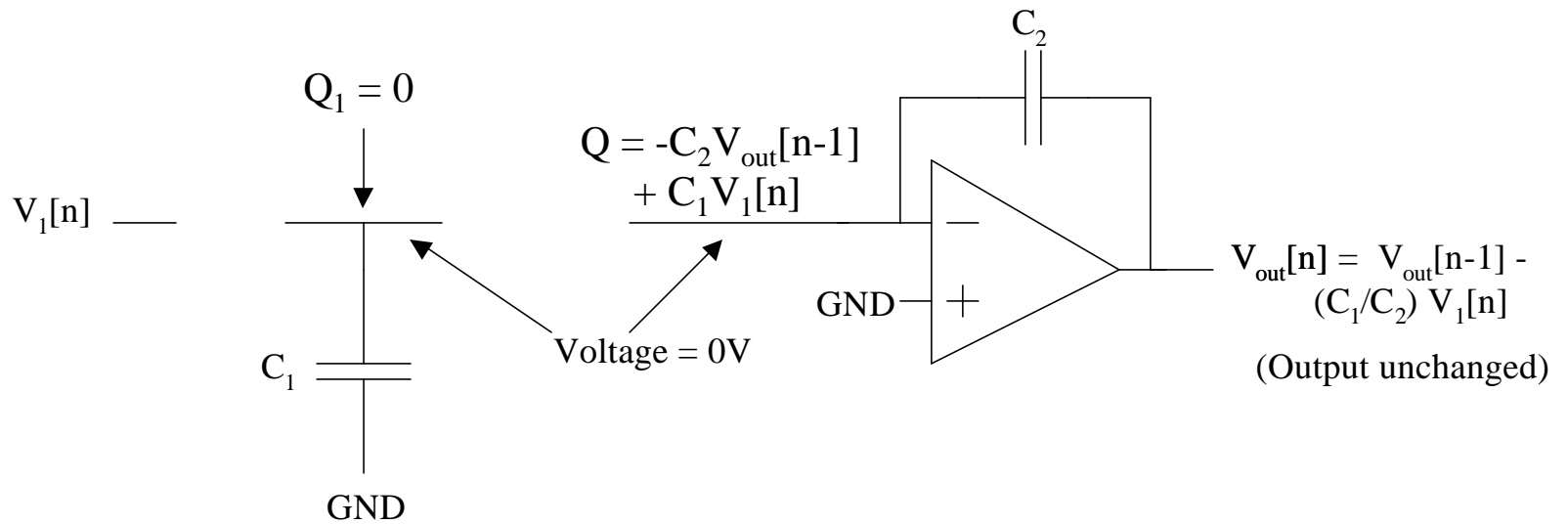

- We disconnect the capacitor from the charge summing node, and return to our initial case

$$V_{out}[n] = V_{out}[n-1] - (C_1/C_2) V_1[n]$$


Basic Switch-Cap Integrator

 

$$V_{\text{out}}[n] = V_{\text{out}}[n-1] - (C_1/C_2) V_1[n]$$

$$\frac{V_{\text{out}}(z)}{V_1(z)} = H(z) = - (C_1/C_2) \frac{1}{1 - z^{-1}}$$

Basic Switch-Cap Integrator

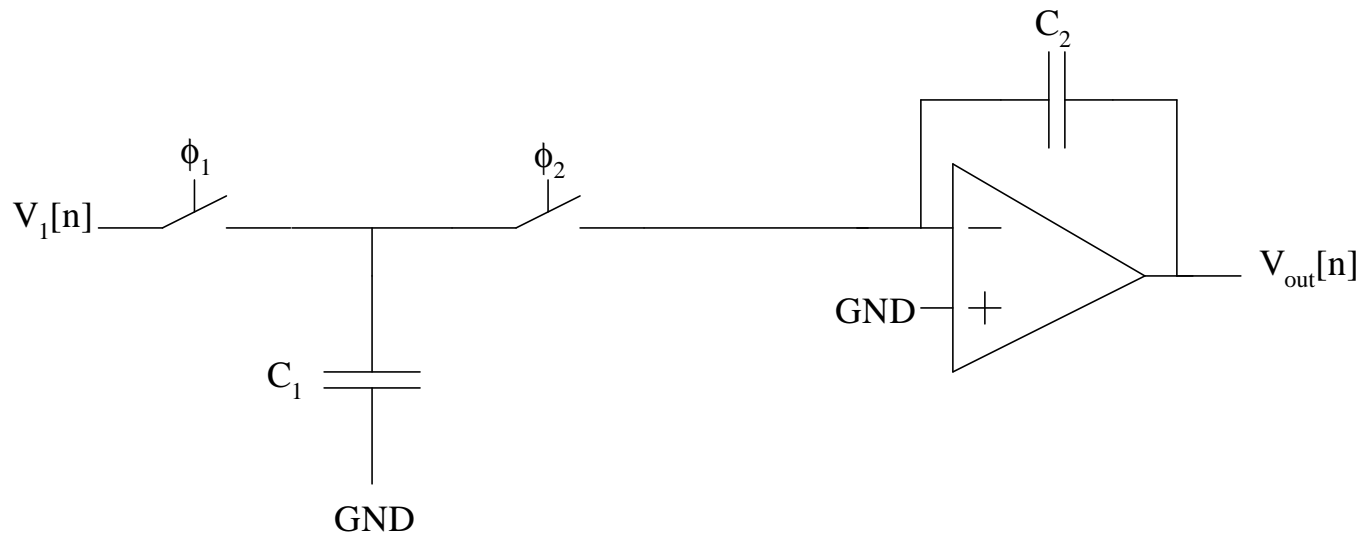

$$V_{\text{out}}[n] = V_{\text{out}}[n-1] - (C_1/C_2) V_1[n]$$

$$\frac{V_{\text{out}}(z)}{V_1(z)} = H(z) = - (C_1/C_2) \frac{1}{1 - z^{-1}}$$

$$H(j\omega) = - (C_1/C_2) \frac{1}{1 - e^{-j\omega T}}$$

$$\sim - (C_1/C_2) / j\omega T$$

assumes $\omega T \ll 1$; therefore
we need to sample much higher
(factor of 10 to 20)
over frequencies of interest.