
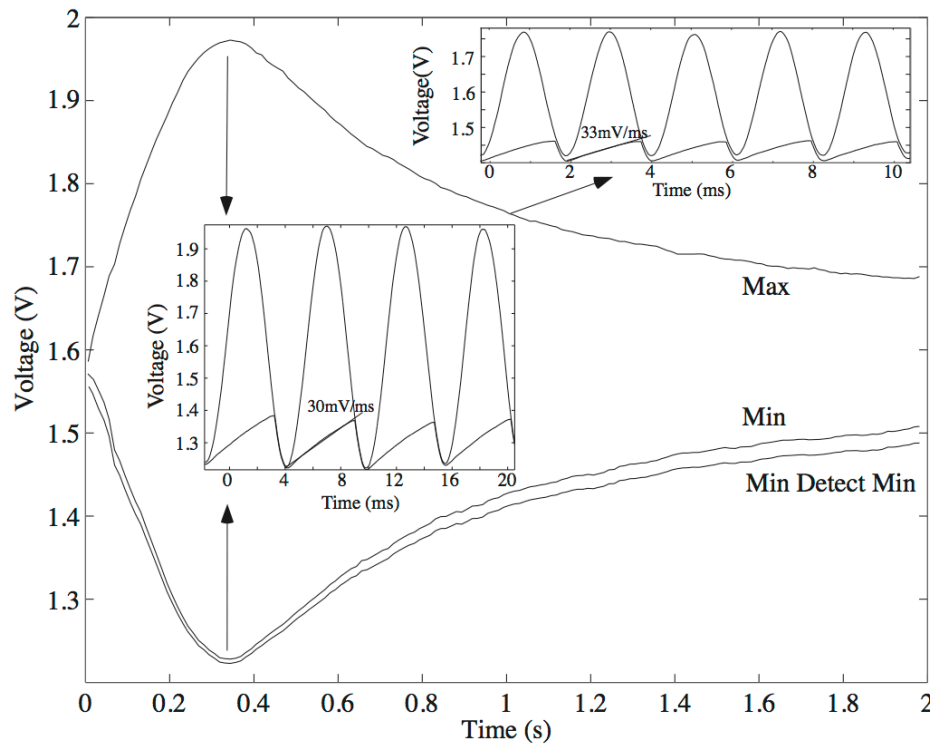


C⁴ Bandpass Filter Structure

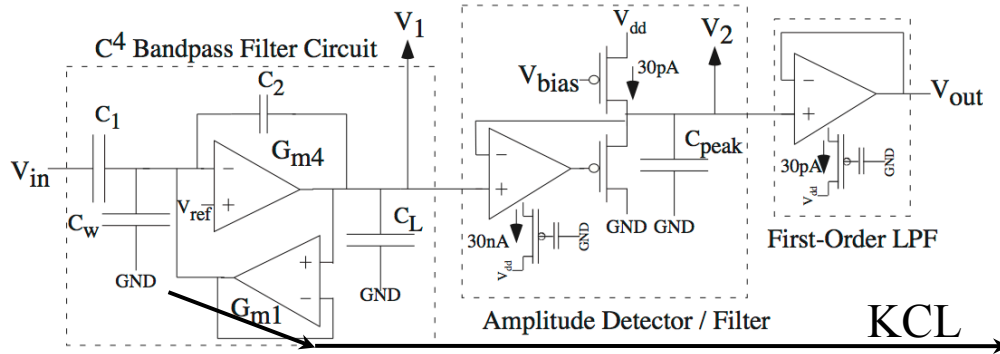

Building a sim model (macromodel)


$$\frac{d\mathbf{V}}{dt} = \mathbf{f}(\mathbf{V}, \mathbf{V}_{in})$$

$$\begin{aligned} (C_1 + C_2 + C_w) \frac{dV_1}{dt} = & C_1 \frac{dV_{in}}{dt} + C_2 \frac{dV_{out}}{dt} \\ & + I_{bias2} \tanh\left(\frac{V_{out} - V_1}{V_L}\right) \\ (C_L + C_2) \frac{dV_{out}}{dt} = & C_2 \frac{dV_1}{dt} + \\ & I_{bias1} \tanh\left(-\frac{\kappa V_1}{2U_T}\right) \end{aligned}$$

Convert
Form

$$\begin{aligned} C_{eq} \frac{dV_1}{dt} = & \frac{C_L + C_2}{C_2} I_2 + I_1 \\ C_{eq} \frac{dV_{out}}{dt} = & I_2 + \frac{C_1 + C_2 + C_w}{C_2} I_1 \\ I_2 = & I_{bias2} \tanh\left(\frac{V_{out} - V_1 + (\beta - \alpha)V_{in}}{V_L}\right) \\ I_1 = & I_{bias1} \tanh\left(-\frac{\kappa(V_2 + \alpha V_{in})}{2U_T}\right) \end{aligned}$$

Output Voltage (V)

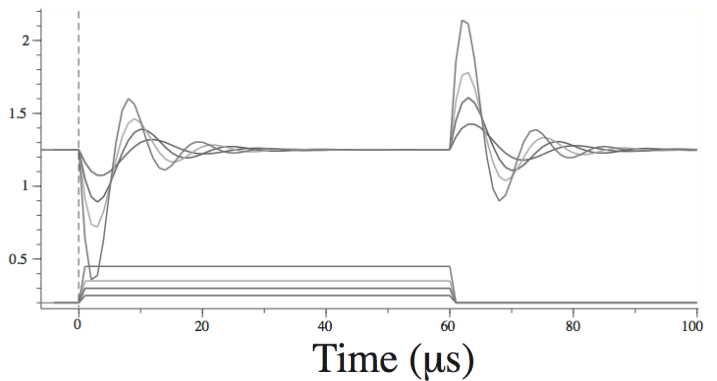


Abstraction in BandPass Filter

One simple analog block, one simple description, many components

BPF →
Two FG OTAs +
One tunable C


FG OTA →
Normal OTA +
FG I_{bias}

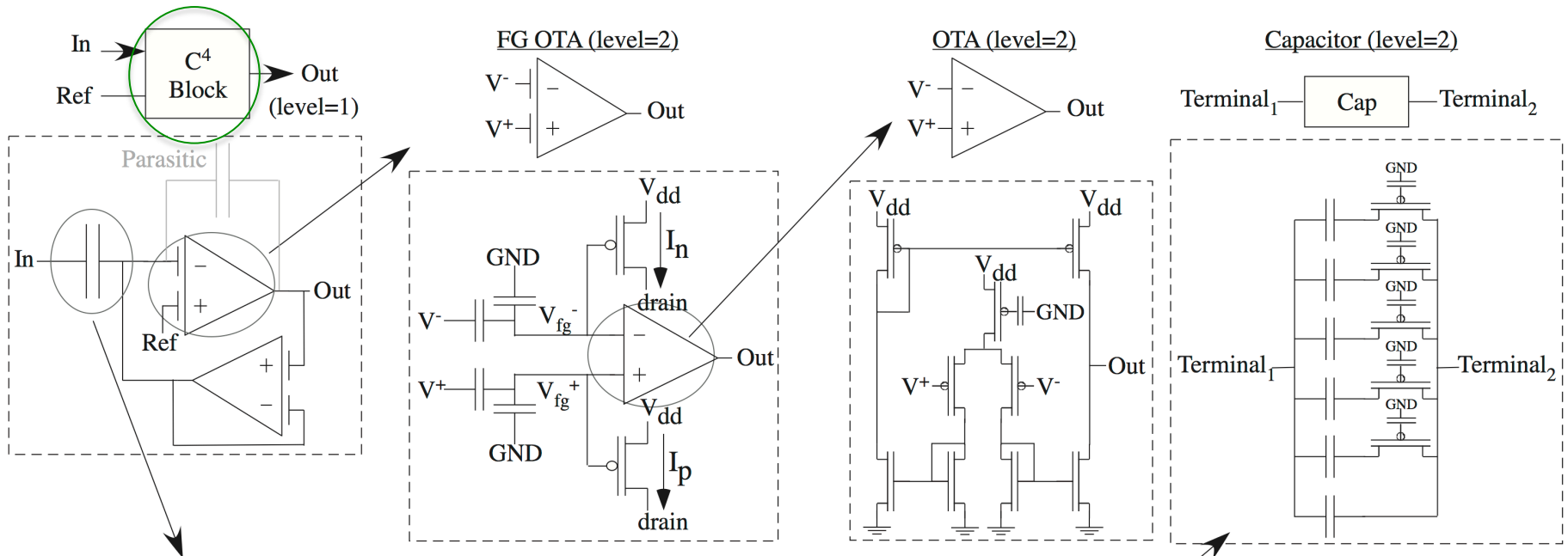

C⁴ Measurement

Compiles to:

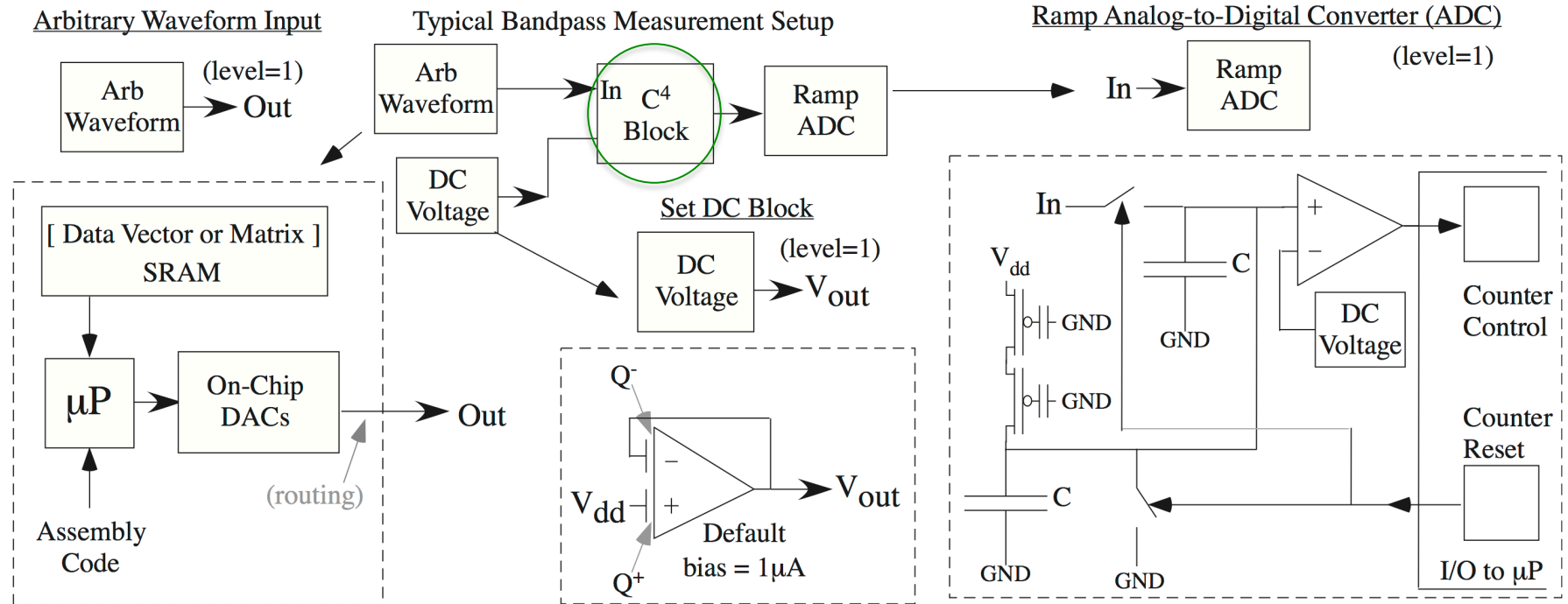- routing
- analog blocks
- signal DACs
- digital Blocks
- μ P code



Experiment Session

Experimental measurements of
C4 Second-Order Section Block,
a core signal processing function.
and various testing modes.

Example set up for step responses.
Perform the first step response.
Remembering the original values,
try different values for corner freq.
Look at different input signals.

