

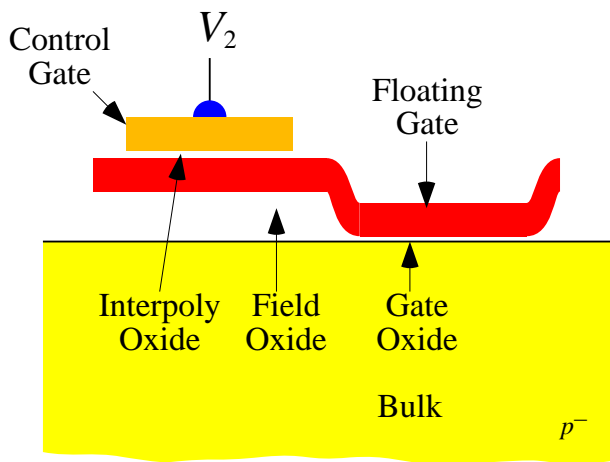
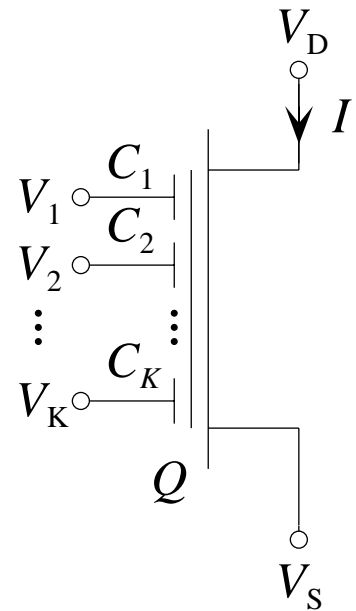

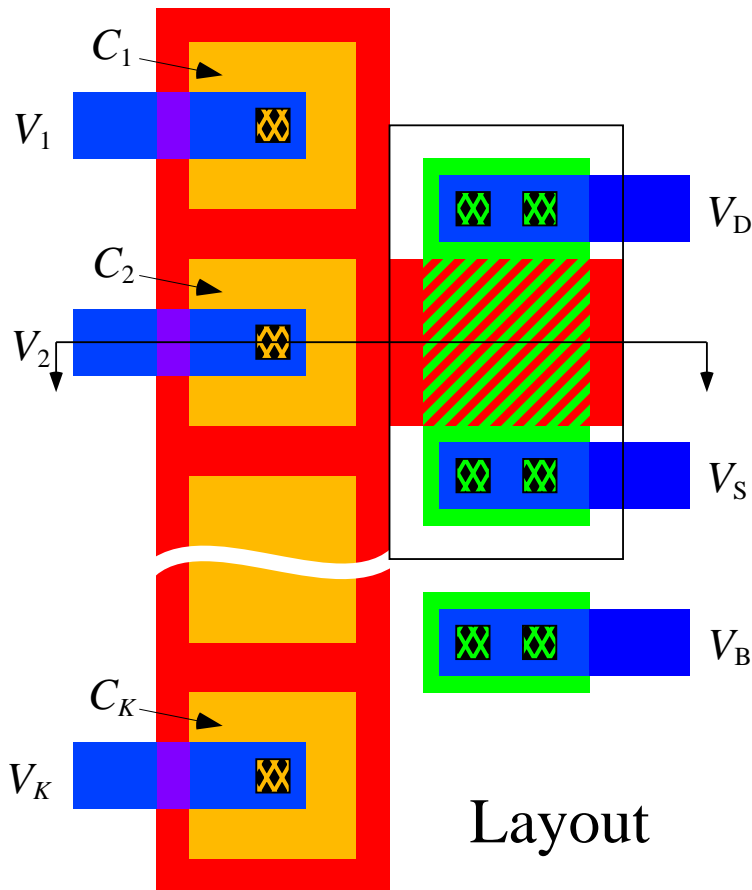
# The $K$ -Input Floating-Gate MOS (FGMOS) Transistor


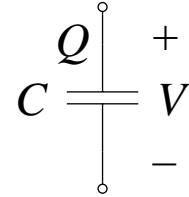
# Capacitive Voltage Dividers

- ▶ When trying to solve capacitor networks, think  $Q = CV$  not  $I = C \frac{dV}{dt}$ !




- ▶ Assume no net charge on the middle node.

- ▶ By conservation of charge,

$$-Q_1 - Q_2 = 0$$

$$\Rightarrow -C_1(V_1 - V) - C_2(V_2 - V) = 0$$
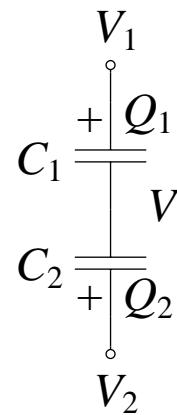
$$\Rightarrow V = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2$$



# Capacitive Voltage Dividers


- ▶ For all  $k$ ,  $Q_k = C_k(V_k - V)$
- ▶ Net charge  $Q$  on the common node.
- ▶ By conservation of charge,

$$-\sum_{k=1}^K Q_k = Q$$

$$\Rightarrow -\sum_{k=1}^K C_k(V_k - V) = Q$$

$$\Rightarrow V \sum_{k=1}^K C_k = \sum_{k=1}^K C_k V_k + Q$$

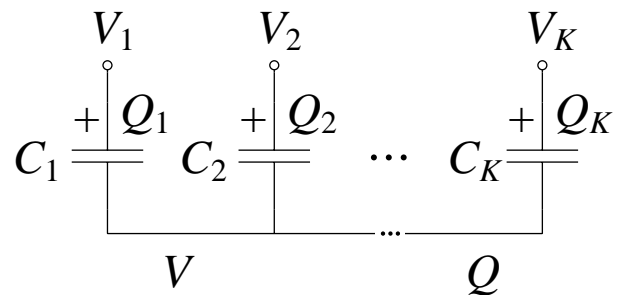
$$\Rightarrow V = \sum_{k=1}^K \frac{C_k}{C_T} V_k + \frac{Q}{C_T}$$



where

$$C_T \equiv \sum_{k=1}^K C_k$$
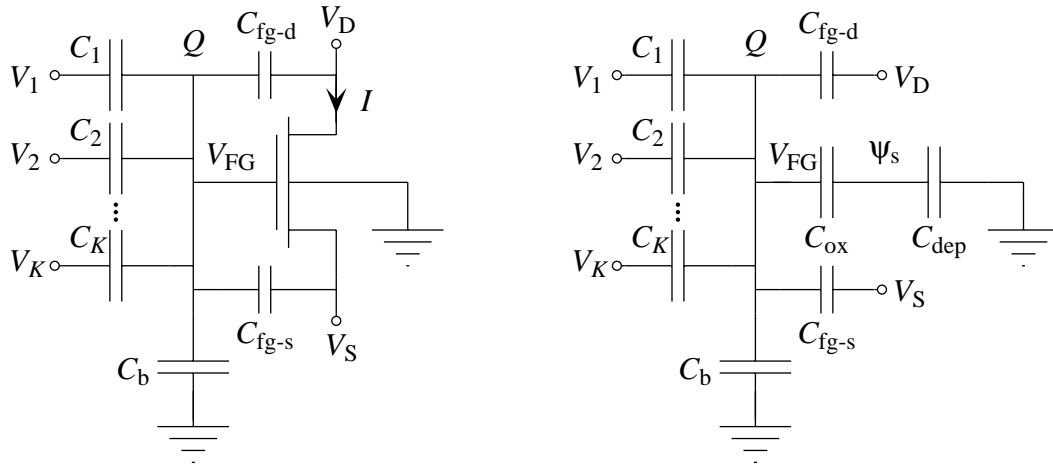
# Capacitive-Divider Model of the Subthreshold FGMOSFET





$$V_{FG} = \sum_{k=1}^K \frac{C_k}{C_T} V_k + \frac{C_{fg-s}}{C_T} V_S + \frac{C_{fg-d}}{C_T} V_D + \frac{Q}{C_T}$$



$$I = I_0 e^{\kappa \frac{V_{FG}}{U_T}} \left( e^{-\frac{V_S}{U_T}} - e^{-\frac{V_D}{U_T}} \right)$$

$$I = I_0 e^{\frac{\kappa Q}{C_T U_T}} e^{\kappa \sum_{k=1}^K \frac{C_k}{C_T} \frac{V_k}{U_T}} e^{\kappa \frac{C_{fg-s}}{C_T} \frac{V_S}{U_T}} e^{\kappa \frac{C_{fg-d}}{C_T} \frac{V_D}{U_T}} \left( e^{-\frac{V_S}{U_T}} - e^{-\frac{V_D}{U_T}} \right)$$

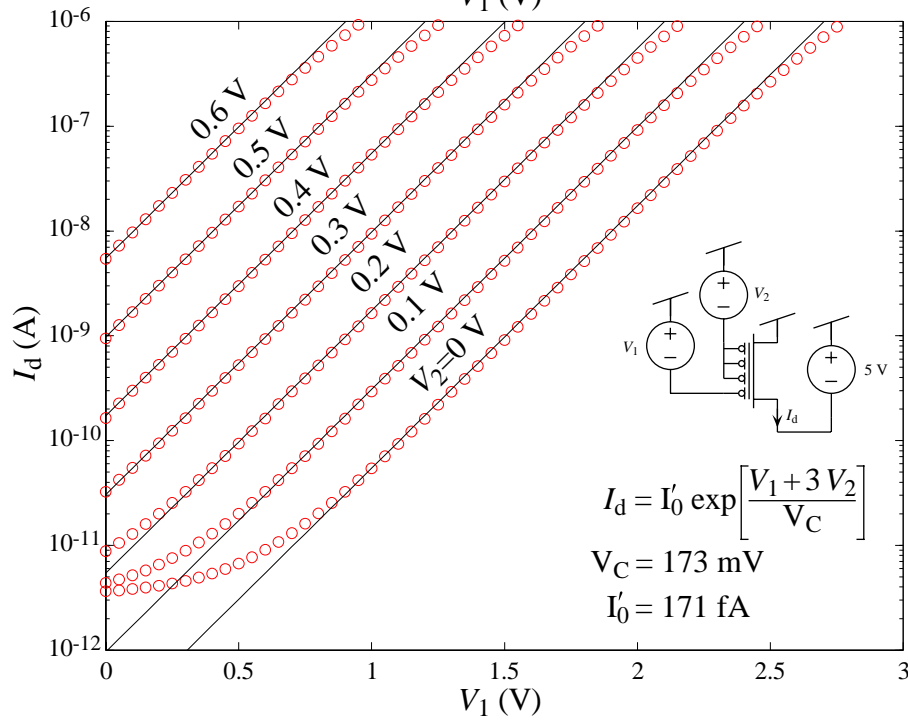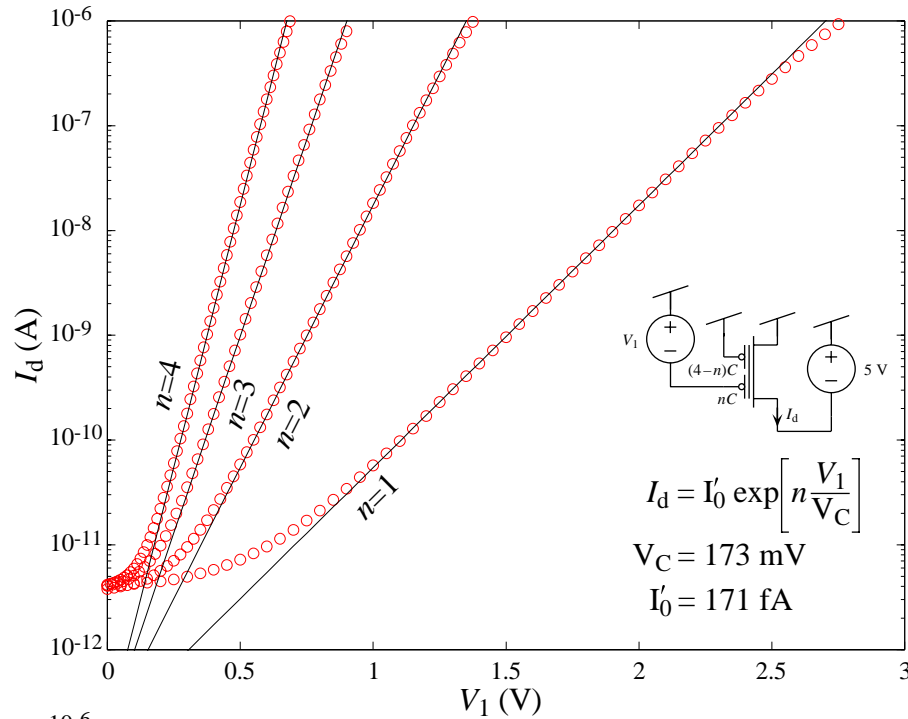
# Subthreshold FGMOS Transistor: Transconductance


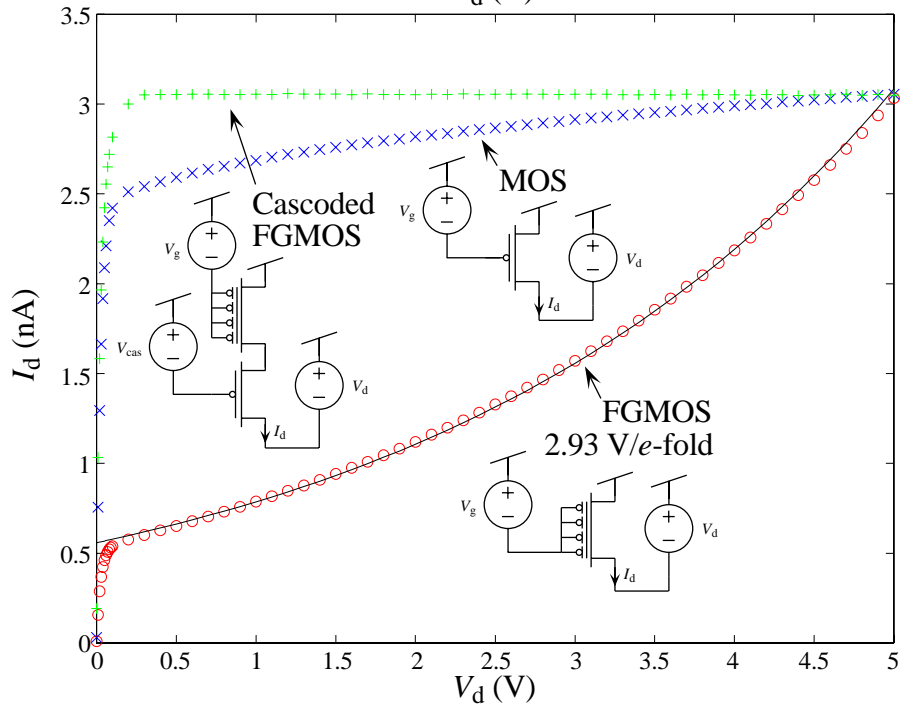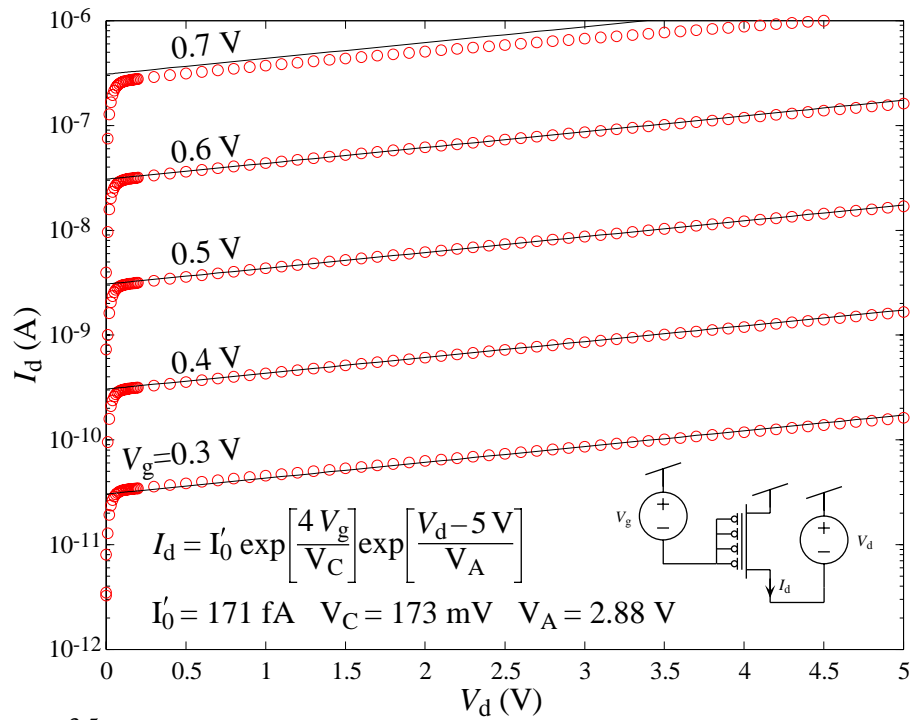
# Subthreshold FGMOS Transistor: Drain Characteristics


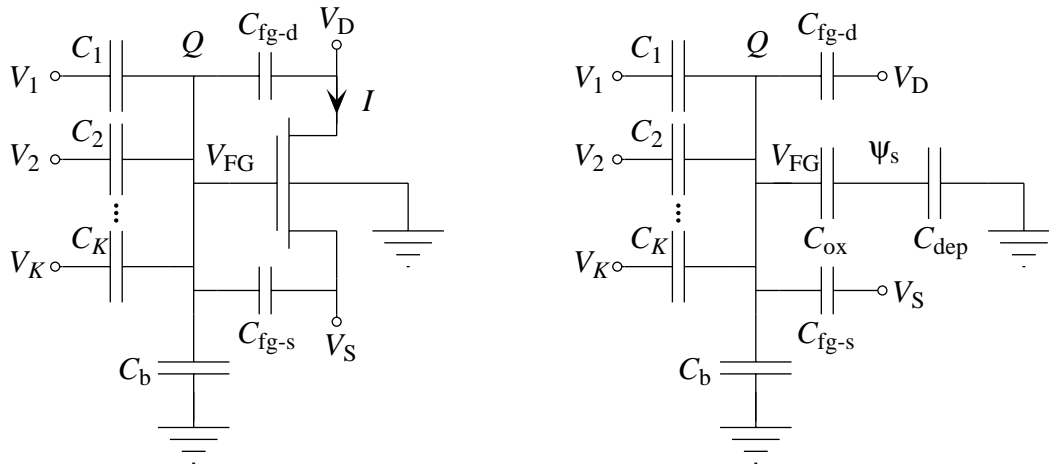
# Capacitive-Divider Model of the Above-Threshold FGMOSFET



$$V_{FG} = \sum_{k=1}^K \frac{C_k}{C_T} V_k + \frac{C_{fg-s}}{C_T} V_S + \frac{C_{fg-d}}{C_T} V_D + \frac{Q}{C_T}$$

$$I = \frac{W \mu C_{ox}}{L} \frac{1}{2\kappa} [(\kappa(V_{FG} - V_{T0}) - V_S)^2 - (\kappa(V_{FG} - V_{T0}) - V_D)^2]$$

$$I = \frac{W \mu C_{ox}}{L} \frac{1}{2\kappa} [(\kappa(\sum_{k=1}^K \frac{C_k}{C_T} V_k - V_{T0}^*) - V_S)^2 - (\kappa(\sum_{k=1}^K \frac{C_k}{C_T} V_k - V_{T0}^*) - V_D)^2]$$

$$V_{T0}^* = V_{T0} - \frac{C_{fg-s}}{C_T} V_S - \frac{C_{fg-d}}{C_T} V_D - \frac{Q}{C_T}$$

# Above-Threshold FGMOSFET

