

 


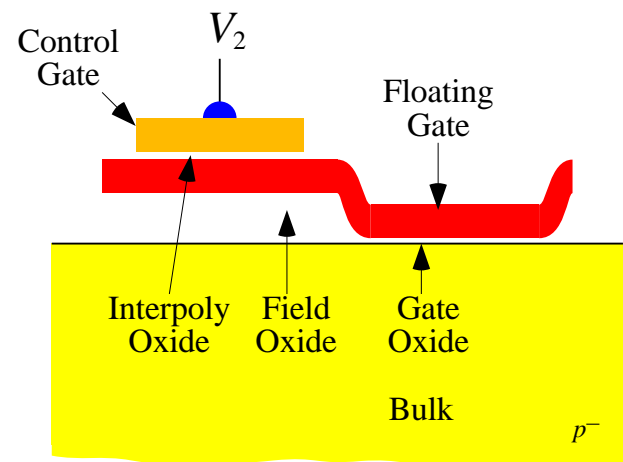The K -Input Floating-Gate MOS (FGMOS) Transistor



Circuit Symbols

 


Cross-section

Capacitive Voltage Dividers

- ▶ When trying to solve capacitor networks, it pays to think $Q = CV$ rather than

$$\cancel{I = C \frac{dV}{dt}}$$

 


- ▶ Assume no net charge on the middle node.
- ▶ By conservation of charge,

$$-Q_1 - Q_2 = 0$$

$$\Rightarrow -C_1(V_1 - V) - C_2(V_2 - V) = 0$$
 
$$\Rightarrow V = \frac{C_1}{C_1 + C_2} V_1 + \frac{C_2}{C_1 + C_2} V_2$$



Capacitive Voltage Dividers

- ▶ For all k , $Q_k = C_k(V_k - V)$
- ▶ Net charge Q on the common node.
- ▶ By conservation of charge,

$$-\sum_{k=1}^K Q_k = Q$$


$$\Rightarrow -\sum_{k=1}^K C_k(V_k - V) = Q$$

$$\Rightarrow V \sum_{k=1}^K C_k = Q + \sum_{k=1}^K C_k V_k$$


$$\Rightarrow V = \frac{Q}{C_T} + \sum_{k=1}^K \frac{C_k}{C_T} V_k$$

where

$$C_T \equiv \sum_{k=1}^K C_k$$

 

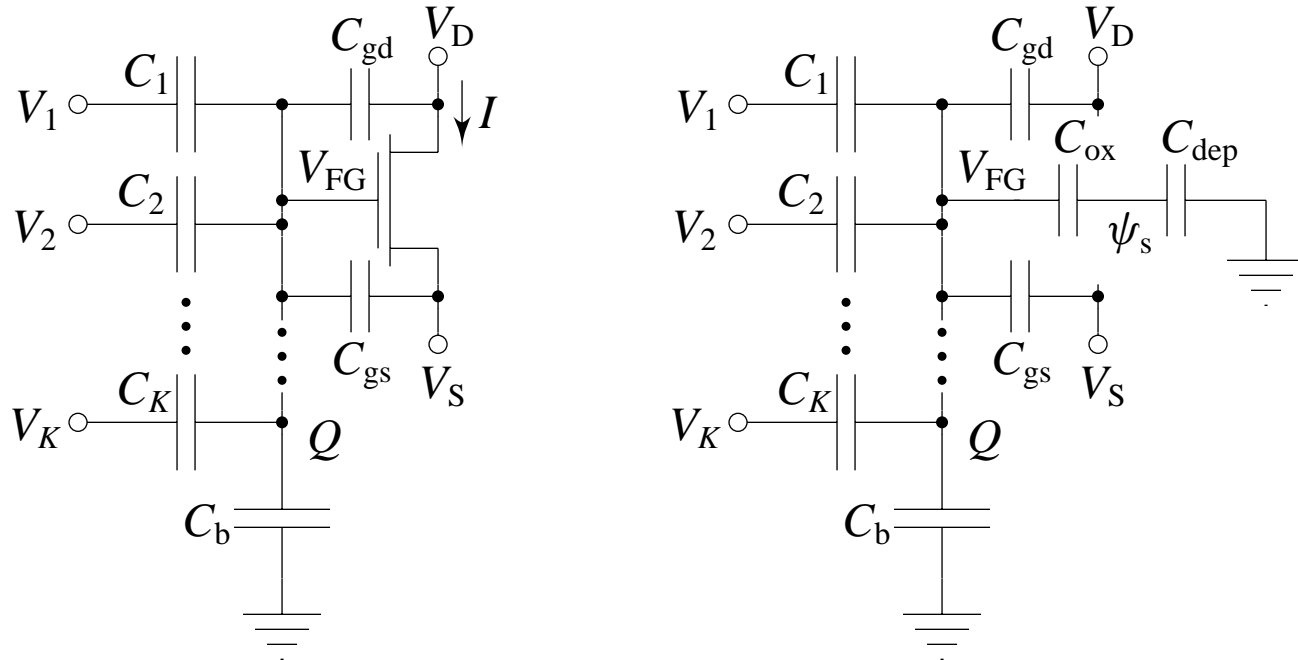Capacitive-Divider Model of the Subthreshold FGMOS Transistor




$$V_{\text{FG}} = \frac{Q}{C_{\text{T}}} + \frac{C_{\text{gs}}}{C_{\text{T}}} V_{\text{S}} + \frac{C_{\text{gd}}}{C_{\text{T}}} V_{\text{D}} + \sum_{k=1}^K \frac{C_k}{C_{\text{T}}} V_k$$

$$C_{\text{T}} = (C_{\text{ox}} \parallel C_{\text{dep}}) + C_{\text{b}} + C_{\text{gs}} + C_{\text{gd}} + \sum_{k=1}^K C_k$$


$$I = I_0 e^{\kappa V_{\text{FG}}/U_{\text{T}}} \left(e^{-V_{\text{S}}/U_{\text{T}}} - e^{-V_{\text{D}}/U_{\text{T}}} \right)$$

$$I = I_0 e^{\kappa Q/C_{\text{T}}U_{\text{T}}} e^{\kappa(C_1V_1+\dots+C_KV_K)/C_{\text{T}}U_{\text{T}}} e^{\kappa C_{\text{gd}}V_{\text{D}}/C_{\text{T}}U_{\text{T}}} e^{\kappa C_{\text{gs}}V_{\text{S}}/C_{\text{T}}U_{\text{T}}} \left(e^{-V_{\text{S}}/U_{\text{T}}} - e^{-V_{\text{D}}/U_{\text{T}}} \right)$$


Subthreshold FGMOS Transistor

 


Subthreshold FGMOS Transistor

 

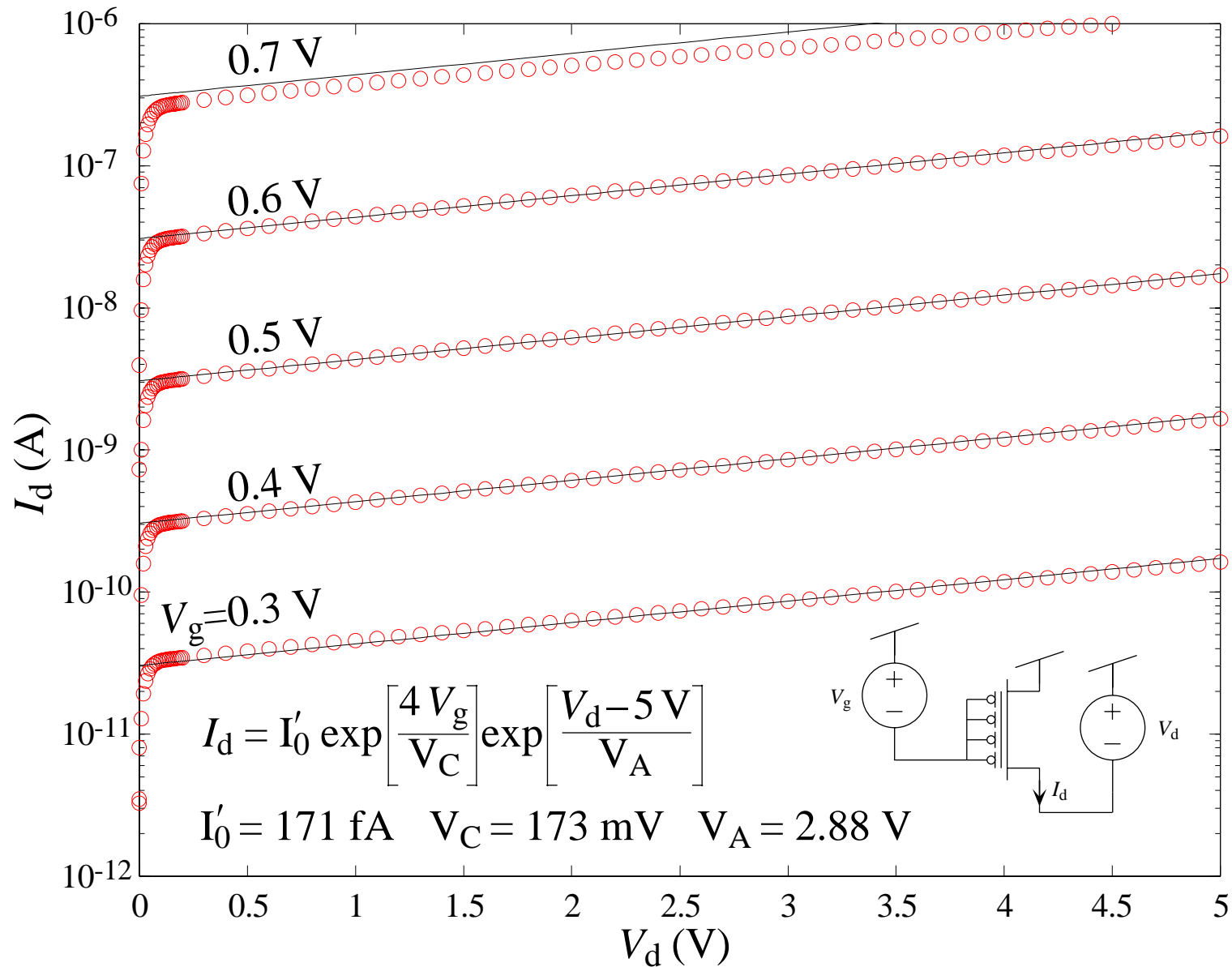
Subthreshold FGMOS Transistor: Drain Characteristics



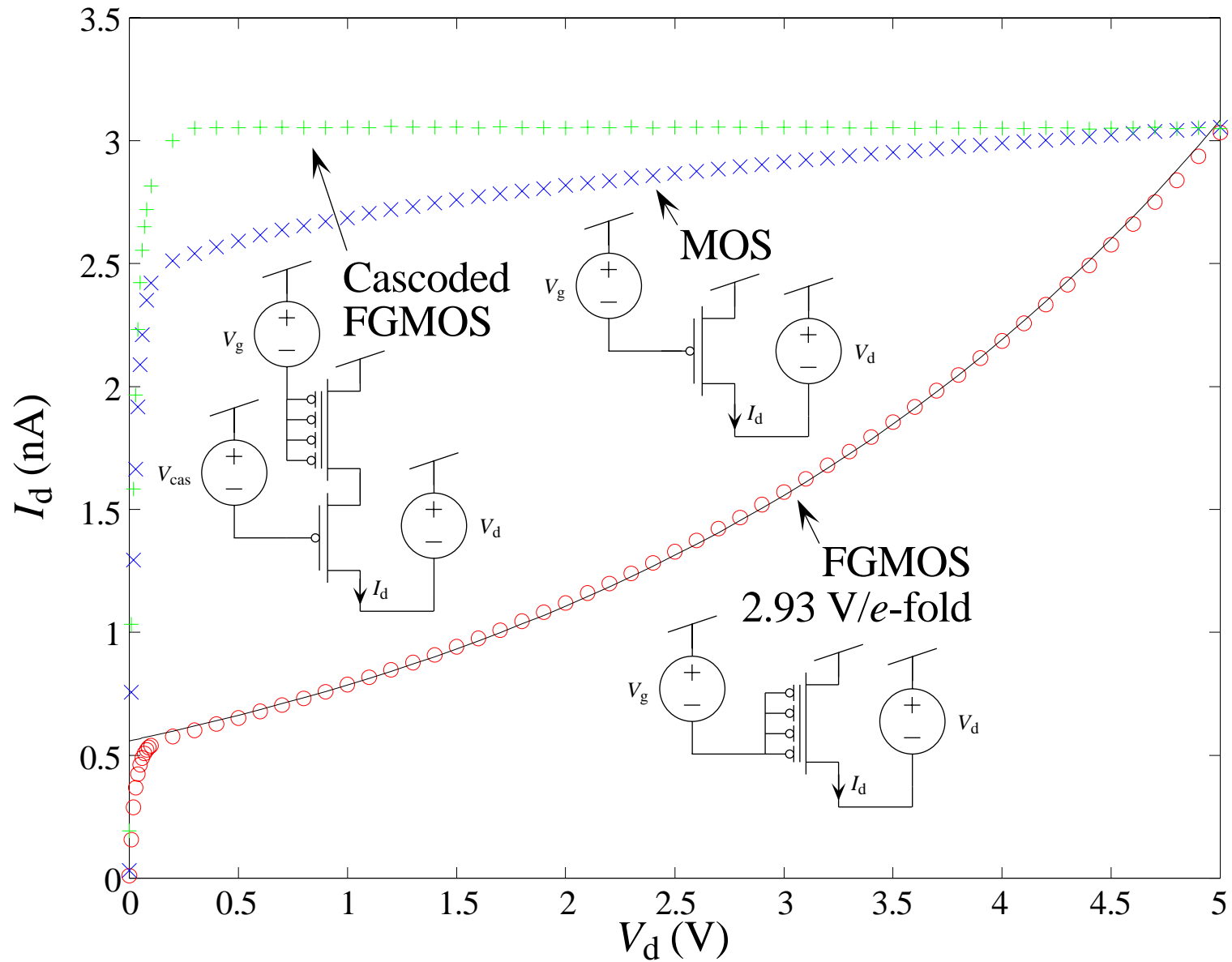Subthreshold FGMOS Transistor: Drain Characteristics



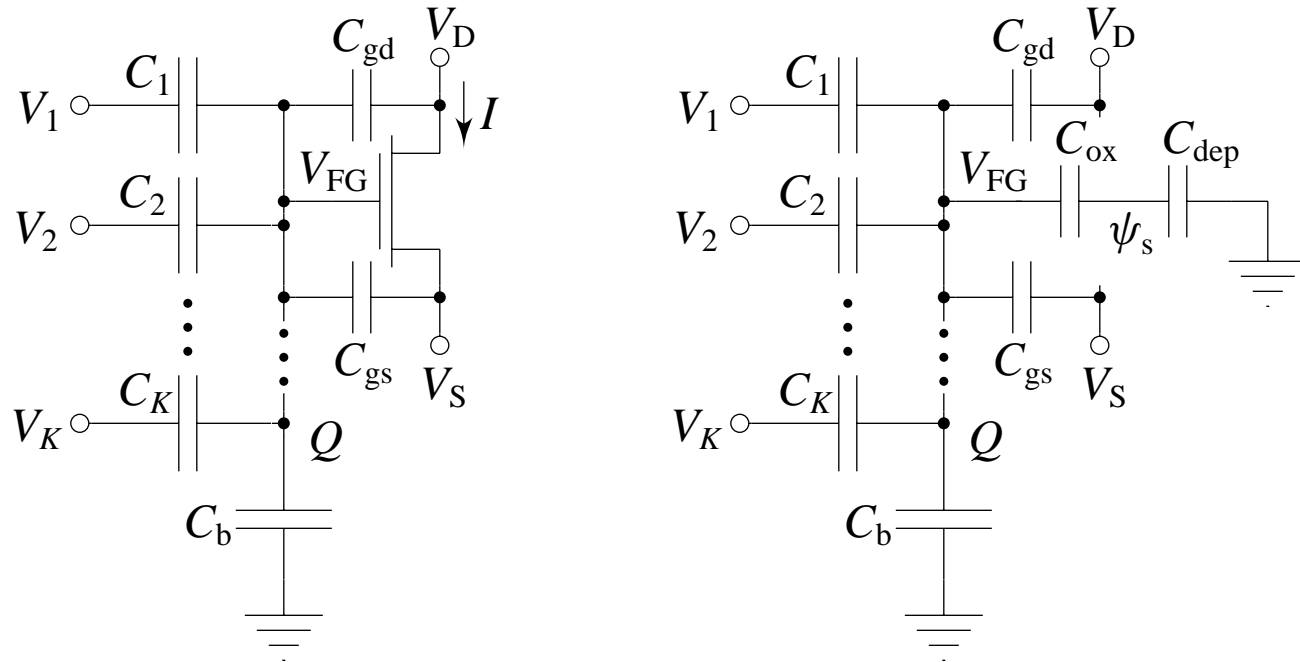Capacitive-Divider Model of the Above-Threshold FGMOS Transistor




$$I = \frac{W}{L} \frac{\mu C_{\text{ox}}}{2\kappa} \left(\left(\kappa(V_{\text{FG}} - V_{\text{T0}}) - V_{\text{S}} \right)^2 - \left(\kappa(V_{\text{FG}} - V_{\text{T0}}) - V_{\text{D}} \right)^2 \right)$$


$$I = \frac{W}{L} \frac{\mu C_{\text{ox}}}{2\kappa} \left(\left(\kappa \left(\sum_{k=1}^K \frac{C_k}{C_{\text{T}}} V_k - V_{\text{T0}}^* \right) - V_{\text{S}} \right)^2 - \left(\kappa \left(\sum_{k=1}^K \frac{C_k}{C_{\text{T}}} V_k - V_{\text{T0}}^* \right) - V_{\text{D}} \right)^2 \right)$$

$$V_{\text{T0}}^* = V_{\text{T0}} - \frac{Q}{C_{\text{T}}} - \frac{C_{\text{gs}}}{C_{\text{T}}} V_{\text{S}} - \frac{C_{\text{gd}}}{C_{\text{T}}} V_{\text{D}}$$


Above-Threshold FGMOS Transistor

 

Above-Threshold FGMOS Transistor

 


How to Make Leaky Floating Gates...

 


- ▶ Keep your floating gates on poly1.
- ▶ If you make a contact to metal, your gate will probably leak, because the oxide surrounding the metal layers are typically deposited rather than thermally grown.

 Beware of Capacitive Coupling from Below...




- ▶ If possible, don't allow a floating gate to cross a well boundary. For a *p*FGMOS, keep it entirely over the well. For an *n*FGMOS, keep it entirely over the substrate.
- ▶ If you split the area evenly between the substrate and the well, your floating-gate voltage will have a dependence on V_{DD} that you didn't expect...

 Beware of Capacitive Coupling from Above...




- ▶ Be careful about routing metal lines over top of your floating gates. The voltages on such lines couple into the floating gate just like the control-gate voltages.
- ▶ Moreover, if you are trying to carefully match C_T for two FGMOS transistors, then you have to count the stray capacitance between these lines and the floating-gate too...

 Which FGMOS Transistor Has
a Higher Output Resistance?




 Which FGMOS Transistor Has a Higher Output Resistance?




- ▶ The transistor on the *left*...
- ▶ For a FGMOS transistor, the Early effect (i.e., channel-length modulation) is always negligible compared to the effect of V_D coupling through C_{gd} to the floating gate. Increasing L does *not* increase r_o .
- ▶ $C_{gd} \propto W$, so making the transistor wider *decreases* r_o .

Matching: Same Size & Shape

 


- ▶ To obtain matched capacitive-divider ratios in different FGMOS transistors, use floating gates with identical geometries.
- ▶ Don't forget that C_T includes parasitics that you won't be able to predict properly at design time.

 Matching: Parallel Unit-Sized Control Gates




- ▶ To obtain accurate control-gate capacitor ratios (e.g., 2:1), connect unit-sized control gates in parallel rather than making composite control gates with the correct area ratios.
- ▶ If you are trying to carefully match C_T , don't connect the unit-sized control gates on top of the floating gate.

Matching: Same Surround

 


- ▶ To improve control-gate matching, use “dummy” control gates at each end to make each “real” control gate have an identical surround.
- ▶ Systematic edge effects are ubiquitous, but the underlying mechanisms are not always clear (e.g., fringing fields, non-uniform etching rates).

 
Relative Capacitance vs Position (1.2- μm Process)



 Relative Capacitance vs Position (.35- μm Process)



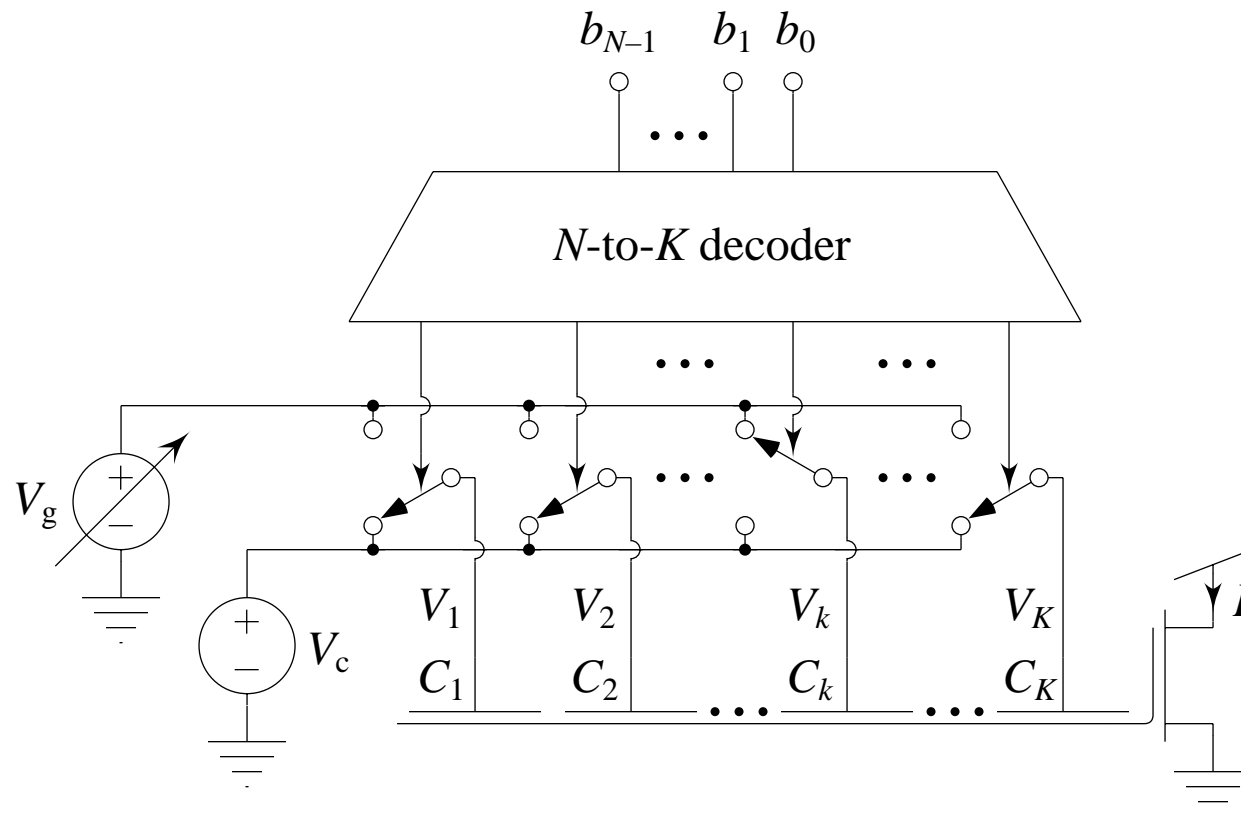Experimental Method for Measuring Capacitor Matching



► In subthreshold,

$$I \propto e^{\kappa C_i V_i / C_T U_T} \Rightarrow \frac{\partial \log I}{\partial V_i} = \frac{\kappa C_i}{C_T U_T} \propto C_i$$

⇒ Mismatch in the slope of $\log I$ vs V_i directly reflects mismatch in C_i .