

ECE 2040 Midterm Exam 1
Fall 2020

General Instructions instructions:


- Exam is closed book / closed notes other than the one-page of handwritten notes.
- Most questions are worth 3 points; first two questions are worth 2 points.
- Only the final answers, as indicated by the question, will be considered correct for each question.
- Choose the best possible answer available in all cases.

Honorlock instructions:


- The only notes allowed is a one-page of handwritten notes. Front and back of the sheet are allowed. Sheet should be shown to the camera.
- Restroom breaks are not encouraged, although if necessary, it is allowed when asking the proctoring system. Timing will be recorded.
- Blank scratch paper is allowed, and needs to be shown to the proctor.
- Music is allowed assuming it is at a low volume and not conveying any exam answers.



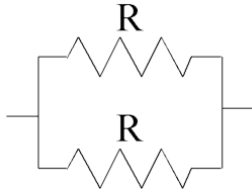
1. (2pt) For the elements above and $R = 10\text{k}\Omega$, the equivalent resistance is
- $2.5\text{k}\Omega$
 - $5\text{k}\Omega$
 - $10\text{k}\Omega$
 - $20\text{k}\Omega$
 - $40\text{k}\Omega$



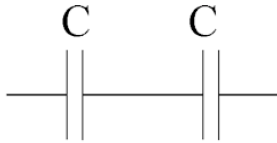2. For these elements and $R = 10\text{k}\Omega$, the equivalent resistance is
- $2.5\text{k}\Omega$
 - $5\text{k}\Omega$
 - $10\text{k}\Omega$
 - $20\text{k}\Omega$
 - $40\text{k}\Omega$



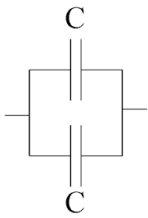
3. For the elements above and $C = 1\text{nF}$, the equivalent capacitance is
- 0.25nF
 - 0.5nF
 - 1nF
 - 2nF
 - 4nF




4. For these elements and $C = 1\text{nF}$, the equivalent capacitance is
- 0.25nF
 - 0.5nF
 - 1nF
 - 2nF
 - 4nF



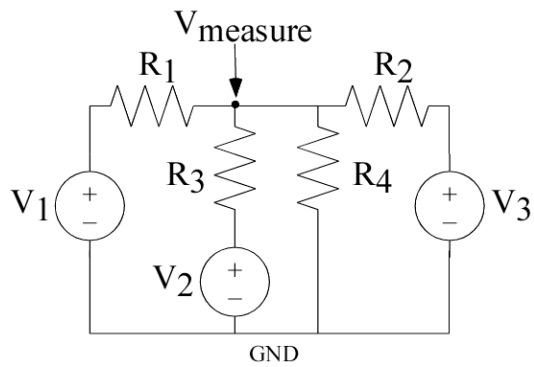5. For the elements above and $L = 1\text{mH}$, the equivalent inductance is
- 0.25mH
 - 0.5mH
 - 1mH
 - 2mH
 - 4mH



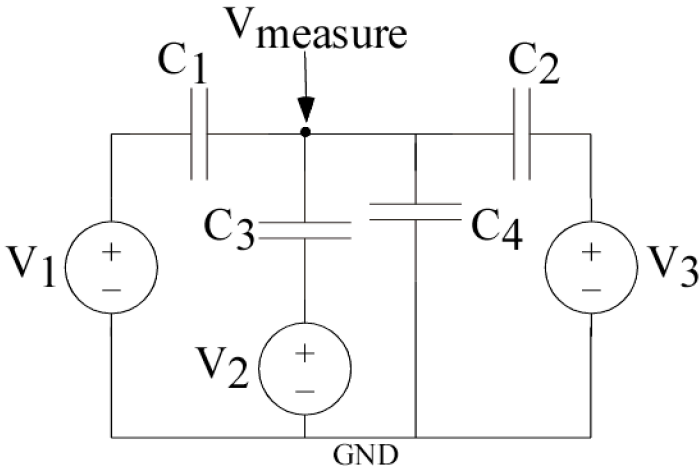6. For $R_1 = 1\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_2 = 4\text{k}\Omega$, and $R_4 = 4\text{k}\Omega$, if $V_2 = V_3 = 0\text{V}$, what is V_{measure} for $V_1 = 4\text{V}$?
- 0.125V
 - 0.25V
 - 0.5V
 - 1V
 - 2V
7. For $R_1 = 1\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_2 = 4\text{k}\Omega$, and $R_4 = 4\text{k}\Omega$, if $V_1 = V_3 = 0\text{V}$, what is V_{measure} for $V_2 = 4\text{V}$?
- 0.125V
 - 0.25V
 - 0.5V
 - 1V
 - 2V
8. For $R_1 = 1\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_2 = 4\text{k}\Omega$, and $R_4 = 4\text{k}\Omega$, if $V_1 = V_2 = 0\text{V}$, what is V_{measure} for $V_3 = 4\text{V}$?
- 0.125V
 - 0.25V
 - 0.5V
 - 1V
 - 2V
9. For $R_1 = 1\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_2 = 4\text{k}\Omega$, and $R_4 = 4\text{k}\Omega$, if $V_1 = V_2 = V_3 = 2\text{V}$, what is V_{measure} ?
- 1.0V
 - 1.25V
 - 1.5V
 - 1.75V
 - 2V
10. T/F: For $R_1 = 1\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_2 = 4\text{k}\Omega$, and $R_4 = 4\text{k}\Omega$, if $V_1 = V_2 = V_3 = 0\text{V}$, V_{measure} could be a voltage other than 0V.



11. For $C_1 = 4\text{pF}$, $C_3 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $C_4 = 1\text{pF}$, assuming $V_{\text{measure}} = 0\text{V}$ when $V_1 = V_2 = V_3 = 0\text{V}$, if $V_2 = V_3 = 0\text{V}$, what is V_{measure} for $V_1 = 4\text{V}$?

- a. 0.125V
- b. 0.25V
- c. 0.5V
- d. 1V
- e. 2V

12. For $C_1 = 4\text{pF}$, $C_3 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $C_4 = 1\text{pF}$, assuming $V_{\text{measure}} = 0\text{V}$ when $V_1 = V_2 = V_3 = 0\text{V}$, if $V_1 = V_3 = 0\text{V}$, what is V_{measure} for $V_2 = 4\text{V}$?

- a. 0.125V
- b. 0.25V
- c. 0.5V
- d. 1V
- e. 2V



13. For $C_1 = 4\text{pF}$, $C_3 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $C_4 = 1\text{pF}$, assuming $V_{\text{measure}} = 0\text{V}$ when $V_1 = V_2 = V_3 = 0\text{V}$, if $V_1 = V_2 = 0\text{V}$, what is V_{measure} for $V_3 = 4\text{V}$?

- a. 0.125V
- b. 0.25V
- c. 0.5V
- d. 1V
- e. 2V

14. For $C_1 = 4\text{pF}$, $C_3 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $C_4 = 1\text{pF}$, assuming $V_{\text{measure}} = 0.5\text{V}$ when $V_1 = V_2, V_3 = 0\text{V}$, if $V_1 = V_2 = V_3 = 2\text{V}$, what is V_{measure} ?

- a. 1.5V
- b. 1.75V
- c. 2.0V
- d. 2.25V
- e. 2.5V

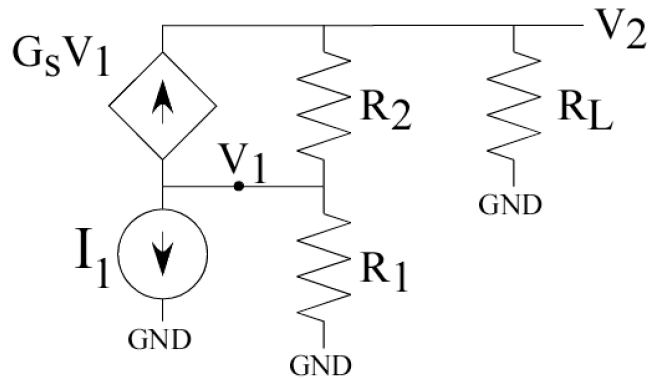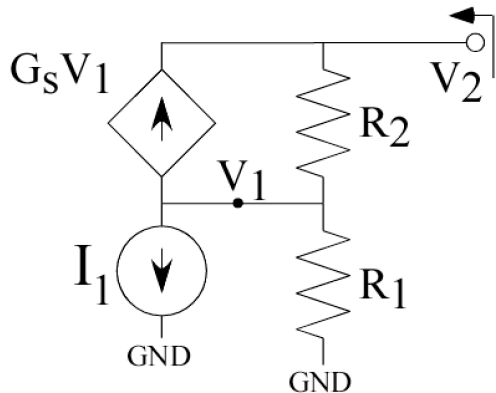15. T/F: For $C_1 = 4\text{pF}$, $C_3 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $C_4 = 1\text{pF}$, if $V_1 = V_2 = V_3 = 0\text{V}$, V_{measure} could be a voltage other than 0V.



16. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 0$, what is the equivalent Thevenin voltage source value for this one-port network?

- a. -2V
- b. -1V
- c. 0.5V
- d. 1V
- e. 2V

17. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 0$, what is the equivalent one-port resistance for this one-port network?

- a. $0.5\text{M}\Omega$
- b. $1\text{M}\Omega$
- c. $2\text{M}\Omega$
- d. $4\text{M}\Omega$
- e. $8\text{M}\Omega$

18. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 0$, what is the equivalent Norton current source value for this one-port network?

- a. $-1\mu\text{A}$
- b. $-0.5\mu\text{A}$
- c. $0\mu\text{A}$
- d. $0.5\mu\text{A}$
- e. $1\mu\text{A}$

19. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 0$ with $R_L = 40\text{k}\Omega$, what is the measured output voltage at V_2 ?

- a. -10mV
- b. -20mV
- c. -40mV
- d. -100mV
- e. -200mV

20. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 1/1\text{k}\Omega$, what is the equivalent Norton current source value for this one-port network?

- a. $-1\mu\text{A}$
- b. $-0.5\mu\text{A}$
- c. $0\mu\text{A}$
- d. $0.5\mu\text{A}$
- e. $1\mu\text{A}$

21. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 1/1\text{k}\Omega$, what is the equivalent one-port resistance for this one-port network?


- a. $1\text{M}\Omega$
- b. $2\text{M}\Omega$
- c. $10\text{M}\Omega$
- d. $100\text{M}\Omega$
- e. $1\text{G}\Omega$

22. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 1/1\text{k}\Omega$, what is the equivalent Thevenin voltage source value for this one-port network?

- a. -1000V
- b. -100V
- c. -10V
- d. -1V
- e. 0V

23. When $I_1 = 1\mu\text{A}$, $R_1 = 1\text{M}\Omega$, and $R_2 = 1\text{M}\Omega$, and for $G_s = 1/1\text{k}\Omega$ with $R_L = 40\text{k}\Omega$, what is the measured output voltage at V_2 ?

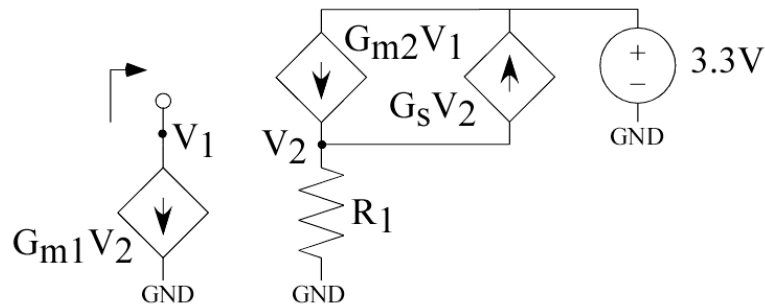- a. -10mV
- b. -20mV
- c. -40mV
- d. -100mV
- e. -200mV



24. For $G_s = 1/1\text{k}\Omega$, $G_{m1} = 1/200\text{k}\Omega$, $G_{m2} = 1/2\text{k}\Omega$, and $R_1 = 1\text{M}\Omega$, what is the equivalent resistance for the one-port network at V_1 ?


- a. $400\text{k}\Omega$
- b. $100\text{k}\Omega$
- c. $4\text{M}\Omega$
- d. $10\text{k}\Omega$
- e. $40\text{k}\Omega$

25. For $G_s = 1/1\text{k}\Omega$, $G_{m1} = 1/200\text{k}\Omega$, $G_{m2} = 1/2\text{k}\Omega$, and $R_1 = 1\text{M}\Omega$, what is the equivalent Thevenin voltage for the one-port network at V_1 ?

- a. -2V
- b. -1V
- c. 0V
- d. 1V
- e. 2V

26. For $G_s = 1/10\text{k}\Omega$, $G_{m1} = 1/10\text{M}\Omega$, $G_{m2} = 1/20\text{k}\Omega$, and $R_1 = 10\text{M}\Omega$, what is the equivalent resistance for the one-port network at V_1 ?

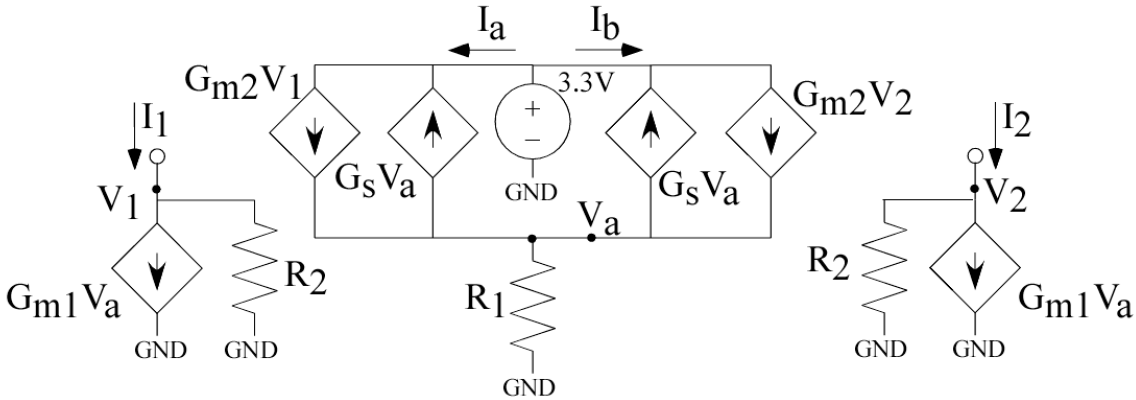- a. $1\text{M}\Omega$
- b. $4\text{M}\Omega$
- c. $10\text{M}\Omega$
- d. $20\text{M}\Omega$
- e. $40\text{M}\Omega$



27. For the Differential Mode Circuit, the G_s element can be ignored. (T/F)

30. Assume we have two inputs, I_1 and I_2 . $G_s = 1/1k\Omega$, $G_{m1} = 1/10k\Omega$, $G_{m2} = 1/10k\Omega$, $R_2 = 1M\Omega$, and $R_1 = 5M\Omega$.

For a Differential current input, $I_1 = -I_2$, the gain from input to differential output, $I_1 = -I_2$, is

- a. 10
- b. 20
- c. 40
- d. 100
- e. 200

33. Assume we have two inputs, $I_1 = 20.1\mu A$ and $I_2 = 19.9\mu A$. $G_s = 1/1k\Omega$, $G_{m1} = 1/10k\Omega$, $G_{m2} = 1/10k\Omega$, $R_2 = 1M\Omega$, and $R_1 = 5M\Omega$. What is the differential input current?

- a. 1nA
- b. 10nA
- c. 100nA
- d. 1 μA
- e. 10 μA

28. For the Differential Mode Circuit, the G_{m2} element can be ignored. (T/F)

31. Assume we have two inputs, I_1 and I_2 . $G_s = 1/1k\Omega$, $G_{m1} = 1/10k\Omega$, $G_{m2} = 1/10k\Omega$, $R_2 = 1M\Omega$, and $R_1 = 5M\Omega$.

For a Common current input, $I_1 = I_2$, the gain from input to common output, $I_1 = I_2$, is

- a. 0.0001
- b. 0.001
- c. 0.01
- d. 0.1
- e. 1

34. Assume we have two inputs, $I_1 = 20.1\mu A$ and $I_2 = 19.9\mu A$. $G_s = 1/1k\Omega$, $G_{m1} = 1/10k\Omega$, $G_{m2} = 1/10k\Omega$, $R_2 = 1M\Omega$, and $R_1 = 5M\Omega$. What is the output at I_a ?

- a. 1nA
- b. 10nA
- c. 100nA
- d. 1 μA
- e. 10 μA

29. For the Common Mode Circuit, the G_{m1} element can be ignored. (T/F)

32. Assume we have two inputs, $I_1 = 20.1\mu A$ and $I_2 = 19.9\mu A$. $G_s = 1/1k\Omega$, $G_{m1} = 1/10k\Omega$, $G_{m2} = 1/10k\Omega$, $R_2 = 1M\Omega$, and $R_1 = 5M\Omega$. What is the common input current?

- a. 2 μA
- b. 4 μA
- c. 10 μA
- d. 20 μA
- e. 40 μA