


ECE 2040 Midterm Exam 2
Fall 2020

General Instructions instructions:


- Exam is closed book / closed notes other than the one-page of handwritten notes.
- Questions are worth 4 points unless otherwise stated.
- Only the final answers, as indicated by the question, will be considered correct for each question.
- Choose the best possible answer available in all cases.

Honorlock instructions:


- The only notes allowed is a one-page of handwritten notes plus the one page of notes from Exam 1. Front and back of the sheet are allowed. Sheet should be shown to the camera.
- Restroom breaks are not encouraged, although if necessary, it is allowed when asking the proctoring system. Timing will be recorded.
- Blank scratch paper is allowed, and needs to be shown to the proctor.
- Music is allowed assuming it is at a low volume and not conveying any exam answers.
- Individuals should be allowed to work using their scratch piece of paper (should not be a violation). The initial scan should include the space around the desk where the individual will be writing so there are no issues when writing on their scratch piece of paper.

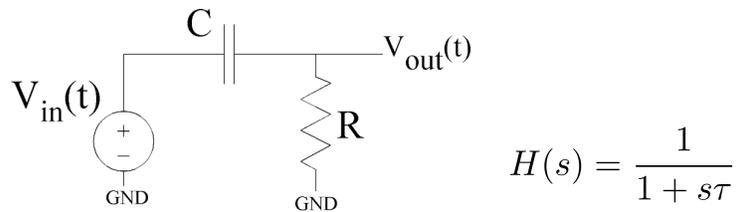


Question 1: (True/False) The circuit has the resulting H(s) transfer function.

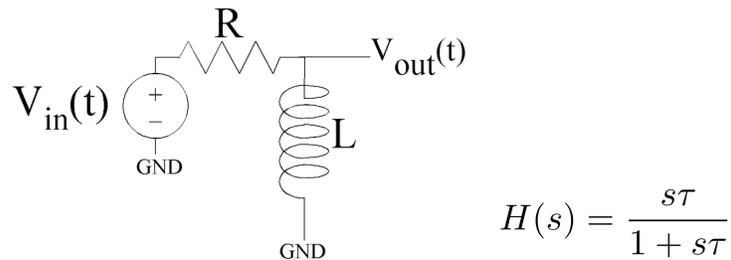


Question 2: (True/False) The circuit has the resulting H(s) transfer function.

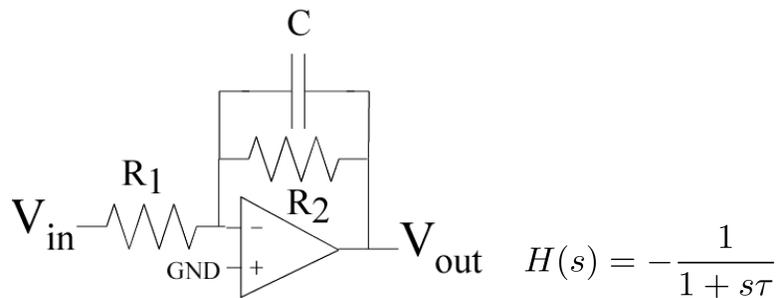


Question 3: (True/False) The circuit has the resulting H(s) transfer function for $R_1 = R_2$.

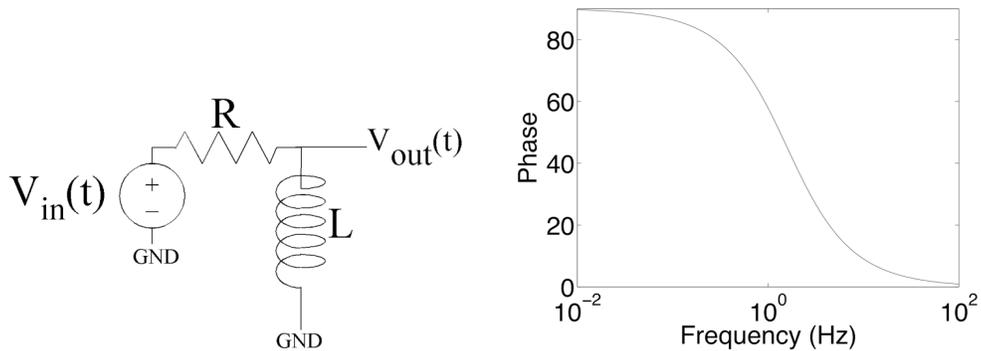


Question 4: (True/False) The circuit has the resulting phase response as shown.

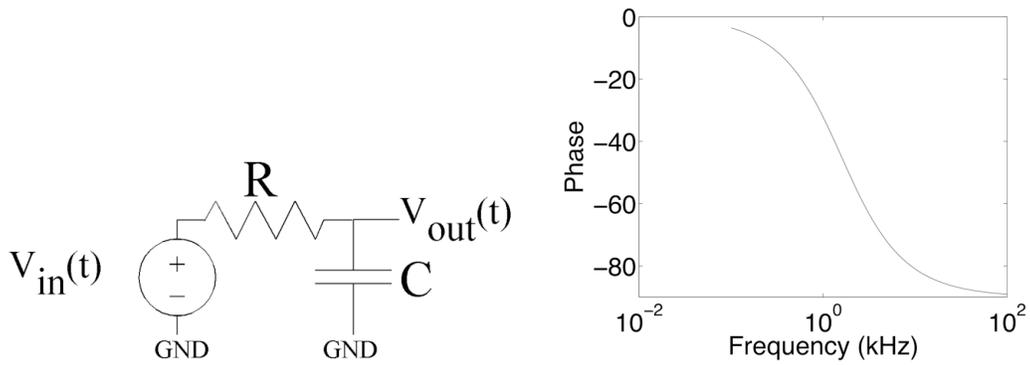


Question 5: (True/False) The circuit has the resulting phase response as shown.

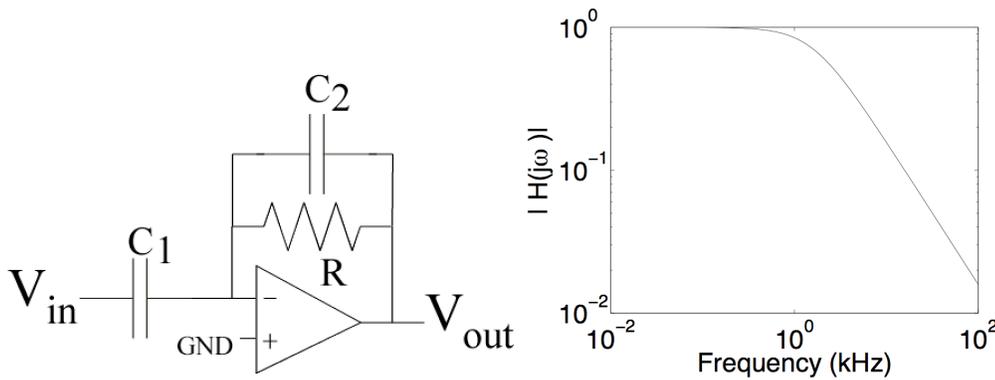


Question 6: (True/False) The circuit has the resulting frequency response shown for $C_1 = C_2$.

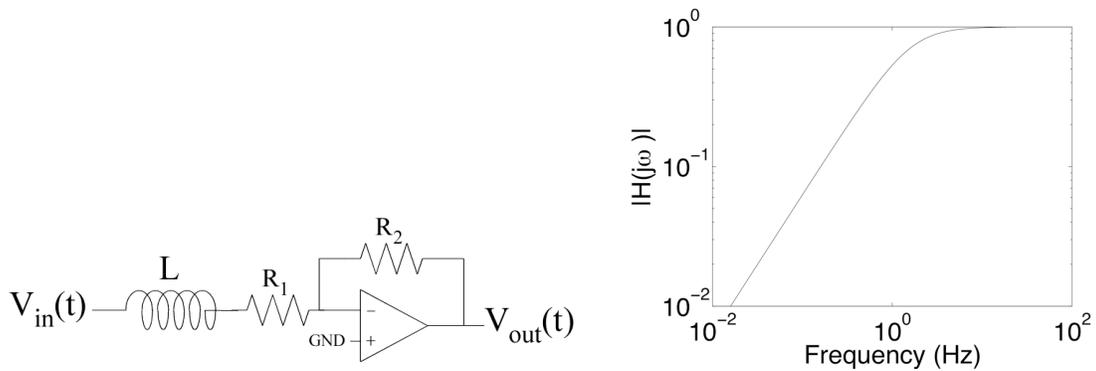


Question 7: (True/False) The circuit has the resulting frequency response shown for $R_1 = R_2$.

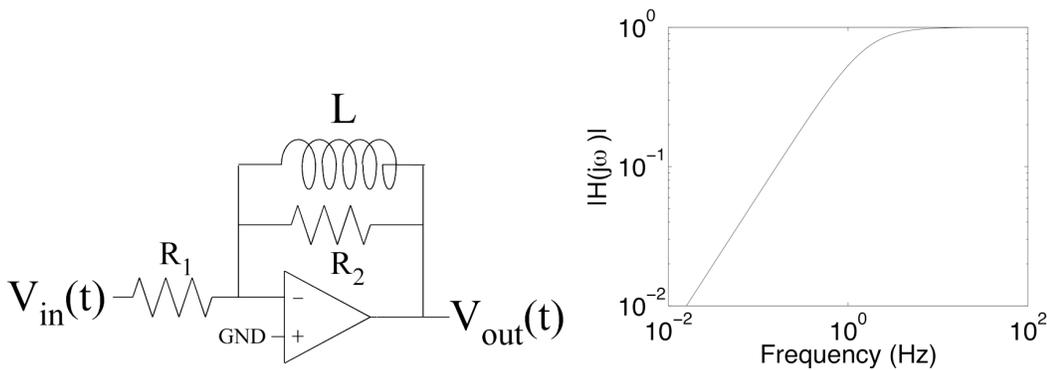


Question 8: (True/False) The circuit has the resulting frequency response shown for $R_1 = R_2$.

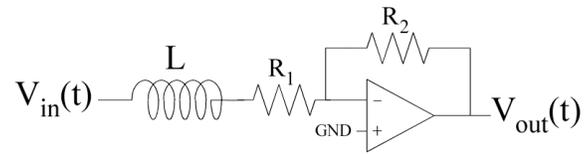

Question 9: (True/False) The circuit is a first-order low-pass filter.

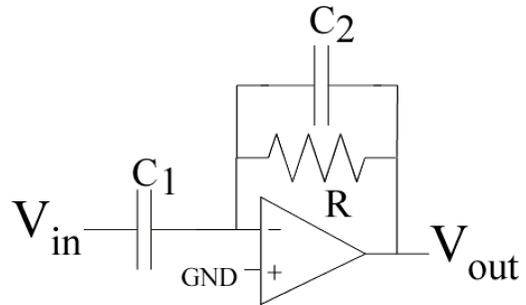

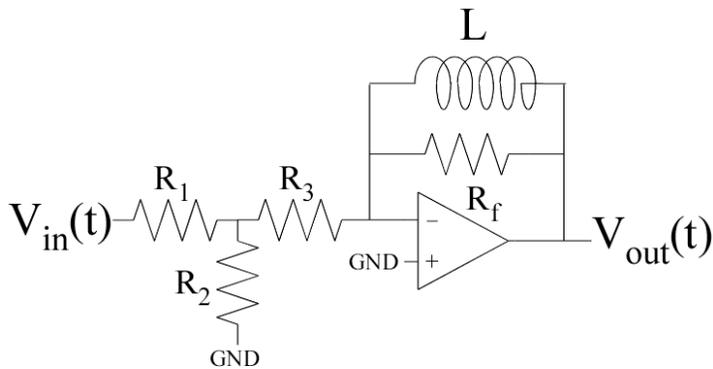Question 10: (True/False) The circuit is a first-order high-pass filter.



The following four questions refer to this circuit figure.

Question 11: Assume the Op-amp is ideal with infinite gain. $R_1 = 300\text{k}\Omega$, $R_2 = 300\text{k}\Omega$, $R_3 = 150\text{k}\Omega$, $R_f = 3\text{M}\Omega$. $L = 6\text{mH}$. The value of the largest (or only) timeconstant:

- a. 2ns
- b. 20ns
- c. 200ns
- d. $2\mu\text{s}$
- e. $20\mu\text{s}$


Question 12: Assume the Op-amp is ideal with infinite gain. $R_1 = 300\text{k}\Omega$, $R_2 = 300\text{k}\Omega$, $R_3 = 150\text{k}\Omega$, $R_f = 3\text{M}\Omega$. $L = 6\text{mH}$. What is the magnitude of the constant gain region for this circuit?

- a. 1
- b. 2
- c. 5
- d. 10
- e. 20

Question 13: (True/False) Assume the Op-amp is ideal with infinite gain. This circuit is a first-order low-pass filter.

Question 14: Assume the Op-amp is ideal with infinite gain. $R_1 = 300\text{k}\Omega$, $R_2 = 300\text{k}\Omega$, $R_3 = 150\text{k}\Omega$, $R_f = 3\text{M}\Omega$. $L = 6\text{mH}$. A 2V input step after starting 0V at $t=0$ would result in the output response:

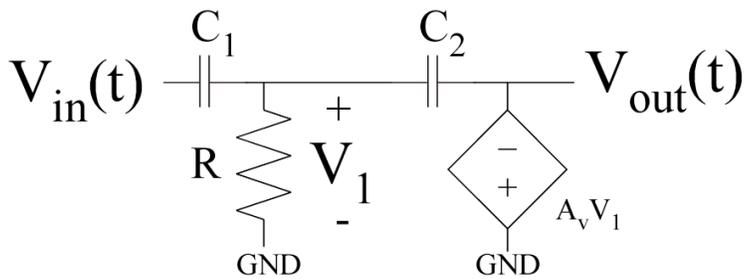- a. $V_{out}(t) = 10e^{-t/(20\text{ns})}u(t)$
- b. $V_{out}(t) = -10e^{-t/(2\text{ns})}u(t)$
- c. $V_{out}(t) = 10\left(1 - e^{-t/(2\text{ns})}\right)u(t)$
- d. $V_{out}(t) = -10\left(1 - e^{-t/(20\text{ns})}\right)u(t)$
- e. $V_{out}(t) = 10\left(1 - e^{-t/(200\text{ns})}\right)u(t)$



The following six questions refer to this circuit figure.

Question 15: (True/False) Assuming R is infinite, the circuit could be minimally reduced for arbitrary inputs to a first-order differential equation.

Question 16: Assuming R is infinite with $C_1 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $A_v = 10,000$, in the region for nearly constant gain for this circuit for a change in V_{in} , resulting in a change in V_{out} , that gain would be

- a. -2
- b. -1
- c. -0.5
- d. 0.5
- e. 2


Question 17: (True/False): V_{out} could be 2V for a constant $V_{in} = 0\text{V}$.

Question 18: Assuming $R = 1\text{M}\Omega$, $C_1 = 2\text{pF}$, $C_2 = 1\text{pF}$, and $A_v = 10,000$, what is the largest timeconstant or single timeconstant (if only one) for this circuit?

- a. $1\mu\text{s}$
- b. $10\mu\text{s}$
- c. $100\mu\text{s}$
- d. 1ms
- e. 10ms

Question 19: (True/False) Assuming $R = 1\text{M}\Omega$, the circuit could be minimally reduced for arbitrary inputs to a first-order differential equation.

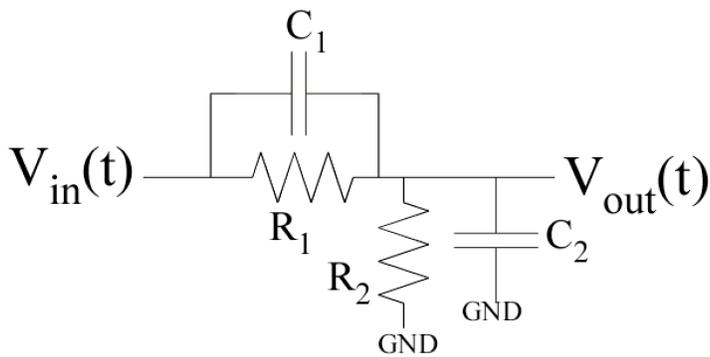Question 20: (True/False): Assuming $R = 1\text{M}\Omega$, V_{out} could be 2V for a constant $V_{in} = 0\text{V}$.



The following five questions refer to this circuit figure.

Question 21: (True/False) The circuit could be minimally reduced for arbitrary inputs to a second-order differential equation.

Question 22: For an input, $V_{in}(t) = 4V u(t)$, where $R_1 = 1k\Omega$, $R_2 = 1k\Omega$, $C_1 = 3\mu F$, $C_2 = 1\mu F$, what is the output voltage, V_{out} , for $t = -1ms$?

- a. 0V
- b. 1V
- c. 2V
- d. 3V
- e. 4V

Question 23: For an input, $V_{in}(t) = 4V u(t)$, where $R_1 = 1k\Omega$, $R_2 = 1k\Omega$, $C_1 = 3\mu F$, $C_2 = 1\mu F$, what is the output voltage, V_{out} , at steady state?

- a. 0V
- b. 1V
- c. 2V
- d. 3V
- e. 4V

Question 24: For an input, $V_{in}(t) = 4V u(t)$, where $R_1 = 1k\Omega$, $R_2 = 1k\Omega$, $C_1 = 3\mu F$, $C_2 = 1\mu F$, what is the output voltage, V_{out} , just after $t=0$?

- a. 0V
- b. 1V
- c. 2V
- d. 3V
- e. 4V

Question 25: For an input, $V_{in}(t) = 4V u(t)$, where $R_1 = 1k\Omega$, $R_2 = 1k\Omega$, $C_1 = 3\mu F$, $C_2 = 1\mu F$, what is the largest timeconstant to converge to steady state?

- a. 1ms
- b. 2ms
- c. 3ms
- d. 4ms
- e. 6ms