

P 3.6-3

Reduce the circuit from the right.

$$i_2 = 6 \text{ A}$$

$$i_3 = 3 \text{ A}$$

$$i_4 = 1.5 \text{ A}$$

$$\bar{i} = \frac{1+1}{2+(1+1)} (1.5) = 0.75 \text{ A}$$

