

 




# Sample and Hold Elements

 



# Sample and Hold Elements

 



# Sample and Hold Elements

  



# Sample and Hold Elements

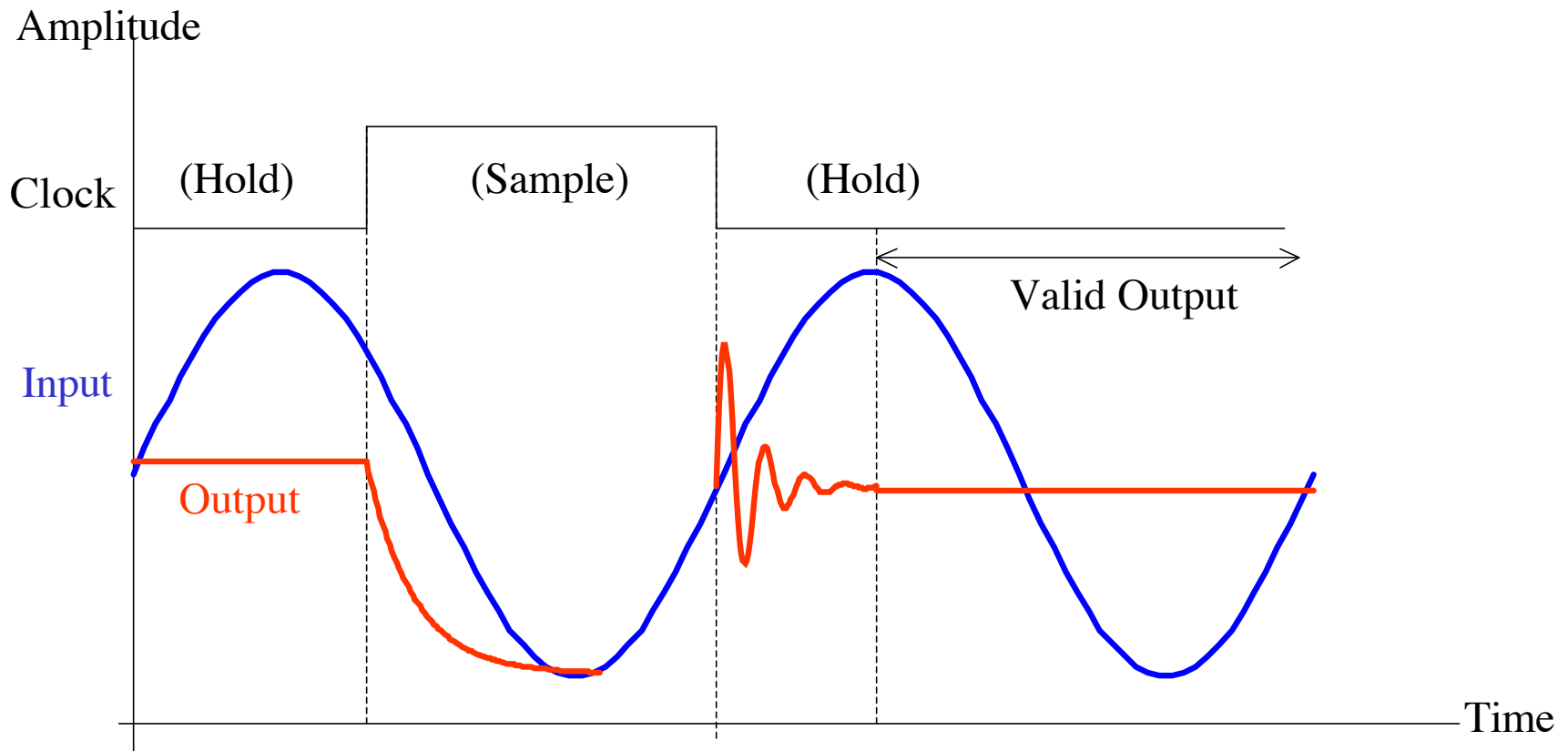 


# Sample and Hold Elements

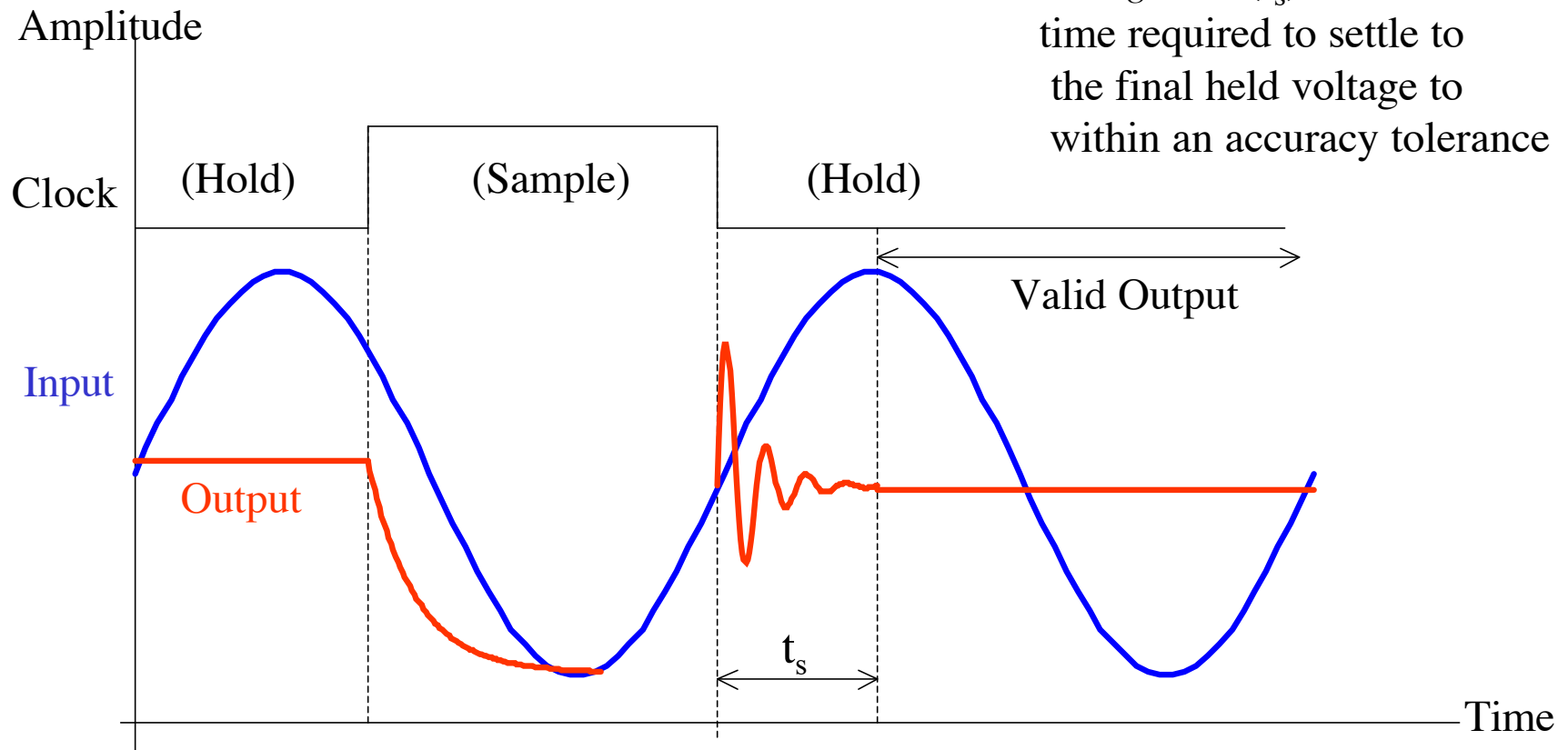 

# Sample and Hold Elements

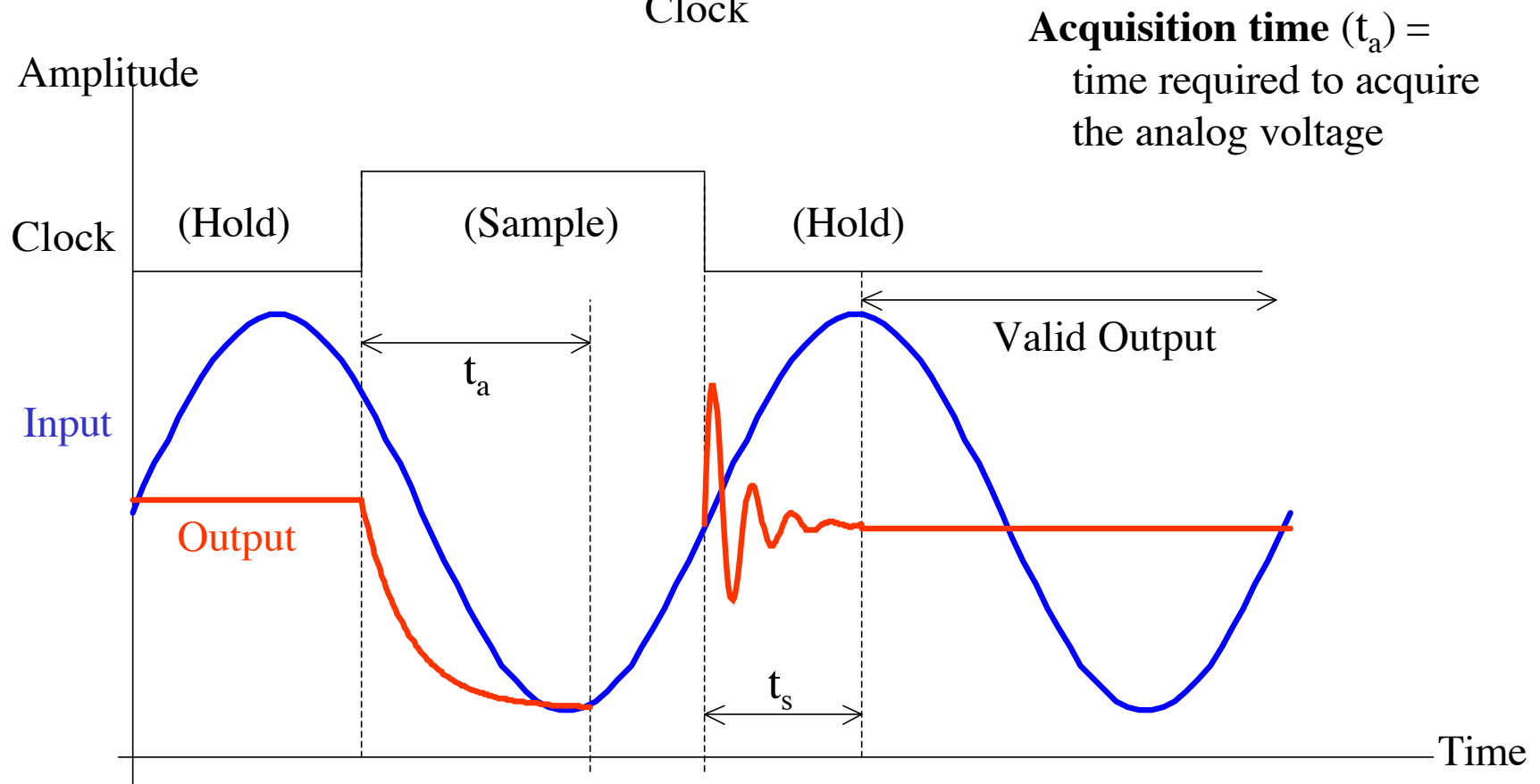 


# Sample and Hold Elements


 


$$T_{\text{sample}} = t_a + t_s$$
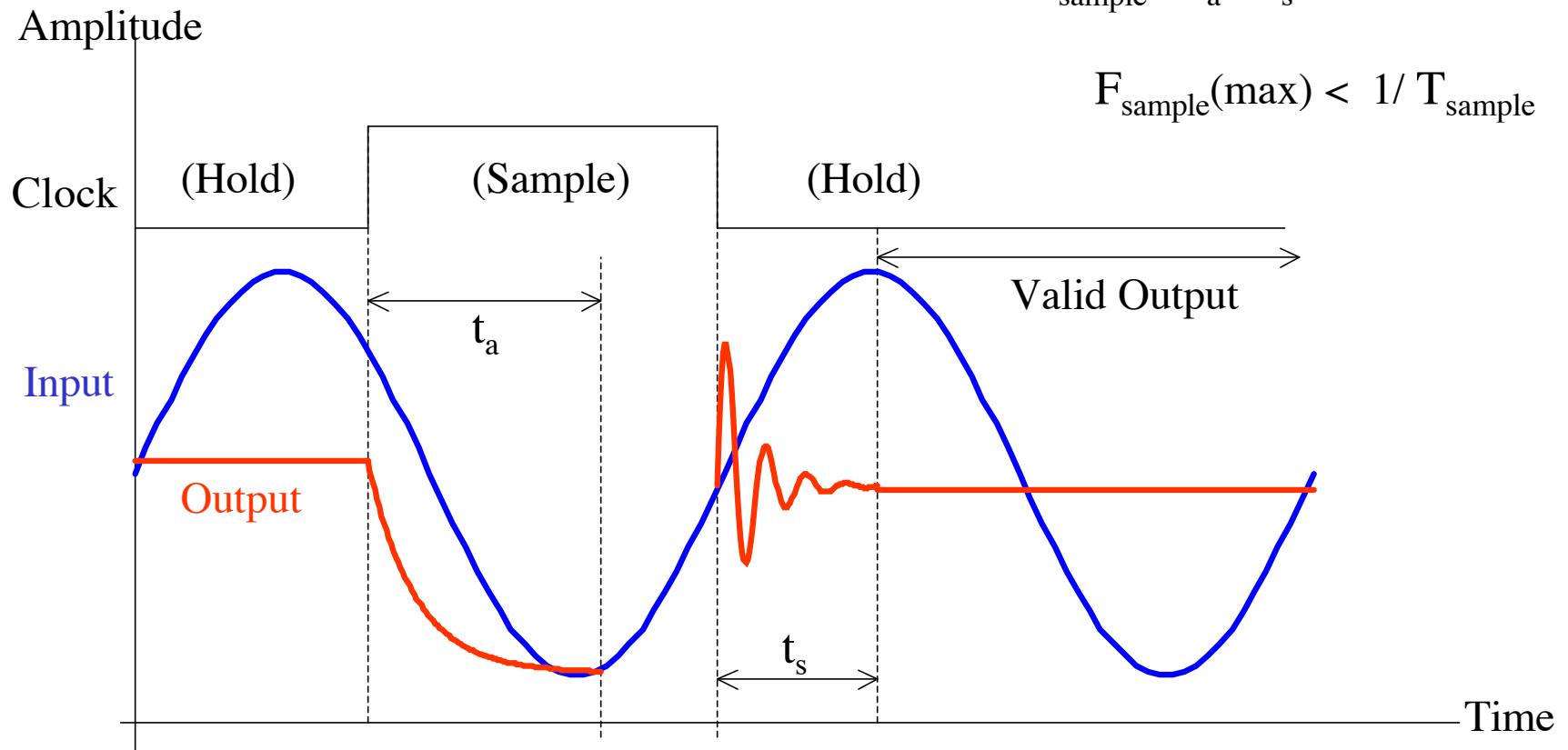
$$F_{\text{sample}}(\text{max}) < 1 / T_{\text{sample}}$$




# Sample and Hold Elements

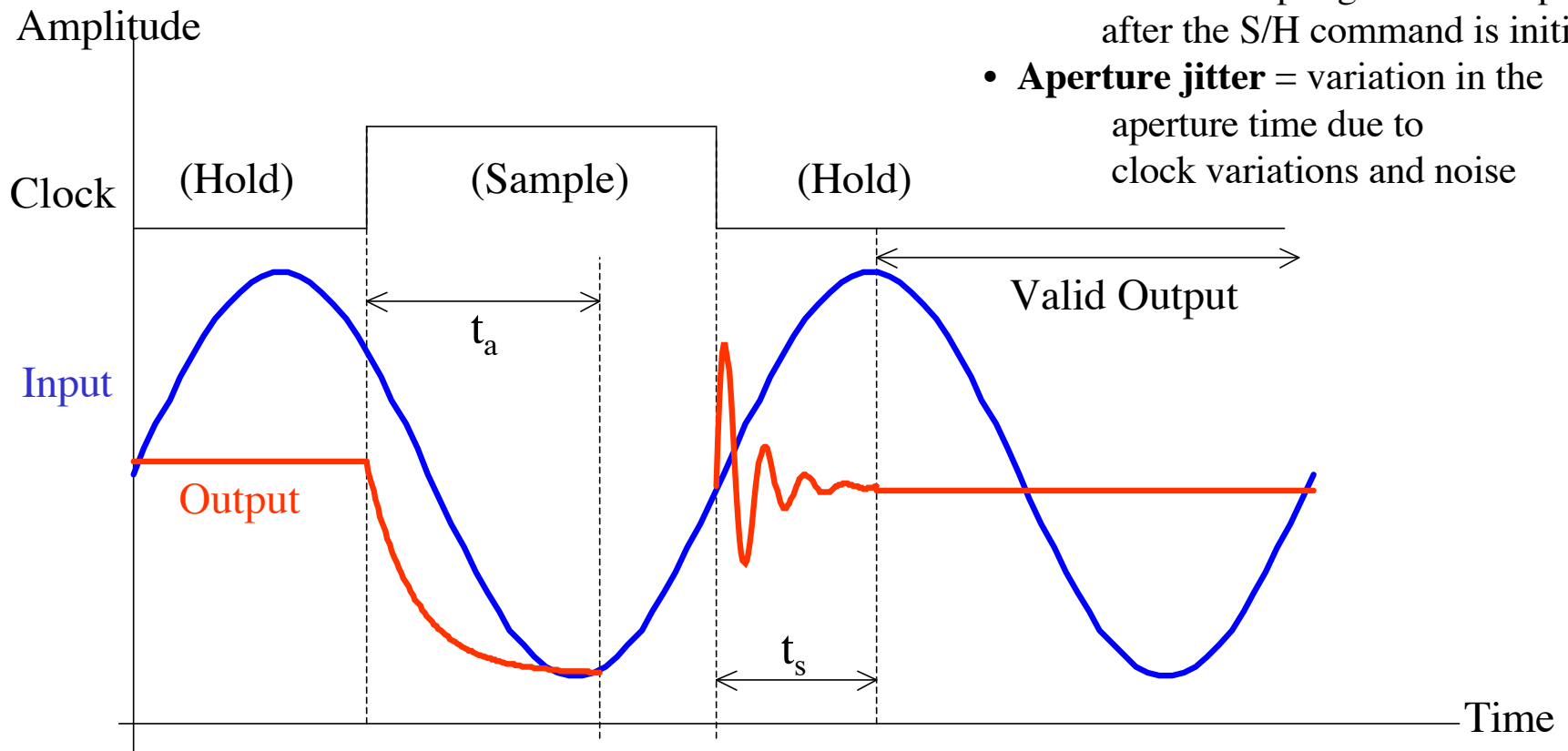 




- **Aperture time** = the time required for the sampling switch to open after the S/H command is initiated
- **Aperture jitter** = variation in the aperture time due to clock variations and noise






# Basic Sample and Hold Element

 


# Basic Sample and Hold Element

   




# Basic Sample and Hold Element

   


$CK = 1 (V_{dd})$

 


# Basic Sample and Hold Element

   


$CK = 1 (V_{dd})$

 

# Basic Sample and Hold Element

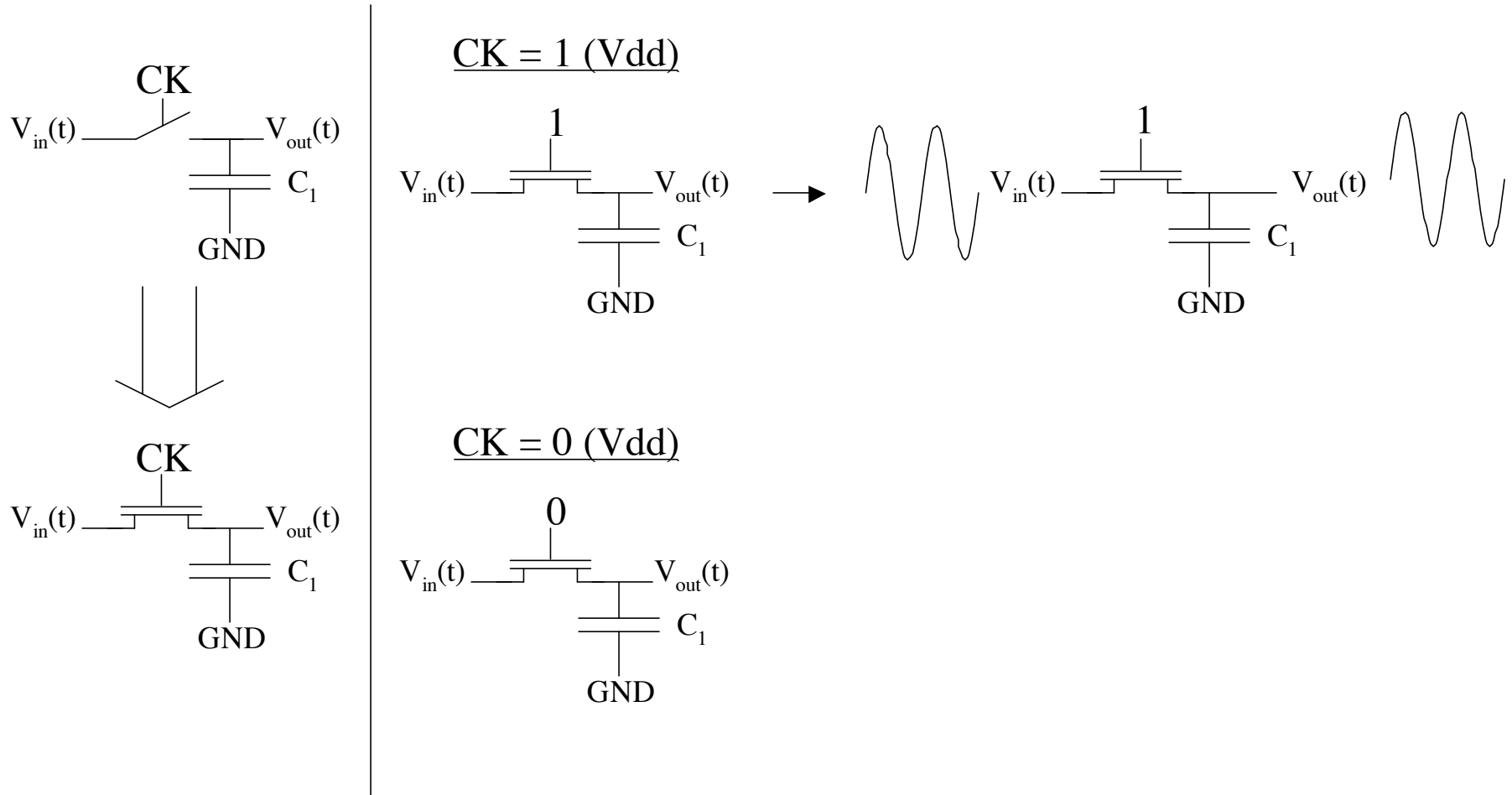


# Basic Sample and Hold Element

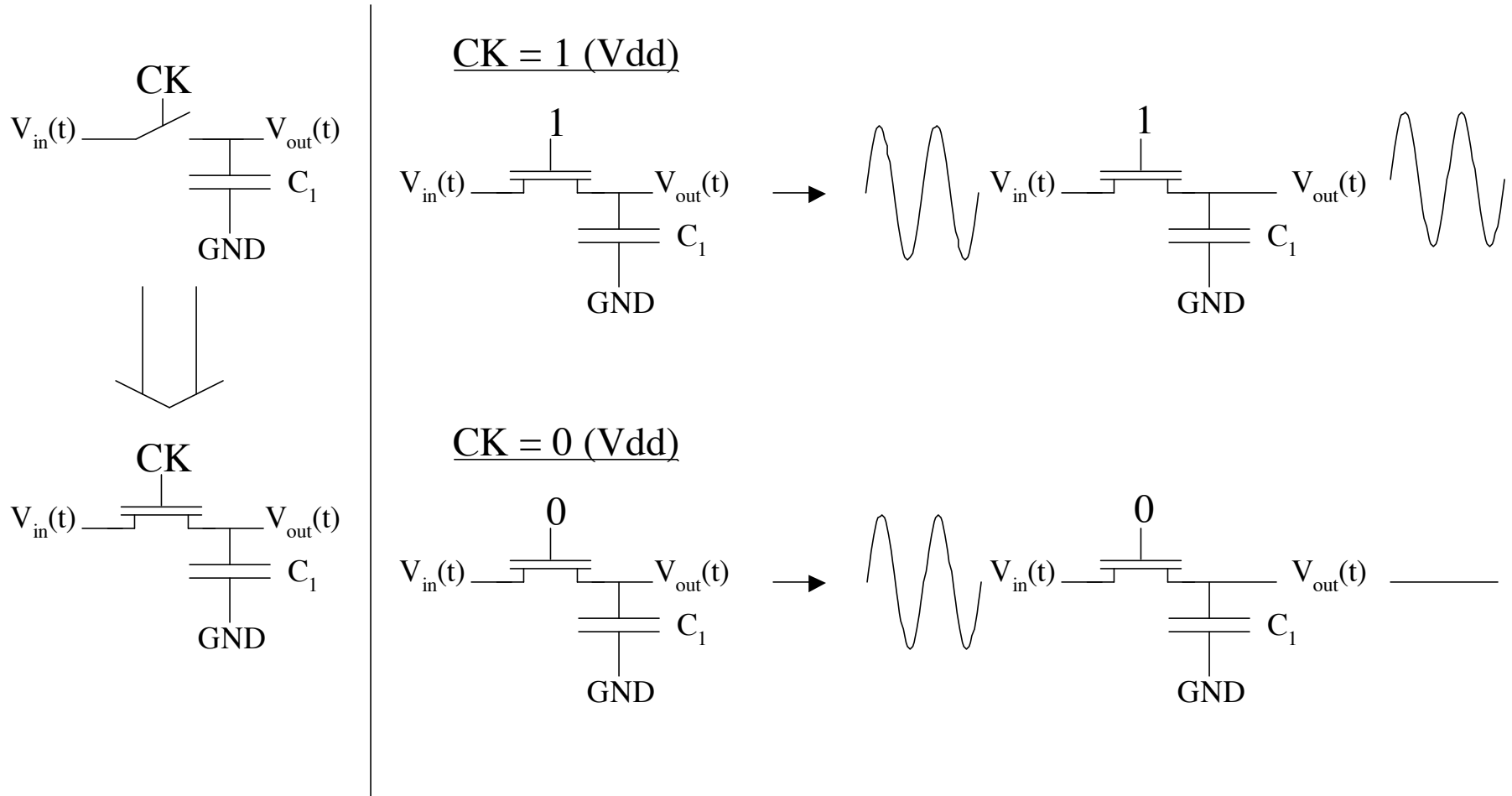


# Acquisition and Hold Time

## Acquisition Time

 

but  $R_{on}$  is not a constant....

## Hold Time

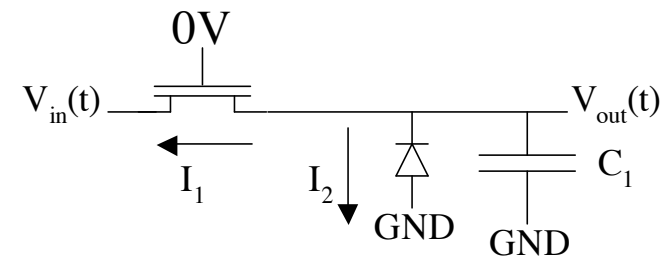


$I_2(t)$ : Leakage through the reversed-biased pn junction  
Typically 1fA to 100fA (dark)

$I_1(t)$ : Leakage through the MOS transistor  
Can be negligible with correct biasing




$C_1$	Hold time (1mV drop) with $I_1(t) = 10\text{fA}$
10pF	1s
1pF	100ms
100fF	10ms
10fF	1ms

# Basic S/H elements



 




# Basic S/H elements

   


# Basic S/H elements

   


Would use a buffer to drive loads that are not purely capacitive

# S/H elements

 


More accurate, but slower

 

$\phi_1$  and  $\phi_2$  are non-overlapping clocks
 
# Non-Overlapping Clocks


We will always be using non-overlapping clocks; therefore, we want a waveform like



We effectively have  
four phases.
 
# Non-Overlapping Clocks

We will always be using non-overlapping clocks; therefore, we want a waveform like




We effectively have four phases.

Would want  $t_d$  as small as possible  
for proper operation

We will also assume that the input  
is held constant through  
the entire  $[n]^{\text{th}}$  cycle
 
# Non-Overlapping Clocks

We will always be using non-overlapping clocks; therefore, we want a waveform like




We effectively have four phases.

 
## Circuit to generate waveform

Would want  $t_d$  as small as possible for proper operation


We will also assume that the input is held constant through the entire  $[n]^{\text{th}}$  cycle




# S/H elements

 


Initial Phase ( $\phi_1, \phi_2 = 0$ )

 

# S/H elements

 


Phase I ( $\phi_1 = 1, \phi_2 = 0$ )

 






# S/H elements

 



Phase II ( $\phi_1, \phi_2 = 0$ )

 

# S/H elements

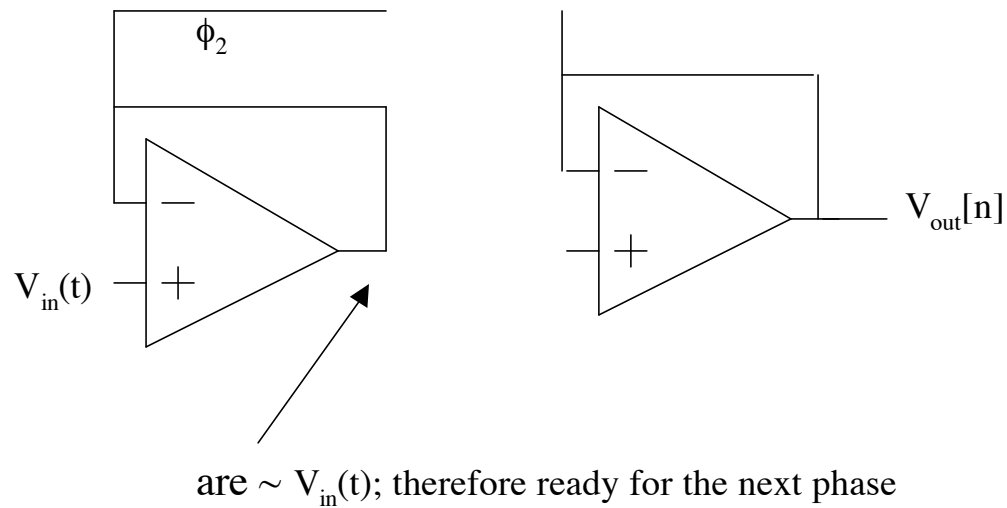 

# S/H elements

  

$\phi_1$  and  $\phi_2$  are non-overlapping clocks