

Switched Capacitor Filters (SCF)

- Passive Filters
 - Components are R, L, C
 - Big, Heavy, discrete
 - Inductors are limited in quality
 - Designed in s-domain
- Active RC filters
 - Components are Opamps, OTAs, R's and C's
 - Can be integrated on the same chip
 - Inaccurate RC in ICs
 - Designed in s-domain
- Switched Capacitor Filters
 - Idea well known for over 80 years
 - Accurate RC, where R is realized using switches and capacitors
 - Clock noise and noise alias
 - Small chip area
 - Designed in z-domain
 - Two most useful filter realizations
 - Cascade
 - Ladder Realization




SCF Design

- Three basic methods
 1. Resistor substitution
 - Replace the resistors in a continuous time active RC filter, with switched capacitor circuits
 2. Uses switched capacitor integrators to simulate passive RLC prototype circuits, RLC ladder networks, for a desired filter realization
 3. Uses a direct building block approach in the Z- domain of which there are two approaches:
 - a. Convert the transfer function into a signal flow diagram consisting of amplifiers, delays and summers
 - b. Break the transfer function into products of first and second order terms.



SC Resistor Simulation

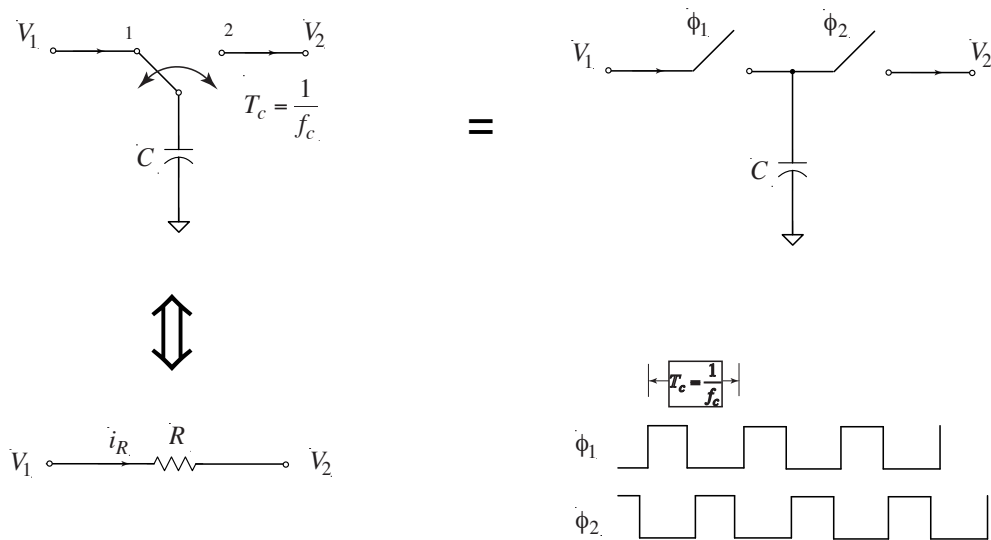

- ϕ_1, ϕ_2 is a two phase nonoverlapping clock



SC Resistor Simulation (Cont'd)

At position 1 the charge on C at steady state is $q_1 = CV_1$

At position 2 the charge on C at steady state is $q_2 = CV_2$

Assuming $V_1 > V_2$, the charge Δq transferred is

$$\Delta q = q_1 - q_2 = C(V_1 - V_2)$$

The current flowing will be on average

$$i(t) = \frac{\delta q(t)}{\delta t} = \lim_{\Delta T_c \rightarrow 0} \frac{\Delta q}{\Delta T_c} \cong \frac{C(V_1 - V_2)}{T_c} \quad (1)$$

Consider now a resistance of value R connected to the same two sources V_1 & V_2 . Then

$$i_R(t) = \frac{(V_1 - V_2)}{R} \quad (2)$$


Equating (1) and (2) yields $R = \frac{T_c}{C} = \frac{1}{f_c C}$

Ex. Using $C = 1\text{pF}, f_c = 100\text{kHz} \rightarrow R = 10\text{M}\Omega$



Conditions for SC-R Approximation

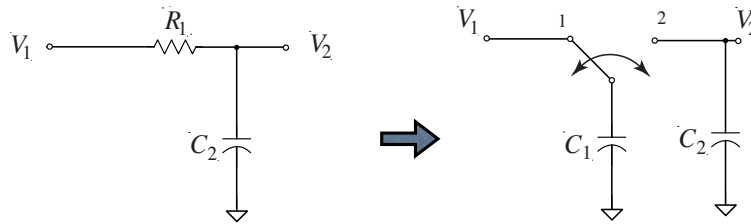
- At least one of the sources must be a voltage source



$$R_1 = T_c \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

- If $C_2 \gg C_1$, $R_1 = \frac{T_c}{C_1}$

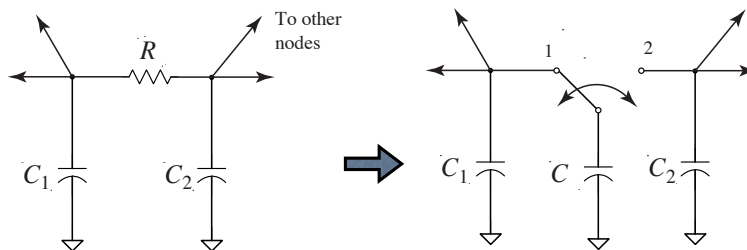Note if neither V_1 nor V_2 are voltage sources then




Show that

$$R = \left[\frac{C_2 C_1 + (C_2 + C_1) C + C^2}{C_2 C_1 C} \right] T_c$$




Conditions for SC-R Approximation (Cont'd)

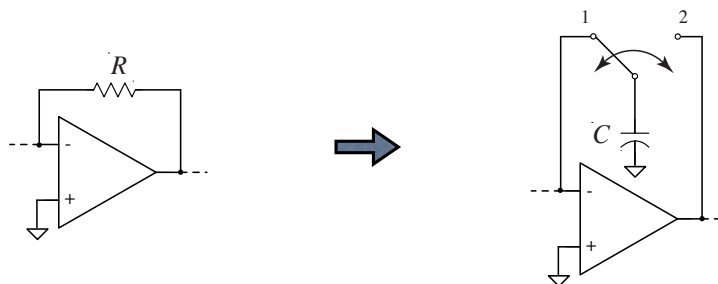- SC Resistors cannot close an opamp feedback path



Not allowed

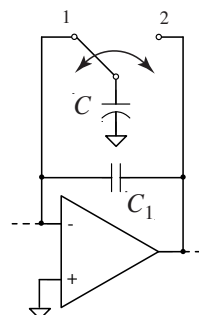


Allowed




Conditions for SC-R Approximation (Cont'd)

- No floating nodes allowed

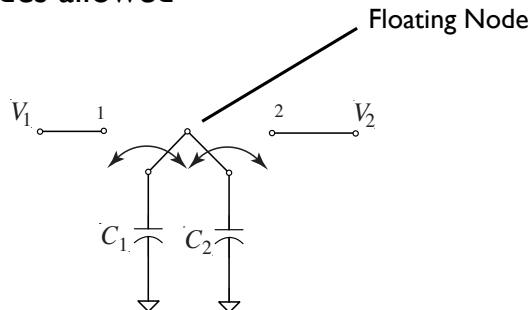


- Switches

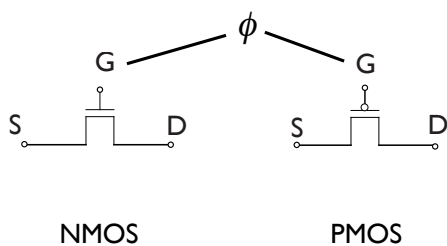

NMOS

PMOS

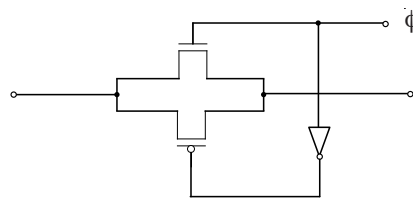


Complementary Switch




Summary of Approximated Resistance of Four Switched Capacitor Resistor Circuits

Parallel

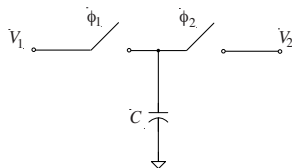


$$R = \frac{T}{C}$$

Series

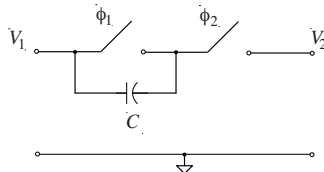


$$R = \frac{T}{C}$$

Series-Parallel

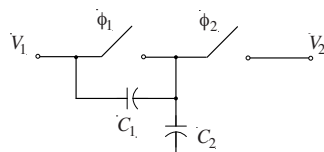

$$R = \frac{T}{C_1 + C_2}$$


Bilinear

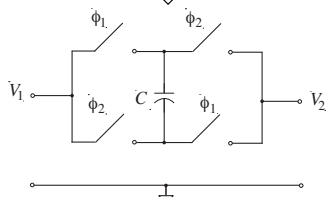


$$R = \frac{T}{4C}$$



MOS Switch Realization

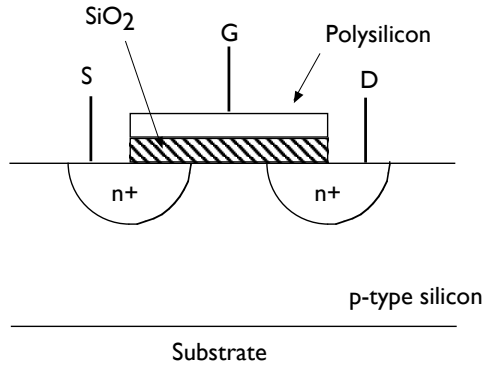

NMOS Switch


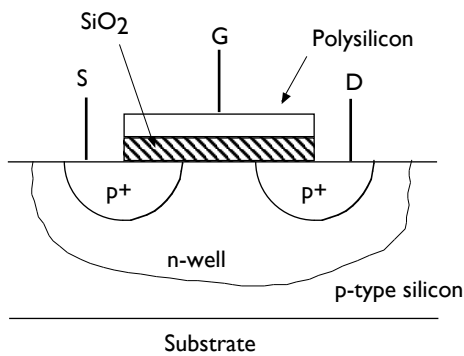


PMOS Switch




Switches Continued

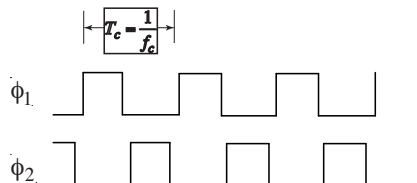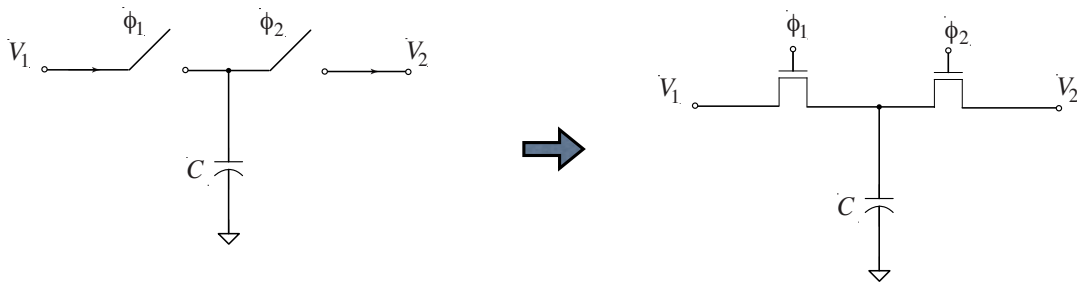- Switch turns on when $V_G > V_{TH}$ and turns off when $V_G < V_{TH}$
- Typically $R_{on} \cong 1k\Omega - 10k\Omega$, and $R_{off} \cong 100M\Omega - 1G\Omega$ for single switches. For complementary MOS switches R_{on} is lower and in the order of $R_{on} \cong 10\Omega - 1k\Omega$





Capacitor Realization


- Basically two types of capacitors
 1. Metal Oxide Crystalline Silicon Capacitor (Grounded capacitor)
 - Best suited for metal to gate CMOS and MOS processes which do not use self alignment procedures.
 2. Polysilicon-Oxide-Polysilicon Capacitor (Floating Capacitor)
 - Found in many processes today
 - Requires little self alignment
- Selling feature of SCs is the capacitor ratio accuracy which can reach 0.1% in some cases. Note transistors can also be used as capacitors!

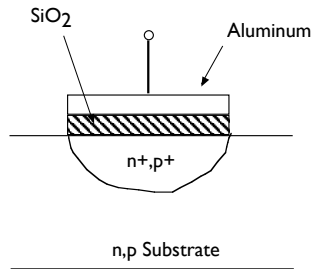

MOS Cap.

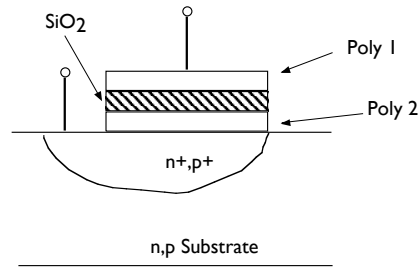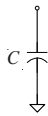


Poly-Poly Cap.

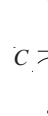


Capacitance Mismatch

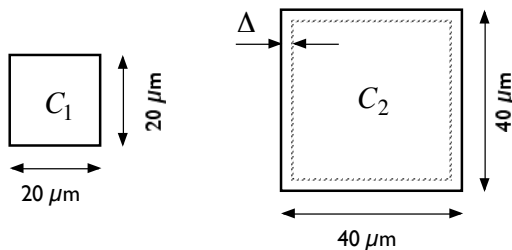- Area Inaccuracy & Oxide Thickness Variation
- Keep Capacitance Ratio Constant



$$\frac{C_2}{C_1} = \frac{(40 - 0.5) \cdot (40 - 0.5)}{(20 - 0.5) \cdot (20 - 0.5)} = 4.103$$


→ 2.6% error

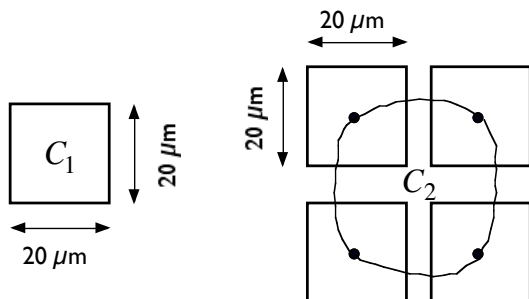


$$\frac{C_2}{C_1} = \frac{4(20 - 0.5) \cdot (20 - 0.5)}{(20 - 0.5) \cdot (20 - 0.5)} = 4$$



Capacitance Layout

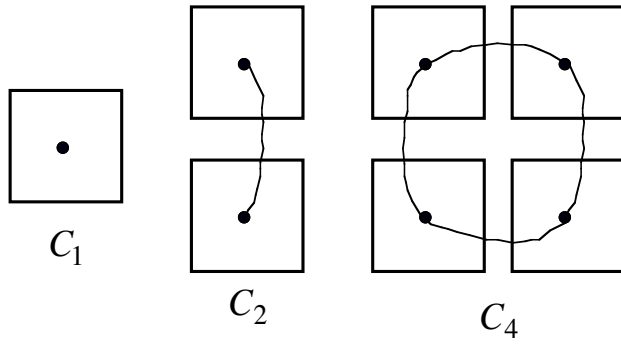

Non optimal approach

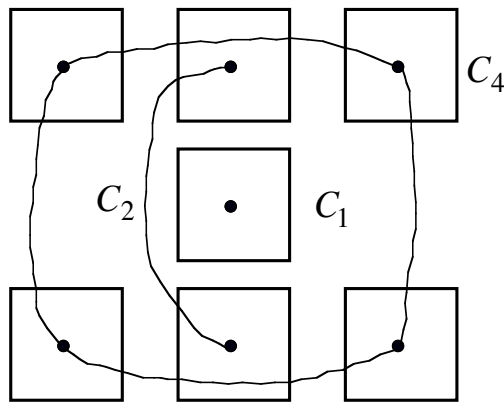



- Optimal layout is the Centroid Approach
- Ground shielding should also be added



Parasitic Capacitances

Parasitic capacitances exist in switches and in capacitors

Switch

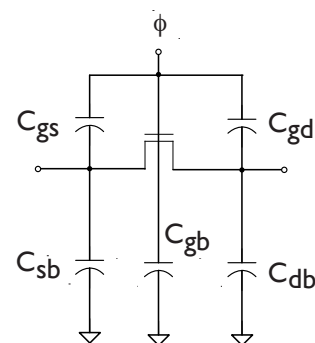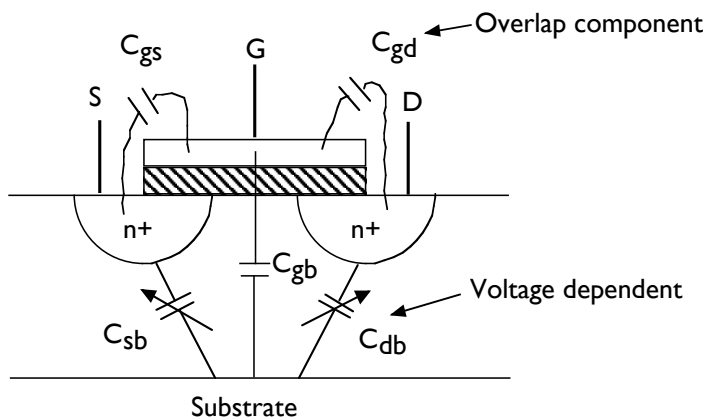



$$C_{gs} = C_{gd} \cong 0.005 \text{ pF}$$

$$C_{sb} = C_{db} \cong 0.02 \text{ pF}$$



Parasitic Capacitances Continued

Poly-poly Capacitor

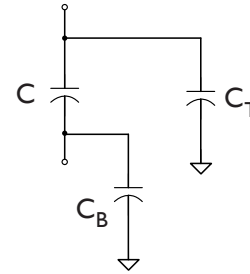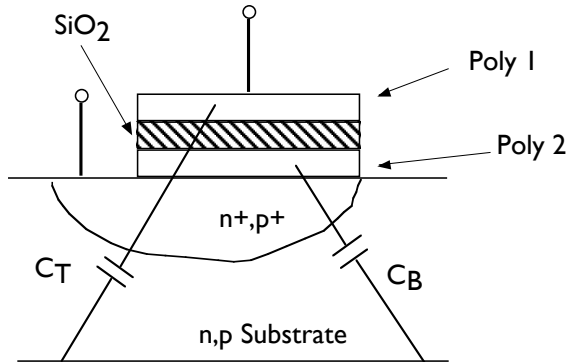


$C_T \cong 0.1\% - 1\%$ of the desired MOS capacitance C

$C_B \cong 5\% - 20\%$ of the desired MOS capacitance C




A Switched Capacitor Integrator

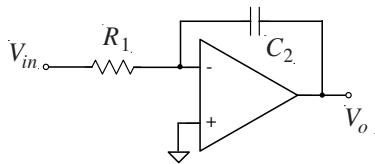

- s - domain "Miller" Integrator

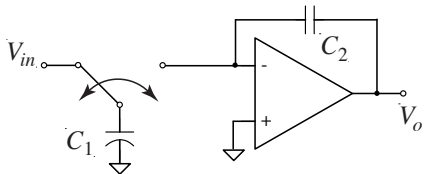
$$\frac{V_o}{V_{in}} = -\frac{1}{R_1 C_2 s}$$




- SC Integrator obtained by replacing "R" with a switched capacitor

$$C_1 \cong \frac{1}{f_c R_1}$$

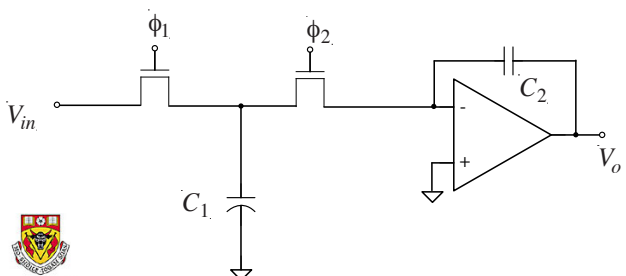
$$\frac{V_o}{V_{in}} = -f_c \left(\frac{C_1}{C_2} \right) \frac{1}{s}$$



- Implementation

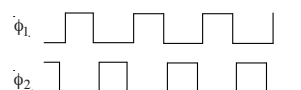

Effects of Parasitics

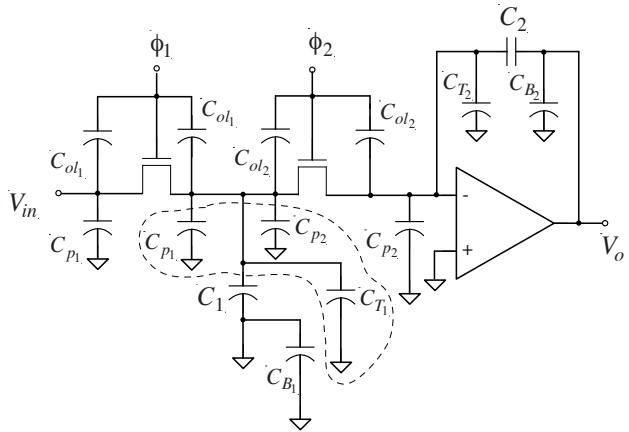


C_p 's are C_{sb} and C_{db}
 C_{ol} 's are C_{gs} and C_{gd}

- C_{p1} is always charging from V_{in} and has no effect
- C_{B1} is shorted
- C_{p2} and C_{T2} have zero voltage across them. This has no effect
- C_{B2} is always charging to V_o
- C_{ol1} and C_{ol2} only affect the output by feeding the clock signal through the integrator. This is known as clockfeedthrough. It can be minimized but never eliminated.
- Thus we are left with $C_p = C_{p1} + C_{p2} + C_{T1}$



8 - 17

Effects of Parasitics (Cont'd)

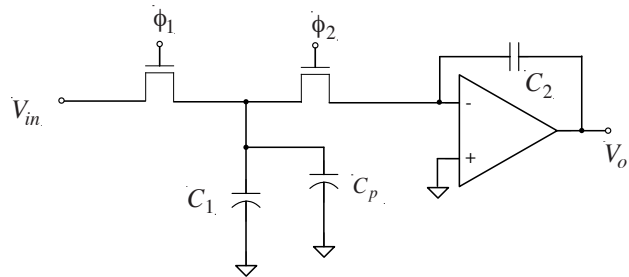


$$\frac{V_o}{V_{in}} = -f_c \left(\frac{C_1 + C_p}{C_2} \right) \frac{1}{s}$$

- The above integrator is said to be parasitic sensitive
- Not desirable if precision is required
- Parasitic insensitive integrators exist.




8 - 18

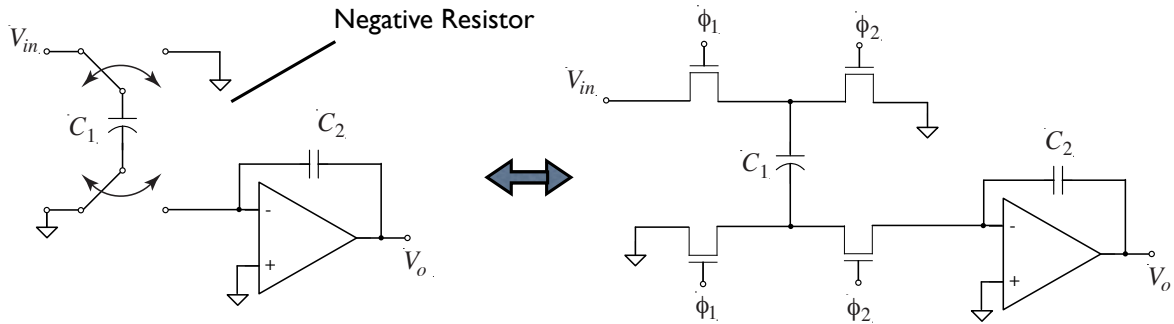A Noninverting (Parasitic Insensitive) Integrator



Examining parasitics

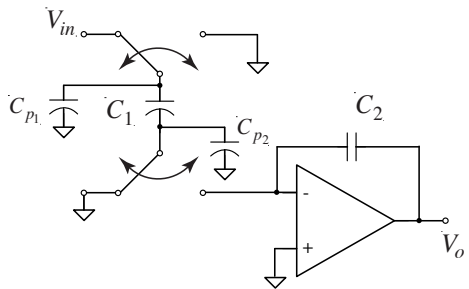


- C_{p2} always has a zero potential
- C_{p1} charges to V_{in} during one cycle and discharges to zero in the next. It has no effect.

$$\frac{V_o}{V_{in}}(s) = f_c \left(\frac{C_1}{C_2} \right) \frac{1}{s}$$



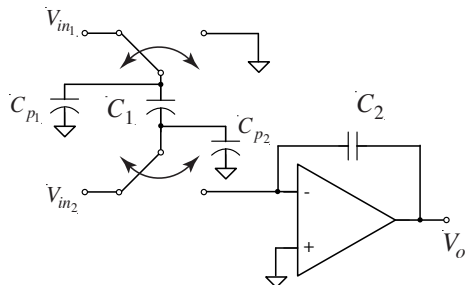A Differential (Parasitic Sensitive) Integrator



- By superposition

$$V_o(s) = \frac{f_c}{s} \left(\frac{C_1}{C_2} \right) \left[V_{in1} - \left(1 + \frac{C_{p2}}{C_1} \right) V_{in2} \right]$$


If $C_{p2} \ll C_1$

$$V_o(s) = \frac{f_c}{s} \left(\frac{C_1}{C_2} \right) [V_{in1} - V_{in2}]$$




Sample Circuits

First order SC section

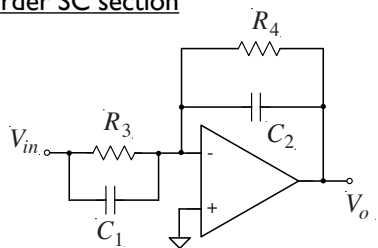

$$\frac{V_o}{V_{in}} = -\left(\frac{C_1}{C_2}\right) \left(\frac{s + \frac{1}{R_3 C_1}}{s + \frac{1}{R_4 C_2}} \right)$$

SC direct replacement

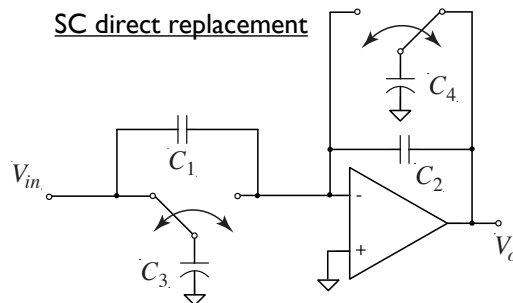


$$\frac{V_o}{V_{in}} = -\left(\frac{C_1}{C_2}\right) \left(\frac{s + f_c \frac{C_3}{C_1}}{s + f_c \frac{C_4}{C_2}} \right)$$



Sample Circuits (Cont'd)


Second order SC section

LP Filter

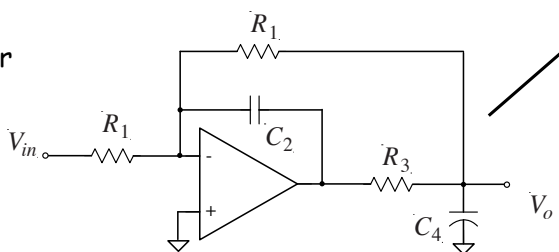

RC opamp realization
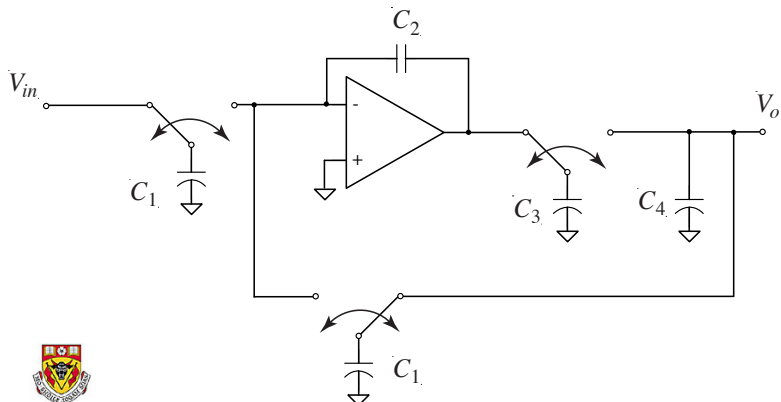
$$\frac{V_o}{V_{in}}(s) = -\frac{1}{s^2 + \frac{1}{R_3 C_4} s + \frac{1}{R_1 R_3 C_2 C_4}}$$



$$\begin{aligned} \frac{V_o}{V_{in}}(s) &= -\frac{\frac{C_1 C_3}{C_2 C_4} f_c^2}{s^2 + f_c \frac{C_3}{C_4} s + \frac{C_1 C_3}{C_2 C_4} f_c^2} \\ &= -\frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2} \end{aligned}$$



Sample Circuits (Cont'd)

Ex. 1

- Design a LP filter with $f_o = 1.59\text{kHz}$ and $Q = 5$. The DC gain is to be unity.

Solution

$$\frac{V_o(s)}{V_{in}} = -\frac{\omega_o^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2} = -\frac{10^8}{s^2 + 2000s + 10^8}$$

Using the previous circuit the design equations are

$$\frac{C_1}{C_2} \frac{C_3}{C_4} f_c^2 = 10^8 \quad \text{and} \quad \frac{C_3}{C_4} f_c = 2000.$$

Choosing $f_c = 16\text{kHz}$ (≈ 10 times f_o)

$$\therefore \frac{C_1}{C_2} = 3.125 \quad \text{and} \quad \frac{C_3}{C_4} = 0.125.$$


Let $C_2 = 1\text{pF}$ and $C_4 = 10\text{pF}$ yields $C_1 = 3.125\text{pF}$ and $C_3 = 1.25\text{pF}$



Note the maximum capacitance ratio is 10

Sample Circuits (Cont'd)

Ex. BP Filter

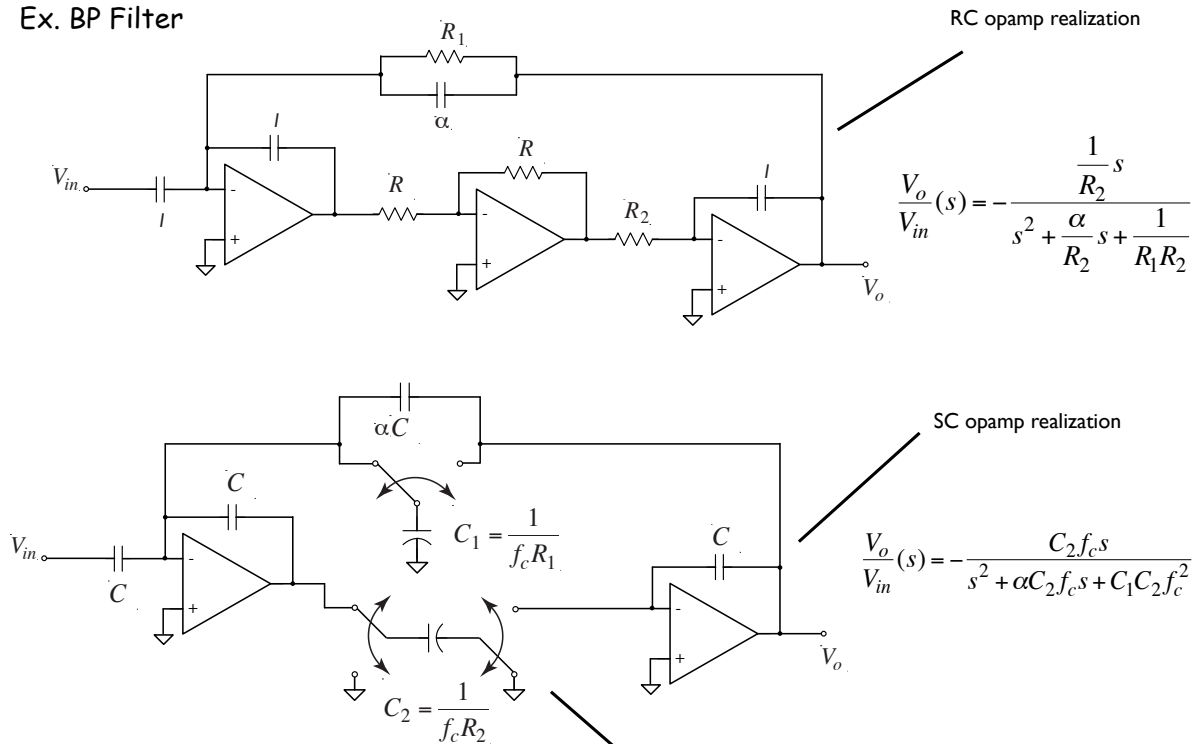

Ex. 2 • Realize a SC BPF with $f_o = 1.59kHz$ and $Q = 5$. The center frequency gain is to be 2.5.

Soln. • Using the previous SC BPF we obtain the following design equations:

$$\omega_o^2 = C_1 C_2 f_c^2$$

$$Q = \frac{1}{\alpha} \sqrt{\frac{C_1}{C_2}}$$

$$CFG = \frac{1}{\alpha}$$

Letting $f_c = 16kHz (\approx 10f_o)$ and solving the above equations, yields

$$\alpha = 0.4$$

$$C_1 = 1.25$$


$$C_2 = 0.3125$$

We may scale by 10^{12} to yield $C_1 = 1.25 pF, C_2 = 0.3125 pF, C = 1 pF$ and $\alpha C = 0.4 pF$. Note the maximum capacitance ratio is 4.0, which is practical.



A Useful Circuit - The Sample & Hold

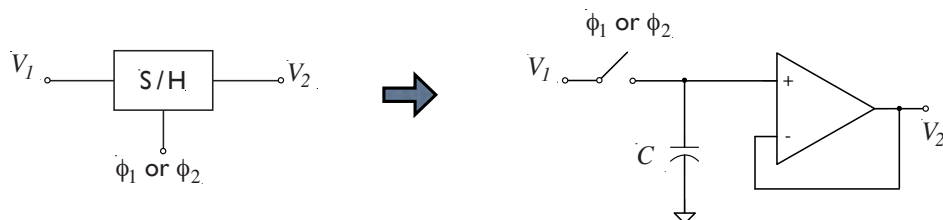
- The sample and hold provides a means for delaying the input or the output of a circuit by half a clock delay in a two phase clock system.
- The simplest sample and hold is an opamp configured as a buffer with a switch clocked on either of the two clock phases and a holding capacitor. Other more elaborate schemes exist.



- In the z - domain $V_2(z) = z^{-\frac{1}{2}} V_1(z)$ regardless of the clock phasing.



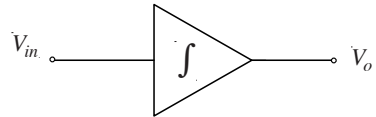Numerical Integration and the s-to-z transformation



$$v_o(t) = \int_{-\infty}^t v_{in}(t) dt = \int_{-\infty}^{t_o} v_{in}(t) dt + \int_{t_o}^t v_{in}(t) dt$$

$$= v_o(t_o) + \text{Area under the } v_{in}(t) \text{ curve from } t_o \rightarrow t$$

- In the frequency domain this can be expressed as,

$$V_o(s) = \frac{1}{s} V_{in}(s) \quad \text{or} \quad \frac{V_o(s)}{V_{in}(s)} = \frac{1}{s}$$

Numerically we can calculate $v_o(t)$ by


$$v_o(nT) = v_o(nT - T) + \text{Area}$$

- There are four well known methods of area calculation

Note others exist!




Four methods of discrete integration

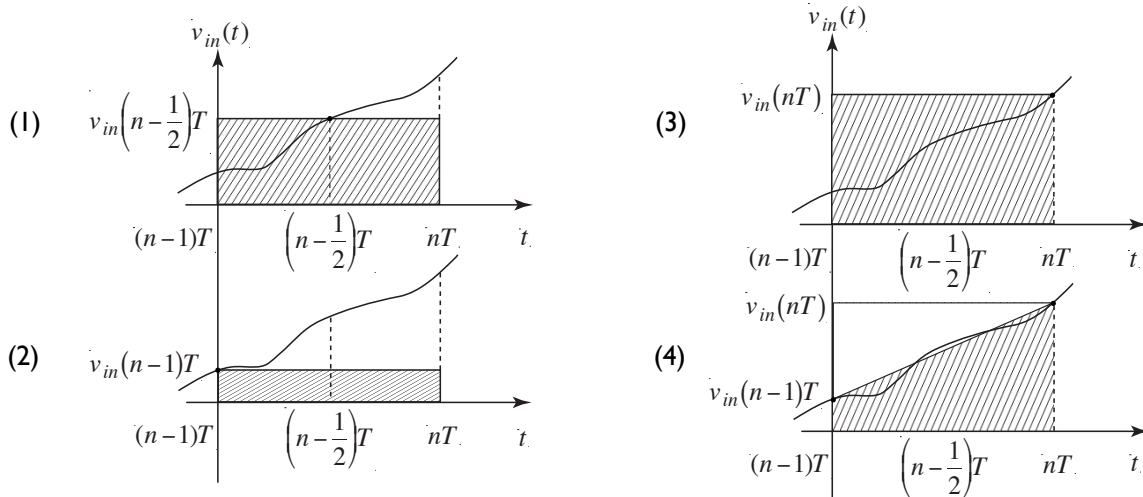

1. Middle Point Integrator or Lossless Discrete Integration (LDI)
2. Forward Euler Discrete Integration (FEDI)
3. Backward Euler Discrete Integration (BEDI)
4. Bilinear Discrete Integration (BDI) or Trapezoidal Integration Rule



Middle Point Integrator

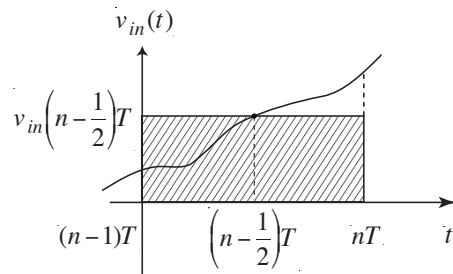

- Area = $Tv_{in}\left(nT - \frac{T}{2}\right)$. Thus $v_o(nT) = v_o(nT - T) + Tv_{in}\left(nT - \frac{T}{2}\right)$

Taking z - transforms

$$V_o(z) = z^{-1}V_o(z) + Tz^{-\frac{1}{2}}V_{in}(z)$$


$$\therefore \frac{V_o(z)}{V_{in}(z)} = T \frac{z^{-\frac{1}{2}}}{1 - z^{-1}} \Leftrightarrow \frac{V_o(s)}{V_{in}(s)} = \frac{1}{s}$$

The corresponding s - to - z transform is then obtained as

$$s = \frac{1}{T} \frac{(1 - z^{-1})}{z^{-\frac{1}{2}}} = \frac{1}{T} \left(z^{\frac{1}{2}} - z^{-\frac{1}{2}} \right)$$



Forward Euler Integrator

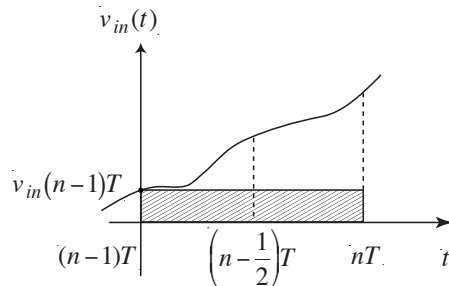

- Area = $Tv_{in}(nT - T)$. Thus $v_o(nT) = v_o(nT - T) + Tv_{in}(nT - T)$

Taking z - transforms

$$V_o(z) = z^{-1}V_o(z) + Tz^{-1}V_{in}(z)$$


$$\therefore \frac{V_o(z)}{V_{in}(z)} = T \frac{z^{-1}}{1 - z^{-1}} \Leftrightarrow \frac{V_o(s)}{V_{in}(s)} = \frac{1}{s}$$

The corresponding s - to - z transform is then obtained as

$$s = \frac{1}{T} \frac{(1 - z^{-1})}{z^{-1}} = \frac{1}{T} (z - 1)$$



Backward Euler Integrator

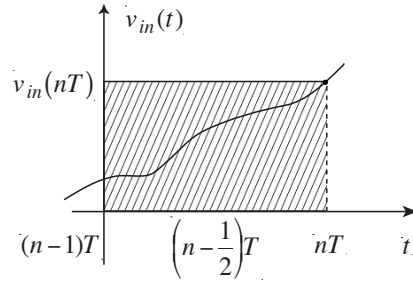

- Area = $Tv_{in}(nT)$. Thus $v_o(nT) = v_o(nT - T) + Tv_{in}(nT)$

Taking z - transforms

$$V_o(z) = z^{-1}V_o(z) + TV_{in}(z)$$


$$\therefore \frac{V_o}{V_{in}}(z) = T \frac{1}{1 - z^{-1}} \Leftrightarrow \frac{V_o}{V_{in}}(s) = \frac{1}{s}$$

The corresponding s - to - z transform is then obtained as

$$s = \frac{1}{T}(1 - z^{-1})$$



Bilinear Discrete Integrator

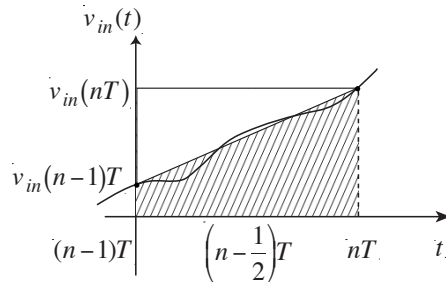

- Area of the trapezoid = $\frac{T}{2}[v_{in}(nT - T) + v_{in}(nT)]$.

$$\text{Thus } v_o(nT) = v_o(nT - T) + \frac{T}{2}[v_{in}(nT - T) + v_{in}(nT)]$$

Taking z - transforms

$$V_o(z) = z^{-1}V_o(z) + \frac{T}{2}[V_{in}(z) + z^{-1}V_{in}(z)]$$

$$\therefore \frac{V_o}{V_{in}}(z) = \frac{T}{2} \cdot \frac{1 + z^{-1}}{1 - z^{-1}} \Leftrightarrow \frac{V_o}{V_{in}}(s) = \frac{1}{s}$$

The corresponding s - to - z transform is then obtained as

$$s = \frac{2}{T} \left(\frac{1 - z^{-1}}{1 + z^{-1}} \right)$$



Bilinear Discrete Integrator (Cont'd)

$$s = \frac{2}{T} \left(\frac{1 - z^{-1}}{1 + z^{-1}} \right) \Leftrightarrow z = \frac{1 + \frac{sT}{2}}{1 - \frac{sT}{2}}$$


For $s = j\Omega$ and $z = re^{j\omega T}$

$$re^{j\omega T} = \frac{1 + \frac{j\Omega T}{2}}{1 - \frac{j\Omega T}{2}}$$

$$\therefore r = 1, \text{ and } \omega = \frac{2}{T} \tan^{-1} \left(\frac{\Omega T}{2} \right)$$

$$\text{If } s = -\sigma \pm j\Omega \rightarrow |r| < 1$$

$$\text{If } s = +\sigma \pm j\Omega \rightarrow |r| > 1$$

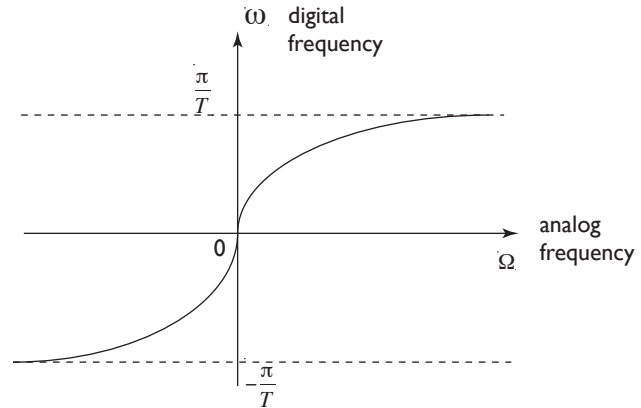

- We have distortion in the digital frequency domain
- Prewarping the digital frequency can compensate for this

8 - 33

Another Transform and Summary

- There exists the impulse-invariance transform which is popular due to its simplicity.
- $z = e^{sT}$ or $s = \frac{1}{T} \ln(z)$

Summary

$$z_1 = \frac{1}{1 - sT}, \quad \text{Backward Euler}$$

$$z_2 = 1 + sT, \quad \text{Forward Euler}$$

$$z_3 = \frac{1 + \frac{sT}{2}}{1 - \frac{sT}{2}}, \quad \text{Bilinear}$$

$$z_4 = e^{sT}, \quad \text{Impulse Invariance}$$



For high sampling rates $sT < 1$

$$z_1 = 1 + sT + (sT)^2 + (sT)^3 + \dots \cong 1 + sT$$

$$z_2 = 1 + sT,$$

$$z_3 = 1 + sT + \frac{(sT)^2}{2} + \frac{(sT)^3}{4} + \dots \cong 1 + sT$$

$$z_4 = 1 + sT + \frac{(sT)^2}{2} + \frac{(sT)^3}{6} + \dots \cong 1 + sT$$



8 - 34

Errors associated with the Discrete Integrators

- Errors exist with each integrator
- Ideal integrator should have zero magnitude and phase error

$$H_I(\omega) = H(s)|_{s=j\omega} = \frac{1}{j\omega}$$

- Let us assume each integrator has a magnitude error ε and phase error θ associated with it. That is,

$$H_{NI}(\omega) = \frac{1}{j\omega} (1 + \varepsilon) e^{j\theta} \quad (3)$$

For the LDI

$$H(z) = T \frac{z^{-\frac{1}{2}}}{1 - z^{-1}} = \frac{T}{z^{\frac{1}{2}} - z^{-\frac{1}{2}}}$$

$$H(e^{j\omega T}) = \frac{T}{e^{j\frac{\omega T}{2}} - e^{-j\frac{\omega T}{2}}} \quad (4)$$

Equating (3) and (4)

$$\frac{1}{j\omega} (1 + \varepsilon) e^{j\theta} = \frac{T}{e^{j\frac{\omega T}{2}} - e^{-j\frac{\omega T}{2}}}$$

$$= \frac{1}{j\omega} \left(\frac{\omega T}{2} \operatorname{Cosec} \left(\frac{\omega T}{2} \right) \right)$$

$$\therefore \varepsilon = \frac{\omega T}{2} \operatorname{Cosec} \left(\frac{\omega T}{2} \right) - 1$$

$$\theta = 0$$







Errors associated with the Discrete Integrators (Cont'd)

	Magnitude Error (ε)	Phase Error (θ)
LDI	$\frac{\omega T}{2} \operatorname{Cosec} \left(\frac{\omega T}{2} \right) - 1$	0
FEDI	$\frac{\omega T}{2} \operatorname{Cosec} \left(\frac{\omega T}{2} \right) - 1$	$-\frac{\omega T}{2}$
BEDI	$\frac{\omega T}{2} \operatorname{Cosec} \left(\frac{\omega T}{2} \right) - 1$	$+\frac{\omega T}{2}$
BDI	$\frac{\omega T}{2} \operatorname{Cot} \left(\frac{\omega T}{2} \right) - 1$	0

- Because $\theta = 0$ (for LDI) Dr. Bruton called this integrator the Lossless Discrete Integrator. Note the LDI has no real part.
- For high sampling rates all errors are low.




Summary

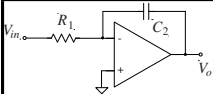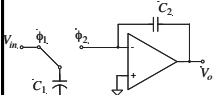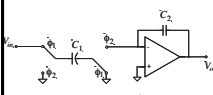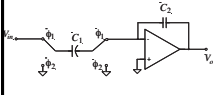Type of Integrator	Magnitude $ H(e^{j\omega T}) $	Phase $\text{Arg}(H(e^{j\omega T}))$	Mapping (Equivalent)	Transfer Function
	$\frac{\omega_o}{\omega}$	$\frac{\pi}{2}$	In the s-plane	$H(s) = -\frac{1}{sR_1C_2} = -\frac{\omega_o}{s}$
 Inverting Stray-sensitive (Forward)	For V_o at ϕ_2 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$	$\frac{\pi}{2}$	LDI	$H(z) = -\frac{C_1}{C_2} \frac{z^{-1/2}}{1 - z^{-1}}$
	For V_o at ϕ_1 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$	$\frac{\pi}{2} - \frac{\omega T}{2}$	Forward	$H(z) = -\frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}}$
 Non-Inverting	For V_o at ϕ_2 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$	$-\frac{\pi}{2}$	LDI	$H(z) = \frac{C_1}{C_2} \frac{z^{-1/2}}{1 - z^{-1}}$
	For V_o at ϕ_1 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$	$-\frac{\pi}{2} - \frac{\omega T}{2}$	Forward	$H(z) = \frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}}$
 Inverting (Backward)	For V_o at ϕ_1 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$	$\frac{\pi}{2} + \frac{\omega T}{2}$	Backward	$H(z) = -\frac{C_1}{C_2} \frac{1}{1 - z^{-1}}$
	For V_o at ϕ_2 $\frac{\omega_o}{\omega} \left(\frac{\omega T/2}{\sin(\omega T/2)} \right)$	$\frac{\pi}{2}$	LDI	$H(z) = -\frac{C_1}{C_2} \frac{z^{-1/2}}{1 - z^{-1}}$



Impulse Invariance Mapping

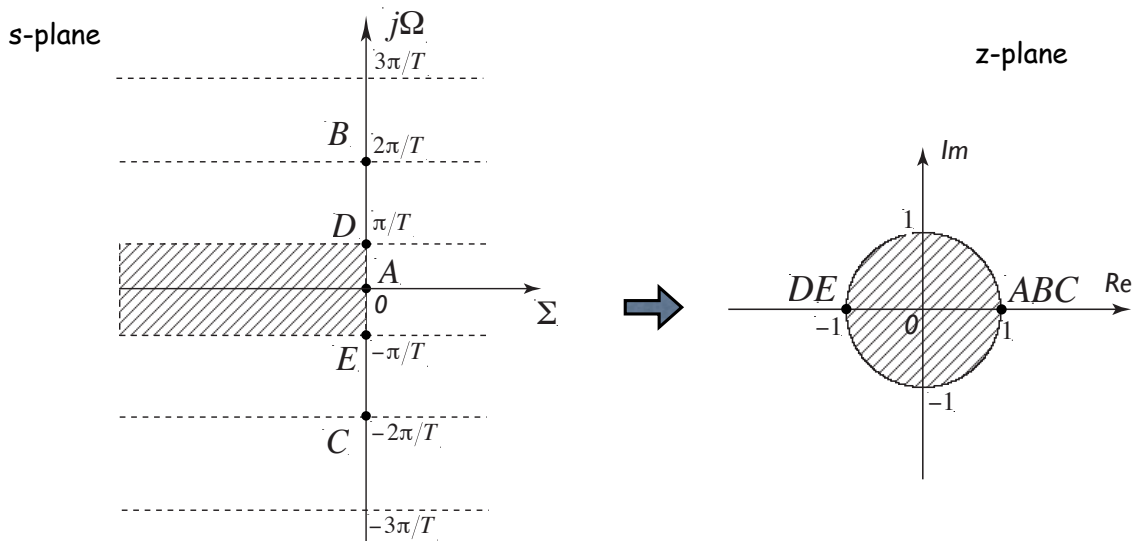


- A strip of length $2\pi/T$ is wrapped once around the unit circle
- Method is only applicable to filters with a bandlimited analog frequency response that satisfies $|H(j\Omega)| \equiv 0$ for $|\Omega| > \Omega_B$




Backward Euler Mapping

s-plane

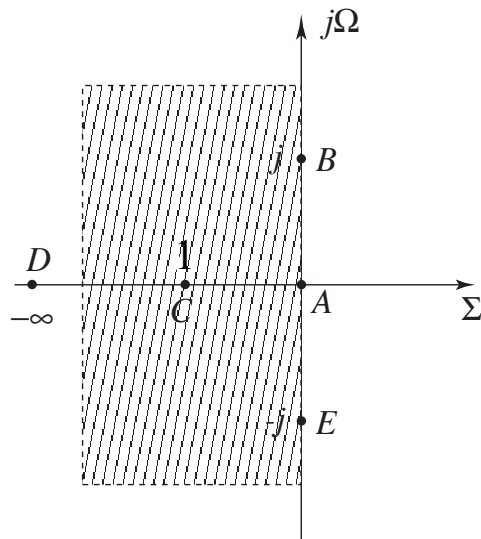

z-plane

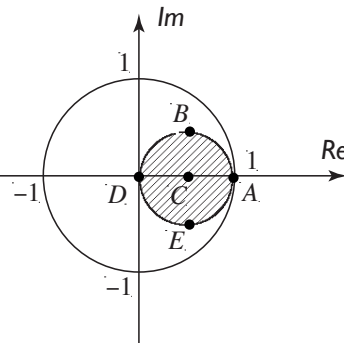


- Poles in the LHP map to a circle of center $1/2$ and radius $1/2$
- Integrator has good performance for low frequency signals. That is signals with discrete frequency close to 1.
- For high frequencies it performs poorly.




8 - 39

Forward Euler Mapping

s-plane

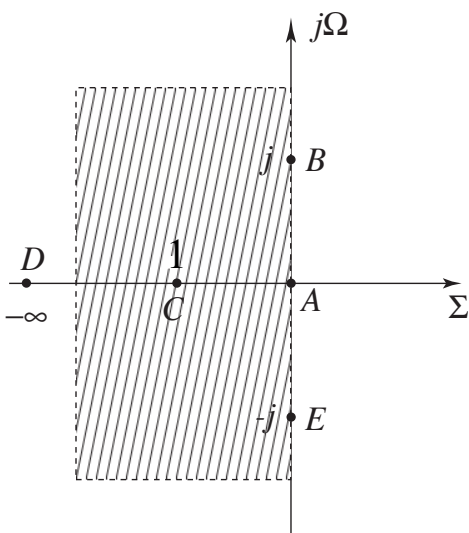

z-plane

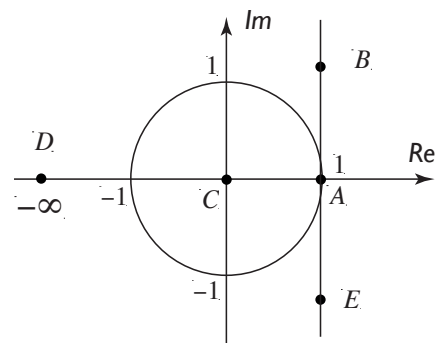


- Like the BEDI this integrator works well with low frequency signals.
- It is possible for points to be mapped outside the unit circle yielding an unstable system.




8 - 40

Bilinear Mapping

s-plane

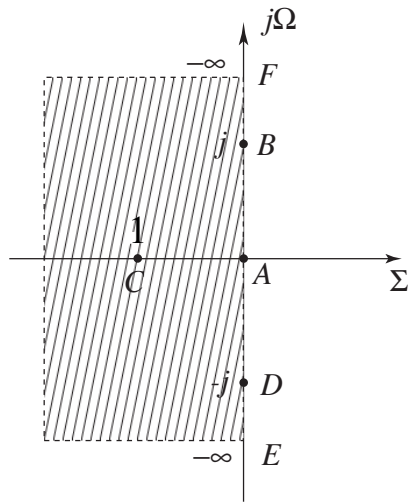

z-plane

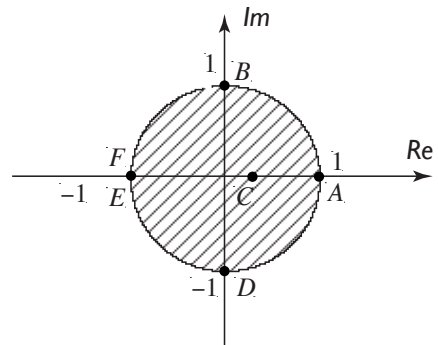


- Points all along the $j\omega$ axis are mapped to the unit circle.



Midpoint Integration

LDI Transformation
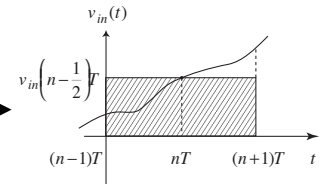
$$s_a = \frac{z^2 - 1}{2Tz} = \frac{1}{2} \left(\frac{z-1}{T} + \frac{z-1}{Tz} \right)$$



Forward Euler

Backward Euler

$$z_{1,2} = s_a T \pm \sqrt{(s_a T)^2 + 1}$$


$$\Rightarrow z_1 \cdot z_2 = \left(s_a T + \sqrt{(s_a T)^2 + 1} \right) \cdot \left(s_a T - \sqrt{(s_a T)^2 + 1} \right) = -1$$

$$\Rightarrow z_1 = -\frac{1}{z_2}$$

- If $|z_2| > 1$ then $|z_1| < 1$ and vice versa
- A stable pole s_a will transform into one stable and one unstable pole in the z -plane
- This implies $H_a(s_a)$ will not transform into a stable $H(z)$
- However, the LDI is still useful in understanding the operation of SCFs based on the LDI transformation



Midpoint Integration Cont'd

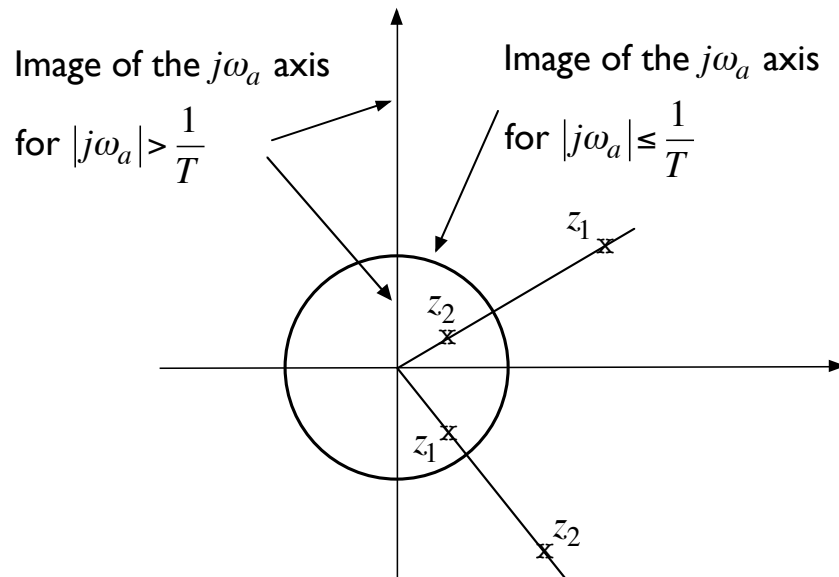



SC Analysis using Charge Equations

The principle of charge conservation can be used to analyze SC circuits.

- Useful guidelines
 1. Charge at the present time = Charge at the instant before + Charge Injected.
 2. If the output is to be evaluated at time $nT - T/2$ draw the circuit at time $(nT - T/2)$ and at $(nT - T)$. Similarly if the output is to be evaluated at time (nT) draw the circuit at time (nT) and at $(nT - T/2)$.
 3. If the polarity of the capacitor injecting charge into another has the same polarity as the one receiving the charge use a -ve sign in the charge equation otherwise use a +ve sign.

The Middle Point Integrator (Parasitic sensitive)

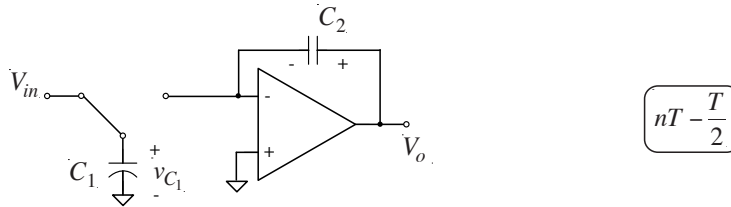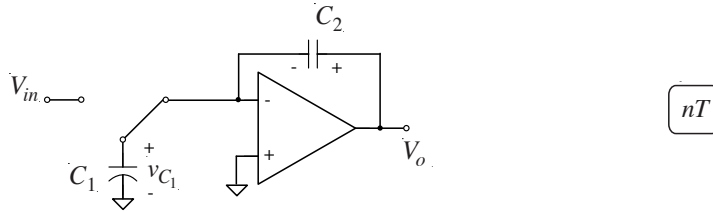- We wish to evaluate $\frac{V_o}{V_{in}}(z)$ at an instant we designate as nT



- Assuming a $+ \rightarrow -$ current flow



$$\boxed{nT - \frac{T}{2}} \quad C_2 v_o \left(nT - \frac{T}{2} \right) = C_2 v_o(nT - T) + 0 \quad (\text{Zero charge Injected}) \quad (5)$$

8 - 45

The Middle Point Integrator (Cont'd)

$$\boxed{nT} \quad C_2 v_o(nT) = C_2 v_o \left(nT - \frac{T}{2} \right) + C_1 \left[v_{C_1}(nT) - v_{C_1} \left(nT - \frac{T}{2} \right) \right]$$

but $v_{C_1}(nT) = 0$ and $v_{C_1} \left(nT - \frac{T}{2} \right) = v_{in} \left(nT - \frac{T}{2} \right)$

$$\Rightarrow C_2 v_o(nT) = C_2 v_o \left(nT - \frac{T}{2} \right) - C_1 v_{in} \left(nT - \frac{T}{2} \right) \quad (6)$$

Substituting (5) in (6) yields

$$C_2 v_o(nT) = C_2 v_o(nT - T) - C_1 v_{in} \left(nT - \frac{T}{2} \right)$$

and taking z - transforms

$$C_2 V_o(z) = C_2 V_o(z) z^{-1} - C_1 V_{in}(z) z^{-\frac{1}{2}}$$



$$\Rightarrow \frac{V_o}{V_{in}}(z) = -\frac{C_1}{C_2} \cdot \frac{z^{-\frac{1}{2}}}{1 - z^{-1}}$$



8 - 46

A Forward Euler Discrete Integrator (PS)

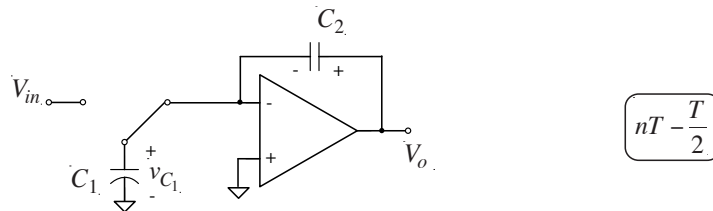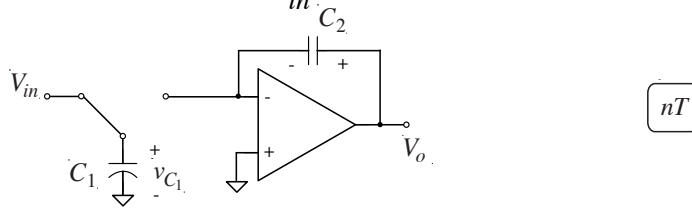- We wish to evaluate $\frac{V_o}{V_{in}}(z)$ at an instant we designate as nT



- Assuming a $+ \rightarrow -$ current flow

$$\boxed{nT} \quad C_2 v_o(nT) = C_2 v_o\left(nT - \frac{T}{2}\right) + 0 \quad (\text{Zero charge Injected}) \quad (7)$$



A Forward Euler Discrete Integrator (PS)-Cont'd

$$C_2 v_o\left(nT - \frac{T}{2}\right) = C_2 v_o(nT - T) + C_1 \left[v_{C_1}\left(nT - \frac{T}{2}\right) - v_{C_1}(nT - T) \right]$$

$$\text{but } v_{C_1}\left(nT - \frac{T}{2}\right) = 0 \text{ and } v_{C_1}(nT - T) = v_{in}(nT - T)$$

$$\Rightarrow C_2 v_o\left(nT - \frac{T}{2}\right) = C_2 v_o(nT - T) - C_1 v_{in}(nT - T) \quad (8)$$

Substituting (7) in (8) yields

$$C_2 v_o(nT) = C_2 v_o(nT - T) - C_1 v_{in}(nT - T)$$

and taking z - transforms


$$C_2 V_o(z) = C_2 V_o(z) z^{-1} - C_1 V_{in}(z) z^{-1}$$

$$\Rightarrow \frac{V_o}{V_{in}}(z) = -\frac{C_1}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}}$$


- Depending on which clock phase the output is sampled the outcome is a parasitic sensitive LDI or FEDI integrator.
- The two outcomes are separated only by half a clock delay.



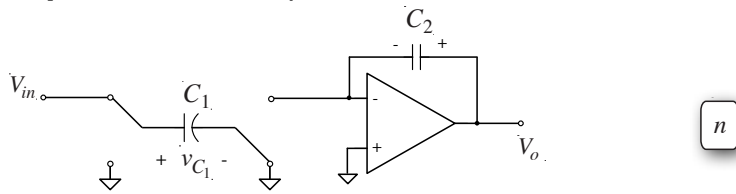A (Stray Insensitive) Forward Euler Discrete Integrator



n

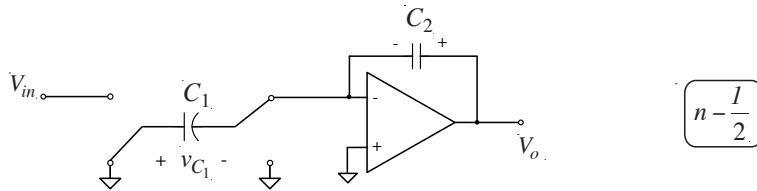

$n - \frac{1}{2}$

$$C_2 v_o(n) = C_2 v_o\left(n - \frac{1}{2}\right) - 0$$

$$C_2 v_o\left(n - \frac{1}{2}\right) = C_2 v_o(n-1) - C_1 \left[v_{C_1}\left(n - \frac{1}{2}\right) - v_{C_1}(n-1) \right]$$

$$\text{but } v_{C_1}\left(n - \frac{1}{2}\right) = 0 \text{ and } v_{C_1}(n-1) = v_{in}(n-1)$$

$$\Rightarrow C_2 v_o(n) = C_2 v_o(n-1) + C_1 v_{in}(n-1)$$

$$\Rightarrow \frac{V_o}{V_{in}}(z) = \frac{C_1}{C_2} \cdot \frac{z^{-1}}{1 - z^{-1}}$$




UNIVERSITY OF CALGARY

8 - 49


Notes

- Output is to be evaluated at time n .
- T can be omitted since it conveys no useful information in the charge equations
- If the output was to be evaluated at time $n-1/2$ instead, the numerator of the answer would be $z^{-1/2}$ instead of z^{-1} . That is the circuit would be non inverting LDI (Stray insensitive).

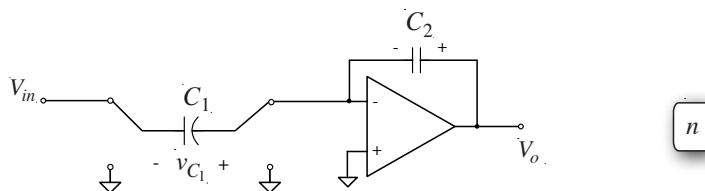A (Stray Insensitive) Backward Euler Discrete Integrator



n

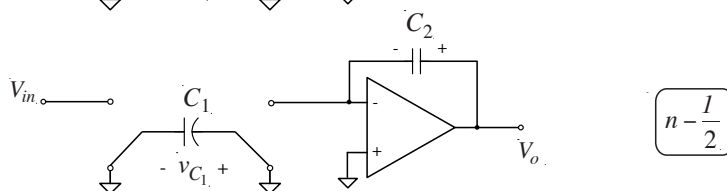

$n - \frac{1}{2}$

$$C_2 v_o(n) = C_2 v_o\left(n - \frac{1}{2}\right) + C_1 \left[v_{C_1}(n) - v_{C_1}\left(n - \frac{1}{2}\right) \right]$$

$$\text{with } v_{C_1}(n) = -v_{in}(n) \text{ and } v_{C_1}\left(n - \frac{1}{2}\right) = 0$$

$$C_2 v_o\left(n - \frac{1}{2}\right) = C_2 v_o(n-1) + 0$$

$$\Rightarrow C_2 v_o(n) = C_2 v_o(n-1) - C_1 v_{in}(n)$$

$$\therefore \frac{V_o}{V_{in}}(z) = -\frac{C_1}{C_2} \cdot \frac{1}{1 - z^{-1}}$$




UNIVERSITY OF CALGARY

8 - 50

Notes

- Output is to be evaluated at time n .
- If the output was to be evaluated at time $n-1/2$ instead, the numerator of the answer would be $z^{-1/2}$ instead of 1 . That is the circuit would be an inverting LDI (Stray insensitive).

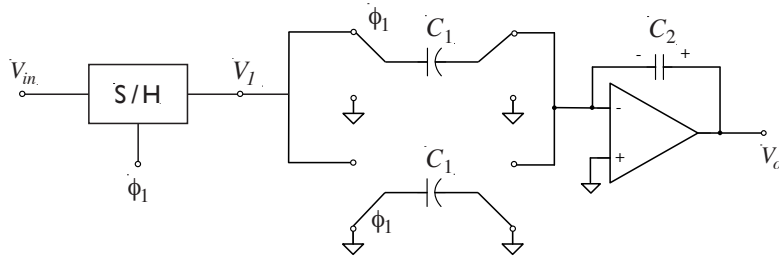A (Stray Insensitive) Bilinear Discrete Integrator



- By superposition the output can be computed by recognizing the presence of a BEDI and a LDI. Loosely speaking therefore,

$$V_o(z) = \{BEDI + LDI\} \cdot V_I(z)$$

$$V_o(z) = \left[-\frac{C_1}{C_2} \cdot \frac{1}{1-z^{-1}} - \frac{C_1}{C_2} \cdot \frac{z^{-\frac{1}{2}}}{1-z^{-1}} \right] \cdot V_I(z)$$


$$= -\frac{C_1}{C_2} \cdot \left[\frac{V_I(z)}{1-z^{-1}} + \frac{V_I(z)z^{-\frac{1}{2}}}{1-z^{-1}} \right]$$

but $V_I(z) = z^{-\frac{1}{2}} V_{in}(z) \Rightarrow V_I(z)z^{-\frac{1}{2}} = z^{-1} V_{in}(z)$

$$\therefore \frac{V_o(z)}{V_{in}(z)} = -\frac{C_1}{C_2} \cdot \left[\frac{1+z^{-1}}{1-z^{-1}} \right]$$



A First Order Building Block

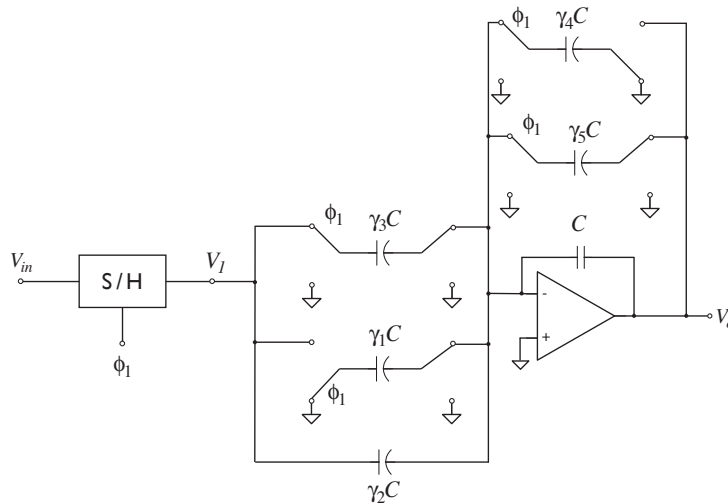

Notes

- All switches discharge into C simultaneously. This eases how fast the opamp has to work.

$$V_o(z) = \left(\frac{\gamma_1 z^{-1}}{1-z^{-1}} - \gamma_2 - \frac{\gamma_3}{1-z^{-1}} \right) V_{in}(z) + \left(\frac{\gamma_4 z^{-1}}{1-z^{-1}} - \frac{\gamma_5}{1-z^{-1}} \right) V_o(z)$$


$$V_o(z) [1 - z^{-1} + \gamma_5 - \gamma_4 z^{-1}] = V_{in}(z) [\gamma_1 z^{-1} - \gamma_2 + \gamma_2 z^{-1} - \gamma_3]$$

$$\frac{V_o}{V_{in}}(z) = \frac{-(\gamma_2 + \gamma_3) + (\gamma_2 + \gamma_1)z^{-1}}{(1 + \gamma_5) - (1 + \gamma_4)z^{-1}}$$

$$= \frac{\alpha_o + \alpha_1 z^{-1}}{\beta_o + \beta_1 z^{-1}}$$



Another First Order Building Block

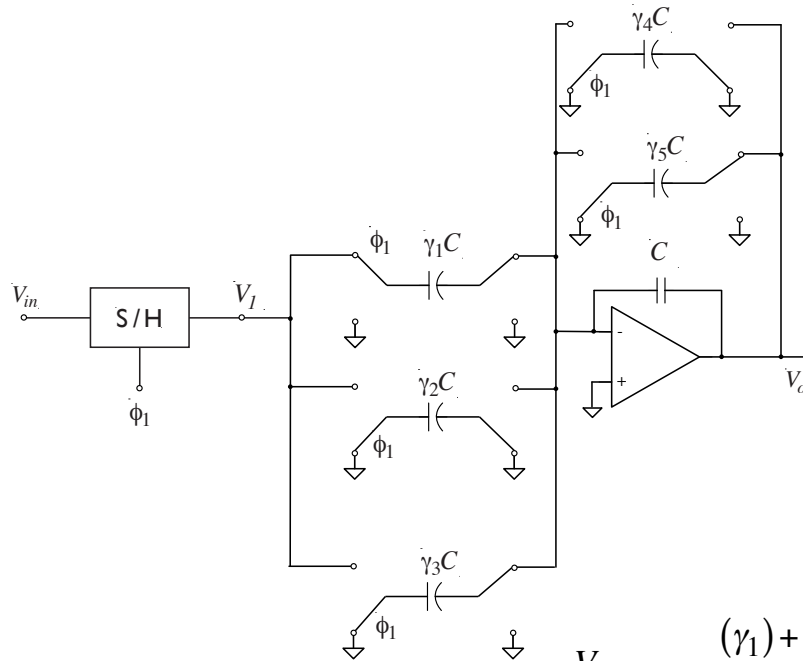

Notes


- Opamp has to work twice as hard.
- Output is available only on one phase

$$\frac{V_o}{V_{in}}(z) = - \frac{(\gamma_1) + \left(\frac{\gamma_2}{1 + \gamma_4} - \gamma_3 \right) z^{-1}}{1 - \left(\frac{1 + \gamma_5}{1 + \gamma_4} \right) z^{-1}}$$



8 - 53

Yet another First Order Building Block

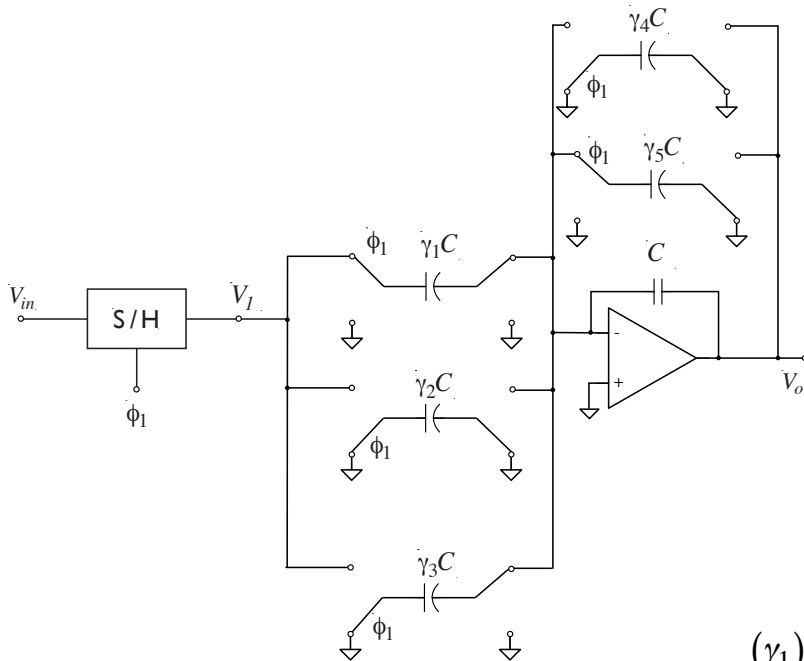

Notes

- Opamp has to work twice as hard.
- Output is available only on one phase

$$\frac{V_o}{V_{in}}(z) = - \frac{(\gamma_1) + \left(\gamma_2 \left(\frac{1 + \gamma_5}{1 + \gamma_4} \right) - \gamma_3 \right) z^{-1}}{1 - \left(\frac{1 + \gamma_5}{1 + \gamma_4} \right) z^{-1}}$$




8 - 54

Signal Flow Graph Analysis

$$\frac{V_o(z)}{V_1} = -\gamma_1$$

$$\frac{V_o(z)}{V_2} = \frac{\gamma_2 z^{-1}}{1 - z^{-1}}$$
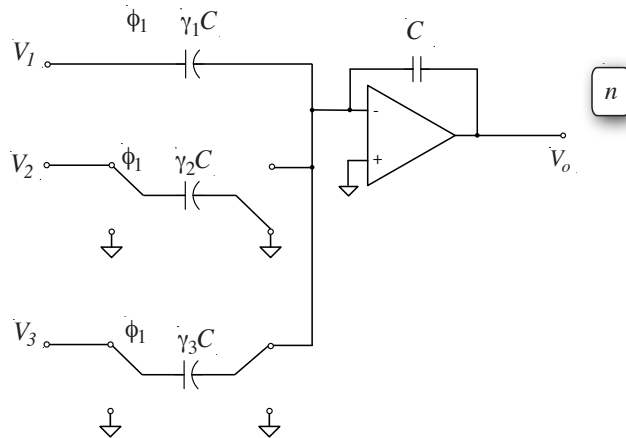
$$\frac{V_o(z)}{V_3} = -\frac{\gamma_3}{1 - z^{-1}}$$




By superposition therefore

$$V_o(z) = \frac{1}{1 - z^{-1}} \left[-\gamma_1 (1 - z^{-1}) V_1(z) + \gamma_2 z^{-1} V_2(z) - \gamma_3 V_3(z) \right]$$




Signal Flow Graph Analysis (Cont'd)

- Equivalent signal flow graph

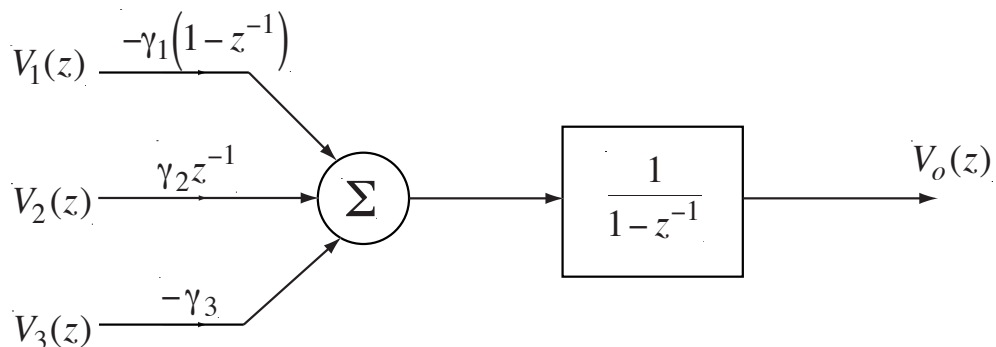


Signal Flow Graph - 1st Order Example


- Active RC Version

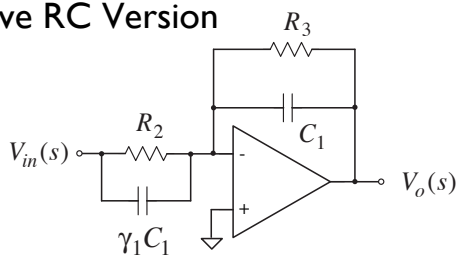

- SC Version

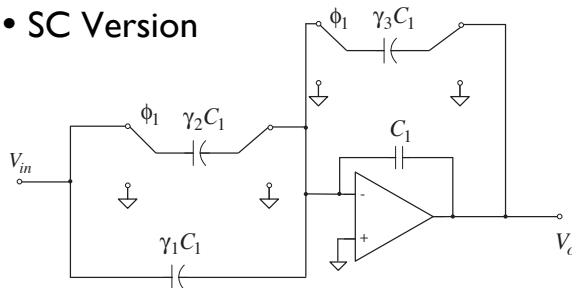


- Signal Flow Graph

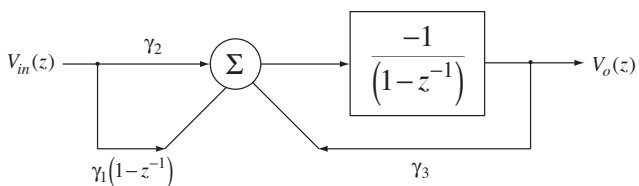

$$\frac{V_o}{V_{in}}(z) = -\frac{\gamma_1 + \gamma_2 - \gamma_1 z^{-1}}{1 + \gamma_3 - z^{-1}}$$



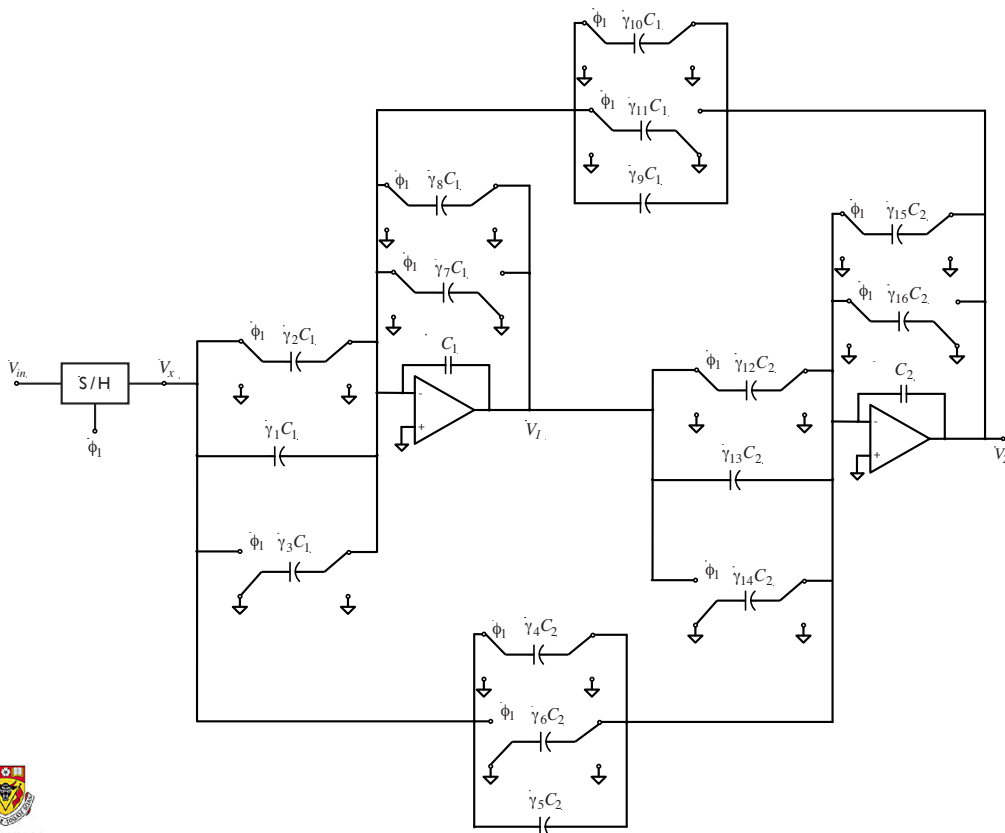General Stray-Insensitive SC Biquad (Dr. El-Masry)



General Stray-Insensitive SC Biquad (Cont'd)

A general SC Biquad can be used to realize the biquadratic transfer function

$$T(z) = \frac{\alpha_0 + \alpha_1 z^{-1} + \alpha_2 z^{-2}}{\beta_0 + \beta_1 z^{-1} + \beta_2 z^{-2}}$$

using two of the SC 1st order building blocks in a feedforward / feedback manner.

For the circuit shown in the figure the equations are:

$$V_1(z) = \left[\frac{\gamma_3 z^{-1}}{1-z^{-1}} - \frac{\gamma_2}{1-z^{-1}} - \gamma_1 \right] V_{in}(z) + \left[\frac{\gamma_7 z^{-1}}{1-z^{-1}} - \frac{\gamma_8}{1-z^{-1}} \right] V_1(z) + \left[\frac{\gamma_{11} z^{-1}}{1-z^{-1}} - \frac{\gamma_{10}}{1-z^{-1}} - \gamma_9 \right] V_2(z)$$

and

$$V_2(z) = \left[\frac{\gamma_{14} z^{-1}}{1-z^{-1}} - \frac{\gamma_{12}}{1-z^{-1}} - \gamma_{13} \right] V_1(z) + \left[\frac{\gamma_{16} z^{-1}}{1-z^{-1}} - \frac{\gamma_{15}}{1-z^{-1}} \right] V_2(z) + \left[\frac{\gamma_6 z^{-1}}{1-z^{-1}} - \frac{\gamma_4}{1-z^{-1}} - \gamma_5 \right] V_{in}(z)$$



General Stray-Insensitive SC Biquad (Cont'd)

$$T_1(z) = \frac{V_1}{V_{in}}(z) = \frac{a_0 + a_1 z^{-1} + a_2 z^{-2}}{c_0 + c_1 z^{-1} + c_2 z^{-2}} \quad \text{and} \quad T_2(z) = \frac{V_2}{V_{in}}(z) = \frac{b_0 + b_1 z^{-1} + b_2 z^{-2}}{c_0 + c_1 z^{-1} + c_2 z^{-2}}$$

where

$$a_0 = (\gamma_4 + \gamma_5)(\gamma_9 + \gamma_{10}) - (\gamma_1 + \gamma_2)(1 + \gamma_{15})$$

$$a_1 = (\gamma_1 + \gamma_2)(1 + \gamma_{16}) + (\gamma_1 + \gamma_3)(1 + \gamma_{15}) - (\gamma_4 + \gamma_5)(\gamma_9 + \gamma_{11}) - (\gamma_5 + \gamma_6)(\gamma_9 + \gamma_{10})$$

$$a_2 = (\gamma_5 + \gamma_6)(\gamma_9 + \gamma_{11}) - (\gamma_1 + \gamma_3)(1 + \gamma_{16})$$

$$b_0 = (\gamma_1 + \gamma_2)(\gamma_{12} + \gamma_{13}) - (\gamma_4 + \gamma_5)(1 + \gamma_8)$$

$$b_1 = (\gamma_4 + \gamma_5)(1 + \gamma_7) + (\gamma_5 + \gamma_6)(1 + \gamma_8) - (\gamma_1 + \gamma_2)(\gamma_{13} + \gamma_{14}) - (\gamma_1 + \gamma_3)(\gamma_{12} + \gamma_{13})$$

$$b_2 = (\gamma_1 + \gamma_3)(\gamma_{13} + \gamma_{14}) - (\gamma_5 + \gamma_6)(1 + \gamma_7)$$

$$c_0 = (1 + \gamma_8)(1 + \gamma_{15}) - (\gamma_9 + \gamma_{10})(\gamma_{12} + \gamma_{13})$$

$$c_1 = (\gamma_9 + \gamma_{11})(\gamma_{12} + \gamma_{13}) + (\gamma_9 + \gamma_{10})(\gamma_{13} + \gamma_{14}) - (1 + \gamma_7)(1 + \gamma_{15}) - (1 + \gamma_8)(1 + \gamma_{16})$$

$$c_2 = (1 + \gamma_7)(1 + \gamma_{16}) - (\gamma_9 + \gamma_{11})(\gamma_{13} + \gamma_{14})$$

The equivalent analog pole frequency ω_o and pole Q are given by


$$\omega_o = 2f_c \sqrt{\frac{c_0 + c_1 + c_2}{c_0 - c_1 - c_2}} \quad \text{and} \quad Q = \frac{\sqrt{(c_0 + c_1 + c_2)(c_0 - c_1 + c_2)}}{2(c_0 - c_1)}$$

where f_c is the clock frequency.

- Note ω_o and Q are obtained by using the bilinear z -transform



Simplified version of the General Biquad

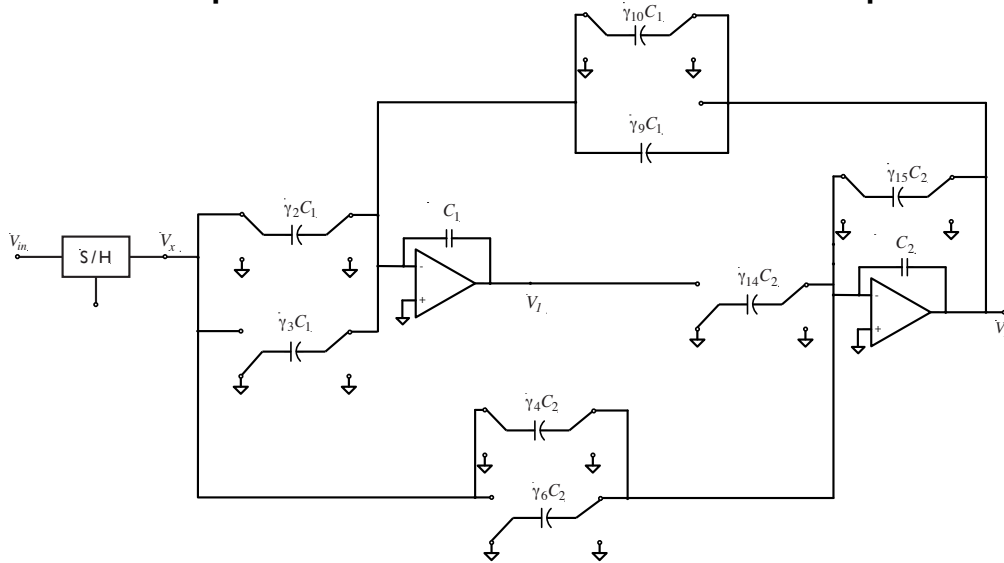

Let us set $\gamma_1 = \gamma_5 = \gamma_7 = \gamma_8 = \gamma_{11} = \gamma_{12} = \gamma_{13} = \gamma_{16} = 0$. Then

$$T_1(z) = \frac{V_1}{V_{in}}(z) = \frac{[\gamma_4(\gamma_9 + \gamma_{10}) - \gamma_2(1 + \gamma_{15})] + [\gamma_2 + \gamma_3(1 + \gamma_{15}) - \gamma_6\gamma_{10} - \gamma_9(\gamma_4 + \gamma_6)]z^{-1} + [\gamma_6\gamma_9 - \gamma_3]z^{-2}}{D(z)}$$


$$T_2(z) = \frac{V_2}{V_{in}}(z) = \frac{-\gamma_4 + [\gamma_2\gamma_{14} - \gamma_4 - \gamma_6]z^{-1} + [-\gamma_3\gamma_{14} + \gamma_6]z^{-2}}{D(z)}$$

where

$$D(z) = (1 + \gamma_{15}) + [\gamma_{14}(\gamma_9 + \gamma_{10}) - \gamma_{15} - 2]z^{-1} + [1 - \gamma_9\gamma_{14}]z^{-2}$$



A SC Low Q Biquad ($Q < 1$)

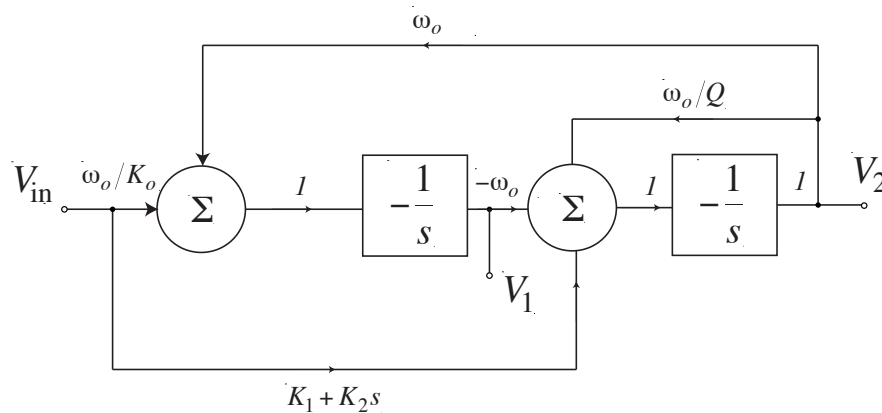


$$V_2(s) = -\frac{1}{s} \left[(k_1 + k_2 s) V_{in}(s) + \frac{\omega_o}{Q} V_2(s) - \omega_o V_1 \right]$$

and

$$V_1(s) = -\frac{1}{s} \left[\frac{k_0}{\omega_o} V_{in}(s) + \omega_o V_2 \right]$$



A SC Low Q Biquad ($Q < 1$)-Cont'd

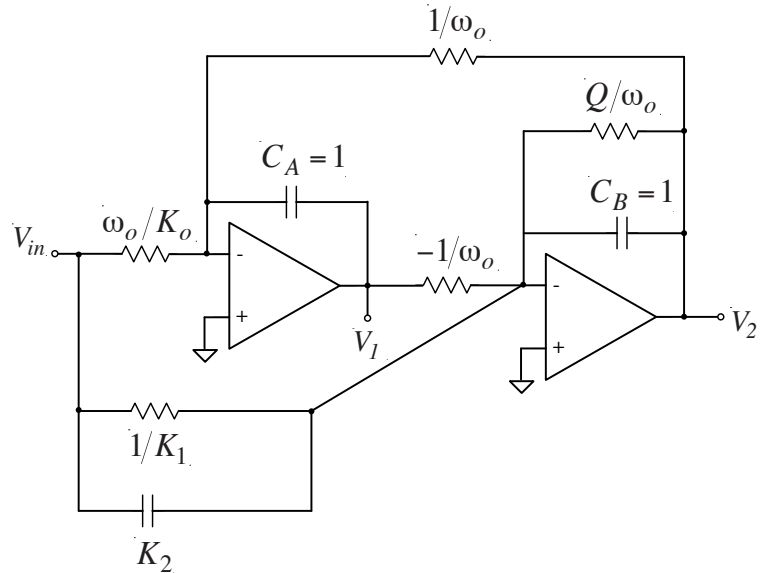


- Note the presence of the negative resistor $-1/\omega_o$ making it not practical as an active RC filter.



8 - 63

A SC Low Q Biquad ($Q < 1$)-Cont'd

SC Equivalent with switch sharing

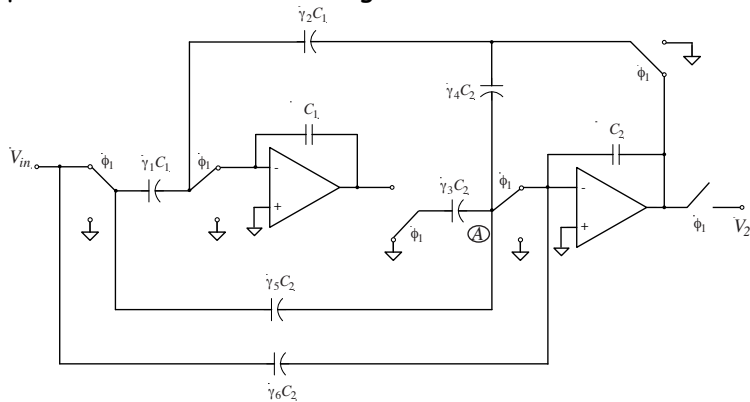

$$\gamma_1 \approx \frac{TK_o}{\omega_o} = |H_a(0)|\omega_o T$$


$$\gamma_2 \approx \gamma_3 \approx \omega_o T$$

$$\gamma_4 \approx \frac{\omega_o T}{Q}$$

$$\gamma_5 \approx K_1 T$$

$$\gamma_6 \approx K_2$$

Signal Flow Graph

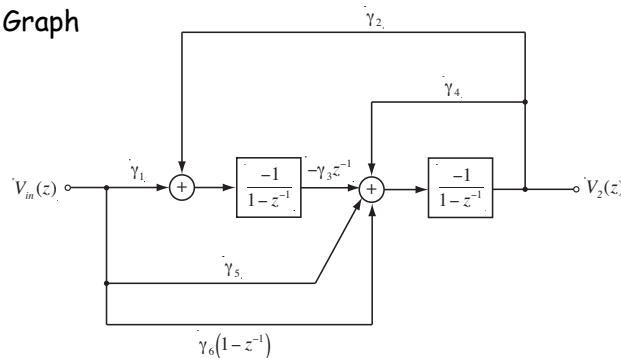

8 - 64

A SC Low Q Biquad ($Q < 1$)-Cont'd

- Note for low Q the capacitance spread $\frac{C_{\max}}{C_{\min}} = \frac{1}{\omega_o T} = \frac{1}{\gamma_2}$

and for frequencies of interest $\omega \ll \omega_c \Rightarrow |\omega_o T| \ll 1$

so that the capacitance spread will be large.

- The direct z -transfer function of the circuit is given by

$$H(z) = \frac{(\gamma_5 + \gamma_6)z^2 + (\gamma_1\gamma_3 - \gamma_5 - 2\gamma_6)z + \gamma_6}{(1 + \gamma_4)z^2 + (\gamma_2\gamma_3 - \gamma_4 - 2)z + 1}$$

$$= \frac{a_2z^2 + a_1z + a_0}{b_2z^2 + b_1z + b_0}$$

$$\Rightarrow \gamma_6 = a_0$$

$$\gamma_5 = a_2 - \gamma_6 = a_2 - a_0$$

$$\gamma_1 = \left(\frac{1}{\gamma_3}\right)(a_1 + \gamma_5 + 2\gamma_6) = \frac{a_0 + a_1 + a_2}{\gamma_3}$$

$$\gamma_4 = b_2 - 1$$

$$\gamma_2\gamma_3 = b_1 + 2 + \gamma_4 = b_1 + b_2 + 1$$

6 unknown values and
5 relations. One
minimization
constraint is to
choose

$$\gamma_2 = \gamma_3 = \sqrt{b_1 + b_2 + 1}$$



A SC Low Q Biquad ($Q < 1$)-Cont'd

Possible Realizations of the low-Q Biquad

Lowpass $\gamma_5 = \gamma_6 = 0$

Highpass $\gamma_1 = \gamma_5 = 0$

Bandpass $\gamma_5 = 0$


Notch $\gamma_1 = \gamma_6 = 0$

Allpass realizations are possible if an inverting SC branch is added between the input terminal and node A with γ_5 removed.




A SC High Q Biquad

- Active RC Version

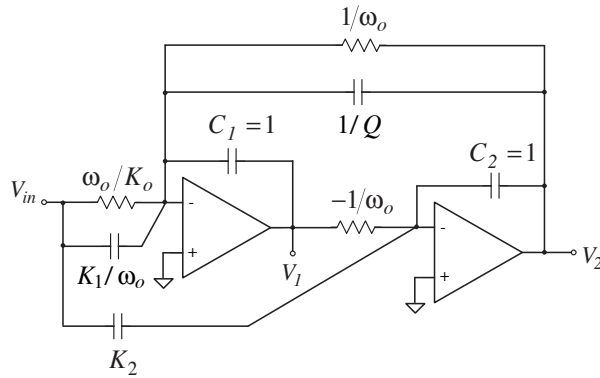


$$H(s) = \frac{V_2}{V_{in}}(s) = -\frac{K_2 s^2 + K_1 s + K_o}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2}$$

- SC Version

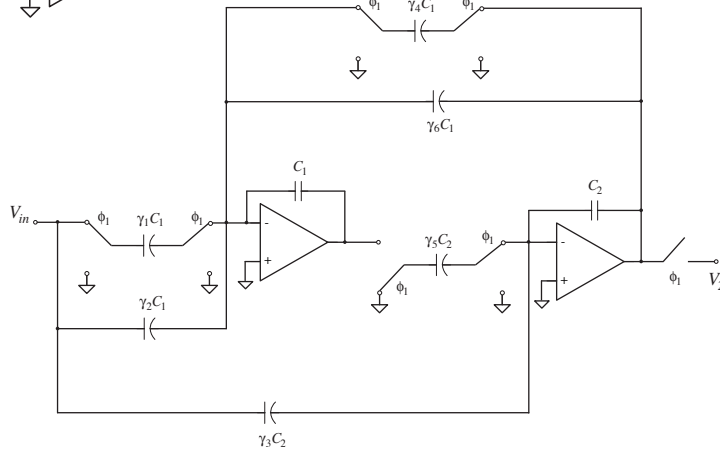

A SC High Q Biquad (Cont'd)

- Signal Flow Graph

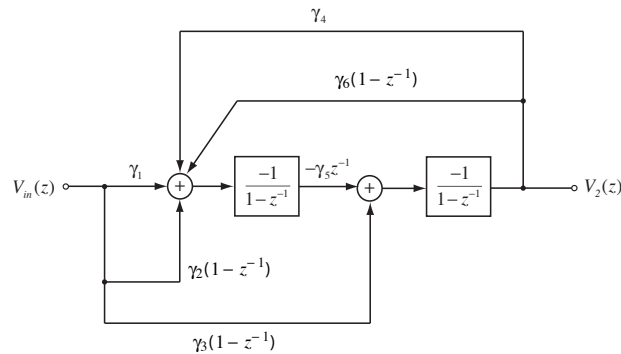

$$H(z) = \frac{V_2}{V_{in}}(z) = -\frac{\gamma_3 z^2 + (\gamma_1 \gamma_5 + \gamma_2 \gamma_5 - 2\gamma_3)z + (\gamma_3 - \gamma_2 \gamma_5)}{z^2 + (\gamma_4 \gamma_5 + \gamma_5 \gamma_6 - 2)z + (1 - \gamma_5 \gamma_6)} = -\frac{a_2 z^2 + a_1 z + a_o}{z^2 + b_1 z + b_o}$$

$$\gamma_3 = a_2$$

$$\gamma_2 \gamma_5 = a_2 - a_o$$

$$\gamma_1 \gamma_5 = a_o + a_1 + a_2$$

$$\gamma_5 \gamma_6 = 1 - b_o$$

$$\gamma_4 \gamma_5 = 1 + b_1 + b_o$$



SC Filter Design Strategy using the Bilinear z-transform

Given the specifications of the SC filter in terms of the discrete frequency (ω) the following is a step by step design strategy:

- Prewarp the specs using the equation $\Omega = 2f_s \tan\left(\frac{\omega}{2f_s}\right)$ to obtain the continuous time specs.
- Using available tables or formula for the continuous time filter (e.g. Butterworth Chebychev, Cauer, etc) obtain $H(s)$ that meets the analog specs
- Apply the Bilinear z - transform $s = 2f_s \cdot \frac{1-z^{-1}}{1+z^{-1}}$ to the analog transfer function $H(s)$ to obtain the discrete time function $H(z)$,

$$H(z) = H(s) \Big|_{s=2f_s \cdot \frac{1-z^{-1}}{1+z^{-1}}}$$

- $H(z)$ can be realized using the cascade approach.




Cascade Realization of SC Filters

- $H(z)$ is realized as a cascade of first and second order SC building blocks.

- For n odd,
$$H(z) = \frac{a_0 + a_1 z^{-1}}{b_0 + b_1 z^{-1}} \cdot \prod_{k=1}^{\frac{n-1}{2}} \frac{\alpha_{0k} + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}}{\beta_{0k} + \beta_{1k} z^{-1} + \beta_{2k} z^{-2}}$$

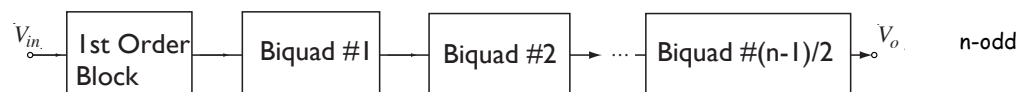- For n even,
$$H(z) = \prod_{k=1}^{\frac{n}{2}} \frac{\alpha_{0k} + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}}{\beta_{0k} + \beta_{1k} z^{-1} + \beta_{2k} z^{-2}}$$



Bilinear z transform of the general biquadratic transfer function

Given $H(s) = \frac{a_0 + a_1s + a_2s^2}{b_0 + b_1s + b_2s^2}$ then

$$H(z) = H(s) \Big|_{s=2f_s \frac{z-1}{z+1}}$$

$$= \frac{\alpha_0 + \alpha_1 z^{-1} + \alpha_2 z^{-2}}{\beta_0 + \beta_1 z^{-1} + \beta_2 z^{-2}}$$

where

$$\alpha_0 = a_0 + 2f_s a_1 + (2f_s)^2 a_2$$

$$\alpha_1 = 2a_0 - 2a_2(2f_s)^2$$

$$\alpha_2 = a_0 - 2f_s a_1 + (2f_s)^2 a_2$$

and

$$\beta_0 = b_0 + 2f_s b_1 + (2f_s)^2 b_2$$

$$\beta_1 = 2b_0 - 2b_2(2f_s)^2$$

$$\beta_2 = b_0 - 2f_s b_1 + (2f_s)^2 b_2$$




8 - 71

SC Design Example using the Cascade approach

- Ex. 3 • Design a SC LP filter with equiripple response in both the passband and the stopband, that meets the attenuation specifications shown below. In your design use a sampling frequency $f_s = 8kHz$.

Soln.

Prewarping the discrete time specs

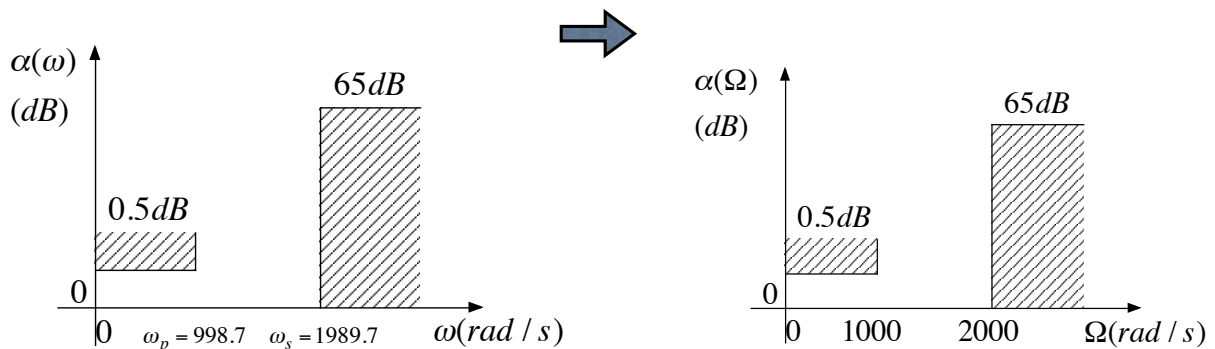

8 - 72

SC Design Example using the Cascade approach (Cont'd)

- From Causer filter tables the desired order is 5th and the normalized transfer function is given by,

$$H(s)_{norm} = \frac{0.0046205}{s + 0.392612} \cdot \frac{s^2 + 4.36495}{s^2 + 0.19255s + 1.03402} \cdot \frac{s^2 + 10.56773}{s^2 + 0.58054s + 0.525}$$

$$\Rightarrow H(s) = H(s)_{norm} \Big|_{s=\frac{s}{1000}}$$

$$\therefore H(s) = \frac{4.6205}{s + 3926.12} \cdot \frac{s^2 + 4.36495 \times 10^6}{s^2 + 192.55s + 1.03402 \times 10^6} \cdot \frac{s^2 + 10.56773 \times 10^6}{s^2 + 580.54s + 5.25 \times 10^6}$$

The discrete time transfer function is therefore


$$H(z) = \frac{2 \times 10^{-4} (1 - z^{-1})}{1 - 0.6059z^{-1}} \cdot \frac{1 - 1.9348z^{-1} + z^{-2}}{1 - 1.9604z^{-1} + 0.9763z^{-2}} \cdot \frac{0.8388 - 1.5446z^{-1} + 0.8388z^{-2}}{1 - 1.2807z^{-1} + 0.9415z^{-2}}$$

$$= H_1(z) \cdot H_2(z) \cdot H_3(z)$$



SC Design Example using the Cascade approach (Cont'd)

The first order building block

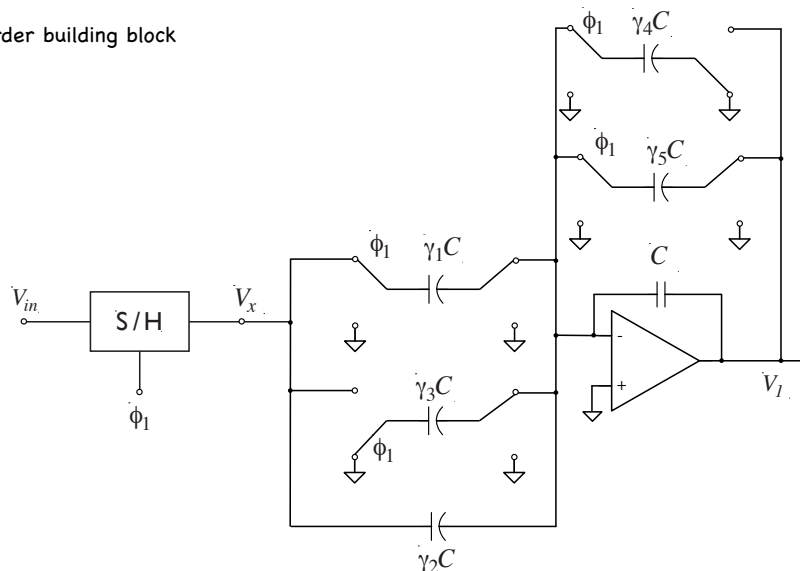

$$\frac{V_1}{V_{in}}(z) = H_1(z) = \frac{-\left(\frac{\gamma_2 + \gamma_3}{1 + \gamma_5}\right) + \left(\frac{\gamma_1 + \gamma_2}{1 + \gamma_5}\right)z^{-1}}{1 - \left(\frac{1 + \gamma_4}{1 + \gamma_5}\right)z^{-1}} = -\frac{2 \times 10^{-4} (1 - z^{-1})}{1 - 0.6059z^{-1}}$$



SC Design Example(Cont'd)

Let us choose $\gamma_1 = \gamma_3 = \gamma_4 = 0$

$$\Rightarrow \frac{\gamma_2}{1 + \gamma_5} = 2 \times 10^{-4} \text{ and } \gamma_5 = 1/0.6059 - 1 = 0.6504 \therefore \gamma_2 = 3.3 \times 10^{-4}$$


This design yields a high capacitance ratio $\left(\frac{1}{3.3 \times 10^{-4}} = 3030\right)$ which is not practical.

A simple solution is to distribute the gain evenly over each section. Hence each

stage would have a gain of $\left(2 \times 10^{-4}\right)^{\frac{1}{3}} = 0.058 \left(= \frac{1}{17}\right)$, which is more practical. For

the new design then $\gamma_2 = 0.058 / 0.6059 = 0.0965$.

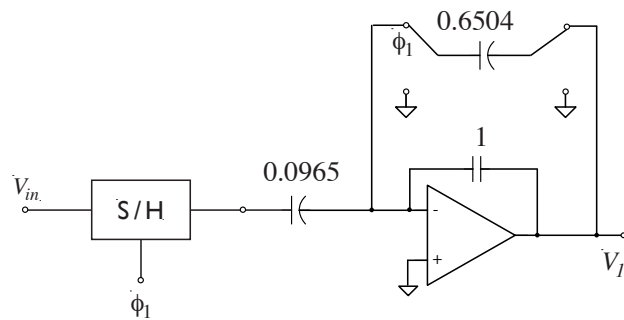Note: The output is valid for both phases



8 - 75

SC Design Example (Cont'd)

Biquad #1

$H_2(z) = -0.058 \frac{1 - 1.9348z^{-1} + z^{-2}}{1 - 1.9604z^{-1} + 0.9763z^{-2}}$. Using the simplified version of the general biquad with the output taken from the second opamp yields.

$$H_2(z) = -\frac{\gamma_4 + [\gamma_2\gamma_{14} - \gamma_4 - \gamma_6]z^{-1} + [\gamma_6 - \gamma_3\gamma_{14}]z^{-2}}{1 + \gamma_{15} + [\gamma_{14}(\gamma_9 + \gamma_{10}) - \gamma_{15} - 2]z^{-1} + [1 - \gamma_9\gamma_{14}]z^{-2}} = -0.058 \frac{1 - 1.9348z^{-1} + z^{-2}}{1 - 1.9604z^{-1} + 0.9763z^{-2}}$$

The design equations are:

$$\gamma_4 = 0.058$$

$$-\gamma_2\gamma_{14} + \gamma_4 + \gamma_6 = 0.058 \times 1.9348 = 0.11222$$

$$\gamma_6 - \gamma_3\gamma_{14} = 0.058$$

$$1 + \gamma_{15} = 1$$

$$-\gamma_{14}(\gamma_9 + \gamma_{10}) + \gamma_{15} + 2 = 1.9604$$

$$1 - \gamma_9\gamma_{14} = 0.9763$$

There are 6 equations and 8 unknowns. We may therefore set $\gamma_3 = 0$ and $\gamma_{14} = 1$. Solving yields

$$\gamma_4 = \gamma_6 = 0.058, \gamma_9 = 0.0237, \gamma_2 = 0.105, \gamma_{10} = 0.0159 \text{ and } \gamma_{15} = 0$$



8 - 76

SC Design Example (Cont'd)

Biquad #2

$H_3(z) = -0.058 \frac{0.8388 - 1.5446z^{-1} + 0.8388z^{-2}}{1 - 1.2807z^{-1} + 0.9415z^{-2}}$. Using the simplified version of the

general biquad with the output taken from the first opamp yields.

$$H_3(z) = -\frac{[\gamma_4(\gamma_9 + \gamma_{10}) - \gamma_2(1 + \gamma_{15})] + [\gamma_2 + \gamma_3(1 + \gamma_{15}) - \gamma_6\gamma_{10} - \gamma_9(\gamma_4 + \gamma_6)]z^{-1} + [\gamma_6\gamma_9 - \gamma_3]z^{-2}}{1 + \gamma_{15} + [\gamma_{14}(\gamma_9 + \gamma_{10}) - \gamma_{15} - 2]z^{-1} + [1 - \gamma_9\gamma_{14}]z^{-2}}$$

The design equations are :

$$\gamma_4(\gamma_9 + \gamma_{10}) - \gamma_2(1 + \gamma_{15}) = 0.058 \times 0.8388 = 0.0487$$

$$\gamma_2 + \gamma_3(1 + \gamma_{15}) - \gamma_6\gamma_{10} - \gamma_9(\gamma_4 + \gamma_6) = -0.058 \times 1.5446 = -0.08959$$

$$\gamma_6\gamma_9 - \gamma_3 = 0.058 \times 0.8388 = 0.04865$$

$$1 + \gamma_{15} = 1$$

$$-\gamma_{14}(\gamma_9 + \gamma_{10}) + \gamma_{15} + 2 = 1.2807$$


$$1 - \gamma_9\gamma_{14} = 0.9415$$

There are 6 equations and 8 unknowns. We may therefore set $\gamma_3 = 0$ and $\gamma_{14} = 1$. Solving yields

$$\gamma_4 = 0.7128, \gamma_6 = 0.8316, \gamma_2 = 0.5474, \gamma_9 = 0.058, \gamma_{10} = 0.6608 \text{ and } \gamma_{15} = 0$$




Final Realization

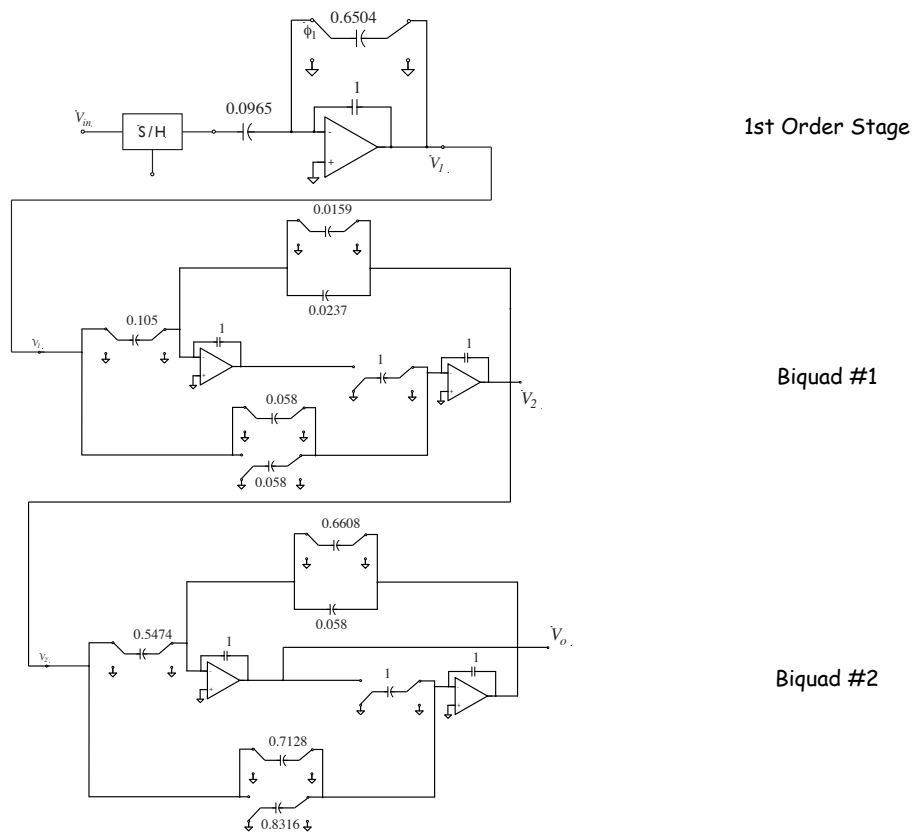

Switch Sharing

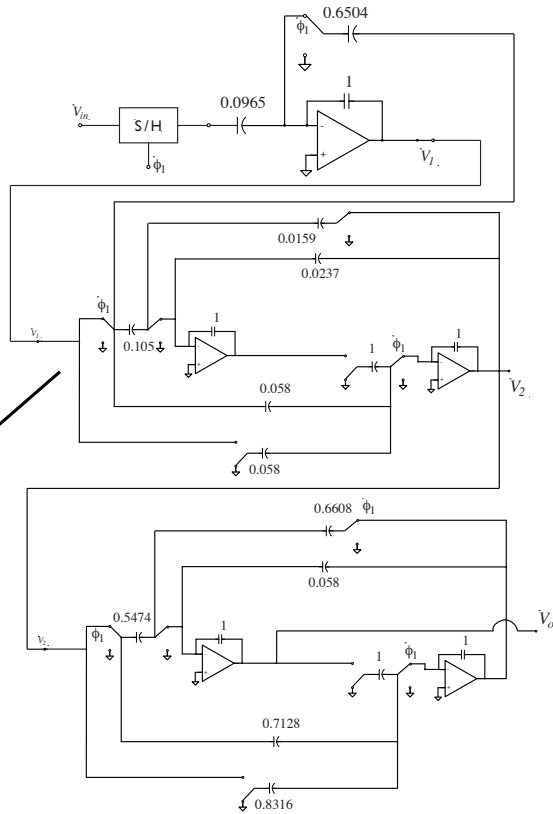Switches can be shared to reduce hardware



Design of SC Ladder Filters

- Procedure very similar to that of analog filters
- We have to employ a transformation because the analog prototype filter operates in s and the corresponding SC filter operates in terms of z .
- Most used s - z transformations are the LDI and the bilinear transformation. Note the bilinear transformation has zero phase error.

LDI (Approximate)


$$s = \frac{1}{T} \left(\frac{1}{z^2} - z \right)$$

↓

$$j\Omega = \frac{1}{T} \left(e^{j\frac{\omega T}{2}} - e^{-j\frac{\omega T}{2}} \right)$$

$$\Omega = \frac{2}{T} \sin\left(\frac{\omega T}{2}\right)$$
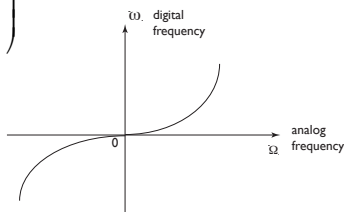
$$\therefore \frac{\omega T}{2} = \sin^{-1}\left(\frac{\Omega T}{2}\right)$$




BDI (Exact)

$$s = \frac{2}{T} \left(\frac{1-z^{-1}}{1+z^{-1}} \right)$$

↓
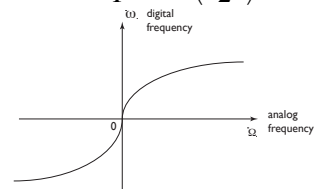
$$\therefore \omega = \frac{2}{T} \tan^{-1}\left(\frac{\Omega T}{2}\right)$$



General procedure for the Approximate Design of SC Ladder filters

- A doubly terminated LC two port is designed from the specifications.

The specifications are prewarped using the relationship



$$\Omega = \frac{2}{T} \sin\left(\frac{\omega T}{2}\right)$$

- Find the state equations of the resulting RLC circuit. The signs of the voltage and current variables must be chosen such that inverting and noninverting integrators alternate in the implementation.
- Construct the block diagram or SFG from the state equations. Transform it directly or via the active RC circuit into the SC filter.
- If necessary, additional circuit transformations can be performed to improve the response of the SCF. These include modifications of the termination sections which improves the passband response or eliminating unnecessary capacitive coupling between opamps in circuits with high clock rates.



8 - 81



Design Example - 3rd Order LPF

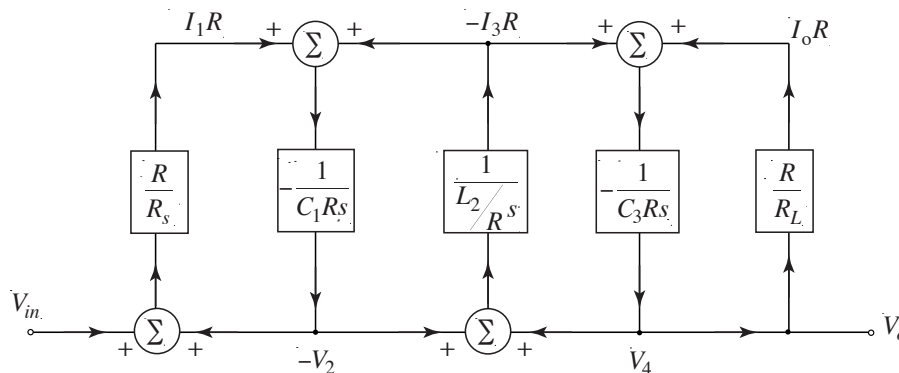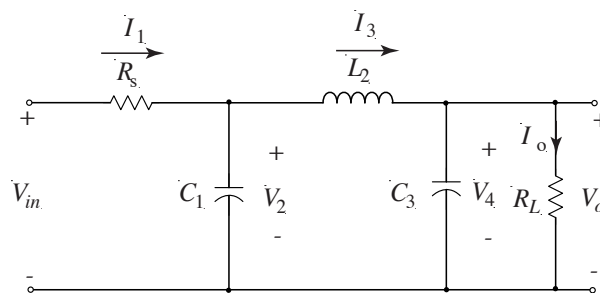

8 - 82

Design Example - 3rd Order LPF (Cont'd)


Equal-R
(R=1 Ohm)

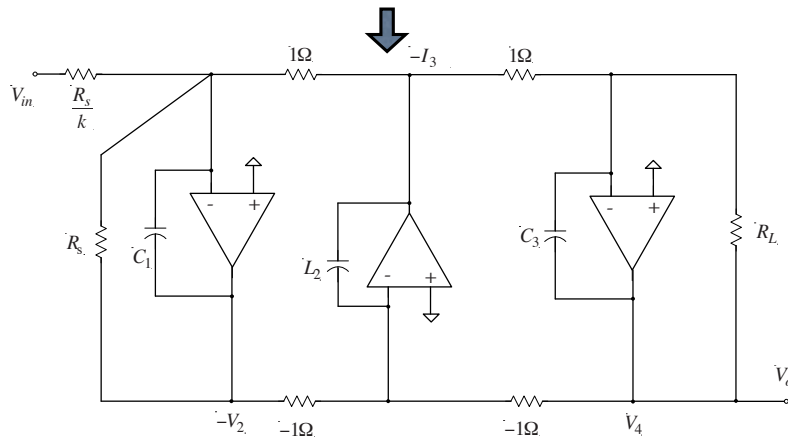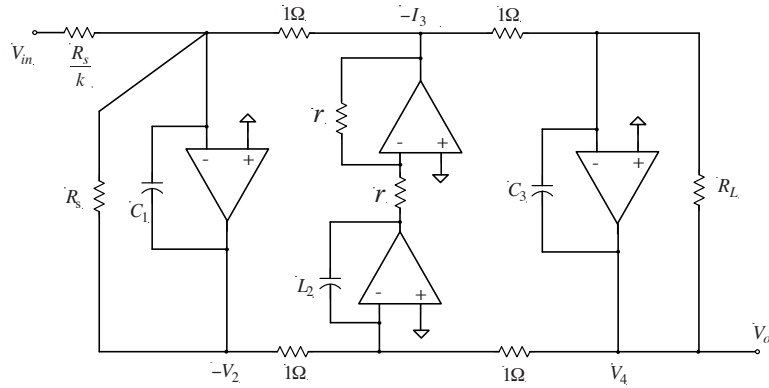


Elimination of
1 opamp by
using negative
resistors



• Inverting Integrator

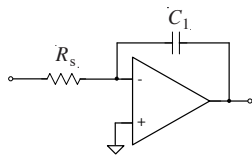


$$H(s) = -\frac{1}{R_s C_1 s}$$

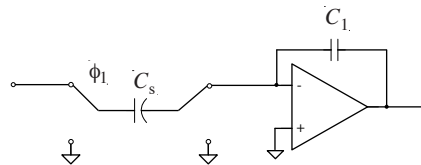


$$H_{inv}(z) = -\frac{C_s}{C_1} \frac{1}{(1-z^{-1})}$$

• Noninverting Integrator

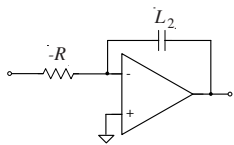

$$H(s) = \frac{1}{R L_2 s}$$

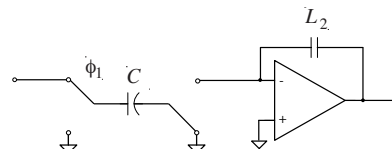

$$H_{noninv}(z) = \frac{C}{L_2} \frac{z^{-1}}{(1-z^{-1})}$$

• Note $H(z) = H_{inv}(z) \cdot H_{noninv}(z) = -\frac{C_s}{C_1} \cdot \frac{C}{L_2} \cdot \frac{z^{-1}}{(1-z^{-1})^2}$

$$= -\frac{K}{\left(z^2 - z^{-1}\right)^2}$$


and

$$H(e^{j\omega T}) = \frac{K}{4 \sin^2\left(\frac{\omega T}{2}\right)}$$

purely real (Zero phase error)



Termination

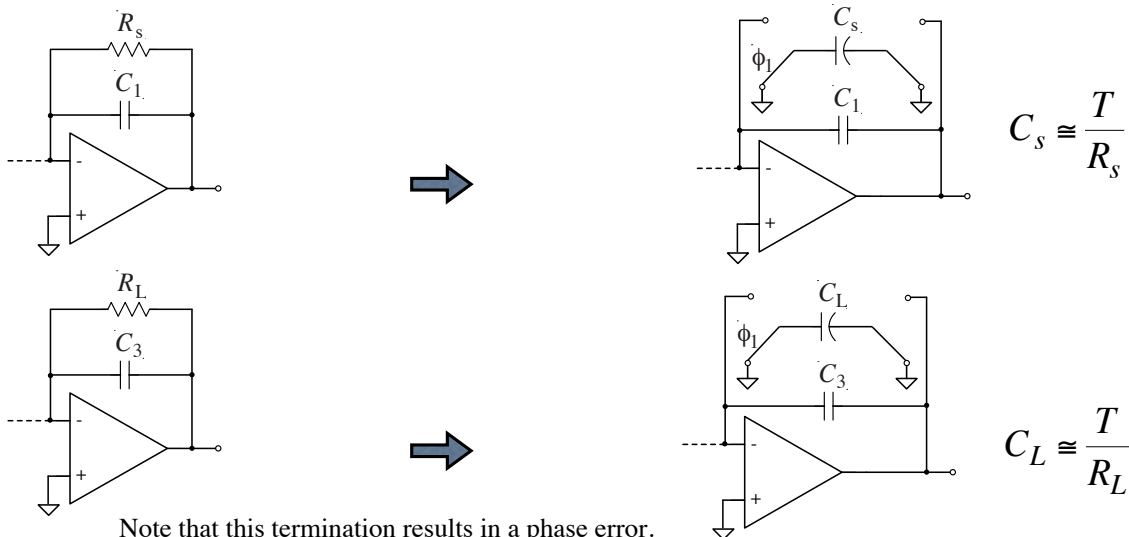

$$C_s \cong \frac{T}{R_s}$$

$$C_L \cong \frac{T}{R_L}$$

Note that this termination results in a phase error.


$$\left. \frac{V_2}{V_{in}}(s) \right|_{-T_3=0} = -\frac{1}{R_s} \cdot \frac{R_s}{(R_s C_1 s + 1)}$$

$$\frac{V_2}{V_{in}}(j\omega) = -\frac{C_s}{T} \cdot \frac{T/C_s}{\left(\frac{TC_1}{C_s} j\omega + 1\right)} = -\frac{C_s}{T} \cdot \frac{T/C_s}{(Qj + 1)}$$

$Q = \omega \frac{TC_1}{C_s}$, represents an approximation error



Final Realization

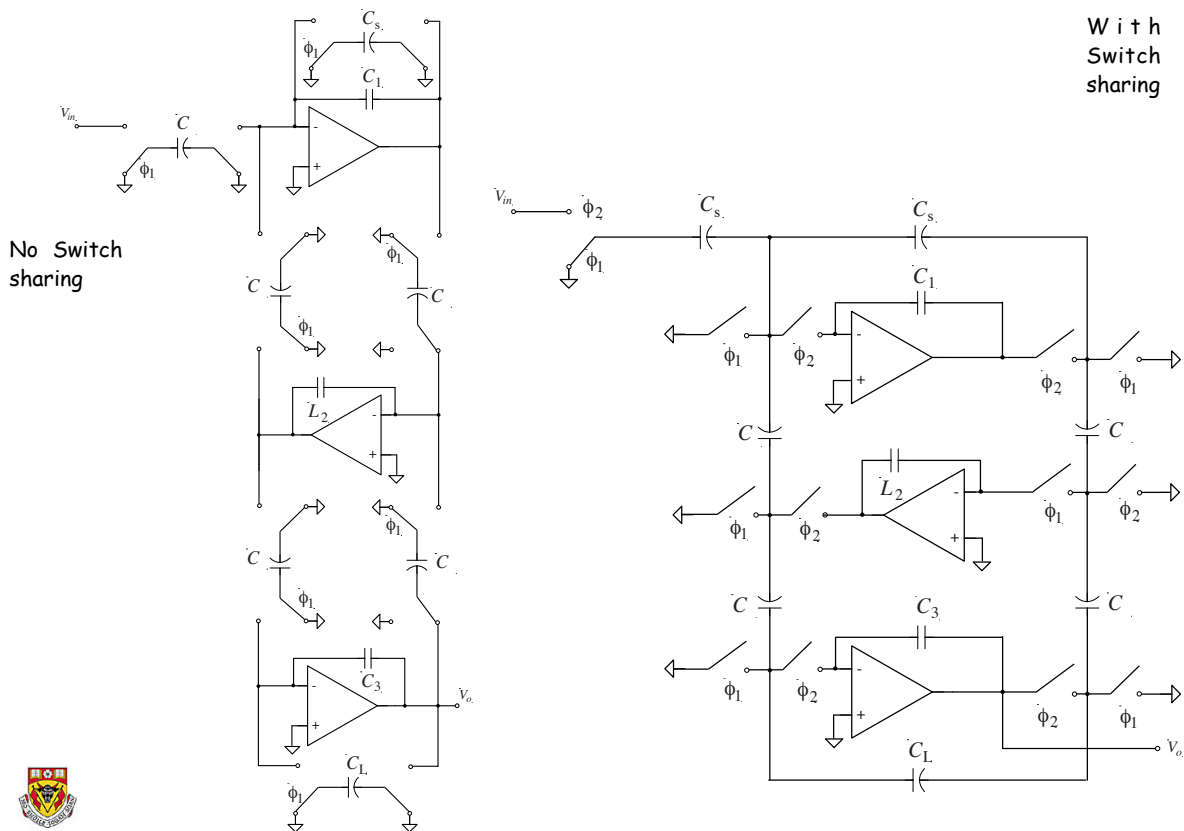


No Switch sharing

With Switch sharing



Ladders with Finite Transmission Zeroes

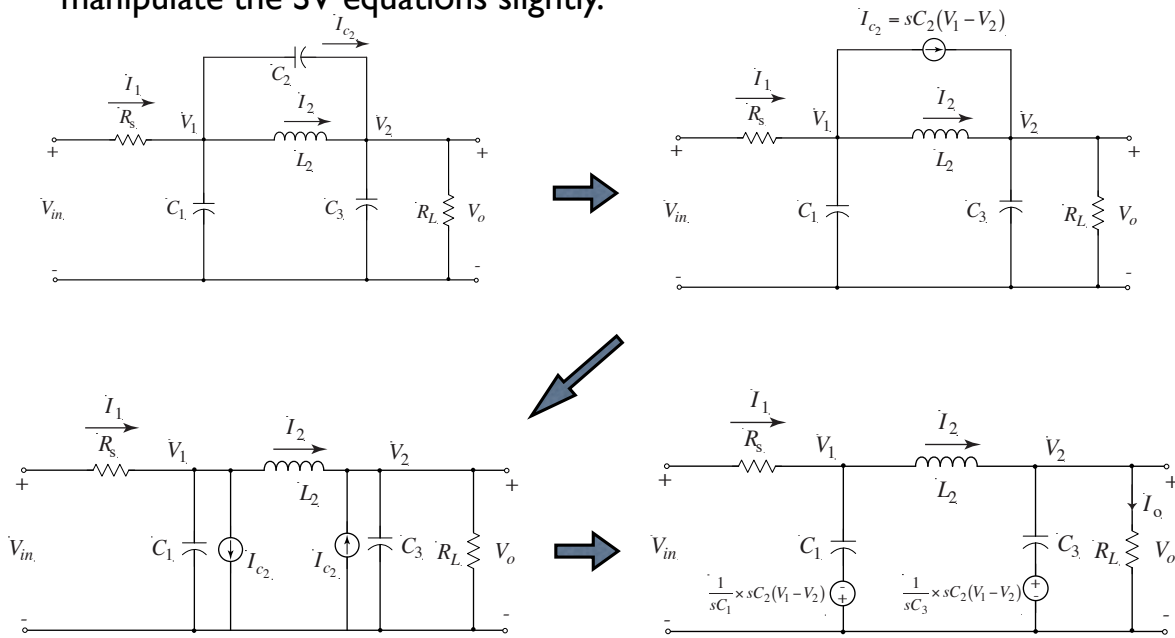- Procedure is the same as before except that we have to manipulate the SV equations slightly.




- SV Equations are

$$I_1 = \frac{V_s - V_1}{R_s}$$


$$V_1 = \frac{1}{s(C_1 + C_2)}(I_1 - I_2) + \frac{sC_2}{s(C_1 + C_2)}V_2$$

$$V_2 = \frac{1}{s(C_2 + C_3)}(I_2 - I_0) + \frac{sC_2}{s(C_2 + C_3)}V_1$$

$$V_o = I_0 R_L = V_2$$

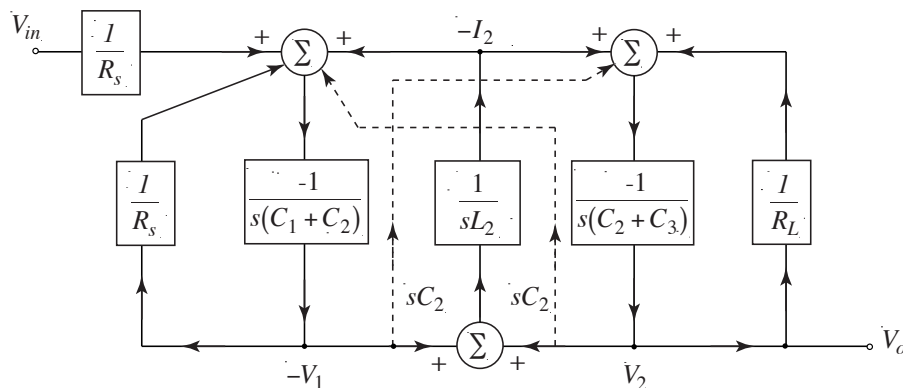


Final Realization (switch sharing)

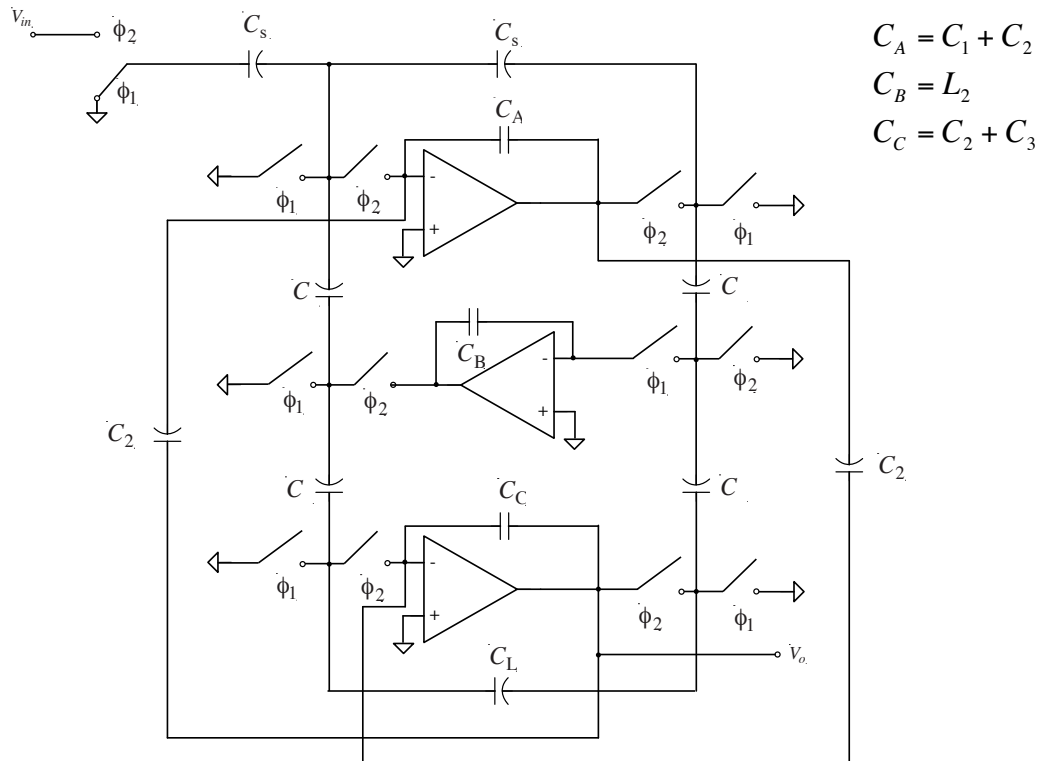

Non-Ideal Opamp Effects

Non-ideal opamp effects such as DC offset voltage, finite DC gain, finite opamp bandwidth, slew rate, and charge injection are important considerations in SC filters.

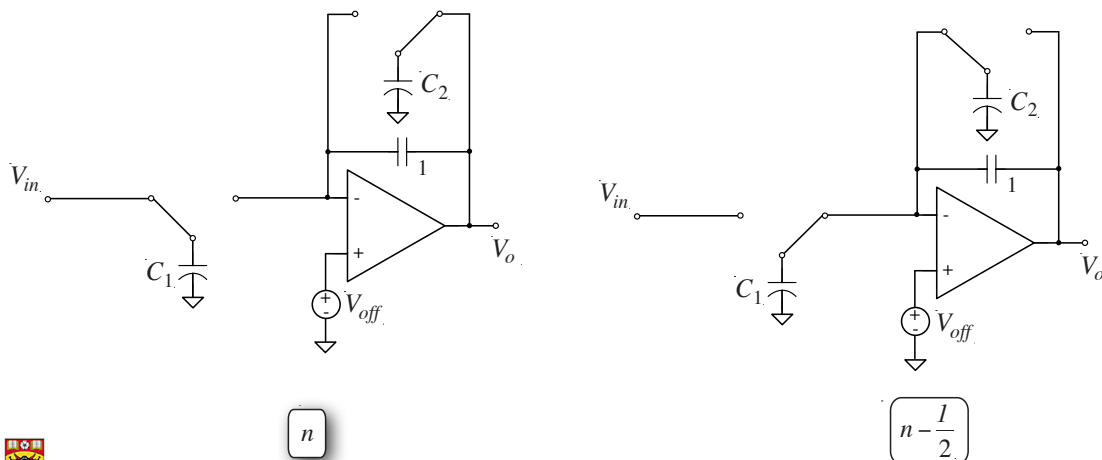- DC Offset voltage effect - consider the simple lossy integrator with opamp offset voltage V_{off}



Non-Ideal Opamp Effects (Cont'd)-DC Offset

n

$$v_o(n) - v_{off}(n) = v_o\left(n - \frac{1}{2}\right) - v_{off}\left(n - \frac{1}{2}\right) + 0$$

$n - \frac{1}{2}$

$$v_o\left(n - \frac{1}{2}\right) - v_{off}\left(n - \frac{1}{2}\right) = v_o(n-1) - v_{off}(n-1) + C_1 \left[v_{c1}\left(n - \frac{1}{2}\right) - v_{c1}(n-1) \right] \\ + C_2 \left[v_{c2}\left(n - \frac{1}{2}\right) - v_{c2}(n-1) \right]$$

but $v_{c1}\left(n - \frac{1}{2}\right) = v_{off}\left(n - \frac{1}{2}\right)$, $v_{c2}\left(n - \frac{1}{2}\right) = v_{off}\left(n - \frac{1}{2}\right)$, $v_{c1}(n-1) = v_{in}(n-1)$

$v_{c2}(n-1) = v_o(n-1)$ and $v_{off}(n) = v_{off}\left(n - \frac{1}{2}\right) = v_{off}(n-1)$

Substitution and taking z - transforms yields,

$$V_o(z) = -\frac{C_1 z^{-1}}{1 - z^{-1} + C_2 z^{-1}} V_{in}(z) + \frac{(C_1 + C_2)}{1 - z^{-1} + C_2 z^{-1}} V_{off}(z)$$

If $V_{in} = 0 \Rightarrow V_o(z) = \frac{(C_1 + C_2)}{1 - z^{-1} + C_2 z^{-1}} V_{off}(z)$


Since V_{off} is constant $s = 0 \rightarrow z = 1$

$$\therefore V_o = \left(1 + \frac{C_1}{C_2}\right) V_{off}$$

- V_o is independent of the feedback capacitor. It depends on the ratio C_1/C_2 .



Simple Offset Cancellation scheme (PIS)

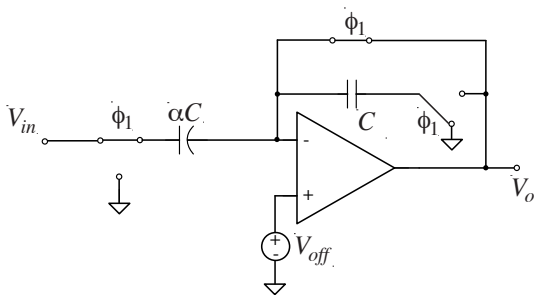

By charge conservation we can write


$$\alpha C \left\{ v_{off} - \left[v_{off} - v_{in}\left(n - \frac{1}{2}\right) \right] \right\} + C \left\{ \left[v_{off} - v_o(n) \right] - v_{off} \right\} = 0$$

$$\Rightarrow v_o(n) = \alpha v_{in}\left(n - \frac{1}{2}\right) \text{ and taking z - transforms yields}$$

$$H(z) = \alpha z^{-\frac{1}{2}}$$

If the clock phases at the input terminal are interchanged, then $H(z) = -\alpha$

Another circuit

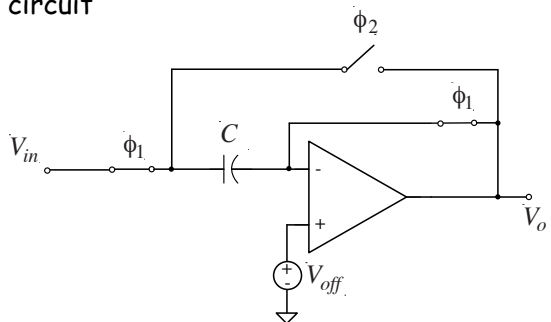


Show that for this circuit $H(z) = z^{-\frac{1}{2}}$

Note the TF only valid for ϕ_2



Effects of the finite DC gain

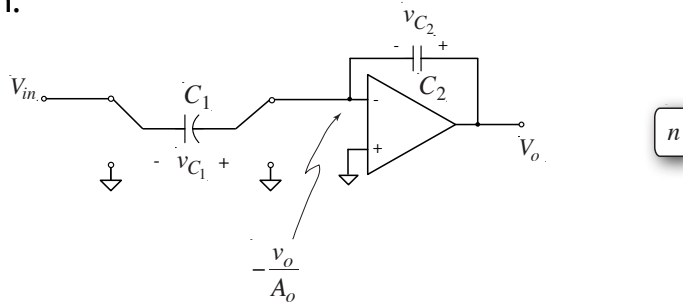- Here we consider the opamp as having a finite DC gain A_o but an infinite bandwidth.



$$C_2 \left[v_o(n) - \frac{-v_o(n)}{A_o} \right] = C_2 \left[v_o \left(n - \frac{1}{2} \right) - \frac{-v_o \left(n - \frac{1}{2} \right)}{A_o} \right] + C_1 \left[v_{C_1}(n) - v_{C_1} \left(n - \frac{1}{2} \right) \right]$$

$$C_2 \left[v_o \left(n - \frac{1}{2} \right) - \frac{-v_o \left(n - \frac{1}{2} \right)}{A_o} \right] = C_2 \left[v_o(n-1) - \frac{-v_o(n-1)}{A_o} \right]$$



8 - 93

Effects of the finite DC gain (Cont'd)

but $v_{C_1}(n) = \frac{-v_o(n)}{A_o} - v_{in}(n)$ and $v_{C_1} \left(n - \frac{1}{2} \right) = 0$

Substitution and taking z - transforms yields,

$$H(z) = \frac{V_o}{V_{in}}(z) = - \frac{C_1}{C_2 + \frac{(C_1 + C_2)}{A_o} - C_2 \left(1 + \frac{1}{A_o} \right) z^{-1}}$$

$$= - \frac{(C_1/C_2) \left[1 + \frac{(1 + C_1/C_2)}{A_o} \right]^{-1} z}{z - \left(1 + \frac{1}{A_o} \right) / \left[1 + \frac{(1 + C_1/C_2)}{A_o} \right]}$$

Compare with the ideal transfer function $H_i(z) = - \frac{(C_1/C_2)z}{z-1} = \frac{-(C_1/C_2)}{1-z^{-1}}$

Two observations:

- The gain is reduced from (C_1/C_2) to a smaller value
- Pole previously at $z = 1$ now has a smaller value



8 - 94

Effects of the finite DC gain (Cont'd)

The ideal frequency response obtained from $z = e^{j\omega T}$ is

$$H_i(e^{j\omega T}) = \frac{-(C_1/C_2)e^{j\omega T}}{2j \sin\left(\frac{\omega T}{2}\right)} \text{ and therefore}$$

$$H(e^{j\omega T}) = \frac{1}{1 - m(\omega) - j\theta(\omega)} \cdot H_i(e^{j\omega T}) \text{ where}$$

$$m(\omega) = -\frac{1}{A_o} \left(1 + \frac{C_1}{2C_2}\right) \text{ and } \theta(\omega) = \frac{(C_1/C_2)}{2A_o \tan\left(\frac{\omega T}{2}\right)} \cong \frac{(C_1/C_2)}{A_o \omega T} \text{ for } \omega T \ll 1$$

- For $A_o > 1000$ and typical values of C_1/C_2 and ωT , $|m| \ll 1$ and $|\theta| \ll 1$ (Except near $\omega = 0$)
- For high sampling rates ($|sT| \ll 1$), $z = e^{sT} \cong 1 + sT$

$$H(s) = H(z)|_{z \cong 1+sT} = \frac{-(C_1/C_2)[1 + (1 + C_1/C_2)/A_o]^{-1}(1 + sT)}{sT + (C_1/C_2 A_o)/[1 + (1 + C_1/C_2)/A_o]}$$

$$H(s) \cong \frac{-(C_1/C_2)T}{s + (C_1/C_2 A_o T)}$$

\therefore The s-domain pole of the integrator is $\sigma_i = \frac{(C_1/C_2)}{A_o T}$ instead of $s = 0$




$$H(s) \cong \frac{-A_o \sigma_i}{s + \sigma_i}$$

8 - 95

Effects of finite DC gain on the Low Q Biquad

Low Q Biquad

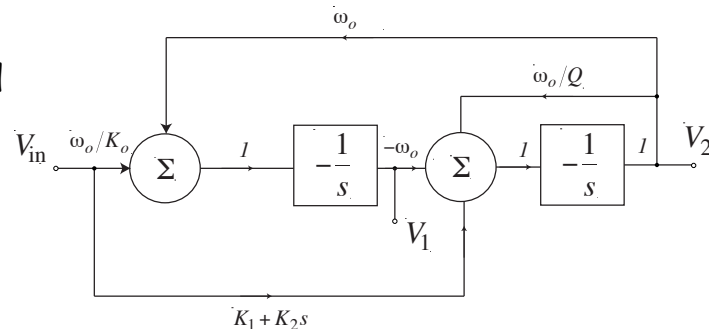

- If each ideal integrator is replaced by its lossy counterpart

$$\frac{1}{Q_{new}} = \frac{1}{Q} + \frac{1}{A_o \omega T} \left[\frac{C_1}{C_F} + \frac{C_2}{C_F} \right], \text{ } C_F \text{ is the feedback capacitor}$$

$$\omega_{o(new)}^2 = \omega_o^2 + \frac{\omega_o \sigma_{i1}}{Q} + \sigma_{i1} \cdot \sigma_{i2}$$

- As an example if $A_o = 1000$, $Q = 15$, and $\frac{C_i}{C_F} \cong \omega T (i = 1, 2) \rightarrow Q_{new} \cong 14.56$

Note the effect is worse for high-Q biquads.





- The change in ω_o is less dramatic.

8 - 96

Effects of finite DC gain on Ladder Filters

- Recall in a ladder filter each integrator simulates a reactive (L or C) element of the passive prototype filter.

If the element is C

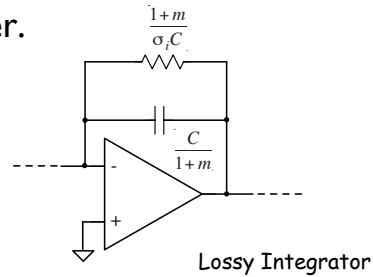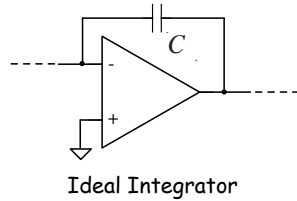

The branch simulated has the impedance $Z(s) = \frac{1}{sC/(1+m) + \sigma_i C/(1+m)}$.

The quality factor of the capacitor is therefore,



$$Q_c = \omega C R_c = \frac{\omega}{\sigma_i} = \frac{A_o \omega T}{(C_1/C_2)} = \frac{1}{\theta(\omega)}$$

- The change in element value $C \rightarrow C/(1+m)$ is usually negligible since the doubly terminated ladder is insensitive to such variations.
- The finite Q_c can result in significant changes in the gain response, especially for narrow-band filters with high- Q poles.



Effects of finite DC gain on Ladder Filters (Cont'd)

If the element is L

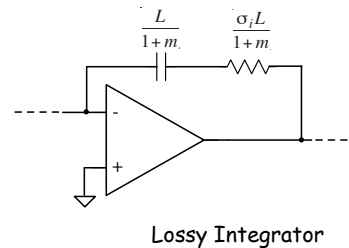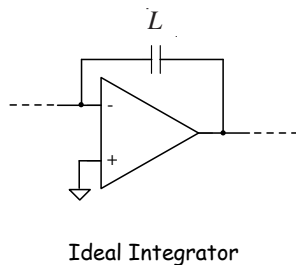

$$Q_L = \frac{\omega L}{R_L} = \frac{\omega}{\sigma_i} = \frac{A_o \omega T}{(C_1/C_2)} = \frac{1}{\theta(\omega)}$$


and

$$Y(s) = \frac{1}{sL/(1+m) + \sigma_i L/(1+m)}$$



Effects of Finite Opamp Bandwidth

Consider the BEDI

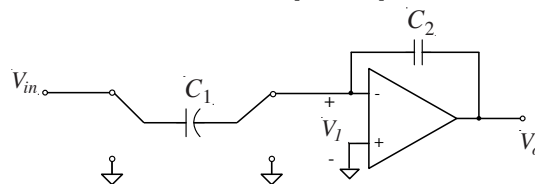

- For the opamp $\frac{V_o}{V_1}(s) = -\frac{\omega_o}{s + \sigma} = -\frac{1}{\frac{1}{A_o} + \frac{s}{\omega_o}}$ where $\omega_o = A_o\sigma$ is the

unity gain bandwidth product of the opamp.

The above equation can be written in the time domain as

$$\frac{1}{A_o} v_o(t) + \frac{1}{\omega_o} \frac{dv_o(t)}{dt} = -v_i(t)$$

Using the opamp time domain behaviour the BEDI can be analyzed for samples $v_o(nT), v_o(nT + T)$, etc and the actual transfer function $H(z) = V_o(z)/V_{in}(z)$ calculated and evaluated for $z = e^{j\omega T}$.

- For the BEDI

$$m(\omega) = -e^{-k_1} [1 - k \cos(\omega T)]$$



Effects of Finite Opamp Bandwidth (Cont'd)

and

$$\theta(\omega) = -e^{-k_1} k \sin(\omega T)$$

where

$$k = \frac{C_2}{C_1 + C_2} \text{ and } k_1 = k \frac{\omega_o T}{2}$$

If we define a unity gain frequency ω_i of the integrator as $|H_i(e^{j\omega_i T})| = 1$ then

$$m(\omega) \cong \theta(\omega) \cong -\omega_i T e^{-\frac{\omega_o T}{2}} \text{ where } \omega_i T \ll 1 \text{ is assumed.}$$

Thus if $\frac{\omega_o T}{2} = \frac{\pi \omega_o}{\omega_c} \gg 1$ (ω_c – clock frequency), then both $m(\omega)$ and $\theta(\omega)$

become negligible. In general $\omega_o \cong 5\omega_c$ is usually adequate.

- The unity gain bandwidth of the opamp should be at least five times as large as the clock frequency ω_c .



Effects of Finite Opamp Bandwidth (Cont'd)

- For the FEDI

$$m(\omega) = -(1 - k)e^{-k_1}$$

and

$$\theta(\omega) \cong 0$$

For $\omega_i \ll \omega_c$,


$$m(\omega_i) \cong -\omega_i T e^{-\frac{\omega_i T}{2}}$$

Hence $\omega_o \geq 5\omega_c$ applies for the FEDI as well.



Effects of Opamp Slew Rate

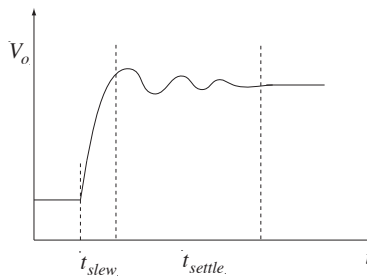- All opamps exhibit finite slew rates that are dependent on currents and capacitances in the output stage of the opamp. A typical output in response to an input step function might therefore look like;



- Slew rate is defined as the maximum rate of change dv_o/dt . Thus

$$S_r = \left| \frac{dv_o}{dt} \right| = \frac{I_L}{C_L}$$

where I_L is assumed to be a load current and C_L the load capacitor.

- Note slew rate is not directly related to the frequency response.



Effects of Opamp Slew Rate (Cont'd)


- For SC circuits based on the assumption of a sine wave input whose highest passband frequency is ω_B and amplitude is V_{\max}

$$S_r \geq \frac{2\omega_B V_{\max}}{(t_{\text{slew}}/T_2)}$$

with $T_1 = T_2 \cong \frac{T}{2} = \frac{1}{2f_c}$ and $t_{\text{slew}} + t_{\text{settle}} < T_2$

- Note positive and negative slew rates exist.

Charge Injection

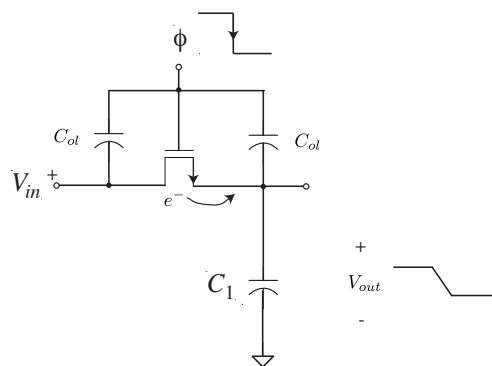

- Due to overlap capacitance $C_{ol} \rightarrow$ Signal Independent


$$\Delta V_{ol} = -\frac{C_{ol}}{C_1 + C_{ol}} \cdot (V_{DD} - V_{SS})$$

- Due to channel charge $\Delta Q_{ch} \rightarrow$ Signal Dependent

$$\Delta V_{ch} = \frac{\Delta Q_{ch} / 2}{C_1} = -\frac{\mu C_{ox} W / L (V_{GS} - V_{TH})}{2C_1} = \frac{\mu C_{ox} W / L (V_{DD} - V_S - V_{TH})}{2C_1}$$

Solution - ΔV_{ol}

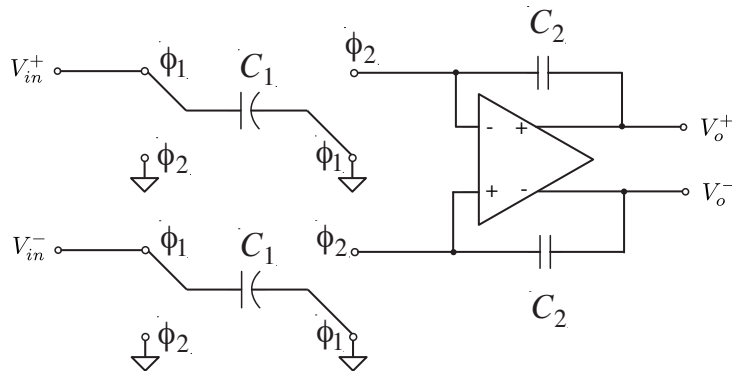- Half-Size Dummy Switch driven by Complementary clocks.
- Transmission Gate
- Fully Differential Approach





$\Rightarrow \Delta V_{ol}(+) \& \Delta V_{ol}(-)$ Cancel each other



8 - 105

Solution - ΔV_{ol}

- Delay Clocking Scheme.

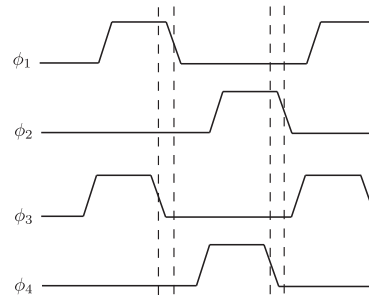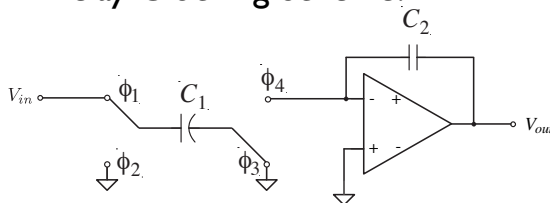

- Due to ϕ_1 : Channel Charge Dependent on V_{in}
- Due to ϕ_3 & ϕ_4 : Channel Charge Dependent on GND \rightarrow Can be removed
- Turning off ϕ_3 & ϕ_4 Earlier \rightarrow Channel Charge of ϕ_1 isolated from C_2
- Use a Compensation Capacitor

\Rightarrow Insert $(-)\Delta Q_{ch}$ which is stored on the compensation capacitor



8 - 106