# Basics of Transconductance – Capacitance Filters

Dr. Paul Hasler

### **Operational Amplifiers**









 $A_v$  is frequency dependent

### Transconductance Amplifiers



• Most op-amps can be used as OTAs, most OTAs can be used as op-amps. (depends which application is being optimized)

# Major Issues for OTAs

#### Major Issues for OTAs:

- Linearity
- Offsets
- Output Resistance (depends upon application)

# How to Build OTAs

Basic transistor differential amplifer, Wide-output-range differential amplifier ...

Build with cascodes or folded cascode or differential approaches.



#### **Differential Pair Currents**



# **Basic Differential Amplifier**



### **Transfer Functions**





#### Wide-Output Range Differential Amplifier





# Simplest Gm-C Filter

If an ideal op-amp, then  $V_{in} = V_{out}$  $V_{in} + V_{out}$   $V_{out}$   $V_{out}$   $V_{in} = V_{out} + \tau \frac{dV_{out}(t)}{dt}$   $V_{in} = V_{out} + \tau \frac{dV_{out}(t)}{dt}$ 

We can set Gm and build C sufficiently big enough (slow down the amplifier), or set by C (smallest size to get enough SNR), and change Gm.

Also, should mention the high-pass version as well.

# Tuning Frequency using Bias Current

Bias Current	Transconductance	Cutoff Frequency
1mA	$1/250\Omega$	600MHz
1µA	$1/25 \mathrm{k}\Omega$	6MHz
1nA	1/25MΩ	6kHz
1pA	1/25GΩ	6Hz

C = 1pF, W/L of input transistors = 30,  $I_{th} \sim 10 \mu A$ .

This approach is the most power-efficient approach for any filter.

All electronically tunable: Advantage: we can electronically change the corner Disadvantage: we need a method to set this frequency (tuning)

#### A Low-Pass Filter





# Another First-Order Low-Pass Filter



#### Second-Order Behavior



#### Second-Order Behavior



# **Basic Second-Order Sections**





# Diff2 Based Second-Order Filter



$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + (\tau/Q) s + \tau^2 s^2} \qquad \tau = (\tau_1 \tau_2)^{1/2} Q = (\tau_2/\tau_1)^{1/2}$$

### Diff2 Responses



# Diff2 Second-Order Section



We will see this circuit again a sample and hold elements

Issue of feedback with an out<sub>1</sub> buffer for an op-amp.

# Tow-Thomas Second-Order Section



# Bandpass Second-Order Section



### Another Second-Order Section



# Even Bigger Gm-C Filter



# Filter Design Problem

Design example(s):

Design a Chebyshev filter with the following specs:

From our MATLAB functions, we get the following  $\tau$ 's and Q's:

Tpb	-1dB ( 0.5088)
Tsb	-25dB
fpb	100kHz
fsb	150kHz

We get the following filter:



Filter Design Example

From MATLAB code: N = 5

Q = 5.5561e+000, tau = 1.6009e-006 Q = 1.3987e+000, tau = 2.4290e-006

tau = 5.4974e-006